

Synchronous Sequential Logic

ENCS2340 - Digital Systems

Dr. Ahmed I. A. Shawahna

Electrical and Computer Engineering Department

Birzeit University

Presentation Outline

❖ Introduction to Sequential Circuits

- ✧ **Combinational versus Sequential Circuits**

- ✧ **Synchronous versus Asynchronous Sequential Circuits**

❖ Storage Elements

- ✧ Latches

- ✧ Flip-Flops

❖ Analysis of Clocked Sequential circuits

- ✧ State and Output Equations

- ✧ State Table

- ✧ State Diagram

❖ Mealy versus Moore Sequential Circuits


Combinational versus Sequential

❖ Two classes of digital circuits

- ✧ Combinational Circuits
- ✧ Sequential Circuits

❖ Combinational Circuit

 - ✧ $\text{Outputs} = F(\text{Inputs})$
- ✧ Function of Inputs only
- ✧ NO internal memory



❖ Sequential Circuit

- ✧ Outputs is a function of Inputs and internal Memory
- ✧ There is an internal memory that stores the state of the circuit
- ✧ Time is very important: memory changes with time

Introduction to Sequential Circuits

A Sequential circuit consists of:

1. Memory elements:

- ✧ **Latches or Flip-Flops**
- ✧ Store the **Present State**


2. Combinational Logic

- ✧ Computes the **Outputs** of the circuit

Outputs depend on Inputs and Current State

- ✧ Computes the **Next State** of the circuit

 Next State also depends on the Inputs and the Present State



Two Types of Sequential Circuits


1. **Synchronous** Sequential Circuit

- ✧ Uses a clock signal as an additional input
- ✧ Changes in the memory elements are controlled by the clock
- ✧ Changes happen at discrete instances of time

2. **Asynchronous** Sequential Circuit


- ✧ No clock signal
 - ✧ Changes in the memory elements can happen at any instance of time
- ❖ Our focus will be on Synchronous Sequential Circuits
- ✧ Easier to design and analyze than asynchronous sequential circuits

Synchronous Sequential Circuits

 


- ❖ Synchronous sequential circuits use a **clock signal**
- ❖ The clock signal is an input to the memory elements
- ❖ The clock determines **when** the memory should be updated
- ❖ The **present state** = output value of memory (stored)
- ❖ The **next state** = input value to memory (not stored yet)

The Clock

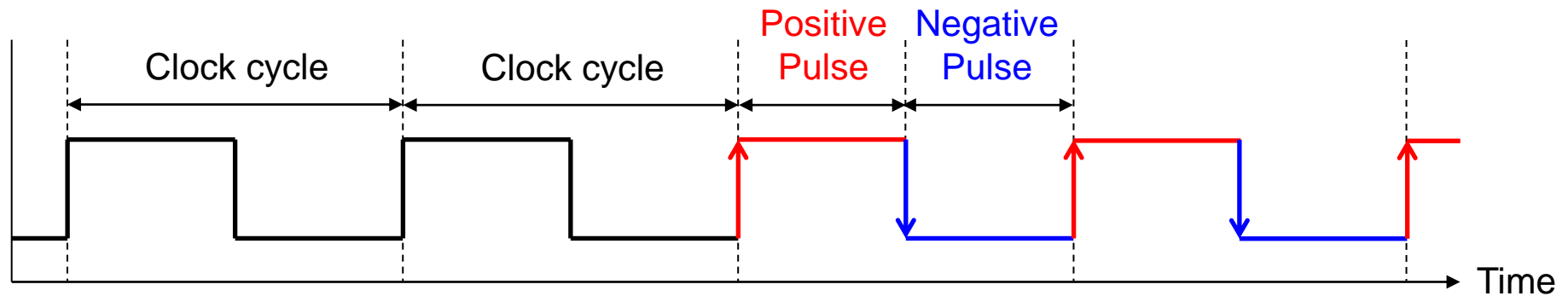

- ❖ Clock is a periodic signal = Train of pulses (1's and 0's)
- ❖ The same clock cycle repeats indefinitely over time
- ❖ **Positive Pulse**: when the **level** of the clock is **1**
- ❖ **Negative Pulse**: when the **level** of the clock is **0**
- ❖ **Rising Edge**: when the clock goes **from 0 to 1**
- ❖ **Falling Edge**: when the clock goes **from 1 down to 0**

Clock Cycle versus Clock Frequency

 

❖ Clock cycle (or period) is a time duration

✧ Measured in seconds, milli-, micro-, nano-, or pico-seconds

✧ $1 \text{ ms} = 10^{-3} \text{ sec}$, $1 \mu\text{s} = 10^{-6} \text{ sec}$, $1 \text{ ns} = 10^{-9} \text{ sec}$, $1 \text{ ps} = 10^{-12} \text{ sec}$

❖ Clock frequency = number of cycles per second (Hertz)

✧ $1 \text{ Hz} = 1 \text{ cycle/sec}$, $1 \text{ KHz} = 10^3 \text{ Hz}$, $1 \text{ MHz} = 10^6 \text{ Hz}$, $1 \text{ GHz} = 10^9 \text{ Hz}$

❖ Clock frequency = $1 / \text{Clock Cycle}$

✧ Example: Given the clock cycle = $0.5 \text{ ns} = 0.5 \times 10^{-9} \text{ sec}$

✧ Then, the clock frequency = $1/(0.5 \times 10^{-9}) = 2 \times 10^9 \text{ Hz} = 2 \text{ GHz}$

Next . . .



- ❖ Introduction to Sequential Circuits
 - ✧ Combinational versus Sequential Circuits
 - ✧ Synchronous versus Asynchronous Sequential Circuits
- ❖ **Storage Elements**
 - ✧ **Latches**
 - ✧ Flip-Flops
- ❖ Analysis of Clocked Sequential circuits
 - ✧ State and Output Equations
 - ✧ State Table
 - ✧ State Diagram
- ❖ Mealy versus Moore Sequential Circuits

Memory Elements

- ❖ Memory can store and maintain binary state (0's or 1's)
 - ✧ Until directed by an input signal to change state
- ❖ Main difference between memory elements
 - ✧ Number of inputs they have
 - ✧ How the inputs affect the binary state
- ❖ Two main types:
 - ✧ **Latches** are **level-sensitive** (sensitive to the level of the clock)
 - ✧ **Flip-Flops** are **edge-sensitive** (sensitive to the edge of the clock)
- ❖ Flip-Flops are used in synchronous sequential circuits
- ❖ Flip-Flops are built with latches


Latch

- ❖ A **latch**, shown in **Figure (a)**, is a memory element that can **store one bit (0 or 1)**
 - ✧ The latch circuit consists of **two inverters**; with the output of one connected to the input of the other
 - ✧ The latch circuit has **two outputs**, one for the stored value (**Q**) and one for its complement (**Q'**)
 - ✧ **Figure (b)** shows the same latch circuit re-drawn to illustrate the two complementary outputs
- ❖ The problem with the latch formed by NOT gates is that **we can't change the stored value**
 - ✧ For example, if the output of inverter B has logic 1, then it will be latched forever; and there is no way to change this value

  

SR Latch

- ❖ An **SR Latch** can be built using two **cross-coupled** NOR gates
- ❖ Two inputs: S (Set) and R (Reset)
- ❖ Two outputs: Q and \bar{Q}
 - ✧ If $S = 1$ and $R = 0$ then **Set** ($Q = 1, \bar{Q} = 0$)
 - ✧ If $S = 0$ and $R = 1$ then **Reset** ($Q = 0, \bar{Q} = 1$)
 - ✧ When $S = R = 0$, Q and \bar{Q} are **unchanged**
 - ✧ When $S = R = 1$, Q and \bar{Q} are **undefined** (should never be used)

 



(a) Logic diagram

| S | R | Q | \bar{Q} | |
|---|---|---|-----------|-------------|
| 1 | 0 | 1 | 0 | Set state |
| 0 | 0 | 1 | 0 | |
| 0 | 1 | 0 | 1 | Reset state |
| 0 | 0 | 0 | 1 | |
| 1 | 1 | 0 | 0 | Undefined |


(b) Function table

SR Latch Operation



Set Operation

  


Store Operation

 

Reset Operation

 
 


Store Operation

 


SR Latch Invalid Operation

Invalid Operation

  

Race Condition

 


$S = R = 1$ should never be used


If S and R change from $1 \rightarrow 0$ simultaneously then race condition (oscillation) occurs

Final Q and \bar{Q} are unknown

Unknown State

 


Timing Diagram of an SR Latch

 

(a) Logic diagram


| S | R | Q | \bar{Q} | |
|---|---|---|-----------|-------------|
| 1 | 0 | 1 | 0 | Set state |
| 0 | 0 | 1 | 0 | |
| 0 | 1 | 0 | 1 | Reset state |
| 0 | 0 | 0 | 1 | |
| 1 | 1 | 0 | 0 | Undefined |

(b) Function table

 


Characteristic Equation of the SR Latch

| $Q(t)$ | S | R | $Q(t+1)$ |
|--------|-----|-----|---------------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | Indeterminate |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | Indeterminate |

 

$$Q(t+1) = S + R'Q$$

Gated SR Latch with Clock Enable

 


| C | S | R | Next state of Q |
|---|---|---|--------------------|
| 0 | X | X | No change |
| 1 | 0 | 0 | No change |
| 1 | 0 | 1 | Q = 0; Reset state |
| 1 | 1 | 0 | Q = 1; Set state |
| 1 | 1 | 1 | Undefined |

- ❖ An additional Clock (enable) input signal **C** is used
- ❖ Clock controls **when** the state of the latch can be changed
- ❖ When **C=0**, the S and R inputs have no effect on the latch

The latch will remain in the same state, regardless of S and R

- ❖ When **C=1**, then normal SR latch operation

$\bar{S} \bar{R}$ Latch with NAND Gates


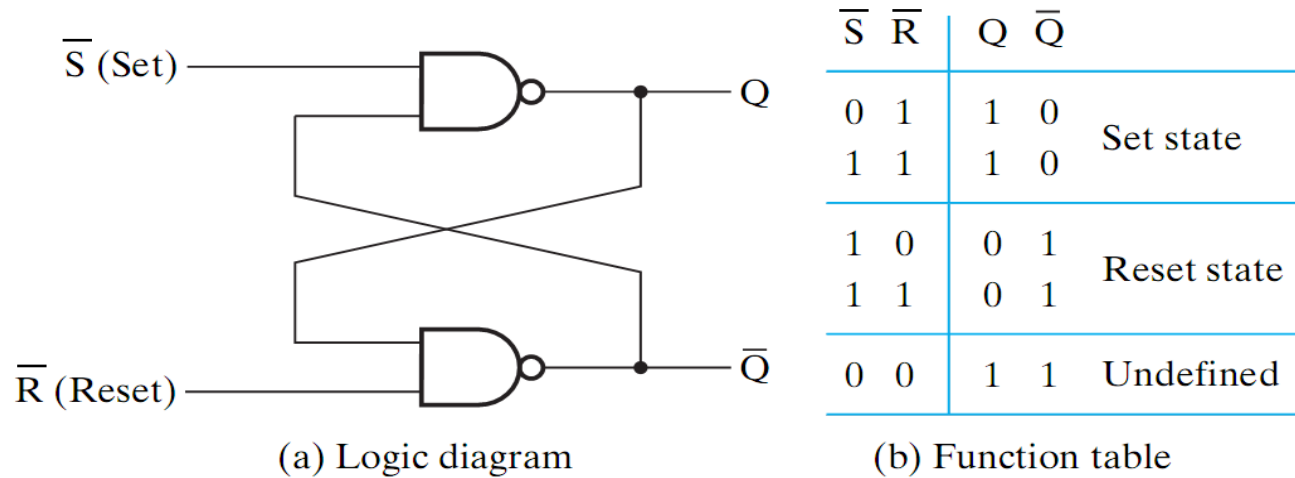


Known as
the $\bar{S} \bar{R}$ Latch


- ❖ If $\bar{S} = 0$ and $\bar{R} = 1$ then **Set** ($Q = 1$, $\bar{Q} = 0$)
- ❖ If $\bar{S} = 1$ and $\bar{R} = 0$ then **Reset** ($Q = 0$, $\bar{Q} = 1$)
- ❖ When $\bar{S} = \bar{R} = 1$, Q and \bar{Q} are **unchanged** (remain the same)
- ❖ The latch stores its outputs Q and \bar{Q} as long as $\bar{S} = \bar{R} = 1$
- ❖ When $\bar{S} = \bar{R} = 0$, Q and \bar{Q} are **undefined** (should never be used)

$\overline{S} \overline{R}$ Latch Operation



Set Operation

  


Store Operation

 

Reset Operation

 
 


Store Operation

 


\bar{S} \bar{R} Latch Invalid Operation

Invalid Operation

  

Race Condition

 


$\bar{S} = \bar{R} = 0$ should never be used


If \bar{S} and \bar{R} change from $0 \rightarrow 1$ simultaneously then race condition (oscillation) occurs

Final Q and \bar{Q} are unknown

Unknown State

 


Gated SR Latch with Clock Enable

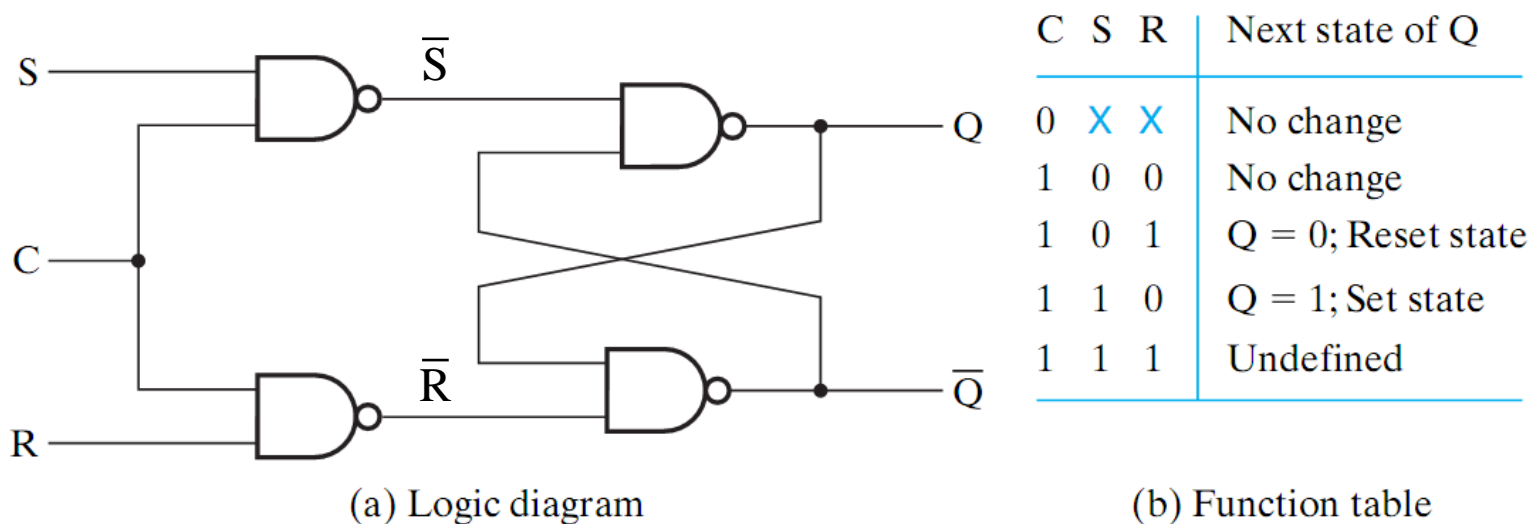

- ❖ An additional Clock (enable) input signal **C** is used
- ❖ Clock controls **when** the state of the latch can be changed
- ❖ When **C=0**, the S and R inputs have no effect on the latch
 - ✧ The latch remains in the same state, regardless of S and R
- ❖ When **C=1**, then normal latch operation

SR Latch with a Clock Input


Logic Diagram

 


Function Table

| C | S | R | Next State |
|---|---|---|---------------|
| 0 | X | X | No Change |
| 1 | 0 | 0 | No Change |
| 1 | 0 | 1 | Q=0; Reset |
| 1 | 1 | 0 | Q=1; Set |
| 1 | 1 | 1 | Indeterminate |


No Change

 


No Change

 


Set

 

Reset

 

 
SR Latch with a Clock Input Timing Diagram



Function Table

| C | S | R | Next State |
|---|---|---|---------------|
| 0 | X | X | No Change |
| 1 | 0 | 0 | No Change |
| 1 | 0 | 1 | Q=0; Reset |
| 1 | 1 | 0 | Q=1; Set |
| 1 | 1 | 1 | Indeterminate |

D-Latch with Clock Enable

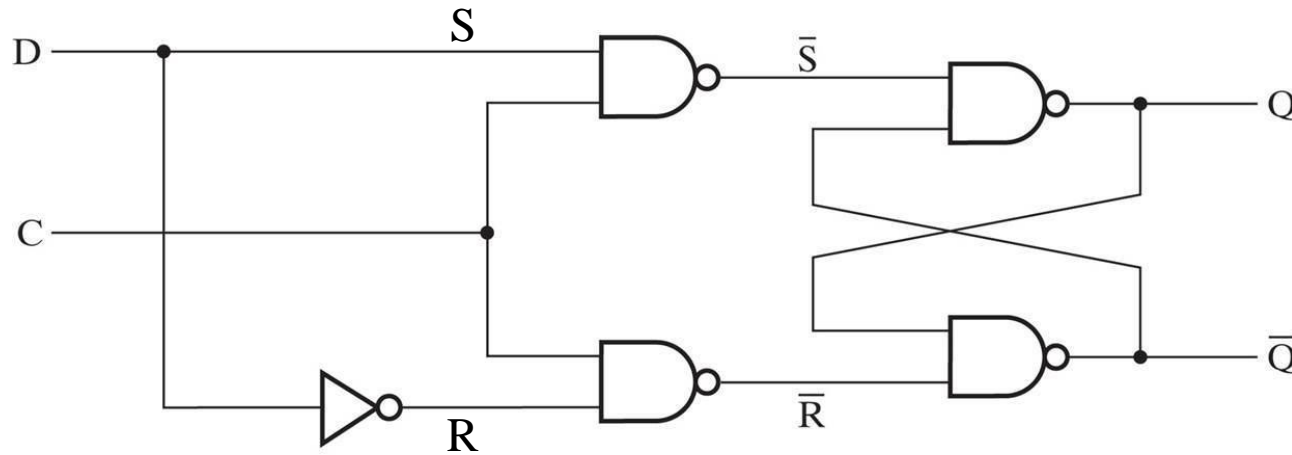


(a) Logic diagram


| C | D | Next state of Q |
|---|---|--------------------|
| 0 | X | No change |
| 1 | 0 | Q = 0; Reset state |
| 1 | 1 | Q = 1; Set state |

 (b) Function table

- ❖ One data input D
- ❖ $S = D$ and $R = \bar{D}$
- ❖ No undefined state
- ❖ Inverter can be removed
- ❖ When $C = 1$, $R = \bar{S} = \bar{D}$




Timing of a D-Latch with Clock Enable

 

| C | D | Next state of Q |
|---|---|--------------------|
| 0 | X | No change |
| 1 | 0 | Q = 0; Reset state |
| 1 | 1 | Q = 1; Set state |

Function table

 


Characteristic Equation of the D-Latch

| $Q(t)$ | D | $Q(t+1)$ |
|--------|-----|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 0 |
| 1 | 1 | 1 |

| | | | |
|-----|---|-----|---|
| | | D | |
| | | 0 | 1 |
| Q | 0 | | 1 |
| | 1 | | 1 |

$$Q(t+1) = D$$

Graphic Symbols for Latches

 

❖ A bubble appears at the complemented output \bar{Q}

Indicates that \bar{Q} is the complement of Q


❖ A bubble also appears at the inputs of an $\bar{S} \bar{R}$ latch

Indicates that **logic-0** is used (not logic-1) to set (or reset) the latch (as in the NAND latch implementation)

 Problem with Latches

- ❖ A latch is **level-sensitive** (sensitive to the level of the clock)
- ❖ As long as the clock signal is **high** ...
 - Any change in the value of input D appears in the output Q
- ❖ Output Q keeps changing its value during a clock cycle
- ❖ Final value of output Q is uncertain

Due to this uncertainty, latches are NOT used as memory elements in synchronous circuits




Next . . .

- ❖ Introduction to Sequential Circuits
 - ✧ Combinational versus Sequential Circuits
 - ✧ Synchronous versus Asynchronous Sequential Circuits
- ❖ **Storage Elements**
 - ✧ Latches
 - ✧ **Flip-Flops**
- ❖ Analysis of Clocked Sequential circuits
 - ✧ State and Output Equations
 - ✧ State Table
 - ✧ State Diagram
- ❖ Mealy versus Moore Sequential Circuits

Flip-Flops

 - ❖ A **Flip-Flop** is a better memory element for synchronous circuits
- ❖ Solves the problem of latches in synchronous sequential circuits
- ❖ A **latch** is sensitive to the **level** of the clock
- ❖ However, a **flip-flop** is sensitive to the **edge** of the clock
- ❖ A flip-flop is called an **edge-triggered** memory element
- ❖ It changes its output value at the **edge** of the clock




Positive Edge-Triggered D Flip-Flop

- ❖ Built using two latches in a **master-slave** configuration
- ❖ A master latch (D-type) receives external inputs
- ❖ A slave latch (SR-type) receives inputs from the master latch
- ❖ Only one latch is enabled at any given time

When **Clk=0**, the master is enabled and the D input is latched (slave disabled)

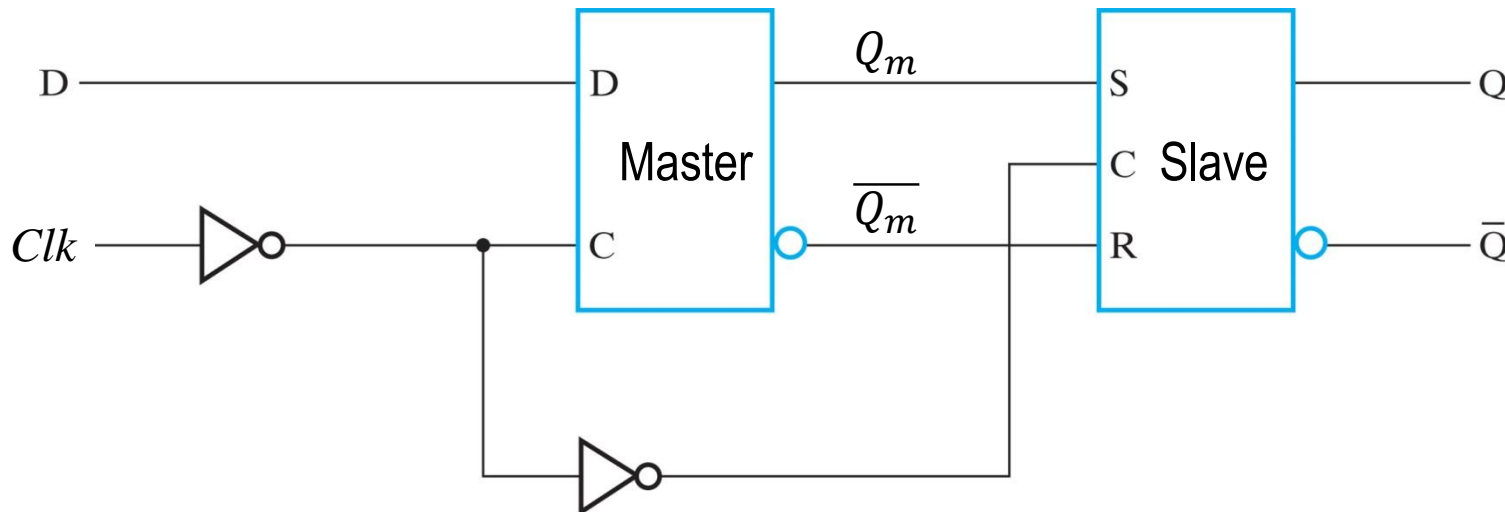
When **Clk=1**, the slave is enabled to generate the outputs (master is disabled)



Outputs
change when
Clk changes
from 0 to 1

D Flip-Flop Timing Diagram

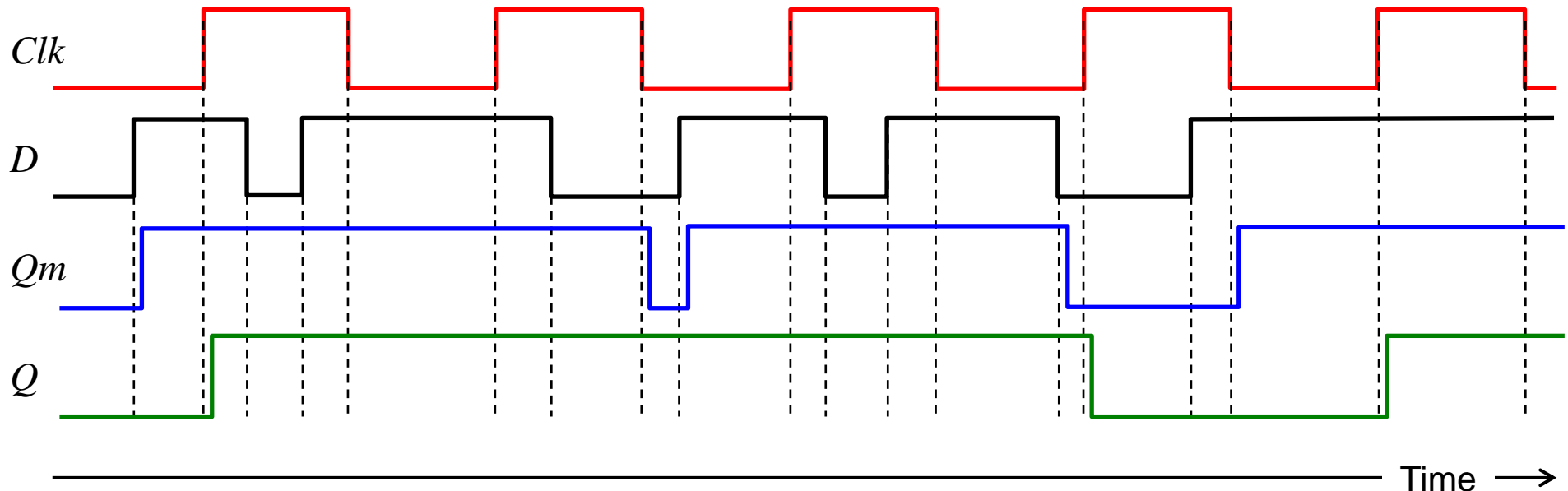- ❖ The diagram shows the timing of a positive-edge D Flip-Flop
- ❖ The master latch changes its output Q_m when the clock C is 0
- ❖ The rising edge of the clock triggers the D Flip-Flop
- ❖ Notice the slight delay in the output Q after the rising edge




Negative Edge-Triggered D Flip-Flop


- ❖ Similar to positive edge-triggered flip-flop
- ❖ The first inverter at the Master C input is removed
- ❖ Only one latch is enabled at any given time

When **Clk=1**, the master is enabled and the D input is latched (slave disabled)

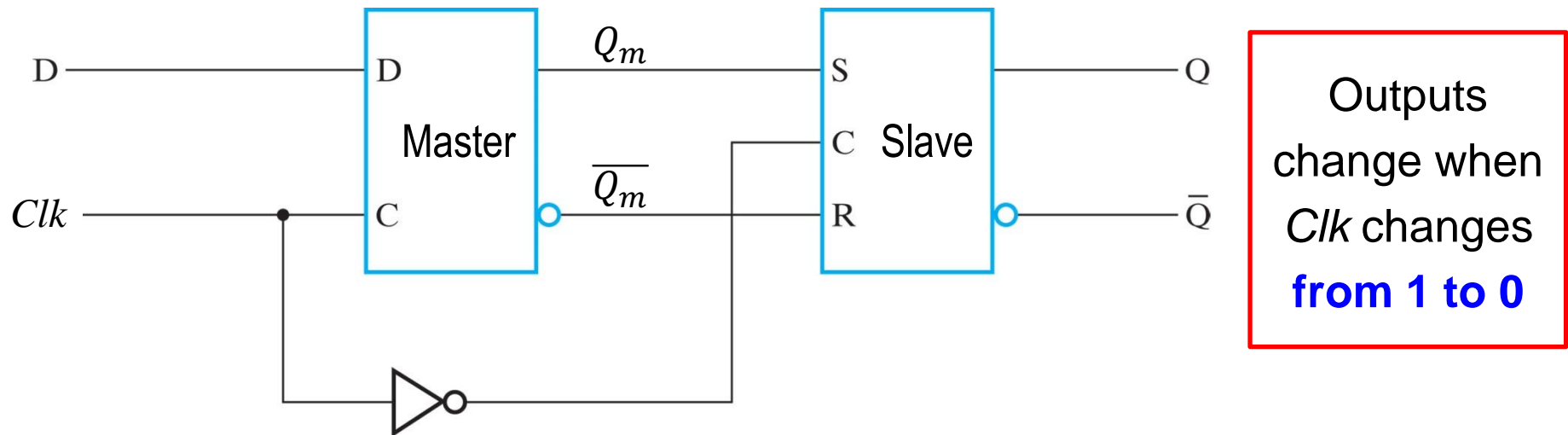
When **Clk=0**, the slave is enabled to generate the outputs (master is disabled)



Negative-Edge D Flip-Flop Timing Diagram




 


(a) Circuit

 


(b) Timing diagram



D-Latch VS Edge-Triggered D Flip-Flop

 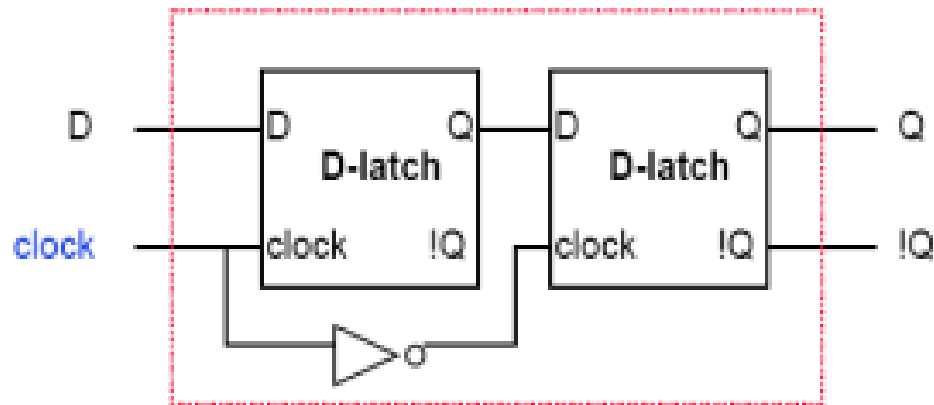  

 Another Construction - Positive Edge D-FF




Graphic Symbols for Flip-Flops

  

- ❖ A Flip-Flop has a similar symbol to a Latch
- ❖ The difference is the arrowhead at the clock input
- ❖ The arrowhead indicates sensitivity to the edge of the clock
- ❖ A circle at the *Clk* input indicates negative edge-triggered FF

D-FF with Asynchronous Set and Reset

 
- ❖ When Flip-Flops are powered, their initial state is **unknown**
- ❖ Some flip-flops have an **asynchronous Set** and/or **Reset** inputs
- ❖ Set forces Q to become **1**, independently of the clock
- ❖ Reset forces Q to become **0**, independently of the clock



| Inputs | | | | Outputs | |
|------------|--------------|-------------|------------|---------|-----------|
| <i>Set</i> | <i>Reset</i> | <i>Data</i> | <i>Clk</i> | Q | \bar{Q} |
| 0 | 1 | X | X | 1 | 0 |
| 1 | 0 | X | X | 0 | 1 |
| 1 | 1 | 0 | ↑ | 0 | 1 |
| 1 | 1 | 1 | ↑ | 1 | 0 |



Function Table

D-FF with Asynchronous Set and Reset

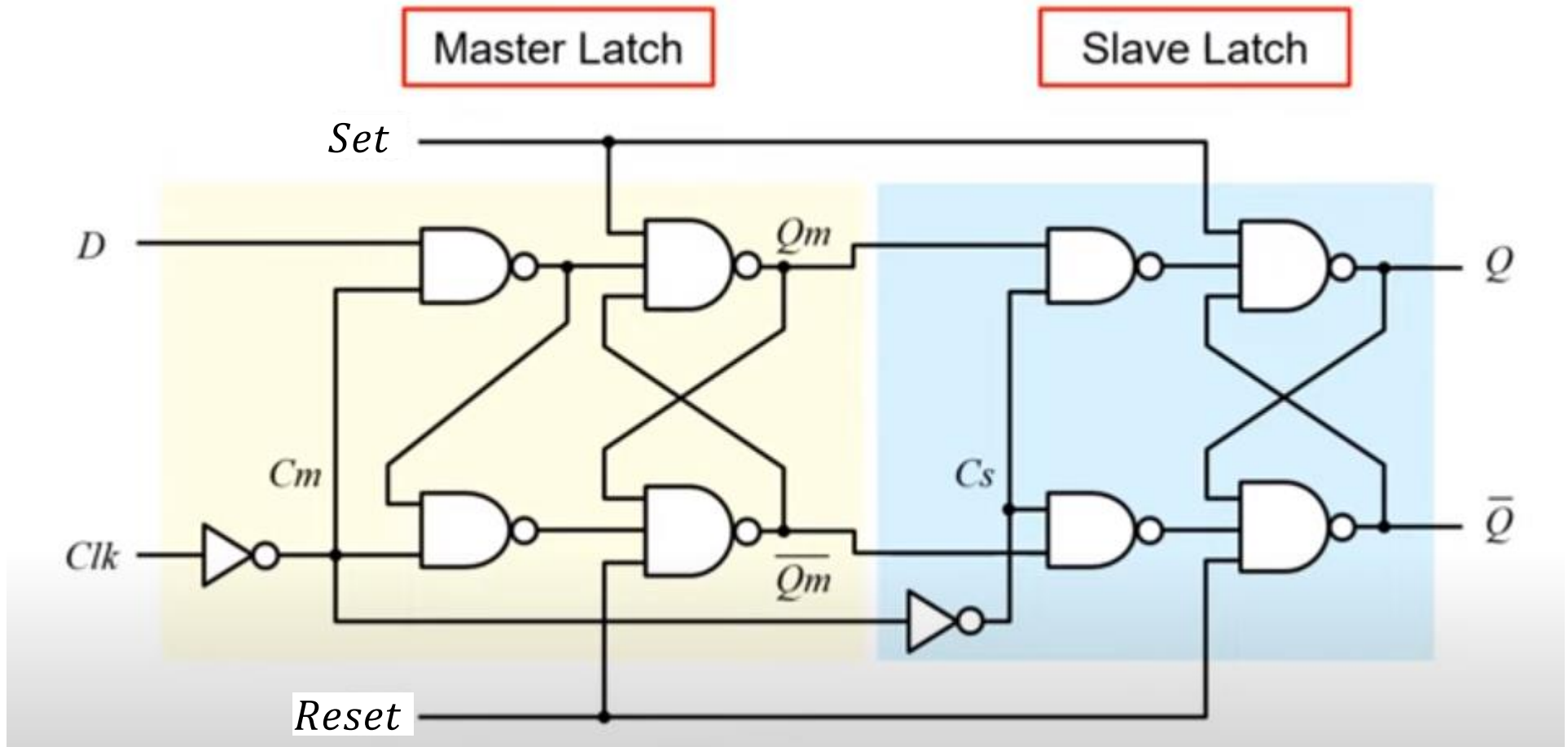


D Flip-Flop with Asynchronous Reset

Circuit Diagram

  


Graphic Symbol

 

Function Table



| R | C | D | Q | Q' |
|-----|-----|-----|-----|------|
| 0 | X | X | 0 | 1 |
| 1 | ↑ | 0 | 0 | 1 |
| 1 | ↑ | 1 | 1 | 0 |

D Flip-Flop with Asynchronous Reset

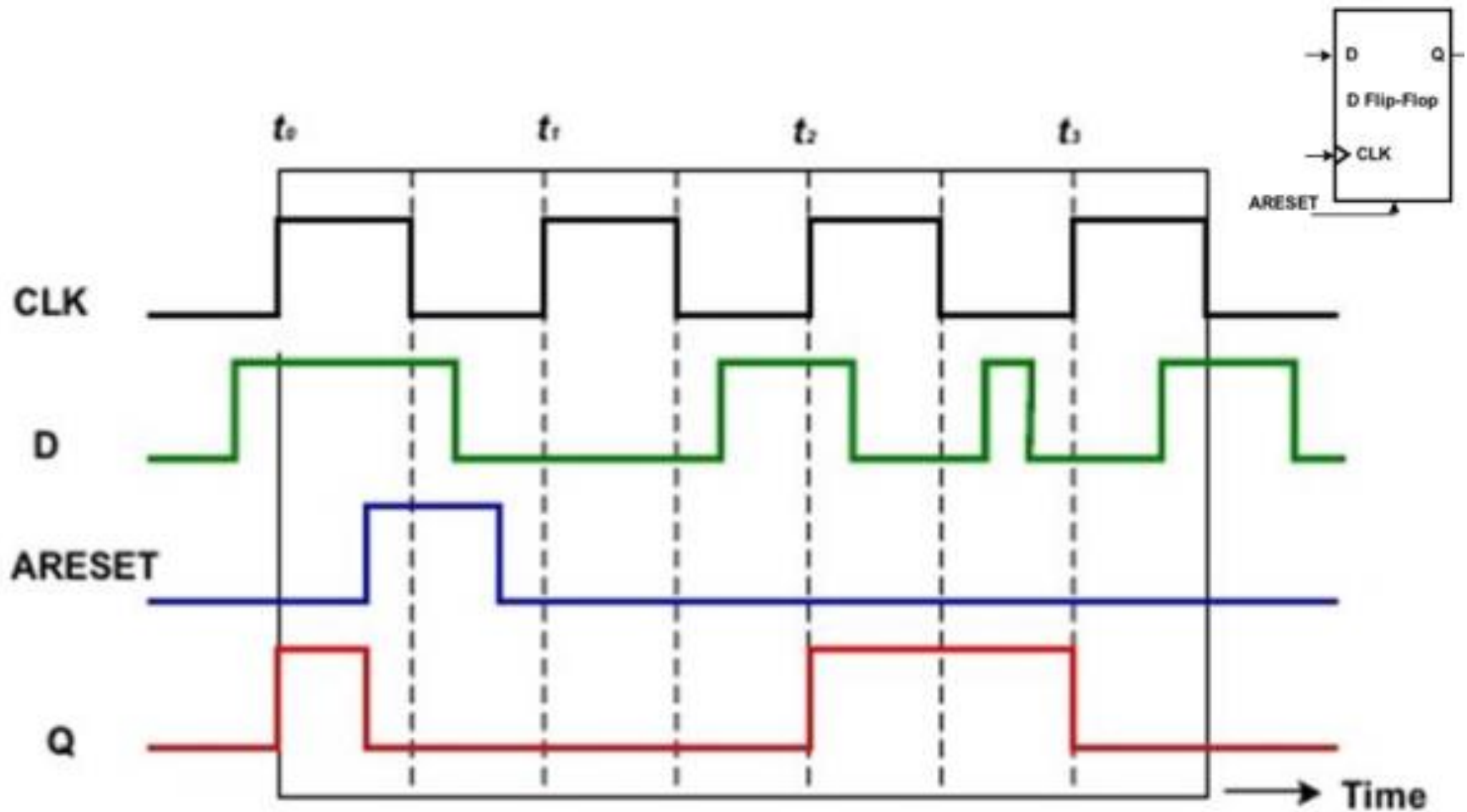


JK Flip-Flop

 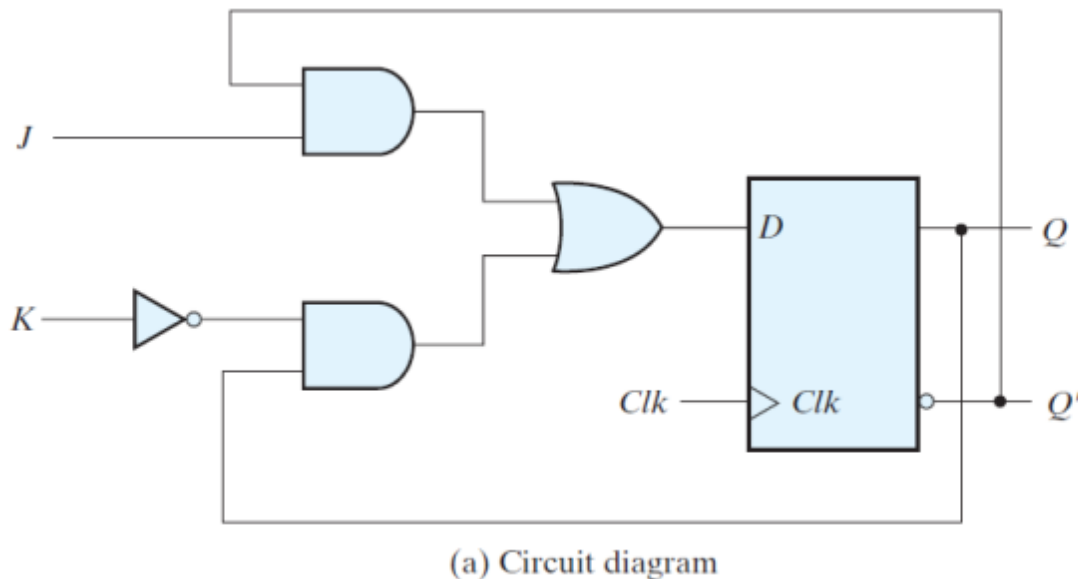- ❖ The *D* Flip-Flop is the most commonly used type
- ❖ The *JK* is another type of Flip-Flop with inputs: *J*, *K*, and *Clk*
- ❖ When $JK = 10 \rightarrow \text{Set}$, When $JK = 01 \rightarrow \text{Reset}$
- ❖ When $JK = 00 \rightarrow \text{No change}$, When $JK = 11 \rightarrow \text{Invert outputs}$
- ❖ *JK* can be implemented using D-FF and gates



| J | K | Q_{t+1} |
|---|---|-------------|
| 0 | 0 | Q_t |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | \bar{Q}_t |

JK Flip-Flop Timing Diagram

 

| J | K | Q_{t+1} |
|---|---|-------------|
| 0 | 0 | Q_t |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | \bar{Q}_t |

Characteristic Equation of the JK Flip-Flop

| J | K | Q_{t+1} |
|---|---|------------------|
| 0 | 0 | Q_t |
| 0 | 1 | 0 |
| 1 | 0 | 1 |
| 1 | 1 | \overline{Q}_t |

| $Q(t)$ | J | K | $Q(t+1)$ |
|--------|---|---|----------|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 0 |

| | | J | | | |
|---|---|----|----|----|----|
| | | 00 | 01 | 11 | 10 |
| Q | 0 | | | 1 | 1 |
| | 1 | 1 | | | 1 |


K

$$Q(t+1) = JQ' + K'Q$$


T Flip-Flop

- ❖ The T (Toggle) flip-flop has inputs: T and Clk
- ❖ When $T = 0 \rightarrow$ No change,
- ❖ When $T = 1 \rightarrow$ Invert outputs
- ❖ The T flip-flop can be implemented using a JK flip-flop
- ❖ It can also be implemented using a D flip-flop and a XOR gate


| T | Q_{t+1} |
|-----|------------------|
| 0 | Q_t |
| 1 | \overline{Q}_t |

 

(a) From JK flip-flop

 


(b) From D flip-flop

 

(c) Graphic symbol


T Flip-Flop Timing Diagram

 

| T | Q_{t+1} |
|---|------------------|
| 0 | Q_t |
| 1 | \overline{Q}_t |

Characteristic Equation of the T-Flip Flop

| $Q(t)$ | T | $Q(t+1)$ |
|--------|-----|----------|
| 0 | 0 | 0 |
| 0 | 1 | 1 |
| 1 | 0 | 1 |
| 1 | 1 | 0 |

 

$$Q(t+1) = TQ' + T'Q$$

| T | Q_{t+1} |
|-----|------------------|
| 0 | Q_t |
| 1 | \overline{Q}_t |

Flip-Flop Characteristic Table

- ❖ Defines the operation of a flip-flop in a tabular form
- ❖ Next state is defined in terms of the current state and the inputs

$Q(t)$ refers to current state **before** the clock edge arrives

$Q(t + 1)$ refers to next state **after** the clock edge arrives

| D Flip-Flop | | |
|-------------|----------|-------|
| D | $Q(t+1)$ | |
| 0 | 0 | Reset |
| 1 | 1 | Set |

| JK Flip-Flop | | | |
|--------------|-----|----------|------------|
| J | K | $Q(t+1)$ | |
| 0 | 0 | $Q(t)$ | No change |
| 0 | 1 | 0 | Reset |
| 1 | 0 | 1 | Set |
| 1 | 1 | $Q'(t)$ | Complement |

| T Flip-Flop | | |
|-------------|----------|------------|
| T | $Q(t+1)$ | |
| 0 | $Q(t)$ | No change |
| 1 | $Q'(t)$ | Complement |

Flip-Flop Characteristic Equation

- ❖ The characteristic equation defines the operation of a flip-flop
- ❖ For D Flip-Flop: $Q(t + 1) = D$
- ❖ For JK Flip-Flop: $Q(t + 1) = J Q'(t) + K' Q(t)$
- ❖ For T Flip-Flop: $Q(t + 1) = T \oplus Q(t)$
- ❖ Clearly, the D Flip-Flop is the simplest among the three


| D Flip-Flop | |
|-------------|----------|
| D | $Q(t+1)$ |
| 0 | 0 Reset |
| 1 | 1 Set |

| JK Flip-Flop | |
|--------------|--------------------|
| $J \ K$ | $Q(t+1)$ |
| 0 0 | $Q(t)$ No change |
| 0 1 | 0 Reset |
| 1 0 | 1 Set |
| 1 1 | $Q'(t)$ Complement |

| T Flip-Flop | |
|-------------|--------------------|
| T | $Q(t+1)$ |
| 0 | $Q(t)$ No change |
| 1 | $Q'(t)$ Complement |

Timing Considerations for Flip-Flops

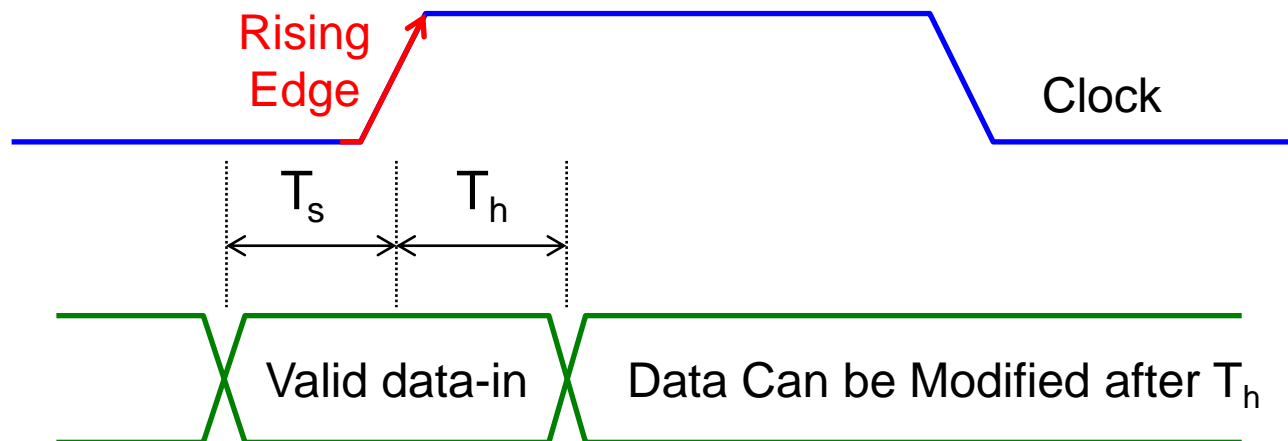- ❖ **Setup Time (T_s):** Time duration for which the data input must be valid and stable **before** the arrival of the clock edge.
- ❖ **Hold Time (T_h):** Time duration for which the data input must not be changed **after** the clock transition occurs.
- ❖ T_s and T_h must be ensured for the proper operation of flip-flops



Summary

- ❖ In a sequential circuit there is internal memory
 - ✧ Output is a function of current inputs and present state
 - ✧ The stored memory value defines the present state
 - ✧ Similarly, the next state depends on current inputs and present state
- ❖ Two types of sequential circuits:
 - ✧ Synchronous sequential circuits are clocked (easier to implement)
 - ✧ Asynchronous sequential circuits are not clocked
- ❖ Two types of Memory elements: Latches and Flip-Flops
- ❖ Latches are level-sensitive, flip-flops are edge-triggered
- ❖ Flip-flops are better memory elements for synchronous circuits
- ❖ A flip-flop is described using a characteristic table and equation

Next . . .

- ❖ Introduction to Sequential Circuits
 - ✧ Combinational versus Sequential Circuits
 - ✧ Synchronous versus Asynchronous Sequential Circuits
- ❖ Storage Elements
 - ✧ Latches
 - ✧ Flip-Flops
- ❖ **Analysis of Clocked Sequential circuits**
 - ✧ **State and Output Equations**
 - ✧ **State Table**
 - ✧ **State Diagram**
- ❖ Mealy versus Moore Sequential Circuits

Analysis of Clocked Sequential Circuits

Analysis is describing what a given circuit will do

The output of a clocked sequential circuit is determined by

1. Inputs
2. State of the Flip-Flops

Analysis Procedure:

1. Obtain the equations at the inputs of the Flip-Flops
2. Obtain the next state and the output equations
3. Fill the state table for all possible input and state values
4. Draw the state diagram

Analysis Example

❖ Is this a clocked sequential circuit?

YES!

❖ What type of Memory?

D Flip-Flops

❖ How many state variables?


Two state variables: A and B

❖ What are the Inputs?

One Input: x

❖ What are the Outputs?

One Output: y

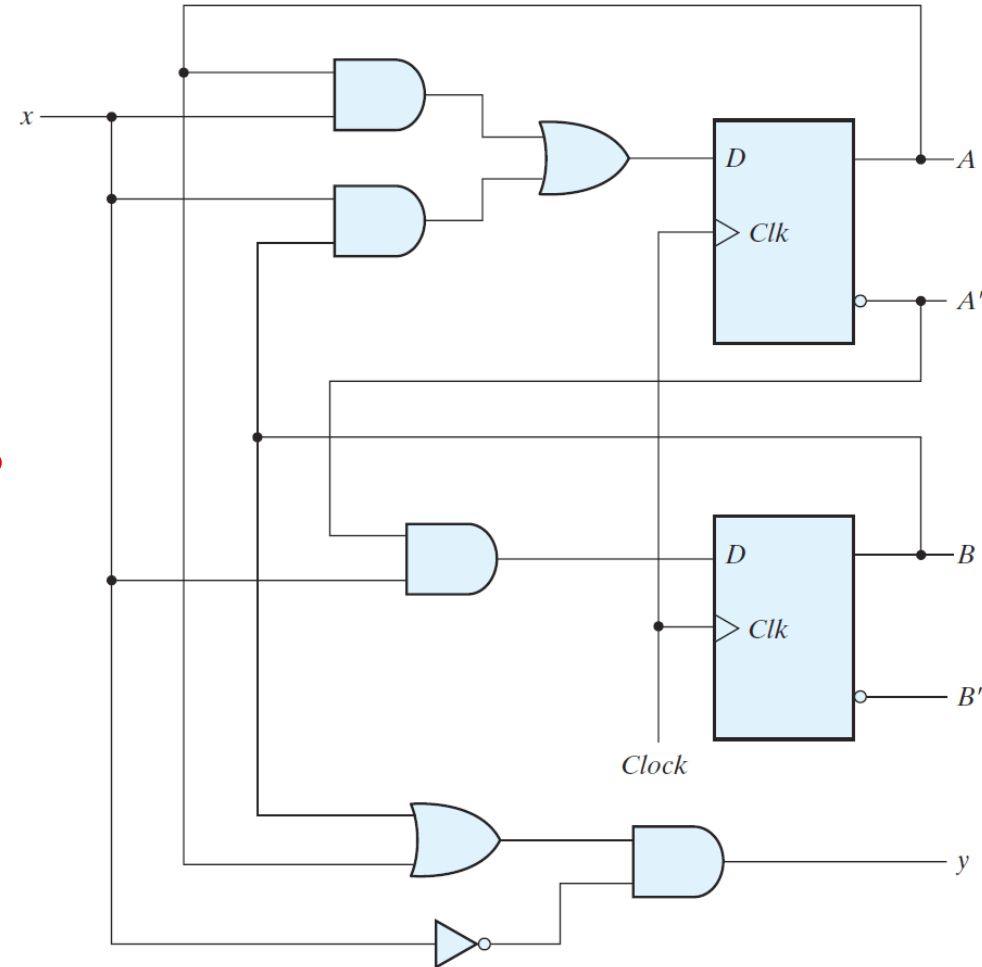

Flip-Flop Input Equations

❖ What are the equations on the D inputs of the flip-flops?

$$D_A = A x + B x$$

$$D_B = A' x$$


❖ A and B are the **current state**

$$A(t) = A, \quad B(t) = B$$

❖ D_A and D_B are the **next state**

$$A(t + 1) = D_A, \quad B(t + 1) = D_B$$

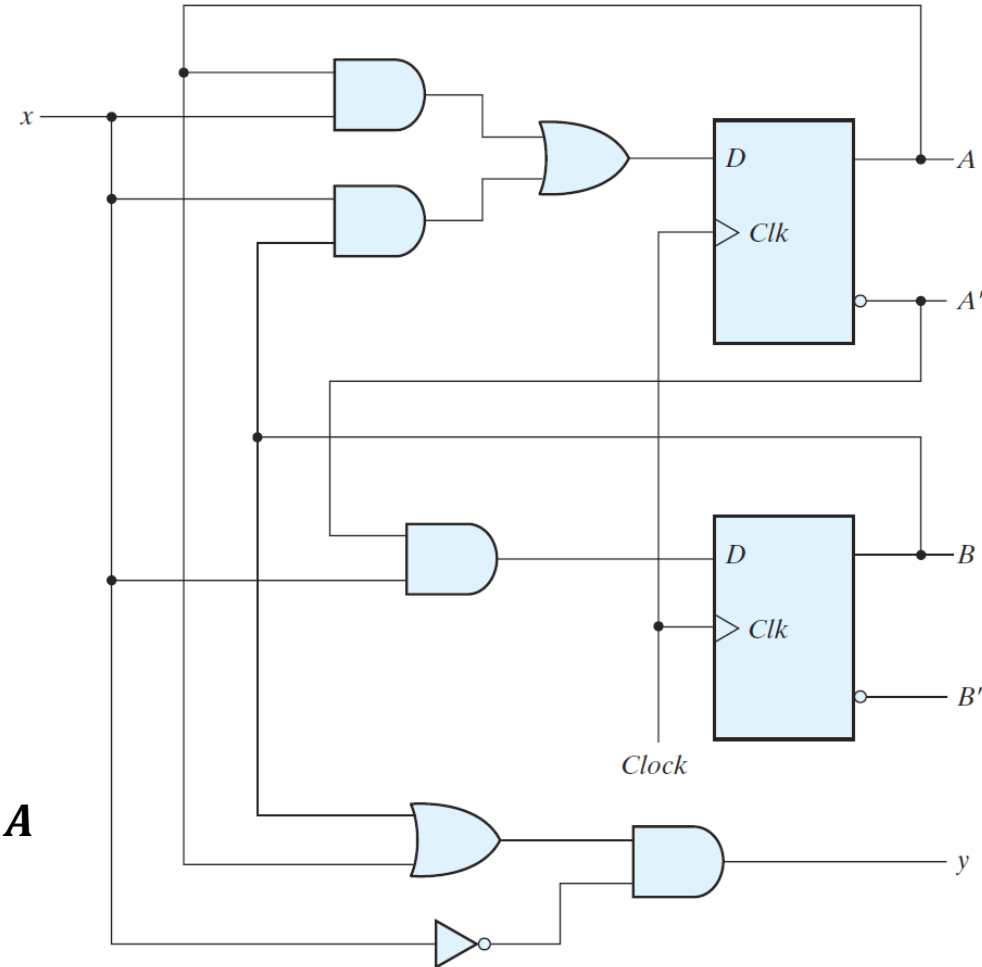❖ The values of A and B will be D_A and D_B at the next clock edge



Next State and Output Equations

- ❖ The next state equations define the **next state**

At the **inputs** of the Flip-Flops


- ❖ Next state equations?

$$A(t + 1) = D_A = A x + B x$$

$$B(t + 1) = D_B = A' x$$

- ❖ There is only one output y
- ❖ What is the output equation?

$$y = (A + B) x'$$

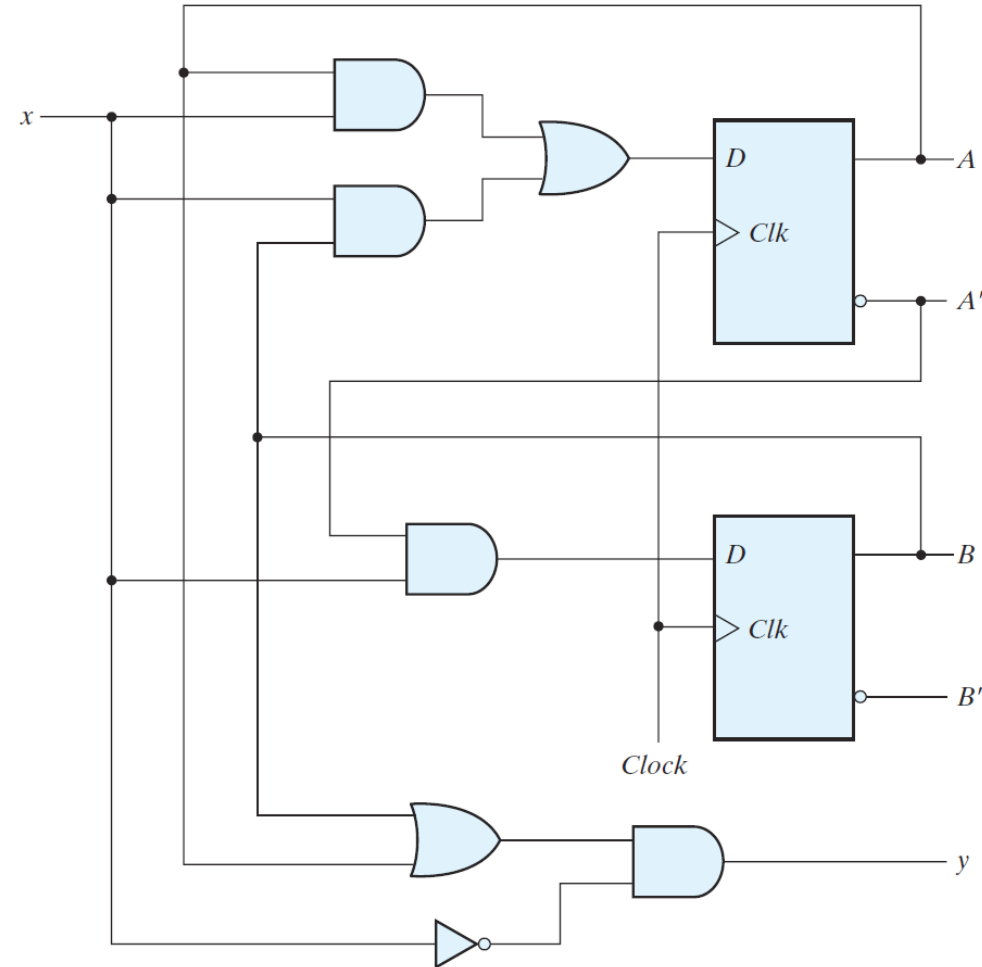

State Table

- ❖ State table shows the Next State and Output in a tabular form
- ❖ Next State Equations: $A(t + 1) = A x + B x$ and $B(t + 1) = A' x$
- ❖ Output Equation: $y = (A + B) x'$

| Present State | | Input x | Next State | | Output y |
|---------------|-----|--------------|------------|-----|---------------|
| A | B | | A | B | |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 0 | 1 |
| 0 | 1 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 | 0 |

Another form of the state table


| Present State | | Next State | | | | Output | |
|---------------|---|------------|-----|---------|-----|---------|---------|
| | | $x = 0$ | | $x = 1$ | | $x = 0$ | $x = 1$ |
| | | A | B | A | B | y | y |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |

State Diagram

- ❖ State diagram is a graphical representation of a state table
- ❖ The circles are the states
- ❖ Two state variable \rightarrow Four states (ALL values of A and B)
- ❖ Arcs are the state transitions

Labeled with: Input x / Output y

| Present State | | Next State | | | | Output | |
|---------------|-----|------------|-----|---------|-----|---------|---------|
| | | $x = 0$ | | $x = 1$ | | $x = 0$ | $x = 1$ |
| A | B | A | B | A | B | y | y |
| 0 | 0 | 0 | 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 | 1 | 0 | 1 | 0 |

 

Combinational versus Sequential Analysis

Analysis of Combinational Circuits

- ❖ Obtain the Boolean Equations
- ❖ Fill the Truth Table

Output is a function of input only

Analysis of Sequential Circuits


- ❖ Obtain the Next State Equations
- ❖ Obtain the Output Equations
- ❖ Fill the State Table
- ❖ Draw the State Diagram

Next state is a function of input and current state


Output is a function of input and current state

 Example with Output = Current State

- ❖ Analyze the sequential circuit shown below
- ❖ Two inputs: x and y
- ❖ One state variable A
- ❖ No separate output \rightarrow Output = current state A
- ❖ Obtain the next state equation, state table, and state diagram




Example with Output = Current State

 

❖ Flip-Flop Input Equation:


$$D_A = A \oplus x \oplus y$$

 ❖ Next State Equation: $A(t + 1) = A \oplus x \oplus y$



| Present state | Inputs | | Next state |
|---------------|--------|---|------------|
| A | x | y | A |
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 1 |
| 0 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

Sequential Circuit with T Flip-Flops

 

Circuit has two T Flip-Flops

One Input x

One output y

Two state variables: A and B

Obtain the T-FF input equations

Obtain the next state equations

Fill the state table

Draw the state diagram

Recall: Flip-Flop Characteristic Equation

❖ For D Flip-Flop: $Q(t + 1) = D$

❖ For T Flip-Flop: $Q(t + 1) = T \oplus Q(t)$

❖ For JK Flip-Flop: $Q(t + 1) = J Q'(t) + K' Q(t)$


These equations
define the Next State

| D Flip-Flop | | |
|-------------|----------|-------|
| D | $Q(t+1)$ | |
| 0 | 0 | Reset |
| 1 | 1 | Set |

| T Flip-Flop | | |
|-------------|----------|------------|
| T | $Q(t+1)$ | |
| 0 | $Q(t)$ | No change |
| 1 | $Q'(t)$ | Complement |

| JK Flip-Flop | | | |
|--------------|-----|----------|------------|
| J | K | $Q(t+1)$ | |
| 0 | 0 | $Q(t)$ | No change |
| 0 | 1 | 0 | Reset |
| 1 | 0 | 1 | Set |
| 1 | 1 | $Q'(t)$ | Complement |

Sequential Circuit with T Flip-Flops

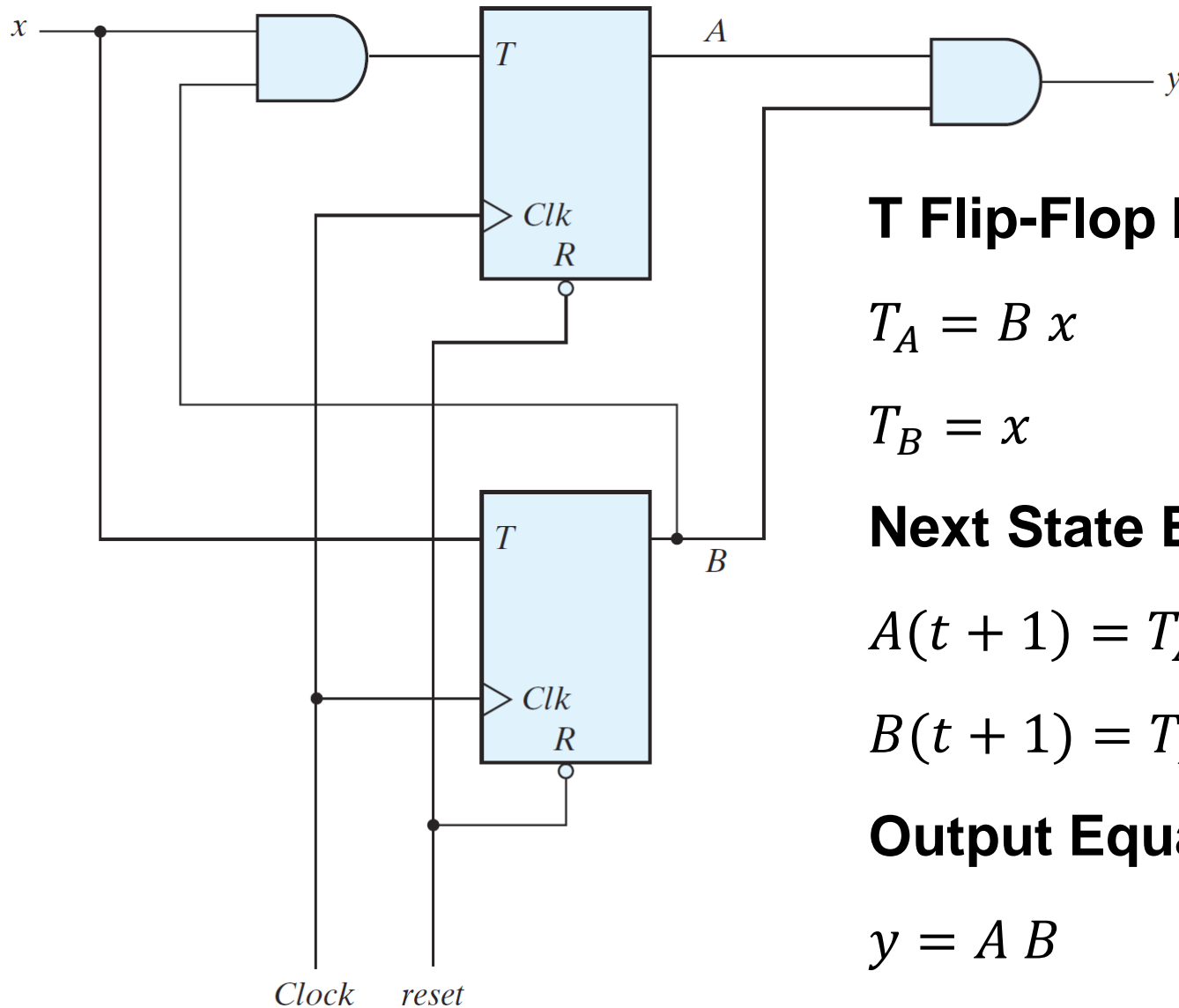

T Flip-Flop Input Equations:

$$T_A = B x$$

$$T_B = x$$

Next State Equations:

$$A(t + 1) = T_A \oplus A = (B x) \oplus A$$

$$B(t + 1) = T_B \oplus B = x \oplus B$$

Output Equation:

$$y = A B$$

From Next State Equations to State Table

T Flip-Flop Input Equations:

$$T_A = B x$$

$$T_B = x$$

Next State Equations:

$$A(t + 1) = (B x) \oplus A$$

$$B(t + 1) = x \oplus B$$

Output Equation:

$$y = A B$$


| Present State | | Input | Next State | | Output |
|---------------|---|-------|------------|---|--------|
| A | B | | A | B | |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 |

Notice that the output is a function of the present state only.

It does **NOT** depend on the input x

From State Table to State Diagram

| Present State | | Input x | Next State | | Output y |
|---------------|-----|--------------|------------|-----|---------------|
| A | B | | A | B | |
| 0 | 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 | 0 |
| 1 | 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 1 | 0 | 0 | 1 |

 

- ❖ Four States: $AB = 00, 01, 10, 11$ (drawn as circles)
- ❖ Output Equation: $y = A B$ (does not depend on input x)
- ❖ Output y is shown inside the state circle (AB/y)

Sequential Circuit with a JK Flip-Flops

One Input x and two state variables: A and B (outputs of Flip-Flops)


No separate output \rightarrow Output = Current state $A B$

Obtain the JK input equations

Obtain the next state equations

Fill the state table

Draw the state diagram

 

JK Input and Next State Equations

JK Flip-Flop Input Equations:

$$J_A = B \text{ and } K_A = B x'$$

$$J_B = x' \text{ and } K_B = A \oplus x$$

Next State Equations:


$$A(t + 1) = J_A A' + K_A' A$$

$$B(t + 1) = J_B B' + K_B' B$$

Substituting:

$$A(t + 1) = B A' + (B x')' A = A' B + A B' + A x$$
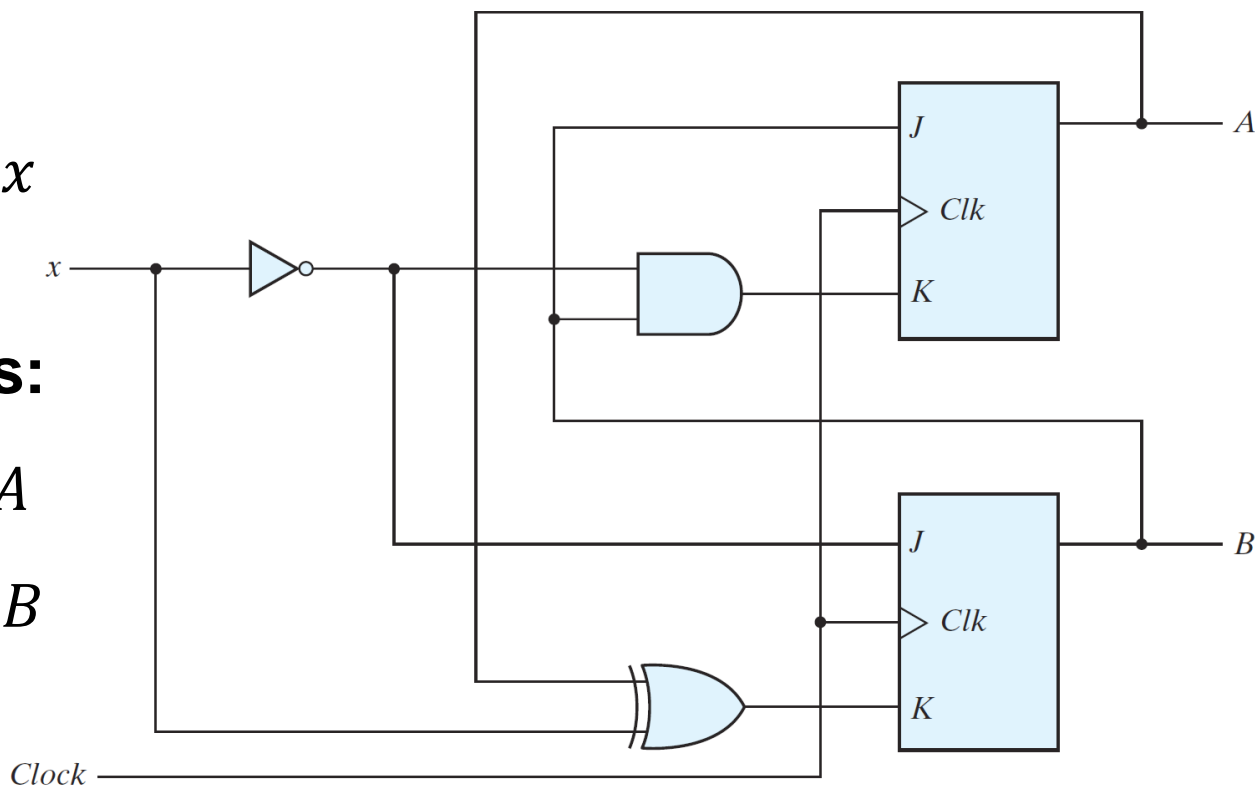
$$B(t + 1) = x' B' + (A \oplus x)' B = B' x' + A B x + A' B x'$$



From JK Input Equations to State Table

JK Input Equations: $J_A = B$, $K_A = B x'$, $J_B = x'$ and $K_B = A \oplus x$


| Present State | | Input | Next State | | Flip-Flop Inputs | | | |
|---------------|---|-------|------------|---|------------------|-------|-------|-------|
| A | B | | A | B | J_A | K_A | J_B | K_B |
| 0 | 0 | 0 | 0 | 1 | 0 | 0 | 1 | 0 |
| 0 | 0 | 1 | 0 | 0 | 0 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 | 0 |
| 0 | 1 | 1 | 1 | 0 | 1 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 | 0 |
| 1 | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 |
| 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 |

From State Table to State Diagram

Four states: $A B = 00, 01, 10, \text{ and } 11$ (drawn as circles)

Arcs show the input value x on the state transition

| Present State | | Input x | Next State | |
|---------------|-----|--------------|------------|-----|
| A | B | | A | B |
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 1 | 0 | 0 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 1 | 1 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

 



Next . . .

- ❖ Introduction to Sequential Circuits
 - ✧ Combinational versus Sequential Circuits
 - ✧ Synchronous versus Asynchronous Sequential Circuits
- ❖ Storage Elements
 - ✧ Latches
 - ✧ Flip-Flops
- ❖ Analysis of Clocked Sequential circuits
 - ✧ State and Output Equations
 - ✧ State Table
 - ✧ State Diagram
- ❖ **Mealy versus Moore Sequential Circuits**

Mealy versus Moore Sequential Circuits

There are two ways to design a clocked sequential circuit:

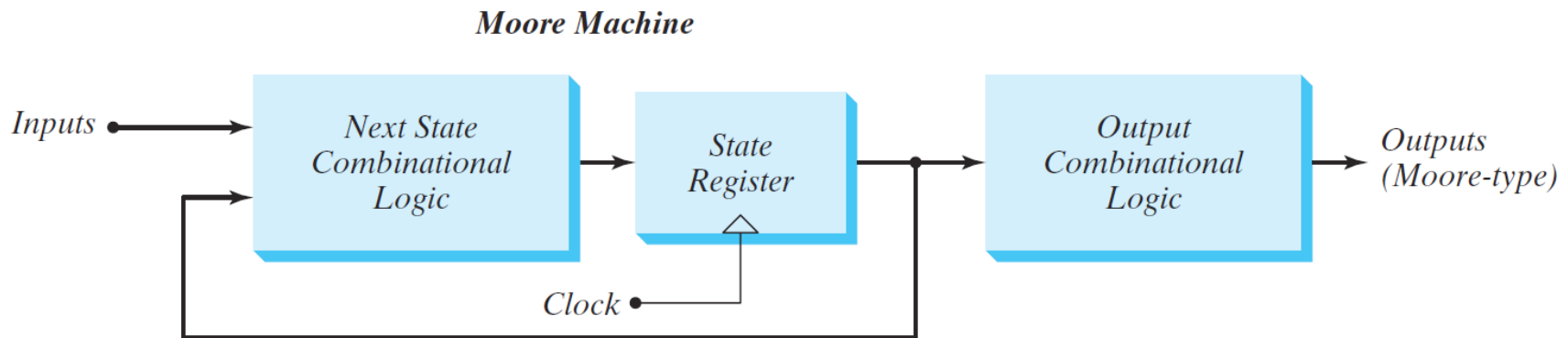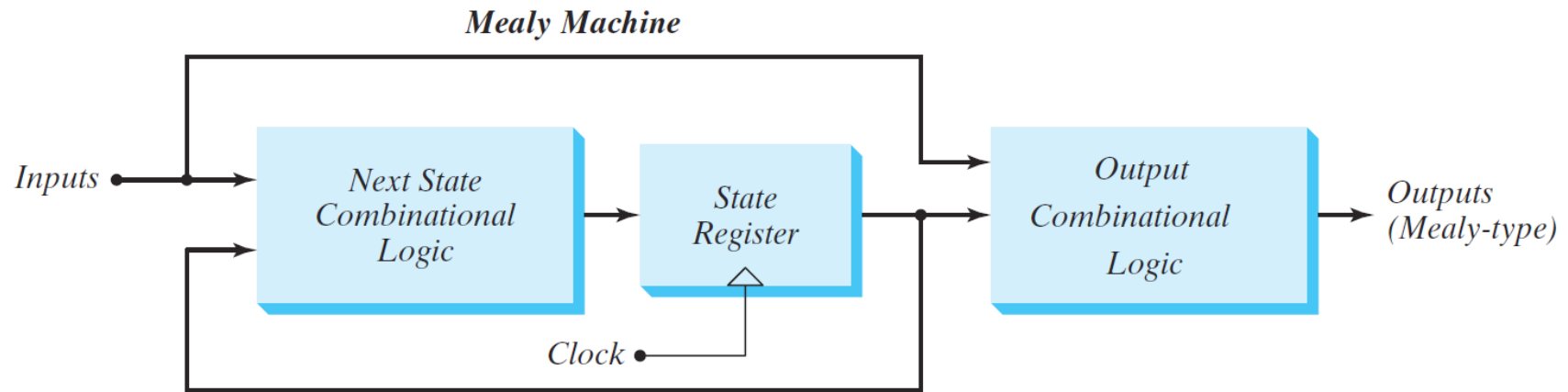
- 1. Mealy Machine:** Outputs depend on present state and inputs
- 2. Moore Machine:** Outputs depend on present state only




Mealy Machine

- ❖ The outputs are a function of the present state and Inputs
- ❖ The outputs are **NOT** synchronized with the clock
- ❖ The outputs may change if inputs change during the clock cycle
- ❖ The outputs may have momentary false values (called glitches)
- ❖ The correct outputs are present just before the edge of the clock

Mealy Machine

 


Example of Mealy Model

 


Mealy State Diagram

 - ❖ An example of a Mealy state diagram is shown on the right
- ❖ Each arc is labeled with:
Input / Output
- ❖ The output is shown on the arcs of the state diagram
- ❖ The output depends on the current state and input
- ❖ Notice that State 11 cannot be reached from the other states



Tracing a Mealy State Diagram



| Cycle | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 |
|-------------------|---|---|---|---|---|---|---|---|---|
| Input x | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| Present State A B | ? | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| Output z | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |

 

- ❖ When the circuit is powered, the initial state (AB) is unknown
- ❖ Even though the initial state is unknown, the input $x = 0$ forces a transition to state $AB = 00$, regardless of the present state
- ❖ Sometimes, a reset input is used to initialize the state to 00


False Output in the Timing Diagram

| Cycle | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 |
|-------------------|---|---|---|---|---|---|---|---|---|
| Input x | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| Present State A B | ? | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| Output z | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 | 0 |

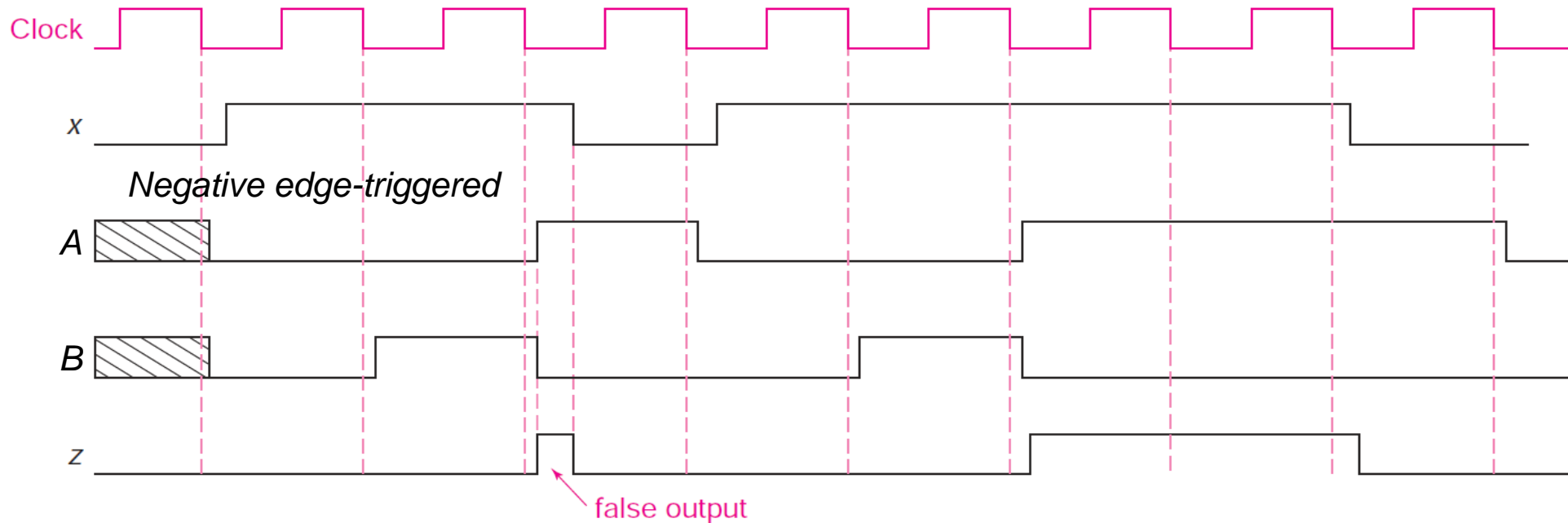 

Moore Machine

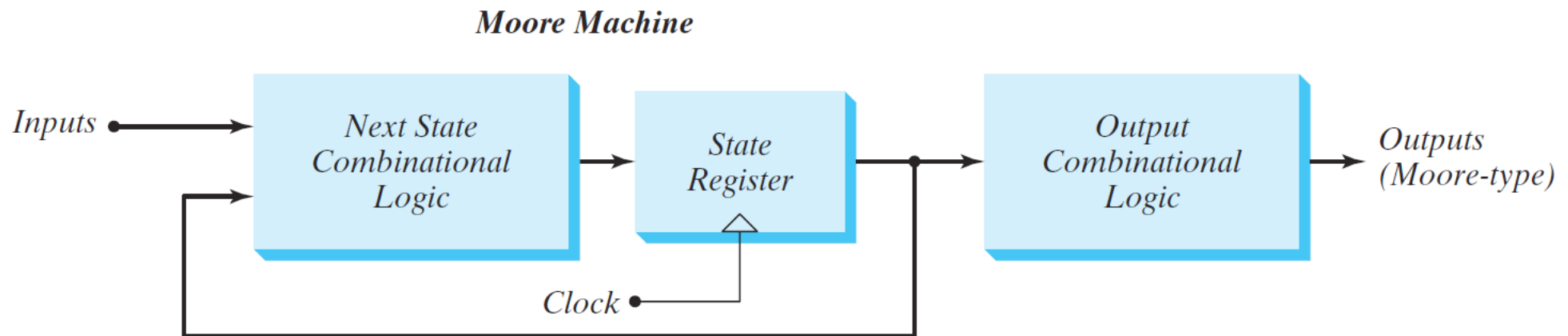- ❖ The outputs are a function of the Flip-Flop outputs only
- ❖ The outputs depend on the current state only
- ❖ The outputs are synchronized with the clock
- ❖ Glitches cannot appear in the outputs (even if inputs change)
- ❖ A given design might mix between Mealy and Moore




Sequential Circuit with JK Flip-Flop



Moore State Diagram

 
- ❖ An example of a Moore state diagram is shown on the right
- ❖ Arcs are labeled with input only
- ❖ The output is shown inside the state: (State / Output)
- ❖ The output depends on the current state only



Tracing a Moore State Diagram

- ❖ When the circuit is powered, the initial state (AB) and output are unknown
- ❖ Input $x = 0$ resets the state AB to 00.
Can also be done with a reset signal.


| Cycle | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 |
|---------------------|---|---|---|---|---|---|---|---|---|
| Input x | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| Present State $A B$ | ? | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| Output z | ? | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |

 

Timing Diagram of a Moore Machine

| Cycle | 0 | 1 | 2 | 3 | 4 | 5 | 6 | 7 | 8 |
|-------------------|---|---|---|---|---|---|---|---|---|
| Input x | 0 | 1 | 1 | 0 | 1 | 1 | 1 | 1 | 0 |
| Present State A B | ? | 0 | 0 | 1 | 0 | 0 | 1 | 1 | 1 |
| Output z | ? | 0 | 0 | 0 | 0 | 0 | 0 | 1 | 1 |

 The output is synchronized with the clock. No false output (or glitch) can appear.



Summary

❖ To analyze a clocked sequential circuit:

1. Obtain the equations at the **Inputs** of the flip-flops

2. Obtain the **Next State** equations

✧ For a D Flip-Flop, the Next State = D input equation

✧ For T and JK, use the characteristic equation of the Flip-Flop

3. Obtain the **Output** equations

4. Fill the **State Table**

✧ Put all the combinations of current state and input

✧ Fill the next state and output columns

5. Draw the **State Diagram**

❖ Two types of clocked sequential circuits: **Mealy** versus **Moore**