

ENEE2360 Analog Electronics


T11: Voltage Regulators

Instructor : Nasser Ismail

1

Dc Power Supply


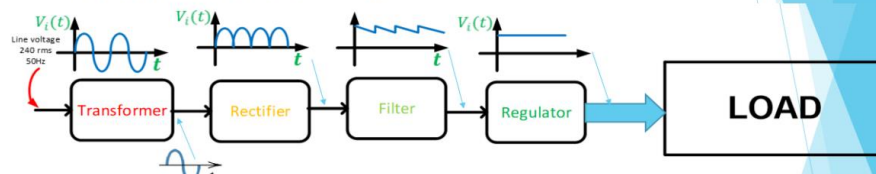
- ▶ All electronic circuits and systems require a stable source of dc voltage and current (or dc power) to operate correctly.



Transformer: Used to increase or decrease the amplitude of the ac line voltage
Rectifier: used to convert the ac voltage (zero- average value) into either positive and negative pulsating dc.
Filter : used to smooth out the pulsating dc produced by the rectifier by removing its ac ripple contents and passing its dc component (average value)
Regulator: used to maintain a constant DC output voltage under variations in the load current drawn from the supply and under variation in AC line voltage

Voltage Regulator


Simple Voltage Regulator

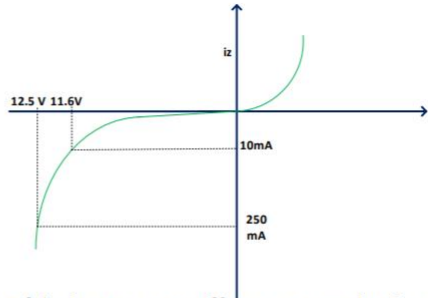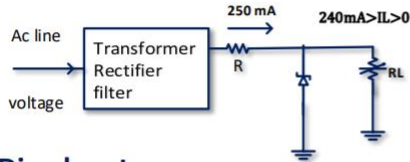

Disadvantages:


1. Variation in I_L will cause I_z to vary. This in turn will cause variation in $V_z = V_o$
2. The Zener power dissipation will increase as I_L decreases.

Types of Regulators

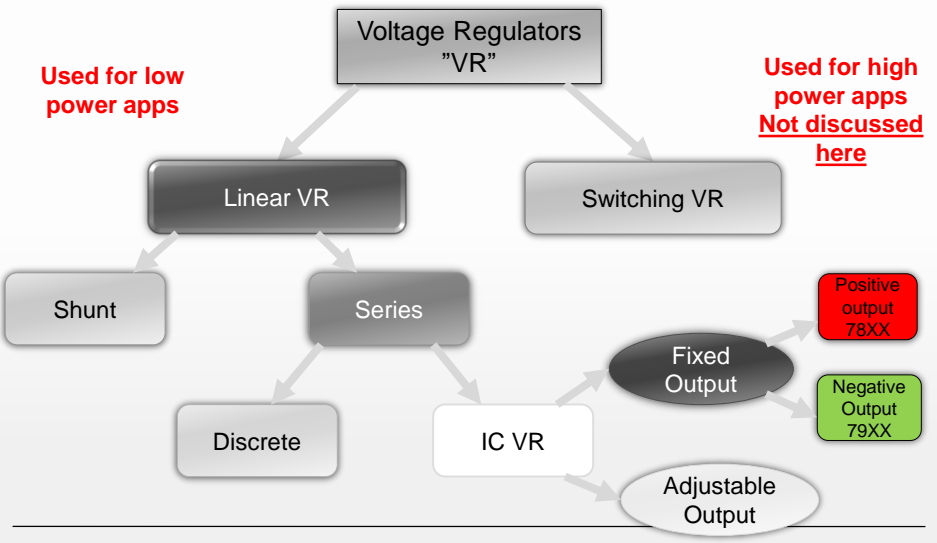


Types of Regulator

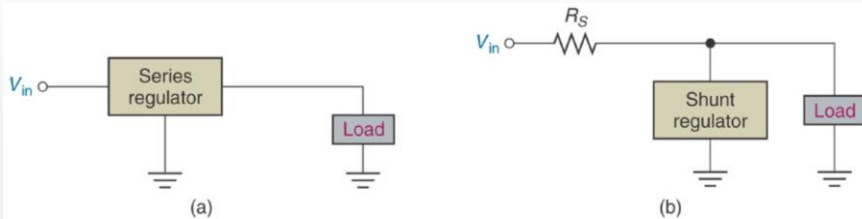
- Fundamental classes of voltage regulators are **linear regulators** and **switching regulators**.
- Two basic types of linear regulator are the **series regulator** and the **shunt regulator**.
- The series regulator is connected in **series** with the load and the shunt regulator is connected in **parallel** with the load.



Types of Regulator

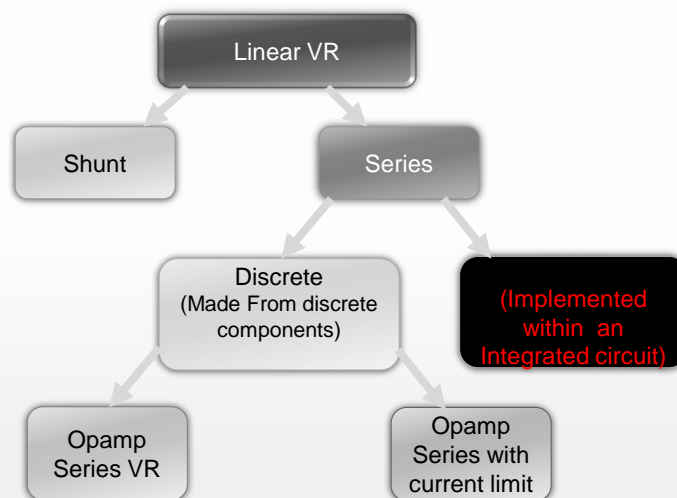

Opamp Series VR

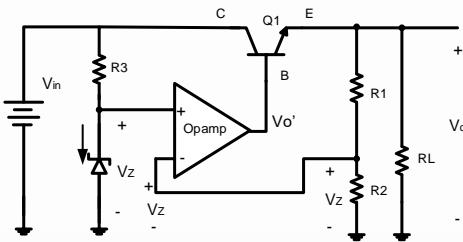


$$V_i = V_o + V_{CE}$$

$$V_o' = A_d V_d$$

$$= A_d \left(V_Z - \frac{R_2}{R_2 + R_1} V_o \right)$$

If $V_o \downarrow, V_o' \uparrow, V_{be} \uparrow, I_E \uparrow, V_o \uparrow$

Opamp Series VR

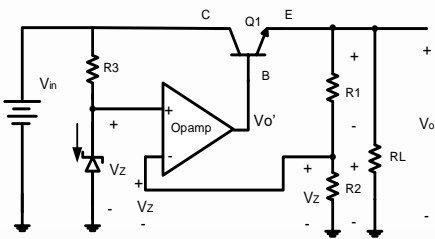

Resistors R_1, R_2 are for sampling of V_o

(the current through these resistors must be small)

$$V_o = V_{R1} + V_{R2}$$

$$I_{R1} = I_{R2} = I$$

$$V_{R2} = V_Z$$

$$I = \frac{V_Z}{R_2}$$


$$V_Z = V_o \frac{R_2}{R_1 + R_2}$$

$$V_o = V_Z \left(1 + \frac{R_1}{R_2} \right)$$

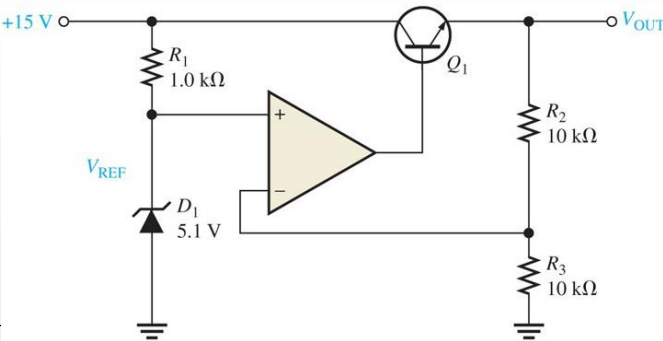Example

- Determine the output voltage for the regulator below.


$$V_o = \left(1 + \frac{R_2}{R_3}\right) V_Z \quad \Rightarrow \quad V_o = \left(1 + \frac{10k}{10k}\right) 5.1 = 10.2 \text{ V}$$



Practical DC Power supply


Determine the output voltage for the regulator below if
 $R_3 = R_2 = 10K$ and $V_z = 5.1V$
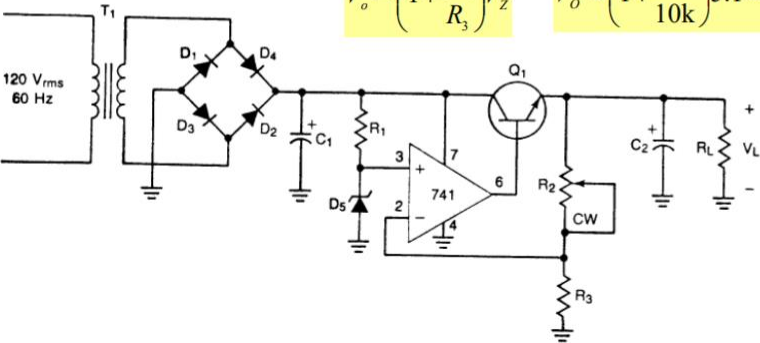
$$V_o = \left(1 + \frac{R_2}{R_3}\right) V_z \quad V_o = \left(1 + \frac{10k}{10k}\right) 5.1 = 10.2 \text{ V}$$



Choosing the right Transistor

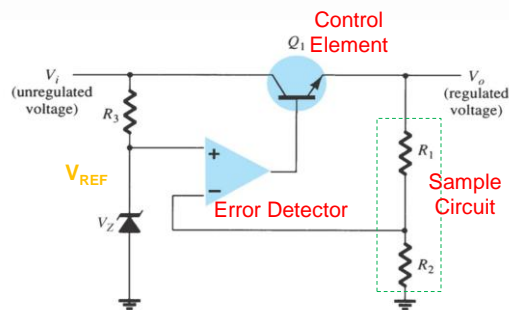
- The transistor must be chosen such that its power rating is suitable
- $P_Q > \text{or} = V_{CE} * I_E$ **otherwise BJT will be damaged**
- $V_{CE} = V_C - V_E = V_{in} - V_o$
- $I_E = I_L + I_{R1}$, but $I_L \gg I_{R1}$



Opamp Series VR with current limit

Current Limiting Circuit

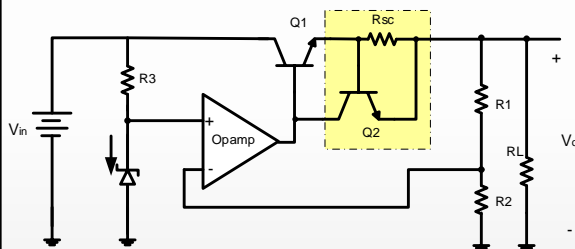
In order to protect the transistor from damage when a very high current passes through it due to a short circuit or excessive current demand at the load



1) In normal operation Q2 is off since $V_{be2} = V_{R_{SC}} < 0.7 \text{ V}$

$$2) R_{SC} = \frac{V_{be}}{I_{L(\text{Max})}} = \frac{0.7 \text{ V}}{I_{L(\text{Max})}}$$

Opamp Series with current limit

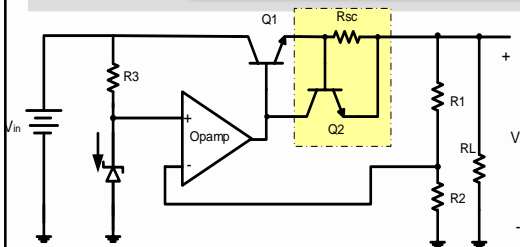

3) When $I > I_{L(Max)}$,
Q2 conducts since
 $V_{be2} = V_{Rsc} \cong 0.7 \text{ V}$

4) Some of I_{B1} is diverted through Q2 (I_{C2})

I_{B1} is reduced so that I_L is limited to a maximum value

$$\text{calculated as : } I_{L(Max)} = \frac{V_{be}}{R_{SC}} = \frac{0.7 \text{ V}}{R_{SC}}$$

5) Since V_{be2} cannot exceed 0.7 V , V_{Rsc} is limited

6) This is constant current limiting

Op-Amp Shunt Regulator

An Op-amp used in Shunt voltage regulators


$$V_o = V_z \left(1 + \frac{R_1}{R_2} \right)$$

Operation:

$$V_{op} = A_d V_d$$

$$V_{op} = A_d \left(\frac{R_2}{R_1 + R_2} V_o - V_z \right)$$


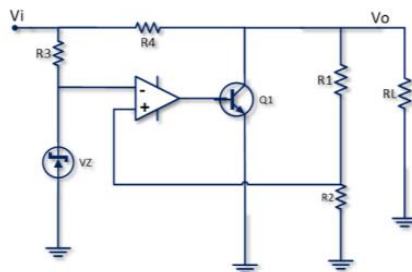
IF $V_o \downarrow$ $V(+)$ \downarrow $V_{op} \downarrow$ $V_{BE} \downarrow$



$$V_{BE} = V_{op}$$

$$I_C = I_S \left(e^{\frac{V_{BE}}{\eta V_T}} - 1 \right)$$

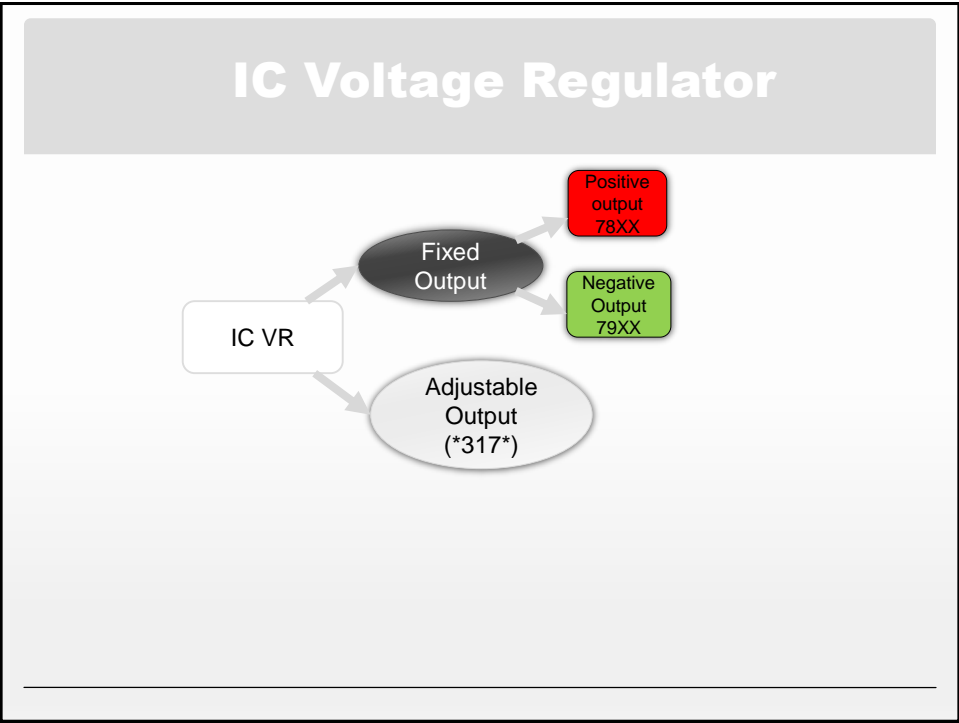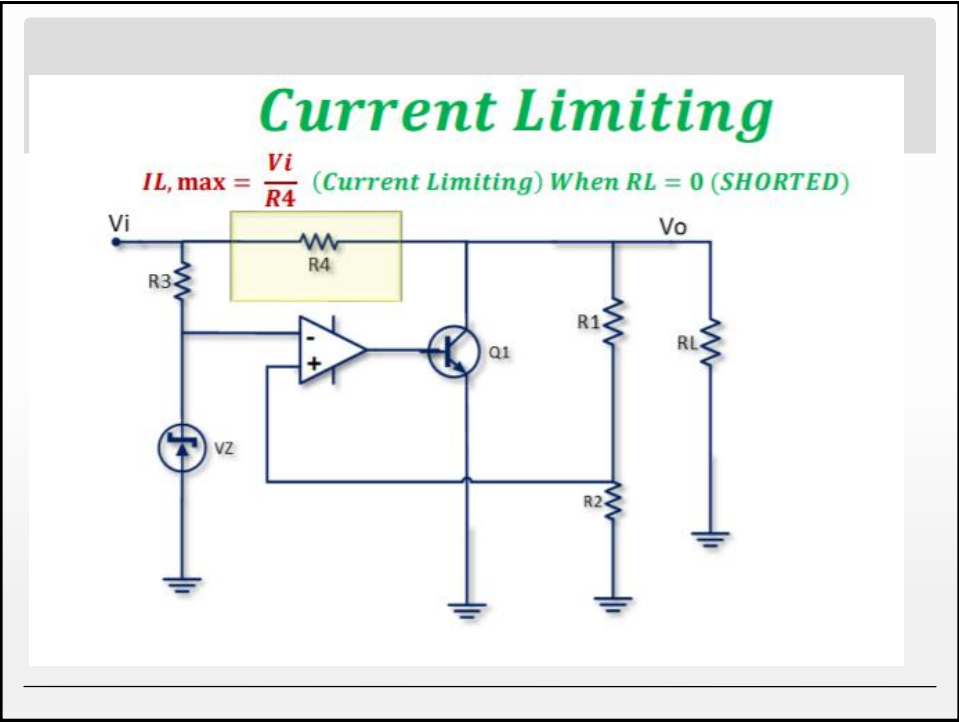\therefore The transistor conduct Less, $I_c \downarrow$, $I_L \uparrow$ $V_o \uparrow$



Three Terminal Circuit Regulators



1- Fixed voltage regulator

a-78xx

- 7805.....5 V
- 7812.....12 V
- 7815.....15V

b- 79xx

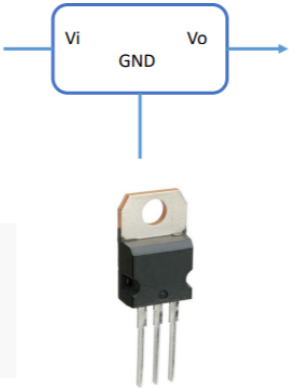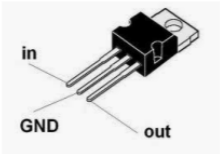- 7905..... -5 V
- 7912..... -12 V
- 7915..... -15V



Fixed Voltage Regulator

Positive-Voltage Regulators in the 78XX Series


IC Part	Output Voltage (V)	Minimum V_i (V)
7805	+5	+7.3
7806	+6	+8.3
7808	+8	+10.5
7810	+10	+12.5
7812	+12	+14.5
7815	+15	+17.7
7818	+18	+21.0
7824	+24	+27.1

V_{in} must be higher than V_o by at least 2V for proper operation of the voltage regulator


Fixed Voltage Regulator

Negative-Voltage Regulators in the 79XX Series

IC Part	Output Voltage (V)	Minimum V_i (V)
7905	-5	-7.3
7906	-6	-8.4
7908	-8	-10.5
7909	-9	-11.5
7912	-12	-14.6
7915	-15	-17.7
7918	-18	-20.8
7924	-24	-27.1

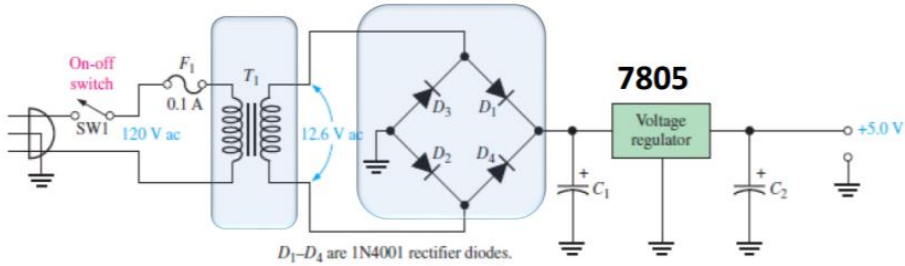

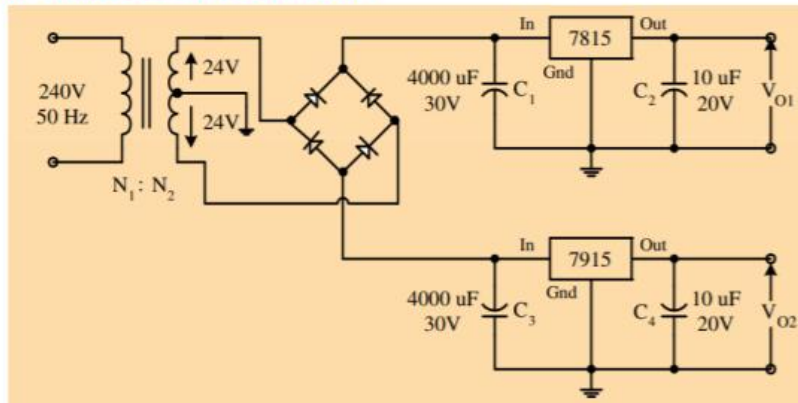Three Terminal Circuit Regulators Dual Polarity Dc Power Supply



Changing the fixed Voltage Regulator to adjustable


$$V_O = V_{REG} + R_2 I_2$$

$$V_O = V_{REG} + R_2 (I_1 + I_Q)$$

$$I_1 = \frac{V_{REG}}{R_1}$$


$$\therefore V_O = V_{REG} \left(1 + \frac{R_2}{R_1}\right) + R_2 I_Q$$

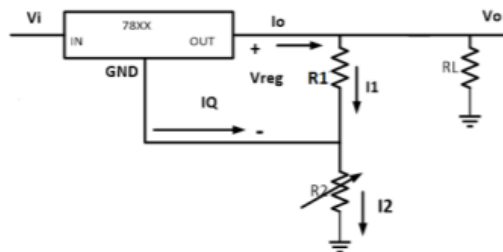I_Q is in milliampere and change with temperature



Adjustable Voltage Regulator based on 78xx family

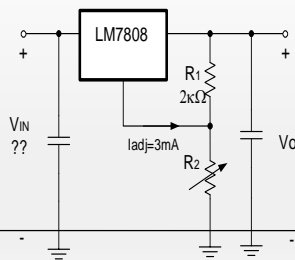- Find the minimum and maximum output voltage (V_o) for the following IC voltage regulator. Note that R_2 is a variable resistor that can be varied from 0 to $3k\Omega$
- What is the range of values of V_{IN} required for proper operation of the circuit
- What is the power dissipation of the LM7808 when $V_o = V_o(\min)$ and $V_{in} = V_{in}(\max)$ and load current $= 0.25A$



Solution **Voltage Regulators**

$$V_{o(MIN)} = V_{REG} = 8V \quad (\text{when } R_2 = 0\Omega)$$

$$V_{o(MAX)} = V_{R1} + V_{R2} = I_{REG}(R_1) + (I_{REG} + I_{adj})(R_2)$$

$$I_{REG} = \frac{V_{REG}}{R_1}$$

$$V_{o(MAX)} |_{R2=3k\Omega} = \frac{V_{REG}}{R_1}(R_1 + R_2) + I_{adj}(R_2)$$

$$= \frac{8V}{2k\Omega}(2k\Omega + 3k\Omega) + 3mA.(3k\Omega)$$

$$= (4mA).(5k\Omega) + 9V = 29V$$

Voltage Regulators

• Solution

V_{IN} must be higher than V_O by at least 2 volts

when $V_O = 8V$, $V_{IN(MIN)} = 8 + 2 = 10V$

when $V_O = 29V$, $V_{IN(MAN)} = 29 + 2 = 31V$

Power Dissipation of LM7808:


$$P_{(LM7808)} \cong (V_{IN} - V_O) * I_L = (31 - 8) * 0.25 = 5.75 W$$

ENEE236 Analog Electronics
Nasser Ismail

Adjustable-Voltage Regulator


Adjustable-Voltage Regulator

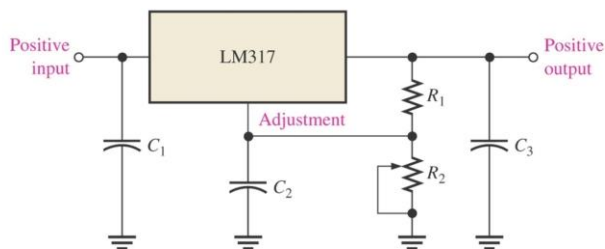- Voltage regulators are also available in circuit configurations that allow to set the output voltage to a desired regulated value.
- The LM317 is an example of an adjustable-voltage regulator, can be operated over the range of voltage from 1.25 to 35 V




Voltage Regulators

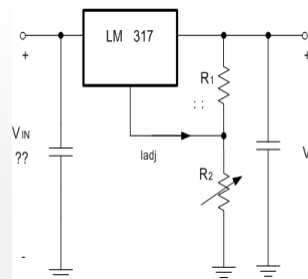- $I_{adj} \approx 50 \mu A$ (constant From data sheet)
- $V_{REF} = 1.25$ (always true for the 317 family)
- $V_o \approx 1.25 - 35V$
- V_o is defined by proper choice of R_1 & R_2
- $V_o = V_{R1} + V_{R2}$
- $V_{R1} = V_{REF} = I_{R1} * R_1$
- $I_{R1} = I_{REF} = V_{REF} / R_1$
- $V_{R2} = (I_{REF} + I_{ADJ}) * R_2$
- $V_o = I_{REF} * (R_1 + R_2) + I_{adj} * R_2$



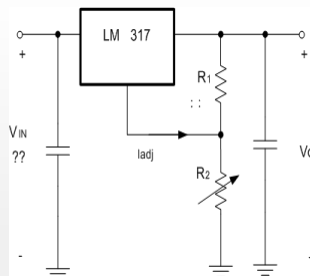Example

- Given $R_1 = 220 \Omega$; $R_2 = 5k\Omega$ potentiometer
- $I_{adj} \approx 50 \mu A$ (constant From data sheet)
- Find $V_o(\min)$ and $V_o(\max)$
- Find range of V_{in} ?



Voltage Regulators

$$I_{REF} = \frac{V_{REF}}{R_1} = \frac{1.25}{220 \Omega}$$

$$V_O = I_{REF}(R_1 + R_2) + I_{adj}(R_2)$$

$$V_{O(MAX)} |_{R2=5k\Omega} = (26.66 + 0.25) = 29.91 V$$

$$V_{O(MIN)} |_{R2=0k\Omega} = V_{REF} = 1.25 V$$


The input voltage must be higher than the output by at least 2 V

$$V_{IN(MIN)} \cong 1.25 + 2 = 3.25 V$$

$$V_{IN(MAX)} \cong 29.91 + 2 = 31.91 V$$

Voltage Regulators example

- Given the following series voltage regulator
- 1) Complete the design of the following voltage regulator (Find of R1, R2 and R3) assuming that the voltage across the load resistor R_L is equal to 12V. Assume $I_{Z(min)} = 2mA$.
- 2) Show how to modify the circuit to limit the load current to 1A.
- 3) Find the output voltage for the modified circuit of part 2) when the load resistor $R_L = 100\Omega$ and when $R_L = 8\Omega$.
- 4) Choose a transistor with suitable power rating

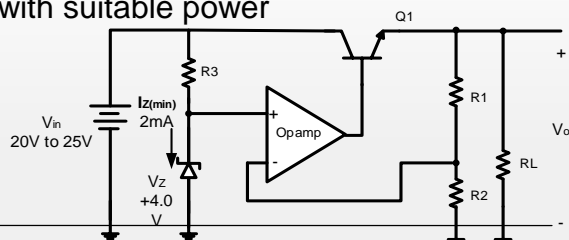

Example Continued

SOLUTION

$$1) R_3 \leq \frac{V_{IN(Min)} - V_Z}{I_{Z(Min)}}$$

$$R_3 \leq \frac{20 - 4}{2 \text{ mA}} = 8 \text{ k}\Omega \text{ in order to make sure } I_Z > I_{Z(Min)}$$


If $I_{Z(max)}$ was known, then lower limit for R_3 can also be found

$$V_o = \left(1 + \frac{R_1}{R_2}\right) V_Z = 12 \text{ V}$$

$$\therefore \frac{R_1}{R_2} = \frac{V_o}{V_Z} - 1 = \frac{12}{4} - 1 = 2$$




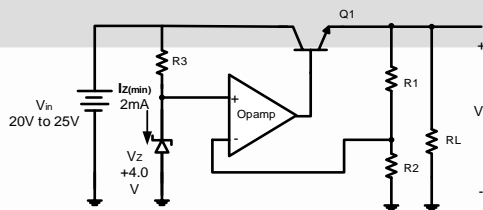choose $R_1 = 20 \text{ k}\Omega$
 $\therefore R_2 = 10 \text{ k}\Omega$



Voltage Regulators

SOLUTION

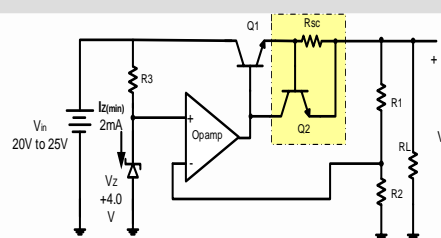


2) — The change for current limit is done by adding Q2 and R_{SC} as shown

$$\& R_{SC} = \frac{V_{be}}{I_{L(Max)}} = \frac{0.7 \text{ V}}{1 \text{ A}} = 0.7 \Omega$$

Ex. Continued

• SOLUTION

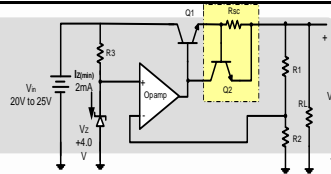

For $R_L = 100 \text{ ohm}$, $V_o = 12 \text{ V}$, then $I_L = \frac{12 \text{ V}}{100 \Omega} = 0.12 \text{ A}$

which is smaller than $I_{L(\text{max})}$,

$\therefore V_o = 12 \text{ V}$ and is not affected by the current limit circuit

For $R_L = 8 \text{ ohm}$, $V_o = 12 \text{ V}$, then $I_L = \frac{12 \text{ V}}{8 \Omega} = 1.5 \text{ A}$

which is bigger than $I_{L(\text{max})}$, and the current limit circuit

limits the current to the maximum allowable value which is 1 A

$\therefore V_o = I_{L(\text{Max})} * R_L = 1 \text{ A} * 8 \Omega = 8 \text{ V}$

Example Continued

$$P_{Q1} = V_{CE(\text{MAX})} * I_{E(\text{MAX})}$$

$$V_{CE(\text{MAX})} = V_{IN(\text{MAX})} - V_{O(\text{MIN})} = 25 - 8 = 17 \text{ V}$$

$$I_{E(\text{MAX})} = I_{R1} + I_{L(\text{MAX})} = \frac{V_Z}{R_1} + I_{L(\text{MAX})}$$

$$= \frac{8 \text{ V}}{20 \text{ k}\Omega} + 1 \text{ A} = 1.0004 \text{ A}$$

$$P_{Q1} = 17 \text{ V} * 1.0004 \text{ A} = 17.0068 \text{ W}$$