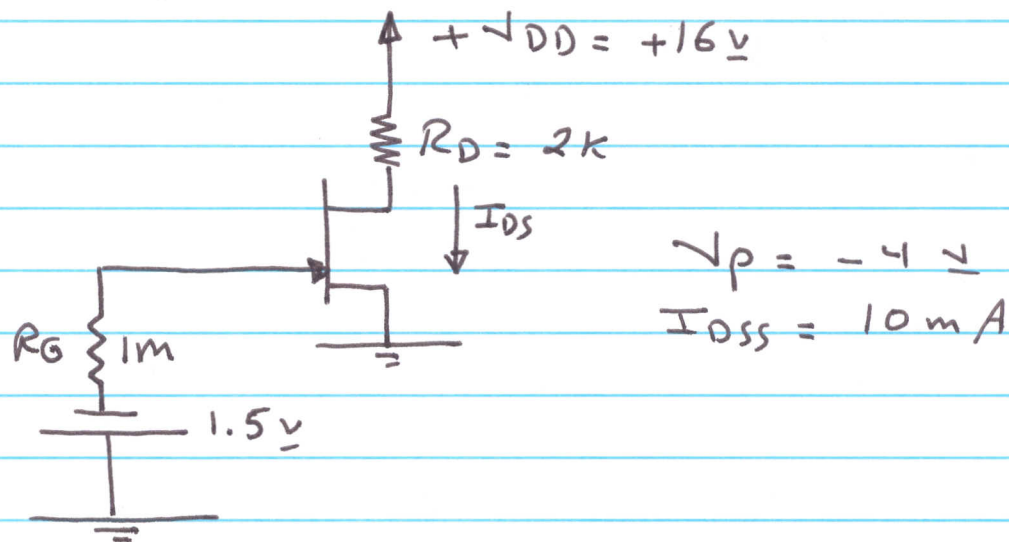


# JFET Biasing Circuits

## 1) Fixed bias Circuit



Find Q point

Since  $V_{GS} = -1.5V$ , the JFET could be either in the ohmic or pinch off region.

assume that the JFET is in the pinch off region

$$\therefore I_D = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2$$

$$V_{GS} = V_G - V_S = -1.5 - 0 = -1.5V$$

$$\therefore I_D = 3.9mA$$

$$V_{DD} = R_D I_{DS} + V_{DS}$$

$$\therefore V_{DS} = 8.2 \text{ V}$$

For the JFET to be in the pinch off region

$$|V_{DS}| > |V_P| - |V_{GS}|$$

$$> |-4| - |-1.5|$$


$$|V_{DS}| > 2.5$$

Since  $V_{DS} > 2.5 \text{ V}$ ,  $\therefore$  our assumption is OK


## graphical method

$$I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = -1.5V$$

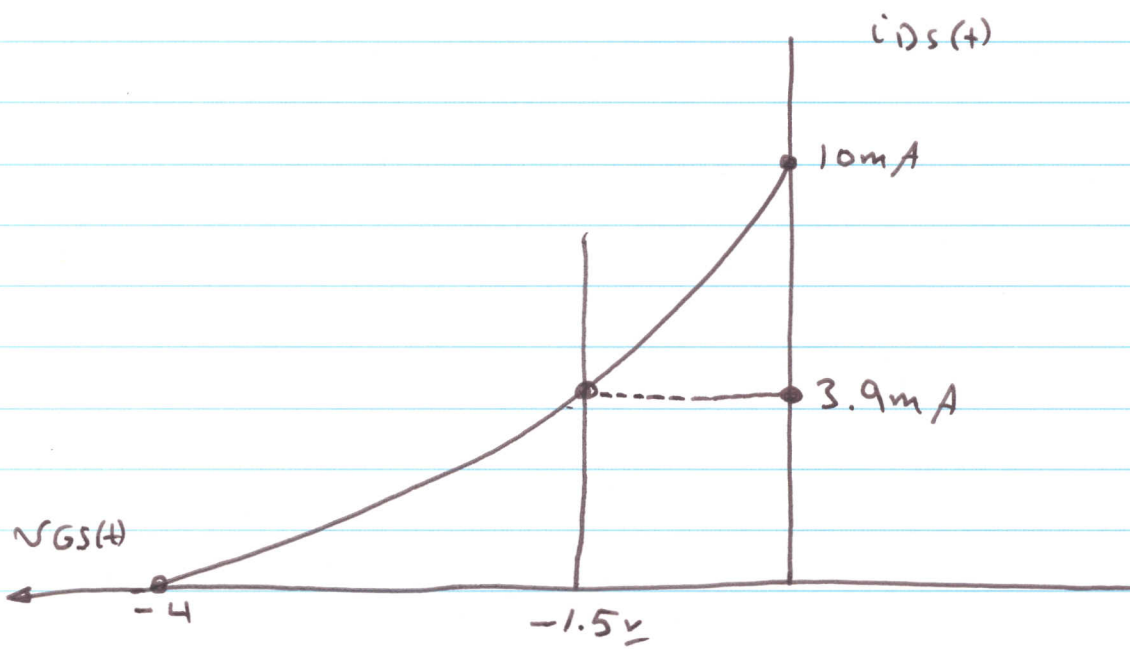

## 2) Self-bias Circuit

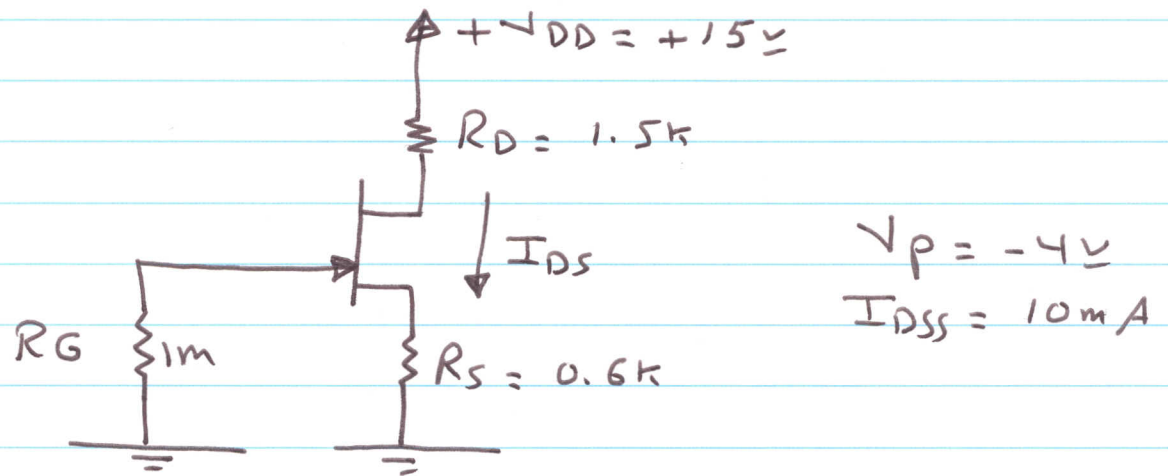

assume that the JFET is in the pinch off region.

$$I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_p} \right)^2 \quad \text{--- (1)}$$

$$V_{GS} = V_G - V_S$$

$$V_{GS} = 0 - R_S I_{DS} = -R_S I_{DS} \quad \text{--- (2)}$$

Sub (2) into (1)

$$I_{DS} = 10 \times 10^{-3} \left( 1 - \frac{-0.6k I_{DS}}{-4} \right)^2$$

$$\therefore I_{DS} = 14.77mA, 3mA$$

$$\text{Since } I_{DS} = 14.77mA > I_{DSS}$$

$$\therefore I_{DS} = 3mA$$

$$\therefore V_{GS} = -1.8V$$

$$V_{DD} = R_D I_{DS} + V_{DS} + R_S I_{DS}$$

$$\therefore V_{DS} = 8.7 \text{ V}$$

For the JFET to be in the pinch off region

$$|V_{DS}| > |V_P| - |V_{GS}|$$

$$> |-4| - |-1.8|$$

$$|V_{DS}| > 2.2 \text{ V}$$

$\therefore$  Since  $|V_{DS}| > 2.2 \text{ V}$ ,  $\therefore$  the JFET

is in the pinch off region and our

assumption is OK and

$$I_{DS} = 3.9 \text{ mA}$$

$$V_{DS} = 8.7 \text{ V}$$

$$\text{and } V_{GS} = -1.8 \text{ V}$$


## graphical method

$$I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = - (0.6 \text{ K}) I_{DS}$$


When  $V_{GS} = 0 \rightarrow I_{DS} = 0 \text{ mA}$

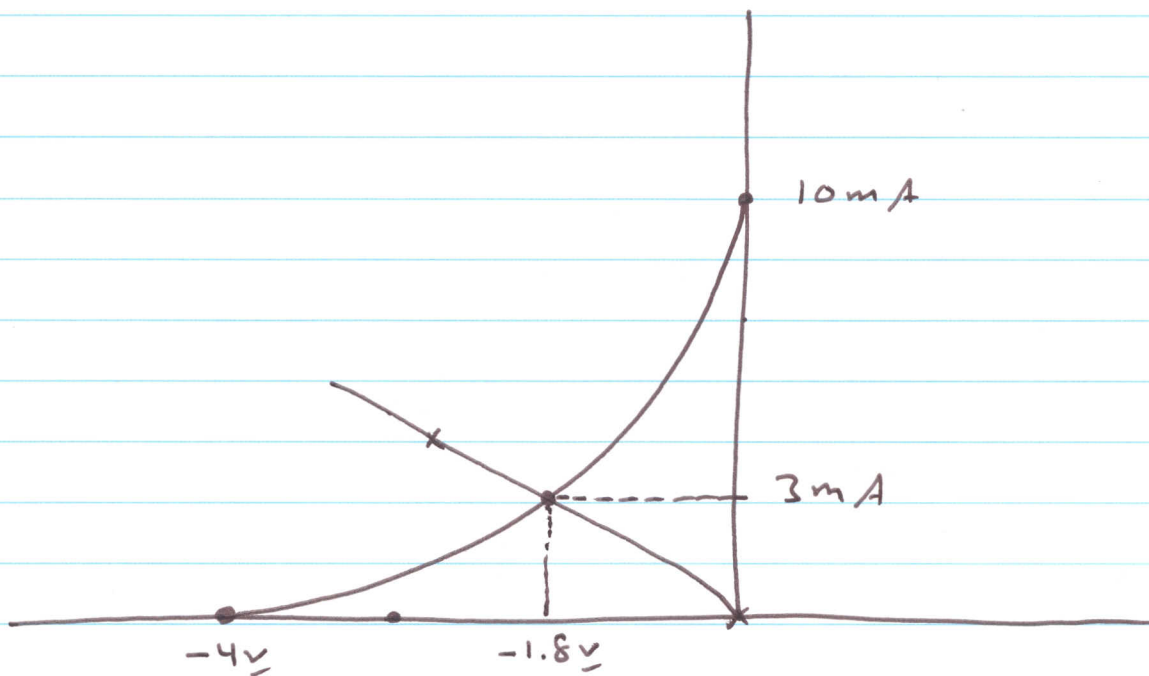When  $V_{GS} = -3 \text{ V} \rightarrow I_{DS} = 5 \text{ mA}$





### 3) Voltage Divider bias Circuit

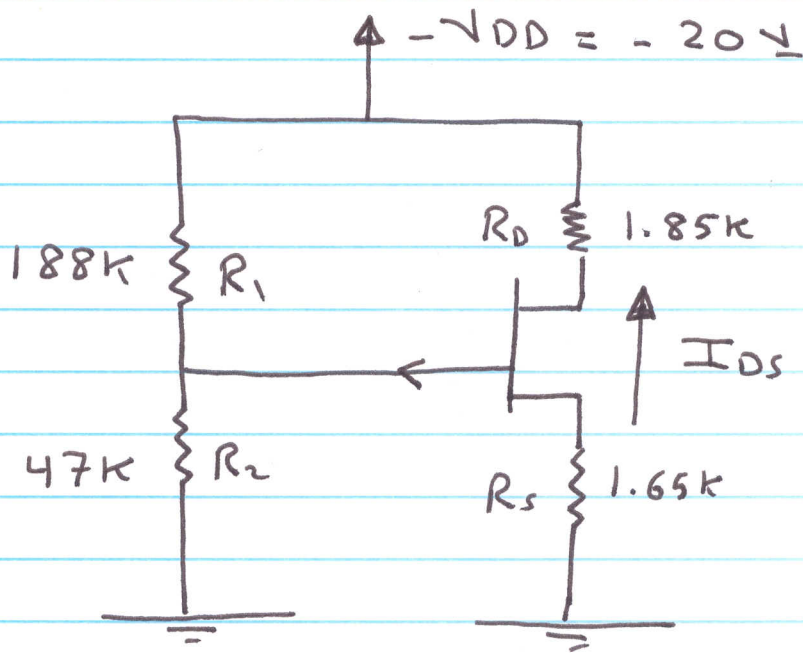

$$I_{DSS} = 18\text{mA}$$

$$V_P = +5\text{V}$$

$$I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2 \quad \text{--- (1)}$$

$$V_{GS} = V_G - V_S$$

$$V_G = \frac{47\text{k}}{47\text{k} + 188\text{k}} (-20) = -4\text{V}$$

$$V_S = -R_S I_{DS} = -(1.65\text{k}) I_{DS}$$

$$\therefore V_{GS} = -4 + (1.65\text{k})(I_{DS}) \quad \text{--- (2)}$$

Sub (2) into (1), we obtain

$$I_{DS} = \begin{cases} 4.02\text{mA} \quad \checkmark \\ 7.4\text{mA} \quad \times \end{cases}$$

$$V_{DS} = -5.93\text{V}$$

-17-

## graphical method

$$I_{DS} = I_{DSS} \left( 1 - \frac{V_{GS}}{V_P} \right)^2$$

$$V_{GS} = -4 + (1.65 \text{ K}) I_{DS}$$

When  $V_{GS} = -4 \text{ V}$ ;  $\rightarrow I_{DS} = 0$

When  $V_{GS} = 0 \text{ V}$ ;  $\rightarrow I_{DS} = 2.42 \text{ mA}$

