

# ENCS 2340

## Summary

### Chapter 3

By : Malak Obaid

# Ch3: Gate-Level Minimization

\* Karnaugh Map (k-Map)

\* كل مربع في (k-map) عَلَمٌ minterm ومثل عدد المربعات يساوي

عدد ال (minterms) (عدد المتغيرات في الدالة)

\* عدد ال (minterms) يساوي عدد الصفوف (rows) في ال (k-map)

\* كل مربعين متجاورين يختلفان في قيمة متغير واحد.  
"Adjacent squares differ in the value of one variable"

Remember that :-

\* Simplified sum-of-product expression (AND-OR circuit)

\* Simplified product-of-sums expression (OR-AND circuit)

$\overline{p}x$	$\overline{p}x$	0	$\overline{p}x$	$\overline{p}x$	0
$\overline{p}x$	$\overline{p}x$	1	$\overline{p}x$	$\overline{p}x$	1



# Karnaugh map

\* Two variable (k-map)

\* Minterms  $m_0, m_1$  are adjacent (جاور)

also ( $m_2$  and  $m_3$ ) but they differ in the

value of variable  $y$ .

\* Minterms ( $m_0$  and  $m_2$ ) are adjacent

also ( $m_1$  and  $m_3$ ) but they differ in the

value of variable  $x$

$x \backslash y$	0	1		$x \backslash y$	0	1
0	$m_0$	$m_1$	$\Rightarrow$	0	$x'y'$	$x'y$
1	$m_2$	$m_3$		1	$xy'$	$xy$



الرمز المشترك الين هو  $y$  وصيغة لفرادى نكتب  $y$   
 ولاننا نأخذ قيمة  $x$  لانها متغيرة

Ex

$x$	$y$	$f$
0	0	1
0	1	0
1	0	1
1	1	1



$x \backslash y$	0	1
0	1	0
1	1	1

الرمز المشترك هو  $x$

وصيغة 1 اذا بقيت  $x$  ولاننا نأخذ قيمة  $y$  لانها متغيرة.

\* أي مربعين متجاورين فيهم رقم 1 بنقدر نؤخذهم و

(Two adjacent cells containing 1's can be combined)

$$f = m_0 + m_2 + m_3$$

$$= x'y' + xy' + xy \quad (6 \text{ Literals})$$

$$\therefore f = x + y' \quad (2 \text{ Literals})$$

Note that :-

$$* m_0 + m_2 = x'y' + xy' = (x' + x)y' = y' \quad (\text{ناتج الحدود})$$

فوق

$$* m_2 + m_3 = xy' + xy = x(y' + y) = x \quad (\text{ناتج الحدود})$$

فوق



# Three-Variable Karnaugh Map

\* it has eight squares (for 8 minterms) numbered 0 to 7

\* Each square is adjacent to three other squares.

$x \backslash yz$	00	01	11	10
0	$m_0$	$m_1$	$m_3$	$m_2$
1	$m_4$	$m_5$	$m_7$	$m_6$

$x \backslash yz$	00	01	11	10
$x' 0$	$x'y'z'$	$x'y'z$	$x'yz$	$x'yz'$
$x 1$	$xy'z'$	$xy'z$	$xyz$	$xyz'$
	$z'$	$z$	$z'$	$z$



# Simplifying Three-Variable Function

\* Simplify this boolean function

$$f = \sum_{(x,y,z)} (3, 4, 5, 7)$$

$$f = x'yz + xy'z' + xy'z + xyz \quad (12 \text{ literals})$$

$x \backslash yz$	00	01	11	10
0	0	0	1	0
1	1	1	1	0

نستخرج الطريقة نجعل فيها اكر غير واحدات  
 اما 2 او 4 او 5 او 7  
 نستخرج الجواب فقط 2 مكانين من 1

$$\therefore f = xy' + yz$$

$f = \sum (3, 4, 6, 7)$

$x \backslash yz$	00	01	11	10
0	0	0	1	0
1	1	1	1	1

$$\therefore f = yz + xz'$$



Note :

\* By combining squares, we reduce number of literals in a product term

" كلما زاد عدد المربعات المشتركة قل عدد الرموز "

### On 3-Variable K-Map

\* One square represent a minterm with 3 variables

\* Two adjacent squares represent a term with 2 variables

\* Four " " " " " with 1 variable

\* Eight " " is the constant '1' (No Variable)

Ex 
$$F = A'C + A'B + AB'C + BC$$
  
(A, B, C)

(1) Express the function as sum-of-minterms.

" عدد اضافة الواو في كل حد كما قلنا سابقا "

$$F = \sum (1, 2, 3, 5, 7)$$



2) Find the minimal sum-of-products expression

A \ BC	$B'$		$B$	
	$C'$	$C$	$C'$	$C$
$A'$	0	1	1	1
$A$	0	1	1	0

$$\therefore f = C + A'B$$



# Four-Variable Karnaugh Map

$Wx \backslash yz$		$y'z$		$y'z'$		$yz$		$yz'$	
		00		01		11		10	
$W'$	00	$m_0$ $W'x'y'z'$	$m_1$ $W'x'y'z$	$m_3$ $W'x'yz$	$m_2$ $W'x'yz'$	$x'$			
	01	$m_4$ $W'xy'z'$	$m_5$ $W'xy'z$	$m_7$ $W'xyz$	$m_6$ $W'xyz'$	$x$			
$W$	11	$m_{12}$ $Wx'y'z'$	$m_{13}$ $Wx'y'z$	$m_{15}$ $Wxyz$	$m_{14}$ $Wxyz'$				
	10	$m_8$ $Wx'y'z'$	$m_9$ $Wx'y'z$	$m_{11}$ $Wx'yz$	$m_{10}$ $Wx'yz'$	$x$			
		$z'$		$z$		$z'$		$z$	

## On 4-Variable K-Map

- \* One square represents a minterm with 4 variables
- \* Two adjacent squares represent a term with 3 variables
- \* Four " " " " " with 2 variables
- \* Eight " " " " " a term with 1 variable
- \* Combining all 16 squares is the constant '1' (No variable)



Ex Given  $f_{(a,b,c,d)} = \sum (0, 2, 4, 5, 6, 7, 8, 12)$

Draw k-map and minimize  $f$  as sum of products

ab \ cd	c'd	c'd'	cd	cd'
a'b'	1			1
a'b	1	1	1	1
ab	1			
ab'	1			

$a'b'd'$  (grouping top-right 1s)  
 $a'b$  (grouping middle-right 1s)  
 $c'd'$  (grouping left column 1s)

$$\therefore f = a'b'd' + a'b + c'd'$$




Ex  $F = W'x'y' + x'yz' + W'xyz' + Wx'y'$

① Express the function as sum-of-minterms

$$\begin{aligned}
 F &= W'x'y'(z+z') + (W+W')x'yz' + W'xyz' + Wx'y'(z+z') \\
 &= W'x'y'z + W'x'y'z' + Wx'yz' + W'x'yz' + Wxyz' + Wx'y'z \\
 &\quad + Wx'y'z'
 \end{aligned}$$

$$= \sum (0, 1, 2, 6, 8, 9, 10)$$

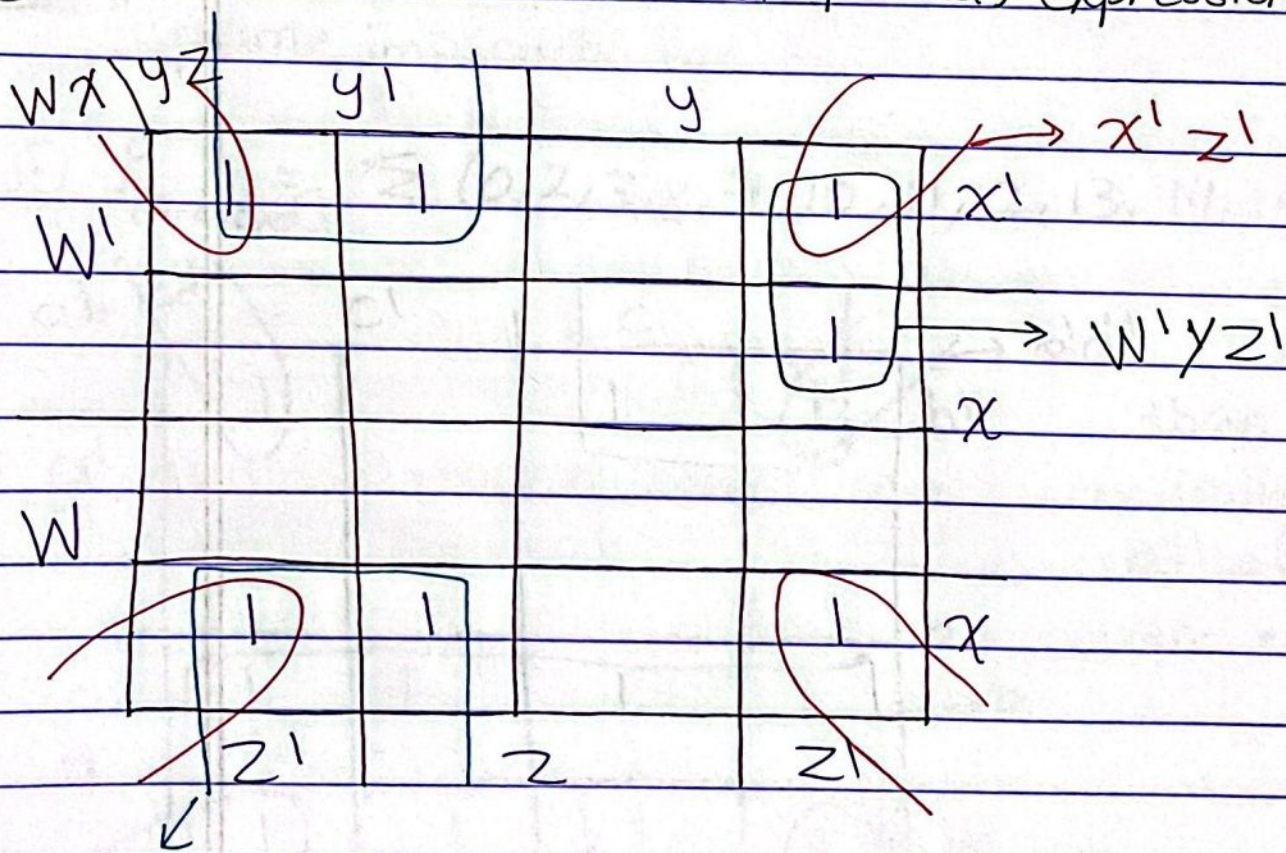② Find the minimal sum-of-products expression



$$x'y$$

$$\therefore F = x'y' + x'z' + W'yz'$$

(7 literals)



# Prime Implicants :-

\* is a product term obtained by combining the maximum number of adjacent squares in k-Map


(يعني اكبر مربع ممكن يتكون من 1 المتجاورة)

\* Essential prime Implicant:

يكون المربع الذي يشمل اكبر عدد من العبارات بحيث انه على الاقل واحد من العبارات لم يتم تغطيته مع العبارات الاخرى

Ex Find all the prime implicants and essential prime implicants for :-

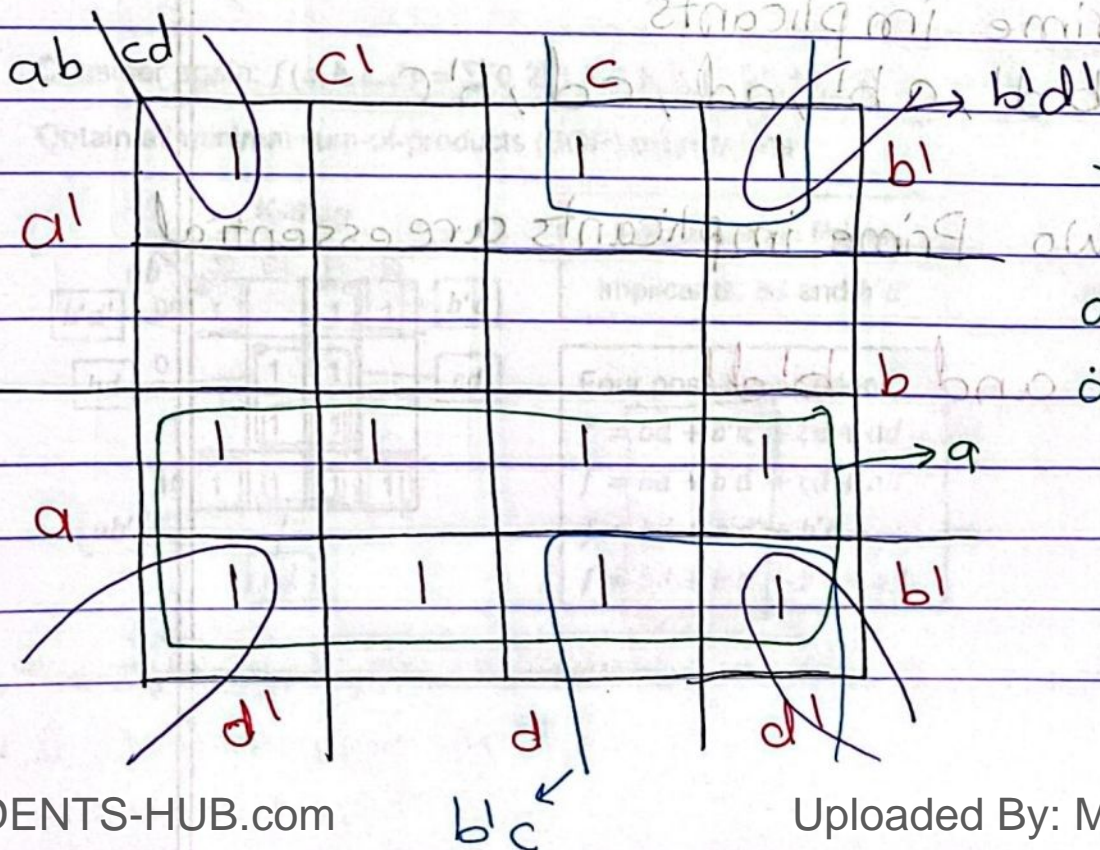
①  $f(a,b,c,d) = \sum (0,2,3,8,9,10,11,12,13,14,15)$



three prime implicants & all of them are essential



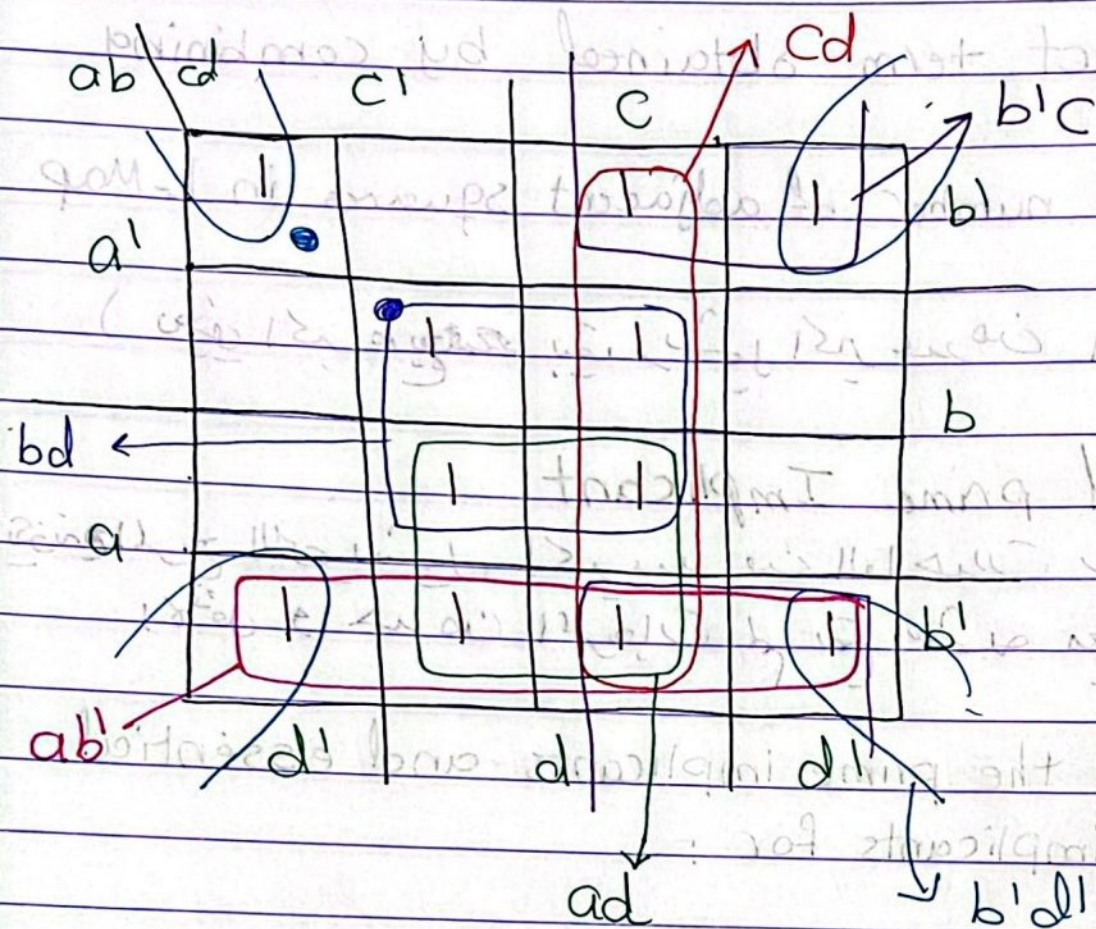②  $f = \sum(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$   
(a, b, c, d)



\* Six prime implicants

$bd, b'd', ab', ad, cd, b'c$

Only two Prime implicants are essential

$bd$  and  $b'd'$



# Simplification Procedure Using K-Map

1) Find All the essential prime implicants

2) Add prime implicant to cover the function


\* في حال ان ال essential prime...  
في الجول نكتبه اول خطوة فوق اذا لم نستطع  
نضيف ال prime implicant

- We choose the minimal subset of prime implicants that covers the remaining 1's.

\* نكتبه التعبير النهائي بأكثر من صورة لكن نفس عدد الرموز

Consider again:  $f(a, b, c, d) = \sum(0, 2, 3, 5, 7, 8, 9, 10, 11, 13, 15)$

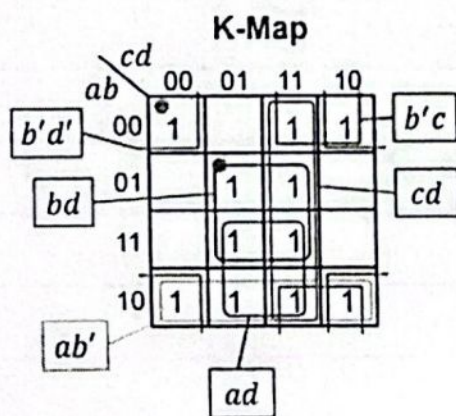Obtain all minimal sum-of-products (SOP) expressions



Two essential Prime Implicants:  $bd$  and  $b'd'$

Four possible solutions:

$$f = bd + b'd' + cd + ad$$

$$f = bd + b'd' + cd + ab'$$

$$f = bd + b'd' + b'c + ab'$$

$$f = bd + b'd' + b'c + ad$$

the essential prime implicants

نكتبهم ثم نقوم باختيار اي 2 من

STUDENT SUBMITTED

Uploaded By: Malak Dar Obaid



# Product-of-Sums (POS) Simplification

❖ Example:  $f(a, b, c, d) = \sum(1, 2, 3, 9, 10, 11, 13, 14, 15)$

K-Map of  $f$

cd \ ab	00	01	11	10
00		1	1	1
01				
11		1	1	1
10		1	1	1

$f = ad + ac + b'd + b'c$   
Minimal Sum-of-Products = 8 literals

All prime implicants are essential

K-Map of  $f'$

cd \ ab	00	01	11	10
00	1			
01	1	1	1	1
11	1			
10	1			

$f' = cd' + a'b$   
 $f = (c+d)(a+b)$

Minimal Product-of-Sums = 4 literals

\* دہے کہ ال الصیغہ لای اقرآن علی سبیل POS

minterms

اؤ کہ ال k-map لقرآن ک SOM

ال k-map ل  $f'$  لقرآن ل 1 بالماکن الفارغة

کما فی الورد وکی الصیغہ ال Sum of product

ثم تحول ال product of sum ال prime

HE

لجواب کما تم توضیح بالکمال



# Simplification procedure

1) Draw k-Map for the function  $F$

(نكتب الفئتين  $F$  بأقل عدد من الرموز العنصرية كما تعلمنا)  
(as sum of product expression)

2) Draw k-Map for  $F'$  (we replace the 0's of  $F$  with 1's in  $F'$ )

3) Obtain a minimal Sum of product expression for  $F'$

(نكتب  $F'$  بأقل عدد من الرموز العنصرية في الواحات)

4) Use DeMorgan theorem to obtain  $F = (F')'$   
(نطبق نبرع ناخدا كومبليت  $F'$  حتى نحصل على  $F$ )

the result ~~is~~ is a minimal Product of sum expression for  $F$  (نتيجة العمل السابقة)

5) Compare the cost of the minimal SOP and POS expression

(نقارن بين عدد رموز  $F$  بأقل وأكبر)

SOP: Sum of product

POS: Product of Sum



Ex : Express the boolean function in Standard form using the minimal number of literals

$$F = \prod (3, 4, 6, 7, 11, 12, 13, 14, 15)$$


(A, B, C, D)

\* نحن نأخذ الجواب بأقل عدد من الرموز نأخذ الأقتران

في ال k-map مرة بـمبغـة POS ومرة بـشكل SOP  
ونقارن ونأخذ الأقل عدداً من الرموز

① نبدأ بال SOP (sum-of-product)

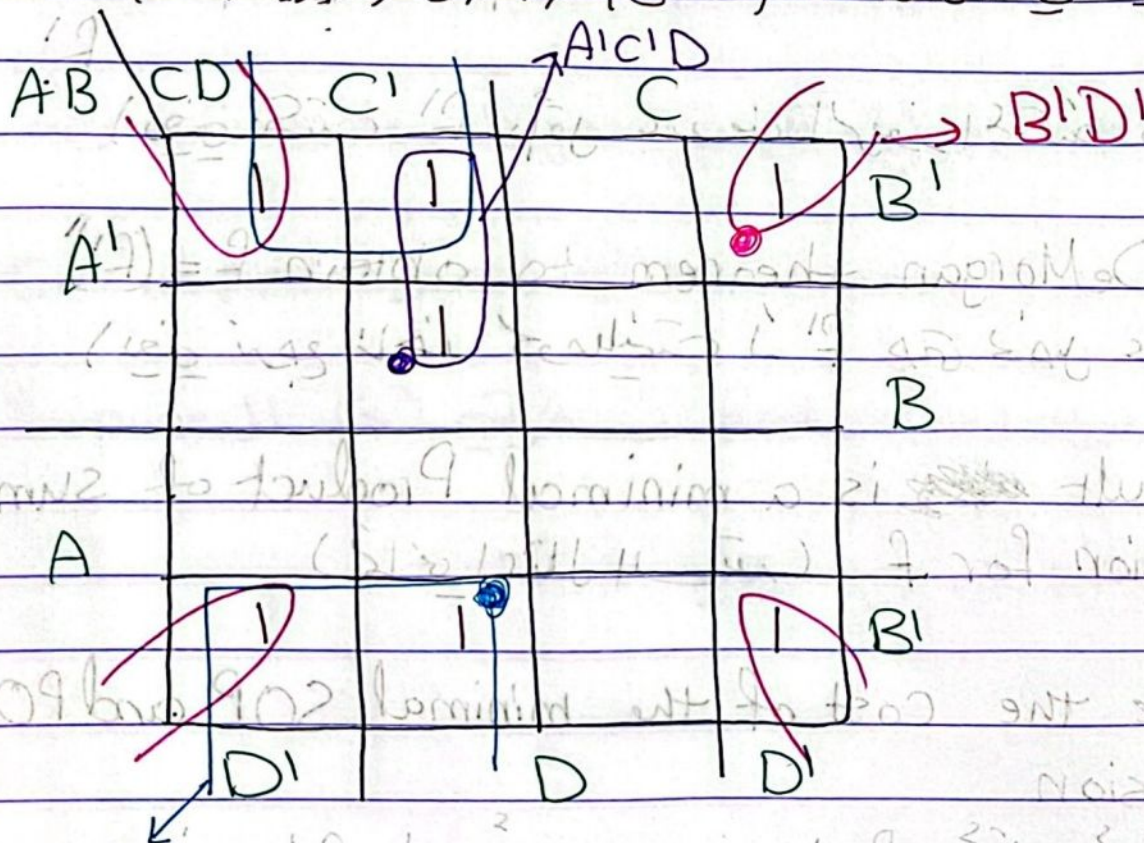لكن نلاحظ أنه يمكننا أيضاً بال POS يعني فنخرج  
1 في الأماكن (0, 1, 2, 5, 8, 9, 10)



$$B'C'$$

$$\therefore F = B'D' + B'C' + A'C'D$$


Minimal Sum-of-product = 7 literals



\* الآن نكتب 1 مكان الارقام في السؤال حتى نحصل على POS

الخطوات

K-Map of F1

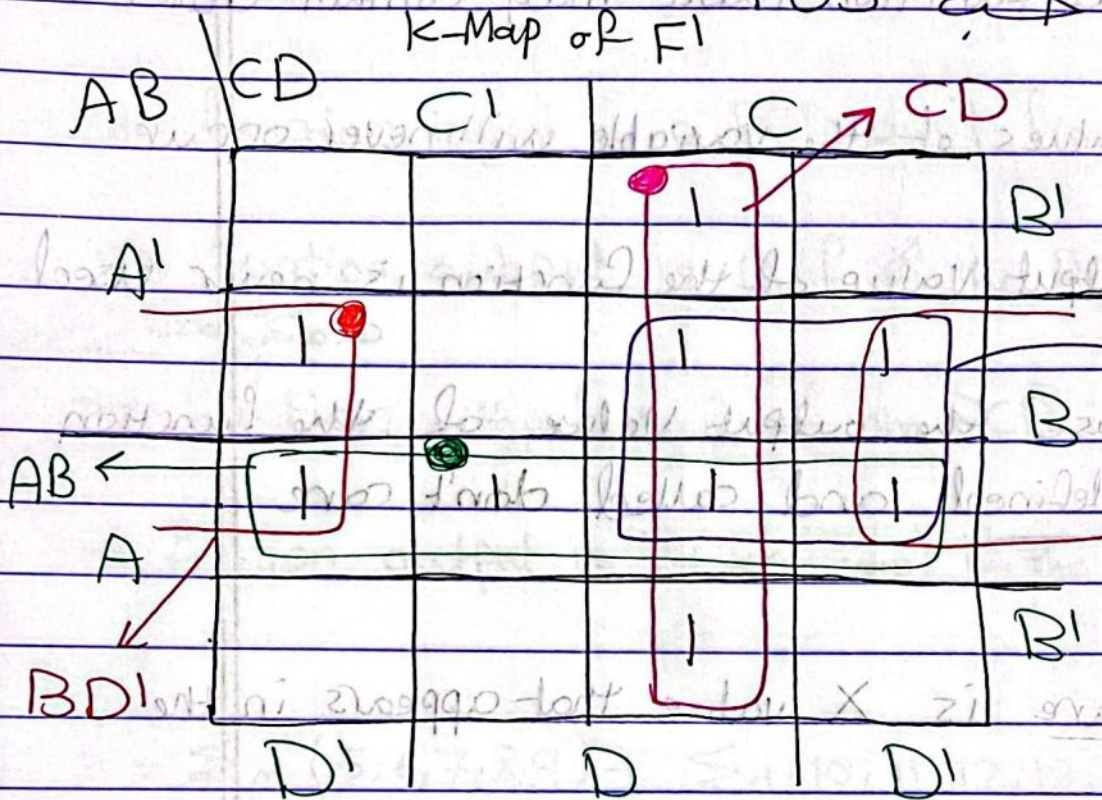

كم أقلية  
من 1 في  
مخطط  
ال essential  
وكن نريد أقل  
عدد من المصطلحات

$$F' = CD + BD' + AB \quad 6 \text{ Literals}$$

$$\therefore F = (C + D')(B' + D)(A' + B')$$

الآن نحصل على SOP من ال POS

الآن نحصل على SOP من ال POS



# Don't Cares

\* Sometimes a function table may contain entries which

- the input values of the variable will never occur

or the output value of the function is never used

\* In this case the output value of the function is not defined and called don't care

\* A don't care is X value that appears in the

function table

\* The X value can be later chosen to be

1 or 0 to minimize the function implementation



# Example of a function with Don't Cares

## \* BCD

- the function input is a BCD digit from 0 - 9
- the function output is 0 if the BCD input 0 to 4
- the function output is 1 if the BCD input is 5 to 9
- the function output is X (don't care) if the input is (10 to 15) (Not BCD)

$$F = \underbrace{\sum_m (5, 6, 7, 8, 9)}_{\text{Minterms}} + \underbrace{\sum_d (10, 11, 12, 13, 14, 15)}_{\text{don't Care}}$$

Maxterm ←  $\sum$   $\bar{A} + \bar{B} + \bar{C}$

$$(2, 0, 1, 3, 5, 7, 15) = F$$

$$(2, 0, 1, 3, 5, 7, 15) = F$$

Note that: the don't care values can be selected to be either 0 or 1 to produce a minimal expression



# Minimize the function with Dont Cares

Consider  $f = \sum_m (5, 6, 7, 8, 9) + \sum_d (10, 11, 12, 13, 14, 15)$

ab \ cd	c'd	c'd'	cd	cd'
a'b'	0	0	0	0
a'b	0	1	1	1
ab	X	X	X	X
ab'	1	1	X	X
	d'	d	d'	d

1\* if the dont cares were treated as 0's (zero's)

We get:  $f = a'bd + a'bc + ab'c'$  (9 literals)

2\* if the dont cares were treated as 1's

We get:  $f = a + bd + bc$  (5 literals)

Note that, the dont care values can be selected to be

either 0 or 1 to produce a minimal expression



# Simplification Procedure with Don't Cares

1- Find all the essential prime implicants

- Covering maximum number (power of two) of 1's & X's (don't care)
- Mark the 1's that make the prime implicants essential

2- Add prime implicants to cover the function

- Choose a minimal subset of prime implicants that cover all the remaining 1's
- make sure to cover all 1's not covered by the essential prime implicants
- minimize the overlap among the additional prime implicants
- You need to cover all the don't cares (some can remain uncovered)

★ Sometimes a function has multiple simplified expressions



# Minimal product-of-sums with Don't Cares

\* Simplify  $g = \sum m(1, 3, 7, 11, 15) + \sum d(0, 2, 5)$

obtain a minimal product of sums expression

كيفية تبسيط (POS) توجد K-Map و  $g'$  ثم

نحوه  $g'$  باستخدام de Morgan

$$g' = \sum m(4, 6, 8, 9, 10, 12, 13, 14) + \sum d(0, 2, 5)$$

كلمة ديت كير

don't care

don't care

ab/cd

c'

نتر كماله

c

ab/cd	c'	c	
a'	X	0	0
a	1	X	0
b	1	0	1
b'	1	0	1

نبدأ بتجميع الكبر عنده من الواحدات من اول 1

Minimal  $g' = d + ac'$

Minimal product of sum:-

$$g = d(a' + c) \quad (3 \text{ literals})$$

K-Map of  $g'$

\* ليس شرطاً ان نعمل كل ال X في المربعات



Uploaded By: Malak Dar Obaid




## Example of Five-Variable K-map

Given:  $f(a, b, c, d, e) = \sum(0, 1, 8, 9, 16, 17, 22, 23, 24, 25)$

Draw the 5-Variable K-Map

Obtain a minimal Sum-of-Products expression for  $f$

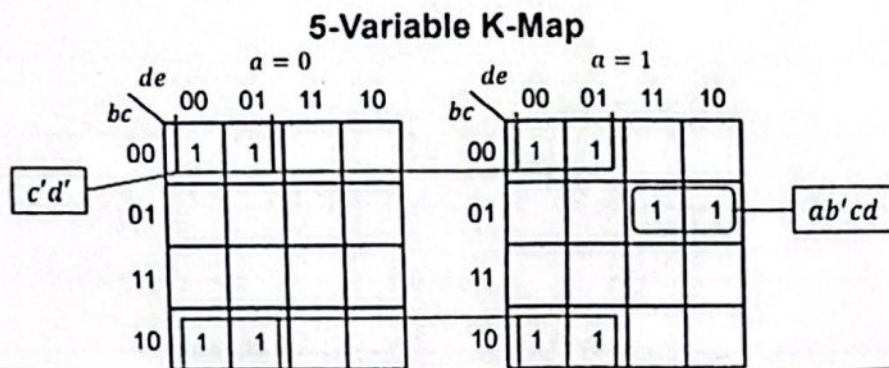Solution:  $f = c'd' + ab'cd$  (6 literals)




## Example of Five-Variable K-Map with Don't Cares

$g(a, b, c, d, e) = \sum_m(3, 6, 7, 11, 24, 25, 27, 28, 29) + \sum_d(2, 8, 9, 12, 13, 26)$

Draw the 5-Variable K-Map

Obtain a minimal Sum-of-Products expression for  $g$

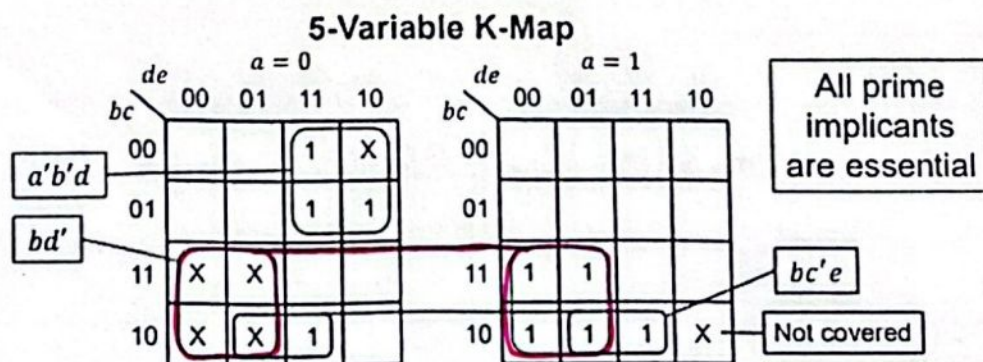**Solution:**  $g = bd' + a'b'd + bc'e$  (8 literals)



don't cares ان نسل كل ال \*



# Six-Variable Karnaugh Map

ef \ cd		ab = 00				ab = 01				ab = 11				ab = 10			
		00	01	11	10	00	01	11	10	00	01	11	10	00	01	11	10
00		$m_0$	$m_1$	$m_3$	$m_2$	$m_{16}$	$m_{17}$	$m_{19}$	$m_{18}$	$m_{48}$	$m_{49}$	$m_{51}$	$m_{50}$	$m_{32}$	$m_{33}$	$m_{35}$	$m_{34}$
01		$m_4$	$m_5$	$m_7$	$m_6$	$m_{20}$	$m_{21}$	$m_{23}$	$m_{22}$	$m_{52}$	$m_{53}$	$m_{55}$	$m_{54}$	$m_{36}$	$m_{37}$	$m_{39}$	$m_{38}$
11		$m_{12}$	$m_{13}$	$m_{15}$	$m_{14}$	$m_{28}$	$m_{29}$	$m_{31}$	$m_{30}$	$m_{60}$	$m_{61}$	$m_{63}$	$m_{62}$	$m_{44}$	$m_{45}$	$m_{47}$	$m_{46}$
10		$m_8$	$m_9$	$m_{11}$	$m_{10}$	$m_{24}$	$m_{25}$	$m_{27}$	$m_{26}$	$m_{56}$	$m_{57}$	$m_{59}$	$m_{58}$	$m_{40}$	$m_{41}$	$m_{43}$	$m_{42}$

adjacents to  $m_{37}$  كسالى الجانبيات  $m_{37}$  الجانبيات

## \* Example of Six-Variable K-map

$$h(a, b, c, d, e, f) = \sum(2, 10, 11, 18, 21, 23, 29, 31, 34, 41, 50, 53, 55, 61, 63)$$

Draw the 6-Variable K-Map

Obtain a minimal Sum-of-Products expression for  $h$

Solution:  $h = c'd'ef' + bdf + a'b'cd'e + ab'cd'e'f$  (18 literals)

ef \ cd		ab = 00				ab = 01				ab = 11				ab = 10			
		00	01	11	10	00	01	11	10	00	01	11	10	00	01	11	10
00		$c'd'ef'$	1						1				1				1
01																	
11																	
10																	






# Multiple Outputs

- Suppose that we have 2 functions  $f$  and  $g$  and they have same inputs  $(a, b, c)$  but 2 outputs

So we can minimize each function separately

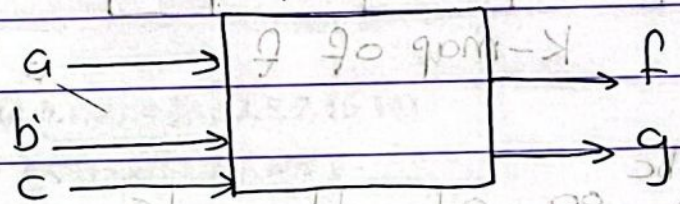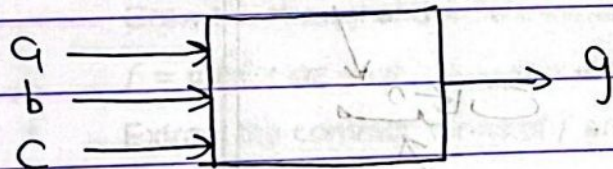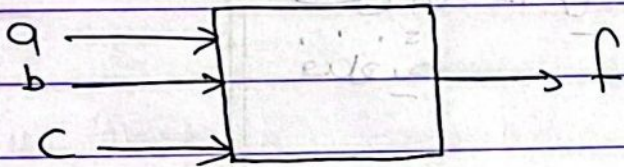or minimize  $f$  and  $g$  as one circuit with 2 outputs



One Circuit with  
two outputs

2 separate circuits




Ex Given  $f_{(a,b,c)} = \sum(0, 2, 6, 7)$

and  $g_{(a,b,c)} = \sum(1, 3, 6, 7)$


① First, we minimize each function separately

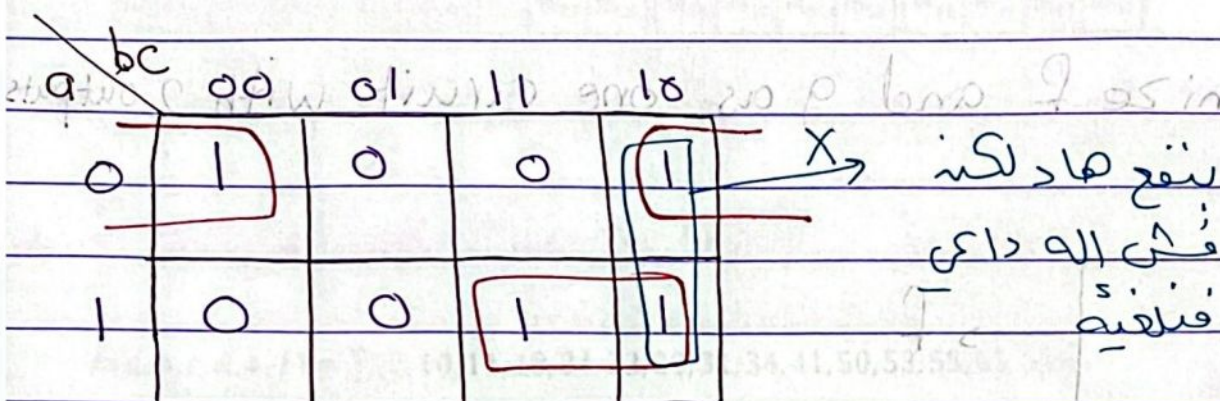② Second, we minimize both functions as one circuit





K-map of f

$$f = a'c' + ab$$

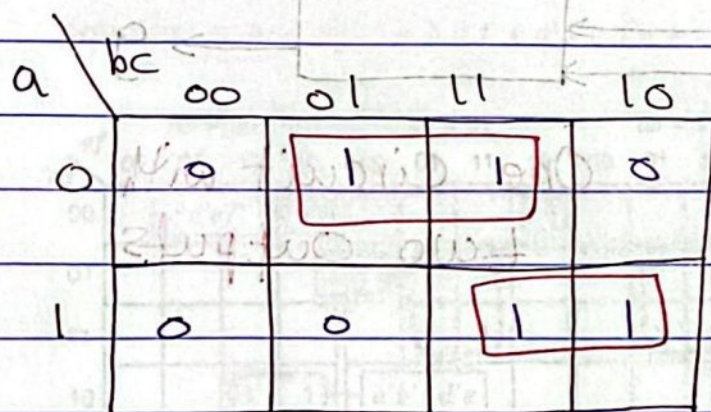

$$g = a'c + ab$$


K-map of g

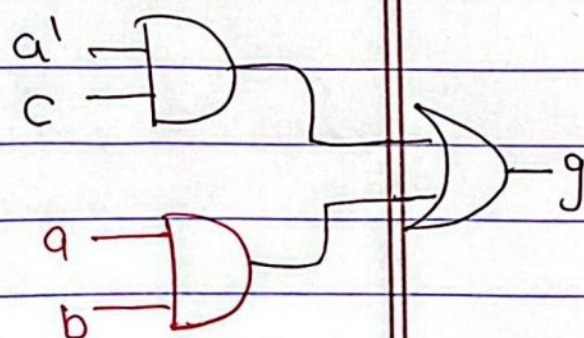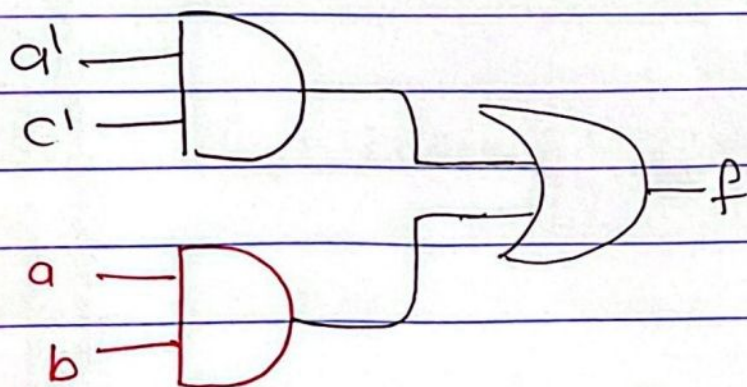



\* بما أنه لدينا term مشترك فنقدر نعمله مشترك

في دائرة و حرم للفنكشنين هكذا

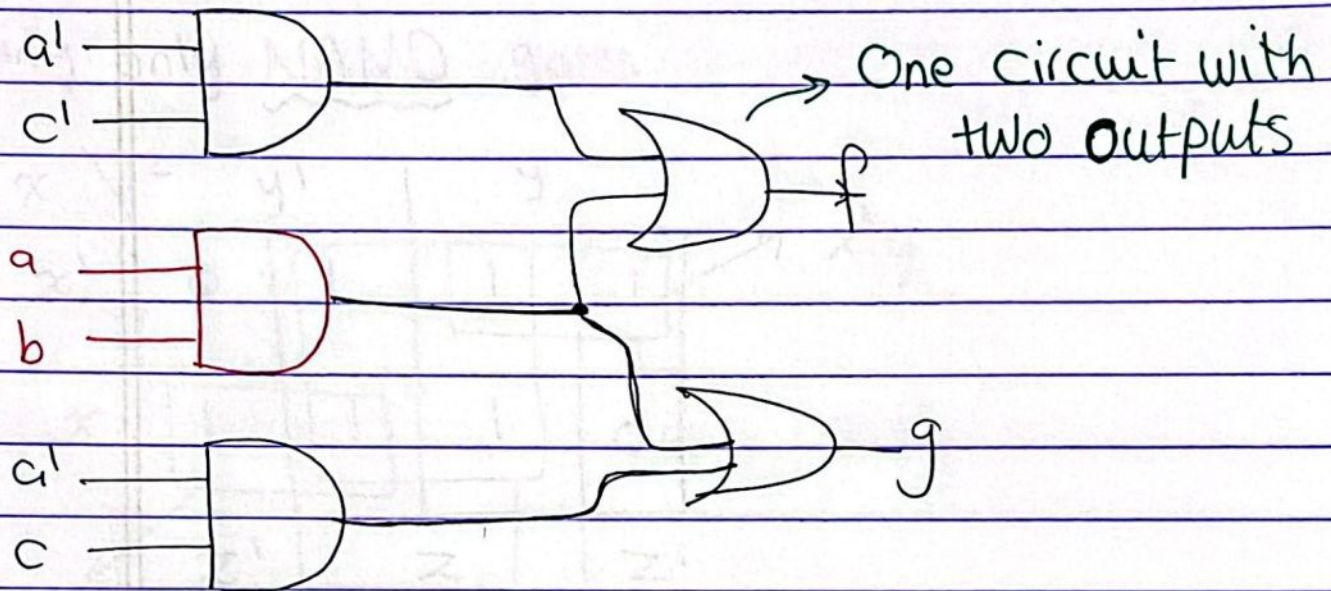

\* Another Example :-

$$f(a, b, c, d) = \sum(3, 5, 7, 10, 11, 14, 15), g(a, b, c, d) = \sum(1, 3, 5, 7, 10, 14)$$

Draw the K-map and write minimal SOP expressions of  $f$  and  $g$

$$f = a'bd + ac + cd \quad g = a'd + acd'$$

Extract the common terms of  $f$  and  $g$

K-Map of  $f$



	cd	00	01	11	10
ab	00			1	
	01		1	1	
	11			1	1
	10			1	1

K-Map of  $g$

	cd	00	01	11	10
ab	00			1	1
	01		1	1	
	11				1
	10				1

Common Terms  
 $T_1 = a'd$  and  $T_2 = ac$

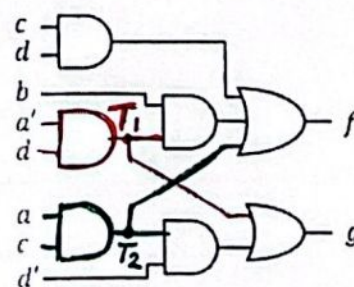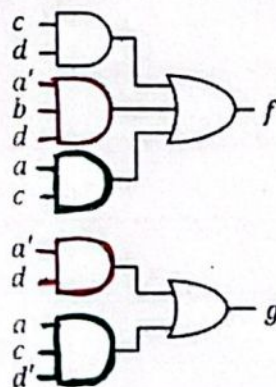Minimal  $f$  and  $g$   
 $f = T_1b + T_2 + cd$   
 $g = T_1 + T_2d'$






## Additional Logic Gates and symbols .


\* لماذا نحتاجها أو نستخدمها ؟

\* التكلفة أقل


\* يمكننا تبسيط الدوائر بعد رموز أقل

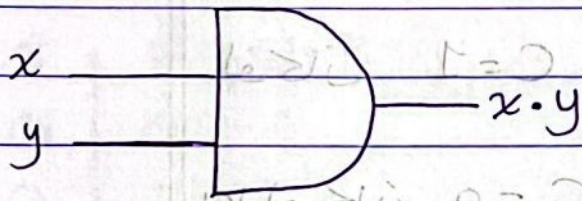


AND gate

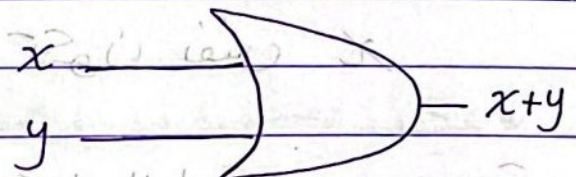


OR gate

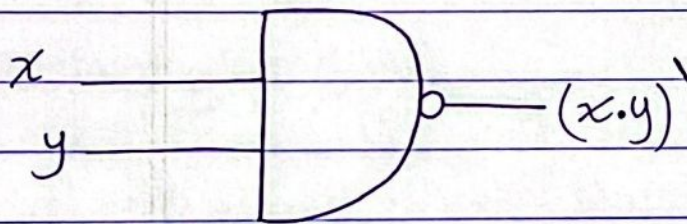


NAND gate

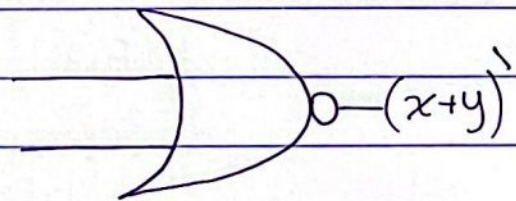


NOR gate

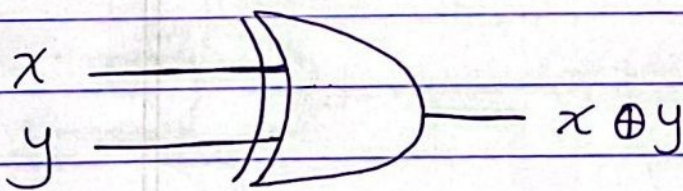


XOR gate

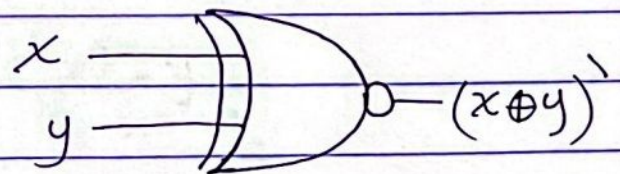


XNOR gate

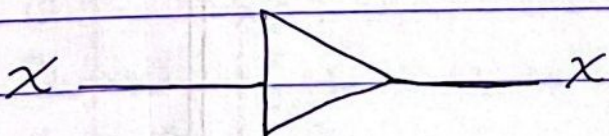

Buffer

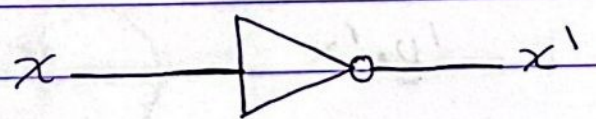


NOT gate (Inverter)

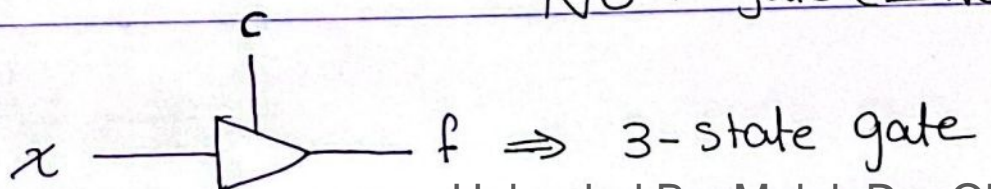




# NAND Gate (NOT AND)

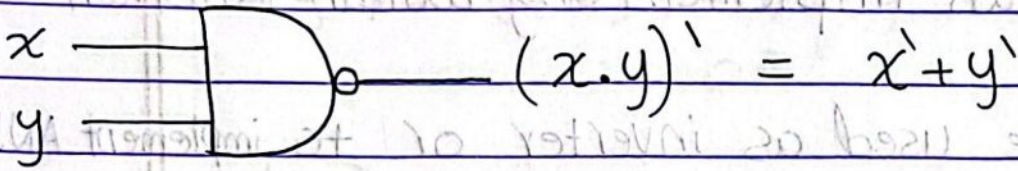


x	y	NAND
0	0	1
0	1	1
1	0	1
1	1	0

\* کہہ سکتا ہے یہاں اس کی انورس

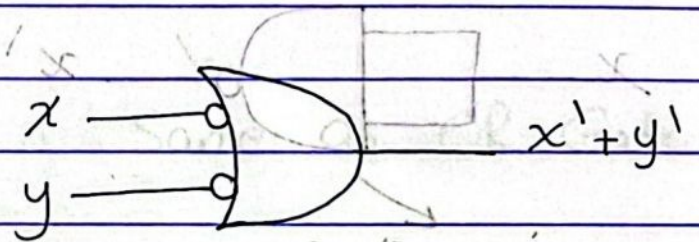


اس کے نتائج ال AND

# NOR Gate (NOT OR)

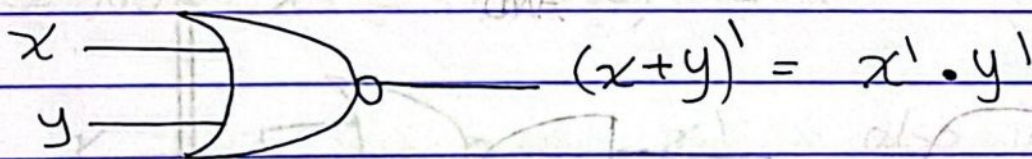

x	y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

\* کہہ سکتا ہے یہاں اس کی انورس

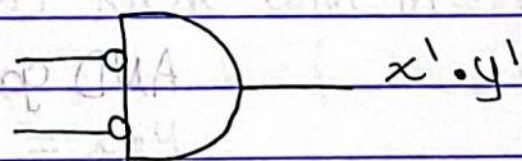

اس کے نتائج ال OR




# NAND Gate is Universal

\* This gate can implement any boolean function

\* also can be used as inverter or to implement AND/OR


$$\text{NAND } x = (x \cdot x)' = x'$$

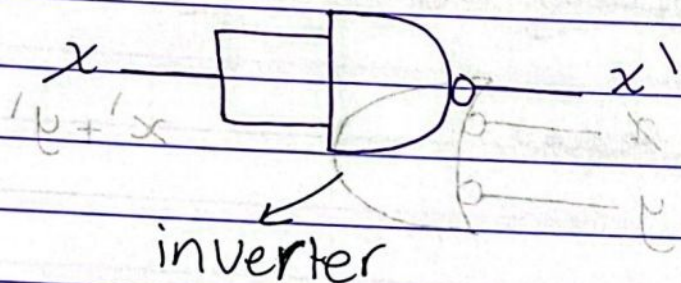

AND is equivalent to NAND with inverted output

$$(x \text{ NAND } y)' = ((x \cdot y)')' = x \cdot y$$

AND

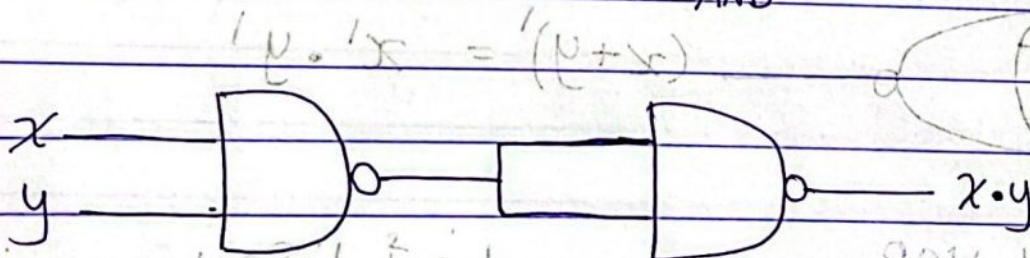


AND gate




# Boolean function with NAND Gates

\* Implement the boolean function:  $F = \sum_{(x,y,z)} (1, 2, 3, 4, 5, 7)$

Using only NAND gates

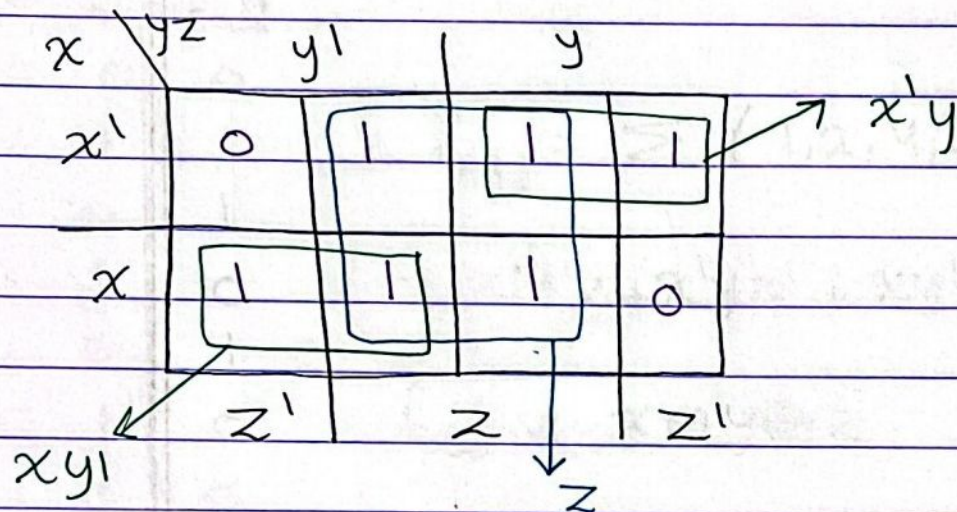


$$\therefore F = xy' + x'y + z$$

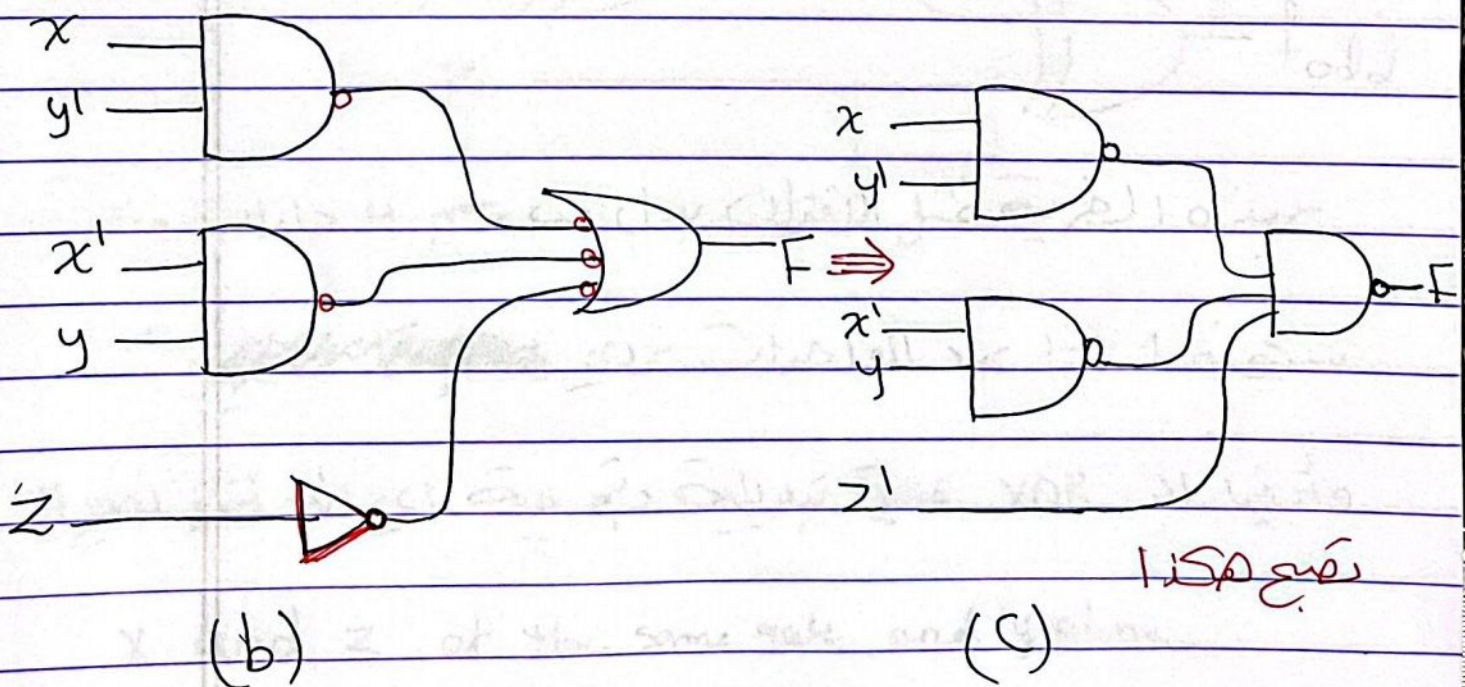




NAND / NOR can have 2, 3, 4 or more inputs

Ex

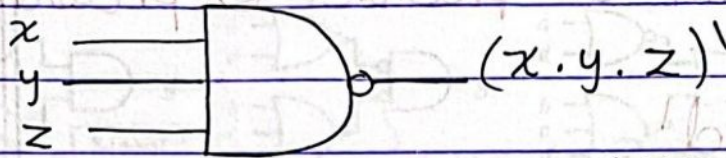

3-input NAND gate

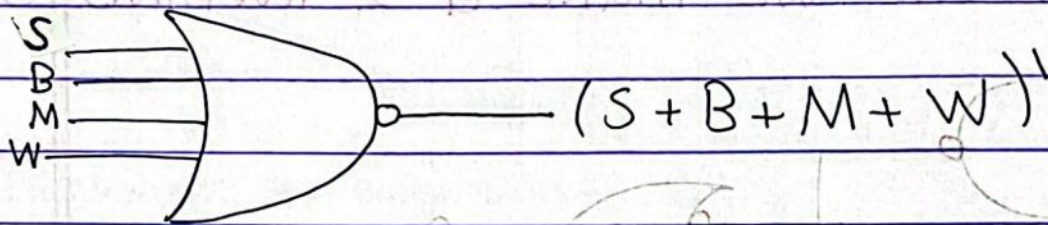

4-inputs NOR gate

NAND/NOR  
gates

slow inputs

Note that all multiple-input NAND/NOR gates are single gates not a combination of 2-input gates.



## NAND-NAND Implementation


يعني 2 level في كل واحد NAND

if we have sum of product expression like


$$f = bd + a'cd'$$

3-input NAND gate

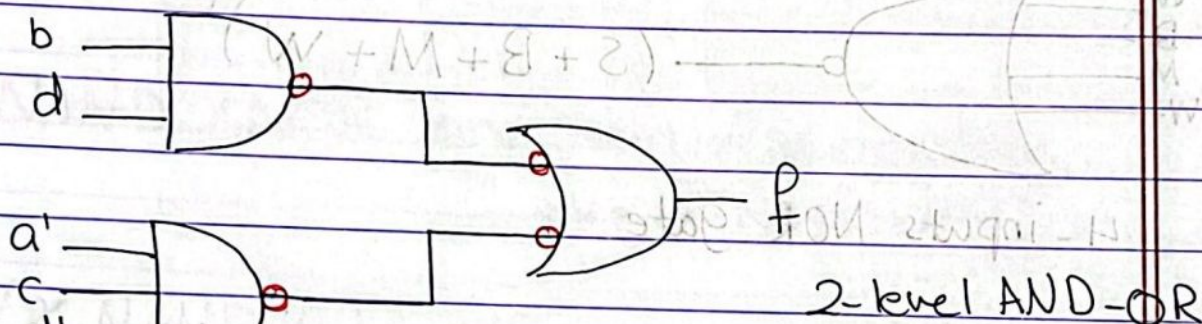\* First of all we make a 2-level AND-OR circuit



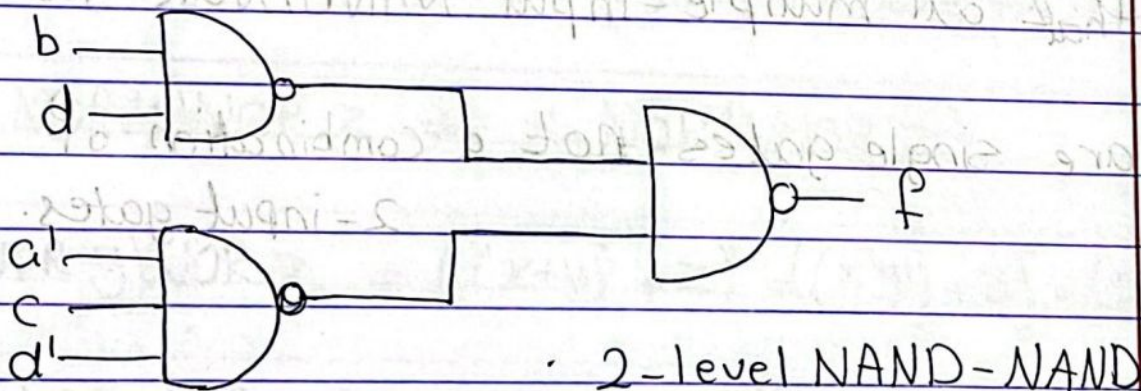\* then we add bubble on the same line  
(they cancel each other)






# NOR-NOR Implementation


❖ Consider the following product-of-sums expression:

$$g = (a + d)(b + c + d')$$

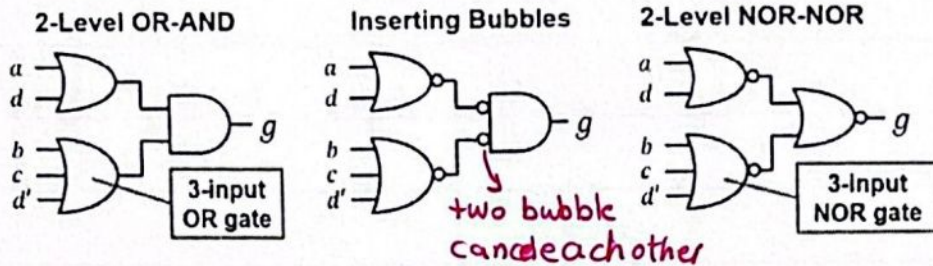❖ A 2-level OR-AND circuit can be converted easily to a 2-level NOR-NOR implementation



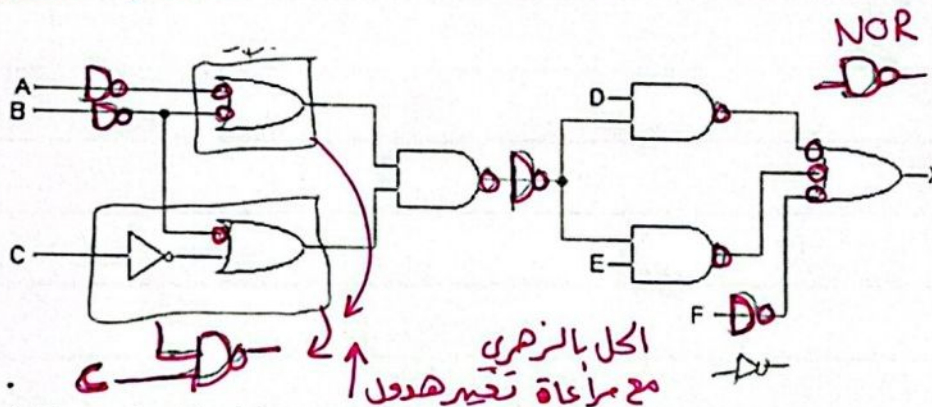Implement the given circuit using only NOR gates





❖ Example: Find the complement of the following expression and implement it using (1) NAND gates, and (2) NOR gates:

$$G(A, B, C) = (A + B' + C)(A'B' + C)(A + B'C')$$

❖ Solution:
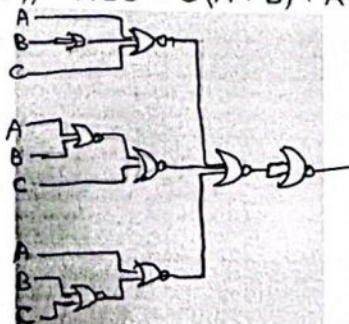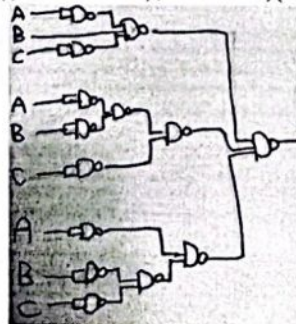
$$G' = ((A + B' + C)(A'B' + C)(A + B'C'))' = A'BC' + C'(A + B) + A'(B + C)$$





# Boolean Function with NOR Gates

Implement the boolean function

$f = \sum(1, 2, 3, 5, 7)$  Using only NOR gates

$x \backslash yz$	$y'z$	$y'z'$	$yz$	$yz'$
$x'$	0	1	1	1
$x$	0	1	1	0


\* نجد ما رسنا ال k-map ال للمقران هنا نريد ان نجد

minimal product of sums to implement the function using NOR gate

نجد صيغة المقران ~~باعتبار~~ باعتبار الصيغ واهيان وكي الصيغة ثم تأخذ ال prime لها.

$$\therefore F' = y'z' + xz'$$

$$F = (y+z)(x'+z)$$

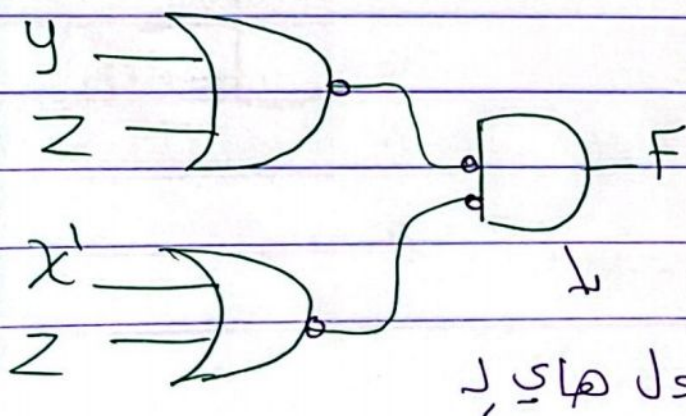

نرى ما رسنا  
bubbles

أو حول هاي




# Exclusive OR / Exclusive NOR

$x$	$y$	$x \oplus y$	$\neg x$	$y$	$x \oplus y$
0	0	0	1	0	1
0	1	1	1	1	0
1	0	1	0	0	0
1	1	0	0	1	1


$x \oplus y$  function is :-  
 $x'y + xy'$

$x \oplus y$  function is :-  
 $xy + x'y'$

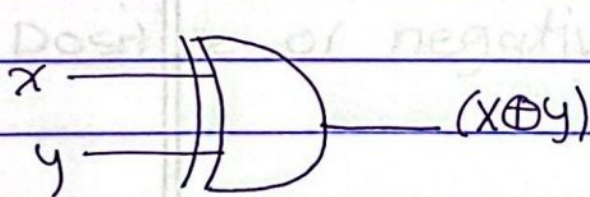$x \oplus y$  and  $x \oplus y$  don't exist for more than two inputs because they are complex for example for 3 inputs we use two gates of them not one



XOR gate

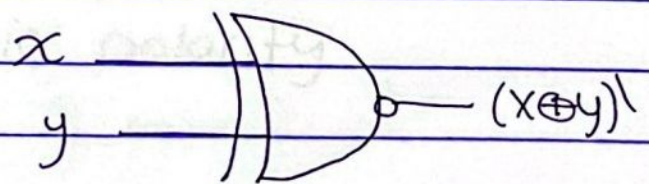

XNOR gate

its also known as equivalence  
 Uploaded By: Malak Dar Obaid



## Odd Functions

\* إذا كان عدد ال 1 فردى في ال input فإن ال Output = 1


وهو نفسه ال XOR على ال inputs الذين عدال 1 فردى

x	y	z	$f_{\text{odd}}$
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$f_{\text{odd}} = \sum (1, 2, 4, 7)$$

$$= x'y'z + x'yz' + xy'z' + xyz$$

$$f_{\text{odd}} = x \oplus y \oplus z$$

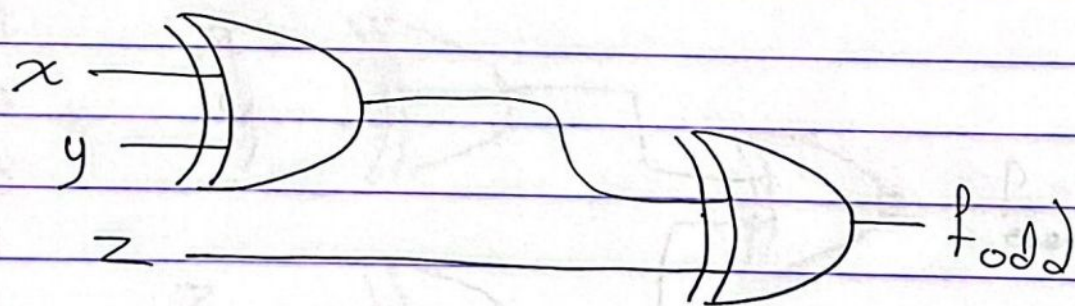

هذه الطريقة تمثل الاقتراح بدل من رسم 4 دارات والناتج

سيكون 1 إذا عدد الواحدات فردى

وأيضا ال XOR على تبديلية وبجعية أى أنه قد نفع ال

x and z at the same gate and y alone



## Even Function


\* هذا عدد الاحداث سيكون زوجي وال output ليرى واحد  
(the complement of odd function)

- Output is XNOR operation on all inputs

x	y	z	w	$f_{\text{even}}$
0	0	0	0	1
0	0	0	1	0
0	0	1	0	0
0	0	1	1	1
0	1	0	0	0
0	1	0	1	1
0	1	1	0	1
0	1	1	1	0
1	0	0	0	0
1	0	0	1	1
1	0	1	0	1
1	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

$$f_{\text{even}} = \sum (0, 3, 5, 6, 9, 10, 12, 15)$$
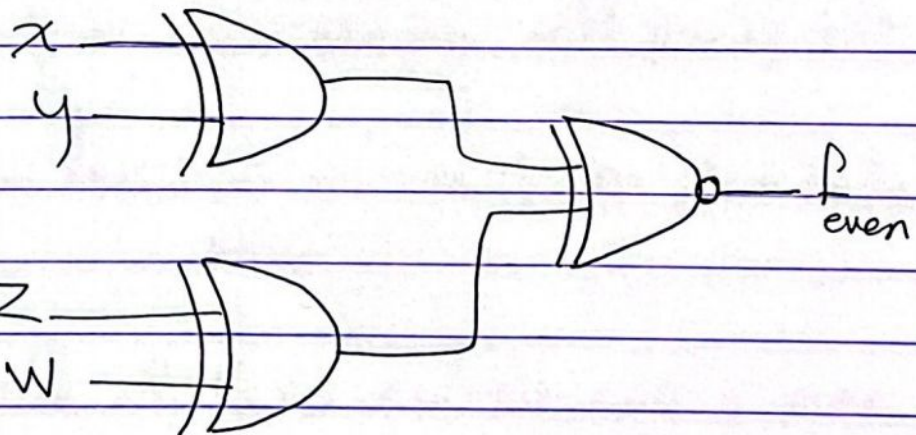
$$f_{\text{even}} = (x \oplus y \oplus z \oplus w)'$$



استخدمنا دارتين XOR و مدخله XNOR


ويمكنه نقل ال bubble الى دائرة  
في ال inputs ونضيفه من عند ال output



# Parity Generators and Checkers

Sender

Receiver

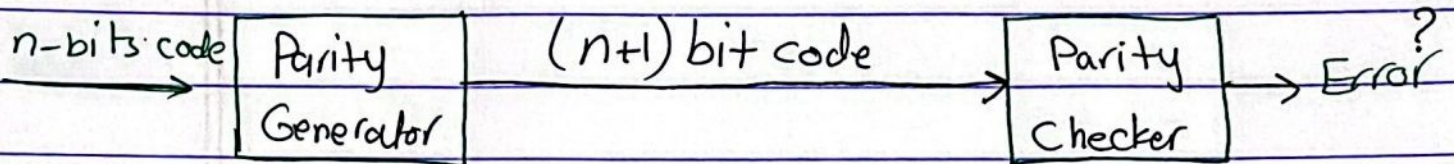

\* A parity bit is added to the n-bit code

إذا parity checker في error فـ 1 وإذا 0 فـ لا error ←  
إذا 1 فـ error وإذا 0 فـ لا error

\* **Odd parity** : num of 1's in (n+1) bit code is odd

- Use even function to generate the odd parity bit

- also we use even function to check (n+1) bit code  
error فـ 1 وإذا 0 فـ لا error ←

\* **Even parity** : num of 1's in (n+1) bit code is even


- we use odd function to generate the even <sup>parity</sup> bit

- also we use odd function to check the (n+1) bit code



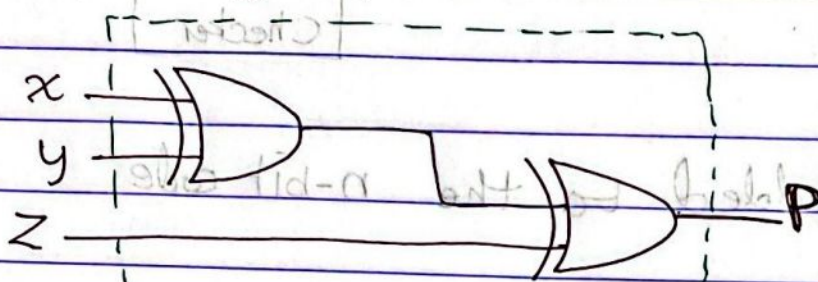
## Ex 1 Design even parity generator & Checker for 3-bit codes

1- We use 3-bit odd function to generate even parity bit (P)



Parity Generator

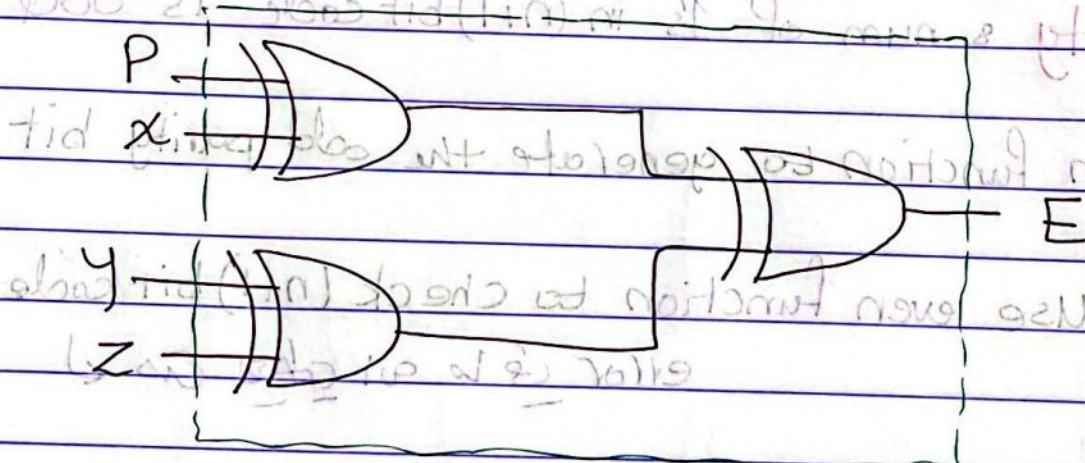2- Use 4-bit odd function to check if there is an error (E) in even parity.



Parity Checker

\* Given that  $XYZ = 001$  then  $P = 1$

$\therefore$  the sender transmits (يُرسَل)  $PXYZ = 1001$

\* في حال أن تُرسَل على هيئة 1001 "PXYZ"

فإننا نصل إلى checker فنجد أن

الرسالة 1001 و 1011

then  $E = 1$