## **Diode Equation**

$$i_D(t) = I_S(e^{\frac{V_D(t)}{\eta V_T}} - 1)$$



Is: Revers saturation current

 $Is=10^{-12}, 10^{-14}A$ 

 $\eta$  : eta

$$\eta = \begin{cases} 1 \text{ for Ge} \\ 2 \text{ for Si (small current)} \\ 1 \text{ for Si (large current)} \end{cases}$$

STUDENTS-HUB.com

VT= Thermal Voltage

$$VT = \frac{T}{11600} \quad ;T \text{ in kelvin}$$

At Room Temp. T=300k

 $\therefore$  VT = 25.69 mv at Room Temp.

$$i_D(t) = I_S(e^{\frac{V_D(t)}{\eta V_T}} - 1)$$

The equation is a non linear equation... The Diode is non linear Device

For positive  $V_D(t)$ 

For negative  $V_D(t)$  $i_D(t) = -I_S$ 

 $i_D(t) = I_S(e^{\frac{V_D(t)}{\eta V_T}})$ 

STUDENTS-HUB.com

#### **Diode V-I Characteristic curve**



STUDENTS-HUB.com

The rectifier diode is a non linear device .

There are essentially three basic approaches to the solution of such problem :

- 1- The use of non linear mathematics
- 2- The use of graphical techniques
- 3- The use of equivalent circuit (models)
  - Piece wise linear models

STUDENTS-HUB.com

## 1)The use of non linear mathematic

For the circuit shown, find ID and VD



Silicon:  
$$\eta=1.1$$
  
 $Is= 10^{-14} A$ 

• KVL : 
$$V_S = R_S I_D + V_D$$
  
 $I_D = I_S (e^{\frac{V_D}{\eta V_T}} - 1)$ 

► Since the diode is forward biased , we could approximate

$$I_D = I_S(e^{\frac{V_D}{\eta V_T}})$$

STUDENTS-HUB.com  $V_D = \eta V_T \ln \frac{I_D}{I_S}$ 

# ... We have two equations and two unknowns

$$V_S = R_S I_D + V_D \dots 1$$
  
$$V_D = \eta V_T \ln \frac{I_D}{I_S} \dots 2$$

$$\therefore V_S = R_S I_D + \eta \operatorname{Vt} \ln \frac{I_D}{I_S}$$

• non linear equation

STUDENTS-HUB.com

## **Iterative Analysis**

 $I_{\rm D} = \frac{V_S - V_D}{R_S}$  $V_{\rm D} = \eta \, V_{\rm T} \ln \frac{I_D}{I_S}$ 

- 1) Let  $V_D = 0.7$ V
  - $I_D = \frac{2 0.7}{0.1k} = 13 \text{ mA}$
- $V_D = 0.7882392$ V The error is large
- 2) Let  $V_D = 0.7882392V$  $I_D = 12.117608 \text{ mA}$

 $V_D = 0.7862529V$  The error is small

STUDENTS-HUB.com

3) Let  $V_D = 0.7862529V$  $I_D = 12.137471 \text{ mA}$  $V_D = 0.7862991V$  The error getting smaller

- 4) Let  $V_D = 0.7862991V$ 
  - $I_D = 12.137009$ mA

 $V_D = 0.786298066V$ 

 $I_{\rm D} = 12.137 \text{ mA}$  $V_D = 0.7863 \text{V}$ 

STUDENTS-HUB.com

#### 2) The use of graphical techniques



$$I_D = - \frac{1}{R_S} V_D + \frac{V_S}{R_S}$$

STUDENTS-HUB.com

#### Drawing the two equations



$$I_D = - \frac{1}{R_S} V_D + \frac{V_S}{R_S}$$

• **Q point = (** $I_{DQ}$ **,**  $V_{DQ}$ **) = Quiescent point** 

STUDENTS-HUB.com

#### The effect of Rs on the Qpoint



STUDENTS-HUB.com

### The effect of Vs on Qpoint



STUDENTS-HUB.com