

Solution Key



BIRZEIT UNIVERSITY

Electrical and Computer Engineering Department

Electrical Machines ENEE 2408

Short Exam # 3 (10mins)

Student Name: _____

ID: _____

May 31, 2023


A 10MVA, 11kV, 0.8 lagging Power factor, 6 poles, Y-connected synchronous generator has a synchronous reactance of 1Ω and negligible armature resistance. If the generator is operating in parallel with a large power system (infinite bus), whose rated line to line voltage is 11kV and frequency is 50Hz, then:

- What is the speed of rotation of the prime mover in rad/s and in rpm?
- Draw the per-phase equivalent circuit of the generator
- What is the magnitude of the internally generated voltage E_a at rated conditions, what is the torque angle at rated conditions?
- What is the static stability limit of the generator?
- Draw the phasor diagram at rated condition and Static stability limit condition

$$V_L = 11 \text{ kV}, \quad \bar{V}_\phi = 6351 \text{ V}$$

$$a) \quad n_s = \frac{120 f_e}{P} = \frac{120(50)}{6} = 1000 \text{ rpm}, \quad \omega_s = \frac{1000 \times 2\pi}{60} = 104.72 \text{ rad/s}$$

b)

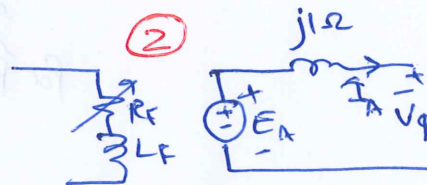

$$c) \quad \bar{E}_A = \bar{V}_\phi + jX_s \bar{I}_A$$

$$= 6351 + j1 \bar{I}_A, \quad \text{but}$$

$$\bar{I}_A = \frac{S}{\sqrt{3} V_L} \angle -\cos^{-1} \text{PF}$$

$$= \frac{10 \text{ MVA}}{\sqrt{3} 11 \text{ kV}} \angle -36.87^\circ$$

$$= 524.86 \angle -36.87^\circ \text{ A}$$

$$\bar{E}_A = 6351 + (1 \angle 90^\circ)(524.86 \angle -36.9^\circ)$$

$$\bar{E}_A = 6351 + 524.86 \angle +53.13^\circ$$

$$= 6351 + 314.9 + j419.9$$

$$= 6665.9 + j419.9 = 6679.1 \angle 3.6^\circ \text{ V}$$

$$\therefore |\bar{E}_A| = 6679.1 \text{ V}, \quad \delta = 3.6^\circ$$

$$d) \quad P_{\max} = \frac{3 V_\phi E_A}{X_s} = \frac{3(6351)(6679.1)}{1} = 127,256,892.9 \text{ W}$$

e

