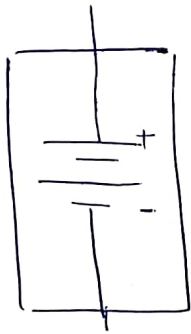



Exp2 :- Source internal resistance, Loading problems and circuit impedance matching.

Voltage Source is characterized by its (emf)

emf: the open circuit voltage difference between its terminals, and the max value of the current it can deliver to a short circuit.



Ideal Battery

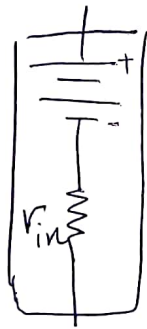

Real Battery


So: Voltage source with small r_{in} ~~and~~ provide the circuit higher current, and maintain most of their emf as voltage differences between their terminals.

Voltage Source: provide useful electrical power to certain circuit component like; electric motors, light bulbs

- Load: any component which consumes electrical power to ~~certain~~ produce useful work

R_L : Load Resistance.

* Loading Problem:-

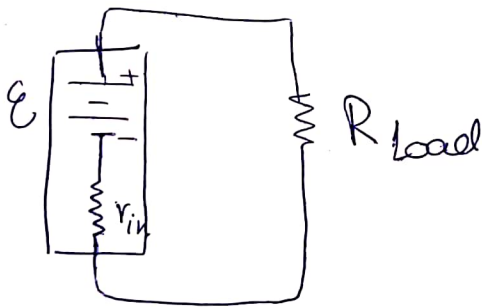

$$I = \frac{V}{R} \quad R = R_L + r_{in}$$

$$I = \frac{\mathcal{E}}{R_L + r_{in}} \quad \text{Current passing through this circuit.}$$

$$\therefore V_{RL} = \frac{\mathcal{E}}{R_L + r_{in}} R_L$$

the voltage difference between the source terminals.

$$R_L \gg r_{in} \quad \therefore V_{R_L} \approx \mathcal{E}$$

- if R_L comparable to r_{in} $\therefore V_{R_L}$ is smaller than $\mathcal{E} \Rightarrow$ in this case the amount of power consumed inside the source and converted to useless heat energy makes the source considered to be load, to avoid this case choose $R_L \gg R_{in}$.

* Impedance Matching

- max power transfer: in real circuits, power consumed in the load produces useful work, therefore we seek to consume the max available power here

$$P = I^2 R_L$$

* power consumed in load resistor


$$P = \frac{\mathcal{E}^2 R_L}{(R_L + r_{in})^2}$$

power as function of R_L

$P(R_L)$ has max value and can be obtained by


$$\frac{dP}{dR_L} = 0$$

max power $\therefore R_L = r_{in}$

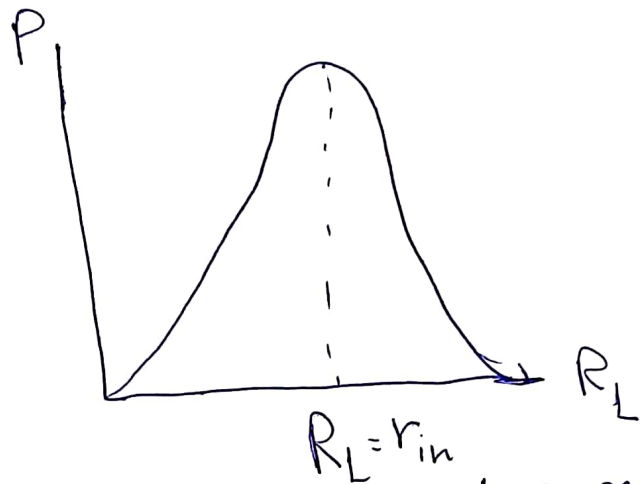

This load resistance called impedance matching

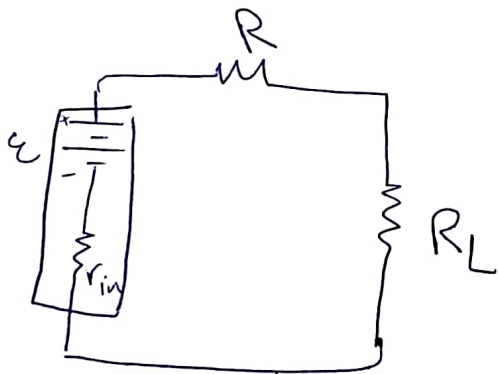- Impedance matching is the process of making one impedance look like another (match a load R_L to the internal R)



So we add R to reach to the condition $R_L = R_{in}$ where $R_{in} = R + r_{in}$

(R_L see R as internal resistance)

$\Rightarrow$ Then this $R \rightarrow$ avoiding the loading problems and fulfilling the condition of Impedance matching.

$\Rightarrow$ The only Disadvantage: this R consumes part of the power delivered to the circuit.


applying conservation of energy.

$$\mathcal{E} = I r_{in} + I R + I R_L$$

rearranging, we get

$$\frac{1}{I} = R_L \frac{1}{\mathcal{E}} + \frac{(r_{in} + R)}{\mathcal{E}}$$

$$\boxed{R_L = R + r_{in}}$$

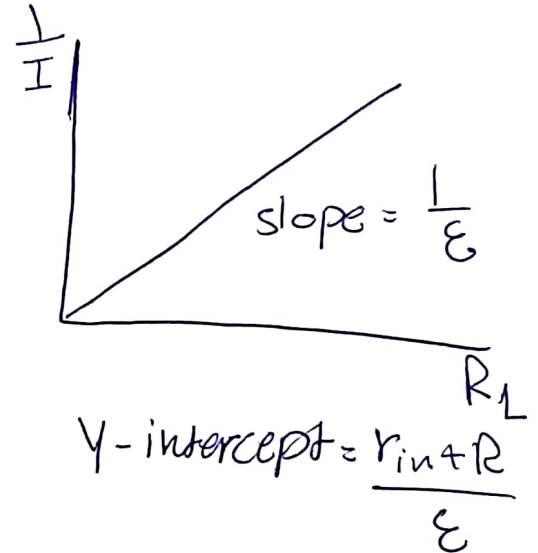


★ Efficiency %: The power dissipated in R_L divided by the power dissipated in the circuit

$$\eta \{R_L\} = \frac{I^2 R_L}{I^2 (R_L + r_{in})} = \frac{R_L}{R_L + r_{in}}$$

procedure

1. Connect the circuit as shown

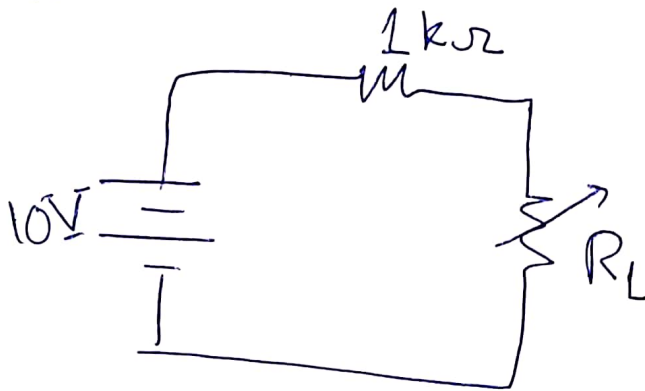

2. Change R_L (0-1 MΩ) and record the I (current)

(take more data points around the value of R_L which satisfies the max power transfer condition)

3. plot $\frac{1}{I}$ with R_L : find ϵ , r_{in}

4. compute $P(R_L)$ and $\eta(R_L)$. From the graph find the value of R_L that satisfies the condition of max power transfer.

