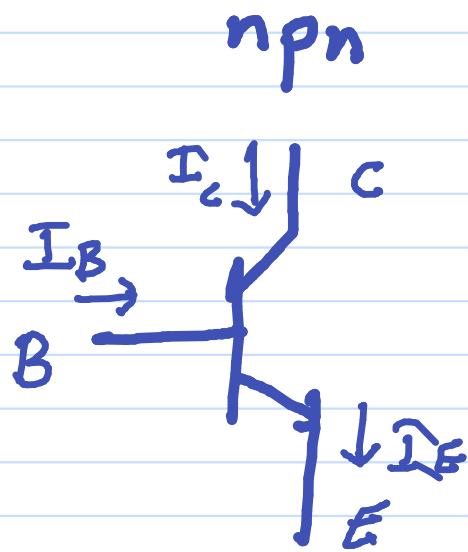


# BJT Transistors





Junction		Mode of operation
BE	BC	
OFF	OFF	Cut-off $\rightarrow I_C = I_B = I_E = 0$
ON	ON	Saturation $\rightarrow V_{CE} = V_{CE(sat)} \approx 0.2V$
ON	OFF	Active/Linear $V_{CE} > V_{CE(sat)}$ $I_C = \beta I_B$ $I_E = I_B + I_C$

## DC Bias

Calculate  $I_B, I_C, I_E, V_{CE}, V_{BC}$

↓ solution

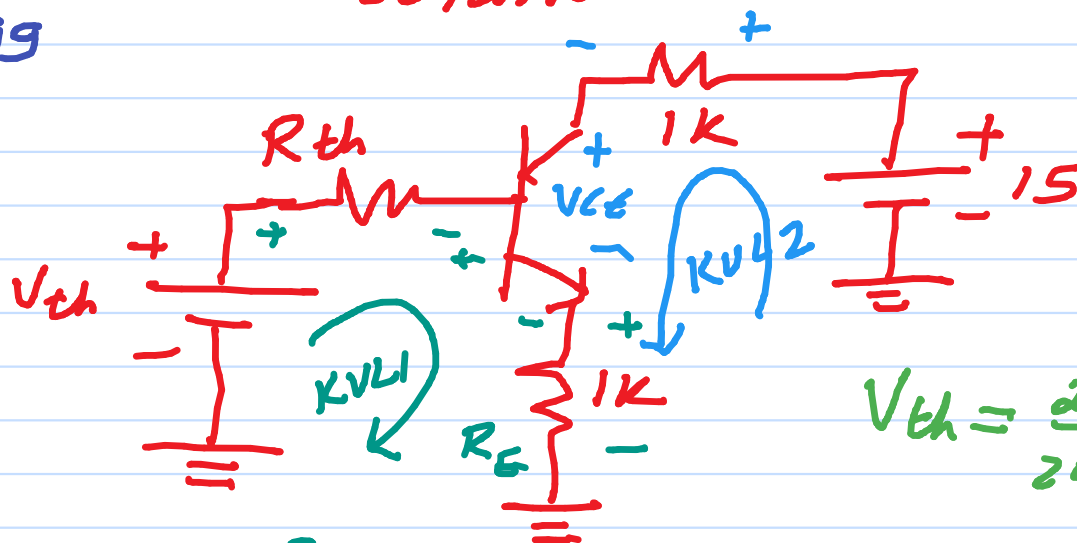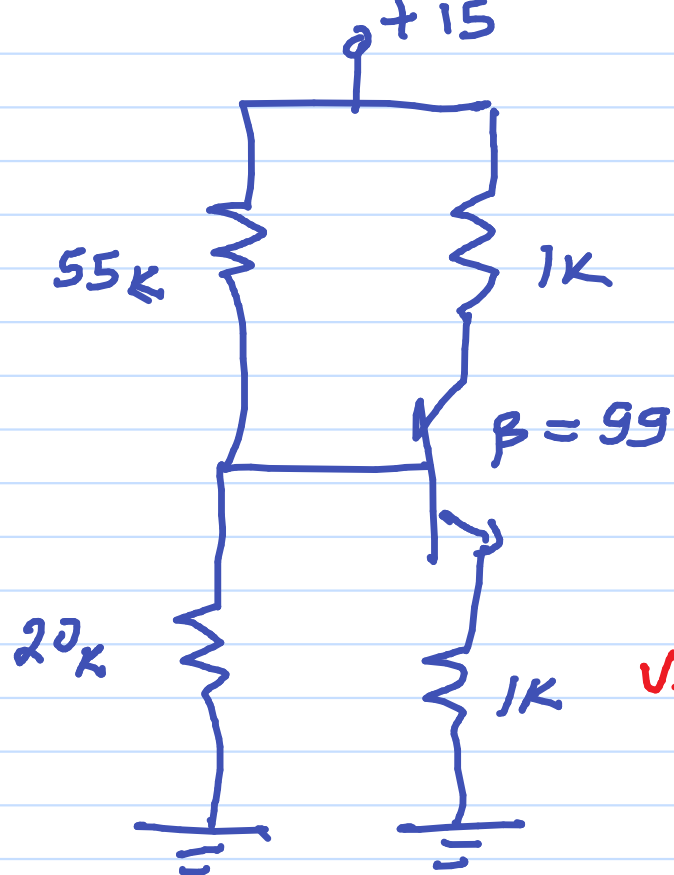

$$V_{th} = \frac{20k}{20k + 55k} \cdot 15$$
$$= 4V$$

$$R_{th} = 20k // 55k = 14.66k$$

KVL 1:  $V_{th} = I_B R_{th} + V_{BE} + I_E R_E$

$$\therefore I_B = \frac{V_{th} - 0.7}{R_{th} + R_E(\beta + 1)} = \frac{4 - 0.7}{14.66k + 1k(99 + 1)} = \frac{3.3}{114.66k} = 28.78 \mu A$$


$$I_C = \beta I_B = 2.85 mA ; I_E = (\beta + 1) I_C = 2.878 mA$$

KVL 2:  $V_{CE} = 15 - I_C \cdot 1k + I_E \cdot 1k = 15 - 2.85 - 2.878 = 9.272 V$


$$V_{BC} = V_{BE} - V_{CE} = 0.7 - 9.27 = -8.57$$

# AC small-signal analysis

Calculate  $A_v$ ,  $Z_i$ ,  $Z_o$

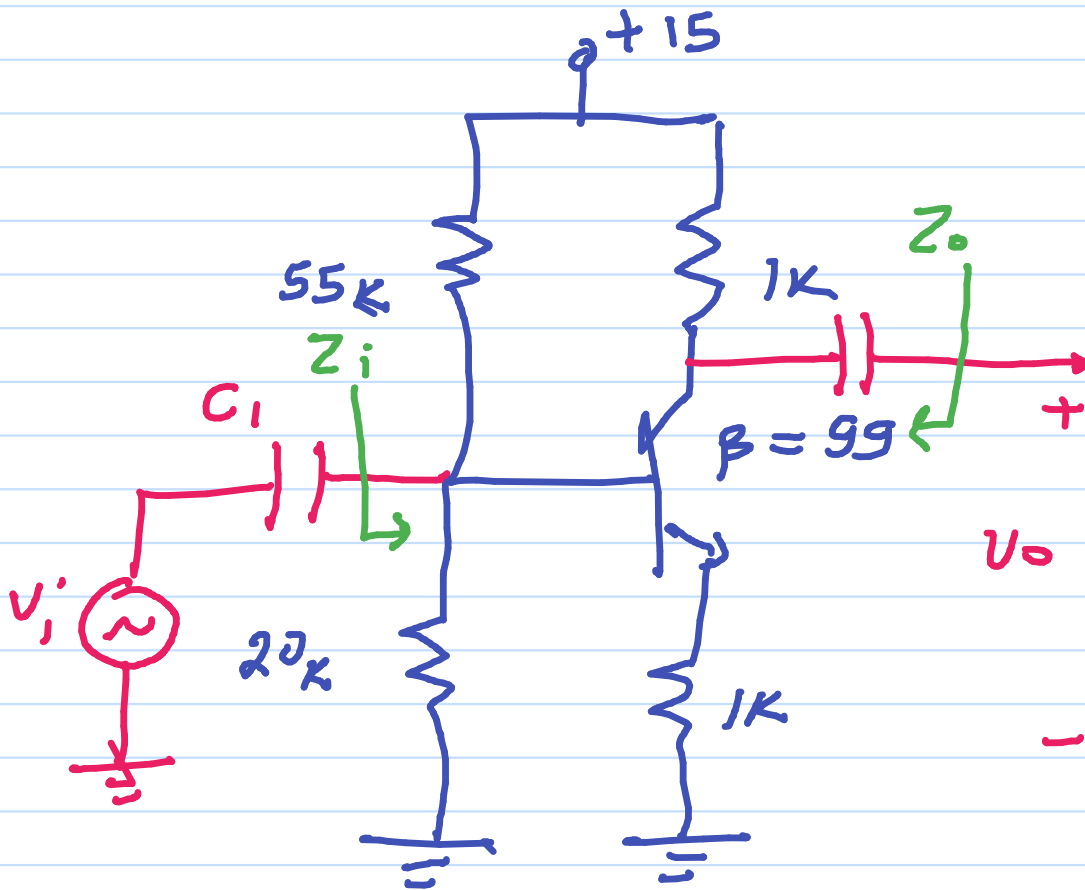

## Solution

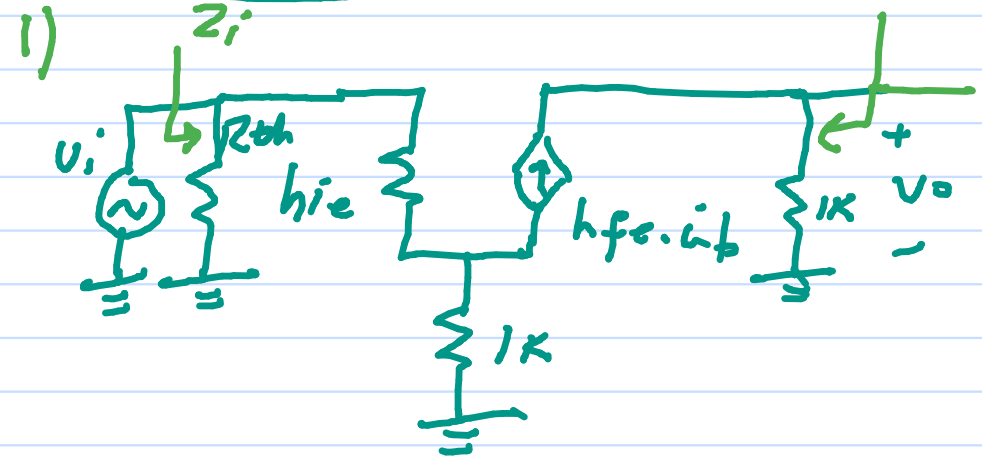

$$V_o = -h_{fe} \cdot i_b (1k)$$

$$i_b = \frac{V_i}{h_{ie} + 1k (h_{fe} + 1)}$$

$$A_v = -\frac{h_{fe} \cdot 1k}{h_{ie} + 1k (h_{fe} + 1)}$$

$$2) Z_i = R_{th} \parallel (h_{ie} + 1k (h_{fe} + 1))$$

$$3) Z_o = 1k$$

$$4) h_{ie} = \frac{V_T}{I_{BQ}} = \frac{25.69mV}{28.78\mu A} = 892\Omega$$