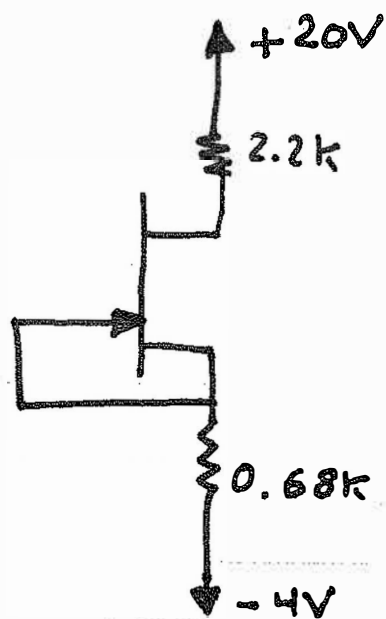


ENEE236 CH7 Homework Solutions

7.10



$$I_{DSS} = 4.5 \text{ mA}$$

$$V_p = -5 \text{ V}$$

$$I_D = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$V_{GS} = 0$$

$$\therefore I_D = I_{DSS} = 4.5 \text{ mA}$$


$$20 = 2.2 \text{ k} I_D + V_D + 0.68 \text{ k} I_D - 4$$

$$\therefore V_D = 11.04 \text{ V}$$

$$V_D = 20 - 2.2 \text{ k} I_D = 10.1 \text{ V}$$

$$V_S = 0.68 \text{ k} I_D - 4 = -0.94 \text{ V}$$

7.11

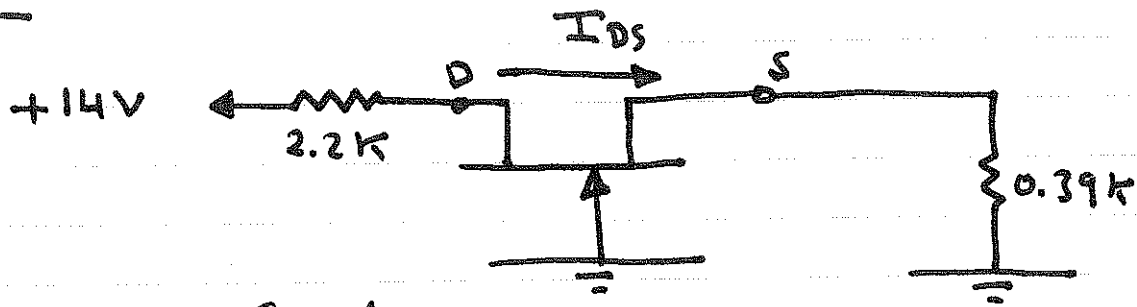

$$I_{DSS} = 6 \text{ mA}$$

$$V_P = -6 \text{ V}$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2 \quad \text{--- ①}$$

$$V_{GS} = V_G - V_S$$

$$V_G = 0 \quad ; \quad V_S = 0.39 \text{ k} I_{DS}$$

$$\therefore V_{GS} = -0.39 \text{ k} I_{DS} \quad \text{--- ②}$$

$$\therefore I_{DS} = 6 \times 10^{-3} \left(1 - \frac{-0.39 \text{ k} I_{DS}}{-6} \right)^2$$

Solving for I_{DS} , we get

$$I_{DS} = 3.55 \text{ mA}$$

$$V_{GS} = -1.384 \text{ V}$$


$$V_S = 1.384 \text{ V}$$

$$V_{DS} = 14 - I_{DS} (2.2 \text{ k} + 0.39 \text{ k})$$

$$V_{DS} = 4.8 \text{ V}$$

$$|V_{DS}| > |V_P| - |V_{GS}| = 4.616 \text{ V} \quad \checkmark$$

7.15

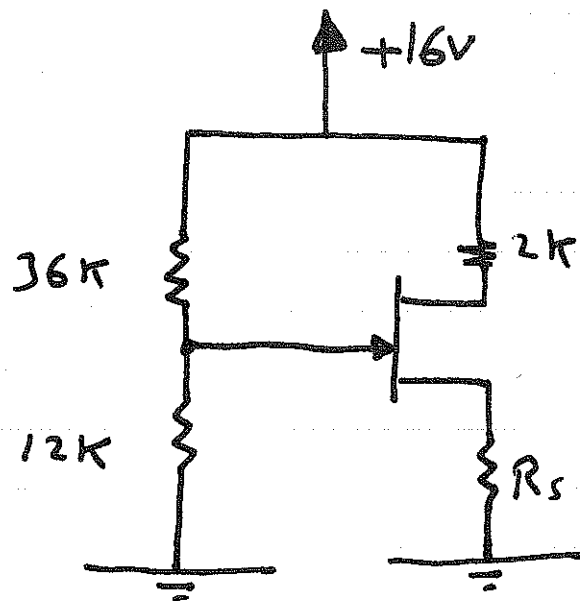

$$I_{DSS} = 12 \text{ mA}$$

$$V_p = -8 \text{ V}$$

$$V_D = 10 \text{ V}$$

$$I_{DS} = \frac{16 - V_D}{2 \text{ K}} = 3 \text{ mA}$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2 = 3 \text{ mA}$$

$$\therefore V_{GS} = V_p \left(1 - \sqrt{\frac{I_{DS}}{I_{DSS}}} \right) = -4 \text{ V}$$


$$V_G = \frac{12 \text{ K}}{12 \text{ K} + 36 \text{ K}} \cdot 16 = 4 \text{ V}$$

$$\therefore V_S = -V_{GS} + V_G = 8 \text{ V}$$

$$V_S = R_S I_{DS}$$

$$\therefore R_S = \frac{V_S}{I_{DS}} = 2.67 \text{ K}$$

7.21

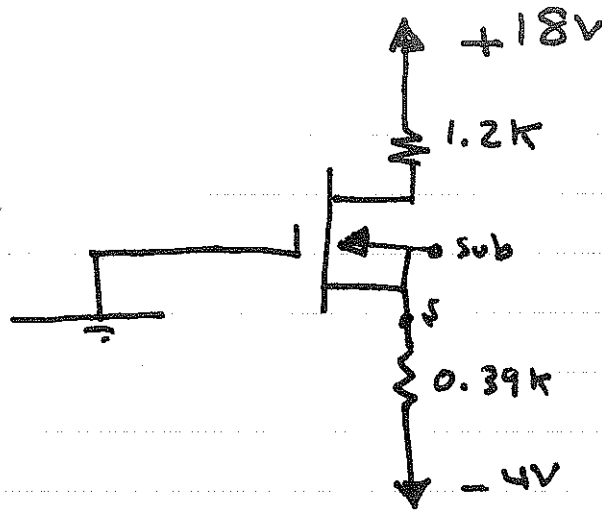

$$I_{DSS} = 8 \text{ mA}$$

$$V_p = -8 \text{ V}$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$V_{GS} = V_G - V_S$$

$$V_G = 0 \quad ; \quad V_S = 0.39 \text{ k} I_{DS} - 4$$

$$\therefore V_{GS} = 4 - 0.39 \text{ k} I_{DS}$$

$$I_{DS} = 8 \times 10^{-3} \left(1 - \frac{4 - 0.39 \text{ k} I_{DS}}{-8} \right)^2$$

Solving for I_{DS} , we get

$$I_{DS} = 9 \text{ mA}$$


$$V_{GS} = 4 - 0.39 \text{ k} I_{DS} = 0.488 \text{ V}$$

$$V_{DS} = 18 - I_{DS} (1.2 \text{ k} + 0.39 \text{ k}) = 7.69 \text{ V}$$

$$V_{DS} > V_{GS} - V_p = 8.488 \quad \times$$

The DMOSFET is in the ohmic region

7.22

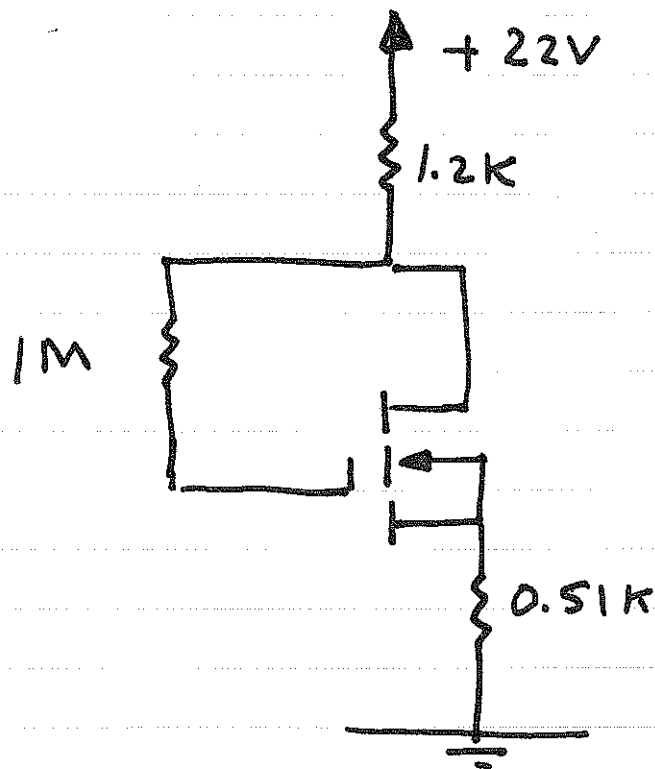

$$K_n = \frac{I_{D(on)}}{[V_{GS(on)} - V_{GS(th)}]^2} = \frac{5mA}{(7-4)^2}$$

$$\therefore K_n = \frac{5}{9} mA/V^2$$

$$I_{DS} = K_n (V_{GS} - V_T)^2 \quad \text{--- (1)}$$

$$V_{GS} = V_G - V_S$$

$$V_G = 22 - 1.2K I_{DS}$$

$$V_S = 0.51K I_{DS}$$

$$\therefore V_{GS} = 22 - 1.71K I_{DS} \quad \text{--- (2)}$$

Sub equation ② into equation ①

and solving for I_{DS} , we get

$$I_{DS} = 8.27 \text{ mA}$$

$$V_{GS} = 22 - 1.71 \text{ k}\Omega I_{DS} = 7.86 \text{ V}$$


$$V_D = 22 - (1.2 \text{ k}\Omega)(8.27 \text{ mA}) \approx 12 \text{ V}$$

$$V_S = R_S I_{DS} = (0.51 \text{ k}\Omega)(8.27 \text{ mA}) = 4.22 \text{ V}$$

$$V_{DS} = V_D - V_S = 7.78 \text{ V}$$

$$|V_{DS}| > |V_{GS} - V_T| = 3.86 \text{ V} \quad \checkmark$$

7.25

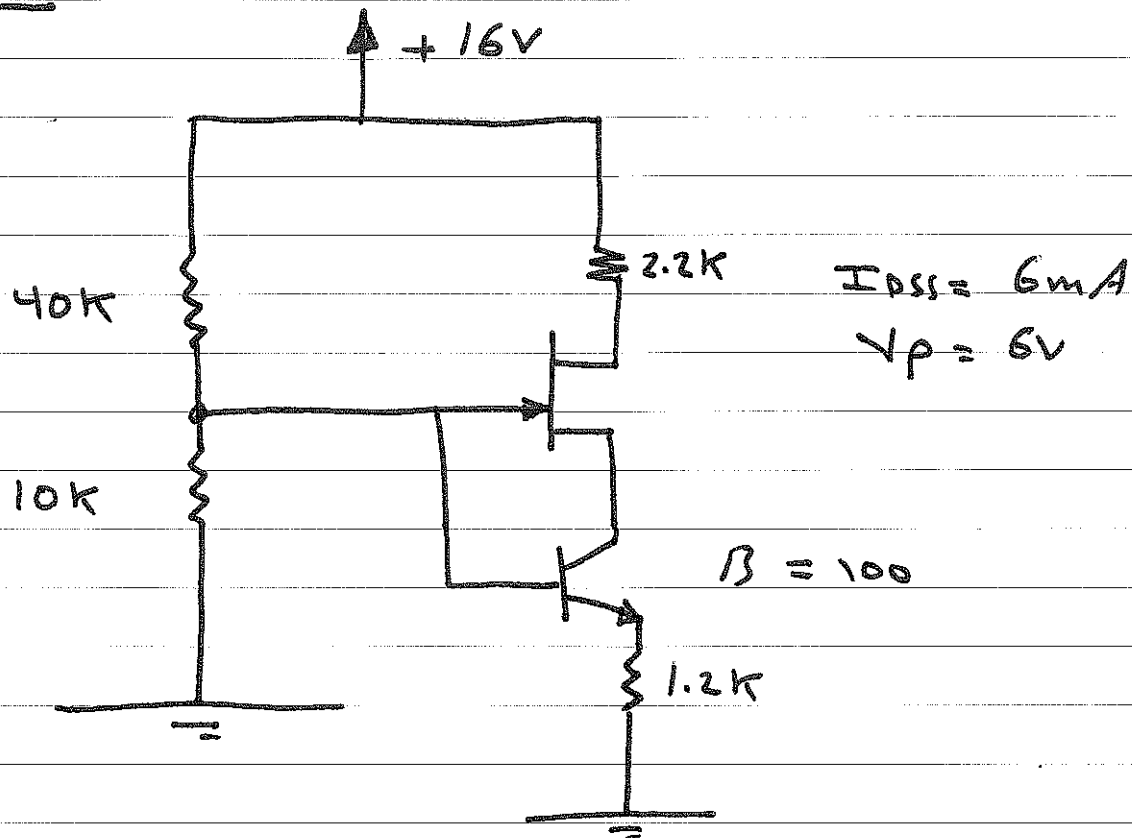

$$R_{TH} = 40k \parallel 10k = 8k$$

$$V_{TH} = \frac{10k}{10k + 40k} (16V) = 3.2V$$

$$V_{TH} = R_{TH} I_B + V_{BE} + 1.2k I_E$$

$$\therefore I_B = \frac{3.2 - 0.7}{8k + (1.2k)(101)} = 19.35 \mu A$$

$$I_C = \beta I_B = 1.935 mA$$

$$I_{DS} = I_C = 1.935 mA$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$\therefore V_{GS} = V_p \left(1 - \sqrt{\frac{I_{DS}}{I_{DSS}}} \right) = -2.6V$$

$$V_C = V_B - V_{GS}$$

$$V_B = 3.2 - 8k I_B \approx 3V$$

$$\therefore V_C = 5.6V$$

$$V_E = V_B - V_{BE} \approx 2.3V$$