

(ايجوز ان افسح لنفسي في مباح الملاهي) ؟
فقال :

(عند نفسك من الغفلة ما يكفيها) (٢) .

ch.6) structure of discrete time system

$$H(z) = \frac{b_0 + b_1 z^{-1}}{1 - \alpha z^{-1}}, \text{ find DE?}$$


$$y[n] = b_0 x[n] + b_1 x[n-1] + \alpha y[n-1]$$

① $x_1[n] \rightarrow \oplus \rightarrow y[n]$, $y[n] = x_1[n] + x_2[n]$ } addition

② $x[n] \xrightarrow{b_0} y[n]$, $y[n] = b_0 x[n]$ } multiplication

③ $x[n] \rightarrow [z^{-1}] \rightarrow y[n]$, $y[n] = x[n-1]$ } time shifting

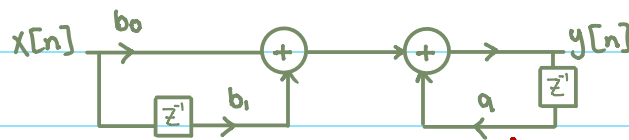Direct Form I : means delay then multiply




• first order

• IIR (since there is feed back)

note that this is infinite loop.

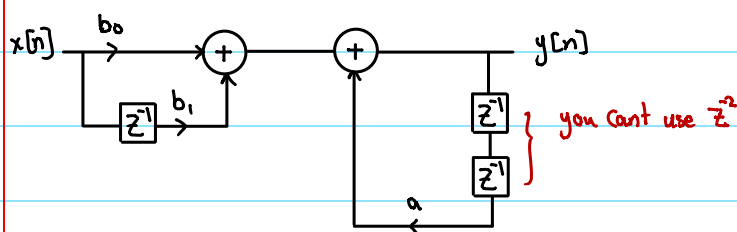
Example 8- $H(z) = \frac{b_0 + b_1 z^{-1}}{1 - \alpha z^{-2}}$

$$y[n] = b_0 x[n] + b_1 x[n-1] + \alpha y[n-2]$$



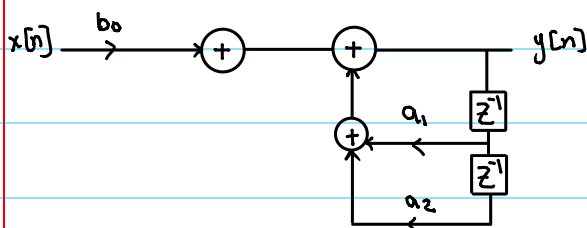Example:- $H(z) = \frac{b_0}{1 - \alpha_1 z^{-1} - \alpha_2 z^{-2}}$


$$y[n] = b_0 x[n] + \alpha_1 y[n-1] + \alpha_2 y[n-2]$$



• 2nd order

Example:- $H(z) = \frac{2z^{-1}}{1-2z^{-2}}$

$y[n] = 2x[n-1] + 2y[n-2]$

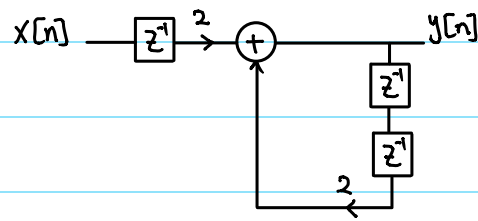

* 2 multiplication

* 1 addition

* 2 shifting

* don't Count multiplications if it scaled by 1


$y[n] = x[n] * h[n]$

$= x[n] * (h_1[n] * h_2[n])$


$= x[n] * (h_2[n] * h_1[n])$

Direct Form II : Means share the delay between the input and output

Direct form I

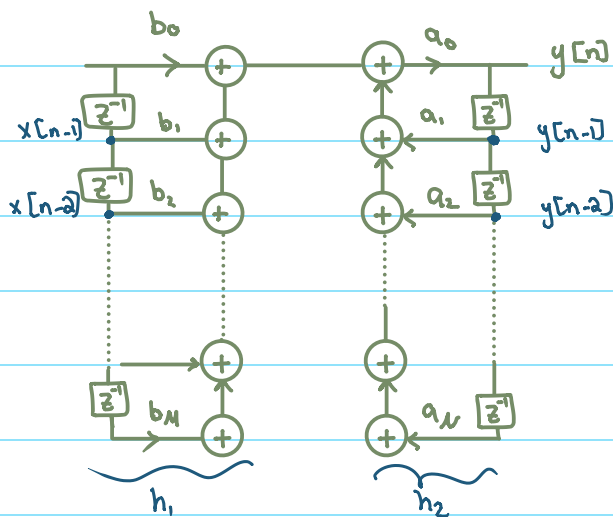


Direct form II

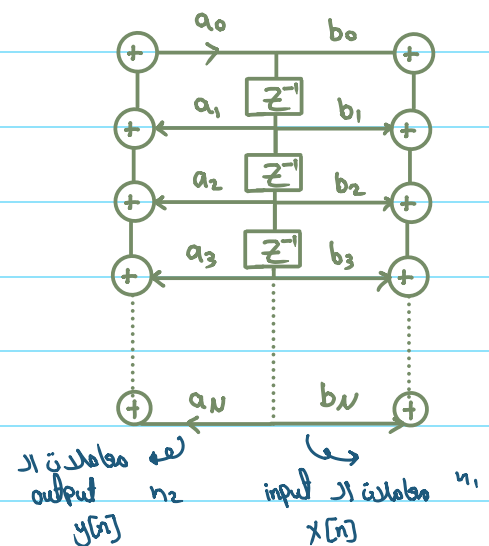

* الفكرة في Direct form II إنه اختصرنا فيها عدد z^{-1} ولأن هذا لا يعني إنه اوقت أقل.


example: $H(z) = \frac{1+2z^{-1}}{1-1.5z^{-1}+0.9z^{-2}}$, Draw Direct form I, Direct form II.
 $y[n] = x[n] + 2x[n-1] + 1.5y[n-1] - 0.9y[n-2]$

① Direct form I

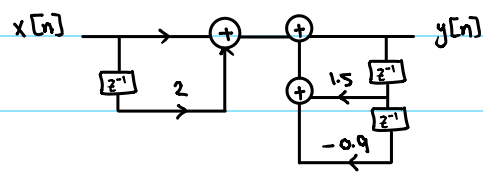


- 3 adders, 3 multipliers, 3 delay
- 2nd order

② Direct form II

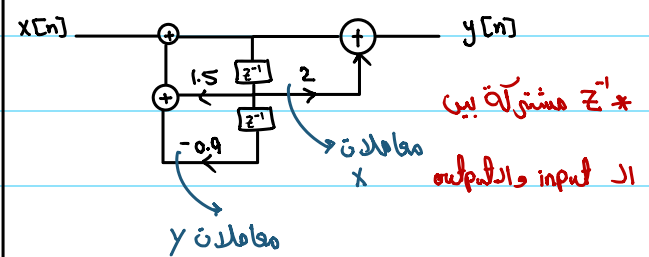

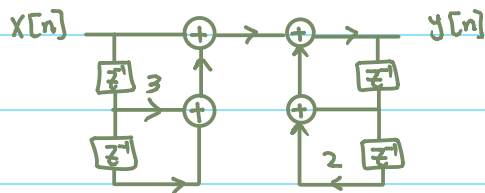Examples- From Direct form I find :- 1) DE, 2) $H(z)$, 3) Direct form II




1) DE $\rightarrow y[n] = x[n] + 3x[n-1] + x[n-2] + y[n-1] + 2y[n-2]$

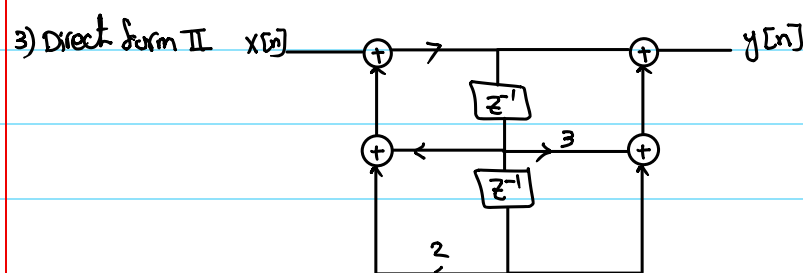2) $H(z) \rightarrow Y(z) = X(z) + 3z^{-1}X(z) + z^{-2}X(z) + z^{-1}Y(z) + 2z^{-2}Y(z)$

$Y(z)(1 - z^{-1} - 2z^{-2}) = X(z)[1 + 3z^{-1} + z^{-2}]$


$\frac{Y(z)}{X(z)} = \frac{(1 + 3z^{-1} + z^{-2})}{(1 - z^{-1} - 2z^{-2})} = H(z)$



- we have 2 multiplications and 4 additions
- in direct form I, it requires 4 storage registers, However, in direct form II it requires 2.





Signal flow graph

- Branch , - Node

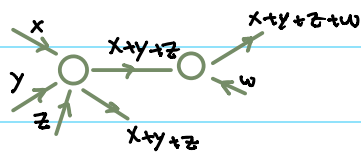


○ → Source

→ ○ Sink

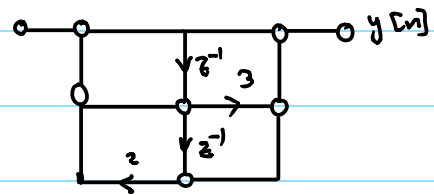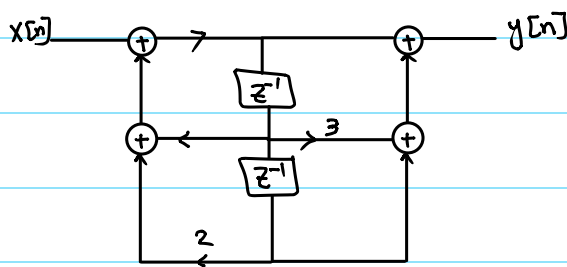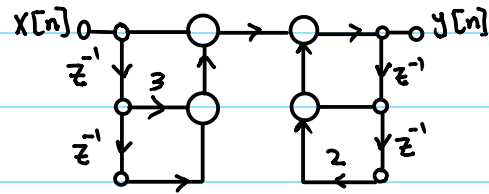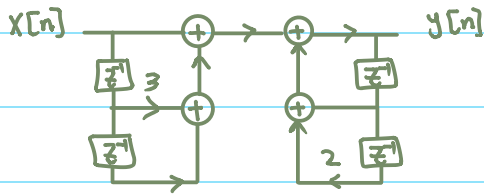

Examples:-

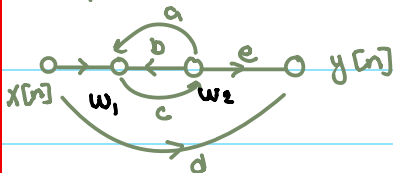



$$w_1[n] = X[n] + a w_2[n] + b w_2[n]$$

$$w_2[n] = c w_1[n]$$


$$y[n] = d w_1[n] + e w_2[n]$$

Example:- first order digital filter $H(z) = \frac{b_0 + b_1 z^{-1}}{1 - a z^{-1}}$

$$y[n] = a y[n-1] + b_0 x[n] + b_1 x[n-1]$$

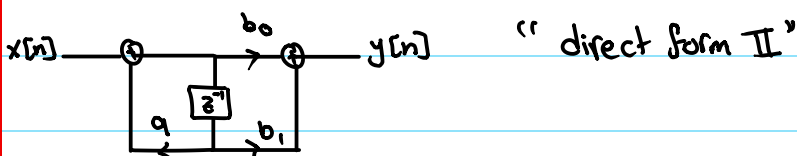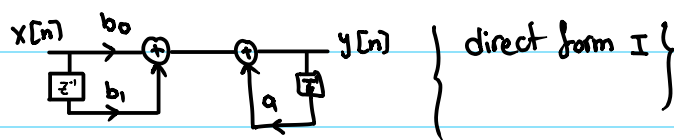

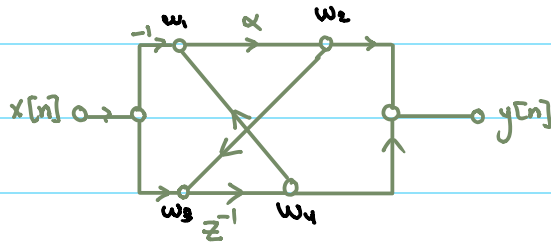Example 8- Find the System Function $H(z)$?



$$w_1[n] = w_4 - x[n] \quad \longleftrightarrow \quad w_1[z] = w_4[z] - x[z]$$

$$w_2[n] = \alpha w_1 \quad \longleftrightarrow \quad w_2[z] = \alpha w_1[z]$$

$$w_3[n] = w_2 + x[n] \quad \longleftrightarrow \quad w_3[z] = w_2[z] + x[z]$$

$$w_4[n] = w_3[n-1] \quad \longleftrightarrow \quad w_4[z] = z^{-1} w_3[z]$$

$$y[n] = w_4 + w_2 \quad \longleftrightarrow \quad y[z] = w_4[z] + w_2[z]$$

$$\begin{aligned} \textcircled{1} \quad w_4[z] &= z^{-1} w_3[z] \\ &= z^{-1} (w_2[z] + x[z]) \end{aligned}$$

$$w_4[z] = z^{-1} w_2[z] + z^{-1} x[z] \rightsquigarrow \textcircled{*1}$$

$$\textcircled{2} \quad w_2[z] = \alpha w_1[z]$$

Substitute $\textcircled{1}$ and $\textcircled{2}$ in $y[z]$

$$= \alpha (w_4[z] - x[z])$$

$$w_2[z] = \alpha w_4[z] - \alpha x[z] \rightsquigarrow \textcircled{*2}$$

↳ Substitute $\textcircled{1}$

$$w_2[z] = \alpha (z^{-1} w_2[z] + z^{-1} x[z]) - \alpha x[z]$$

$$w_2[z] = \alpha z^{-1} w_2[z] + \alpha z^{-1} x[z] - \alpha x[z]$$

$$w_2 (1 - \alpha z^{-1}) = x[z] [\alpha z^{-1} - \alpha]$$

$$w_2 = \left[\frac{\alpha z^{-1} - \alpha}{1 - \alpha z^{-1}} \right] x[z] \rightsquigarrow \textcircled{*}$$

$$w_4 = z^{-1} w_2 + z^{-1} x[z]$$

$$= z^{-1} \left[\frac{\alpha z^{-1} - \alpha}{1 - \alpha z^{-1}} \right] x[z] + z^{-1} x[z]$$

$$= x[z] \left[\frac{\alpha z^{-2} - \alpha z^{-1}}{1 - \alpha z^{-1}} + z^{-1} \right]$$

$$= x(z) \left[\frac{\cancel{\alpha z^2} - \alpha z^{-1} + \cancel{z} - \cancel{\alpha z^2}}{1 - \alpha z^{-1}} \right]$$

$$w_4 = x(z) \left[\frac{-\alpha z^{-1} + z^{-1}}{1 - \alpha z^{-1}} \right]$$

$$y = w_4 + w_2$$

$$= x(z) \left[\frac{-\cancel{\alpha z^{-1}} + z^{-1}}{1 - \alpha z^{-1}} \right] + x(z) \left[\frac{\cancel{\alpha z} - \alpha}{1 - \alpha z^{-1}} \right]$$




$$y(z) = x(z) \left[\frac{z^{-1} - \alpha}{1 - \alpha z^{-1}} \right]$$

$$H(z) = \frac{z^{-1} - \alpha}{1 - \alpha z^{-1}}$$

$$h[n] = (\alpha)^{n-1} u[n-1] - (\alpha)^{n+1} u[n]$$

$$y[n] = \alpha y[n-1] + x[n-1] - \alpha x[n]$$

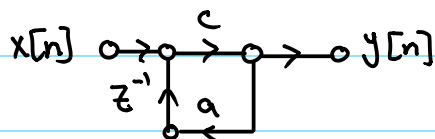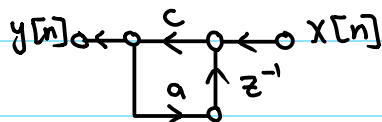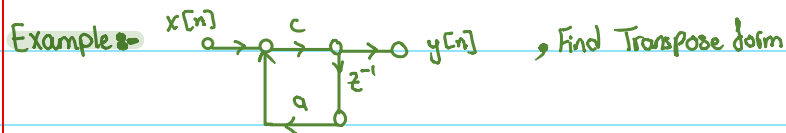- 1) Reverse Direction for all Branches.
- 2) Interchange Input and output.
- 3) Flip the structure to make the input to the left and the output to the right.





$$y[n] = (x[n] + ay[n-1])c$$

$$y[n] = cx[n] + acy[n-1]$$

$$y[z] = cx[z] + acz^{-1}y[z]$$




$$y[z](1 - acz^{-1}) = cx[z]$$

$$H(z) = \frac{c}{1 - acz^{-1}}$$

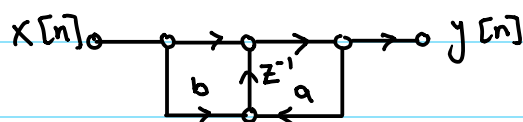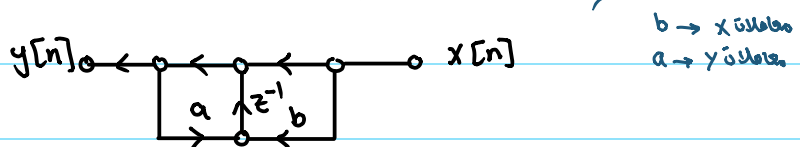

$$y[n] = x[n] + bx[n-1] + ay[n-1]$$

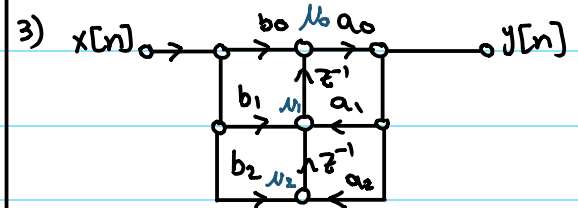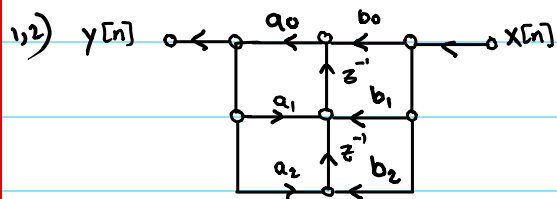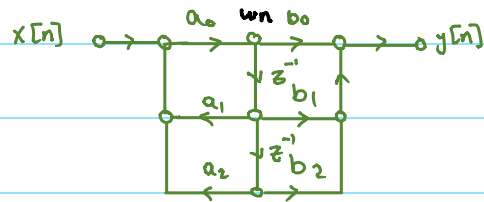Example 8- Second-order IIR system , Draw the transposed form ?




$$w_0 = b_0 x[n] + w_1(n-1)$$

$$w_1 = b_1 x[n] + a_1 w_0 + w_2(n-1)$$

$$w_2 = b_2 x[n] + a_2 w_0$$

ربنا تقبل منا إنك
أنت السميع العليم ..

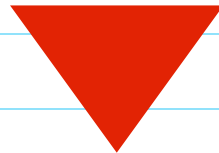

suggested problems



system function?

