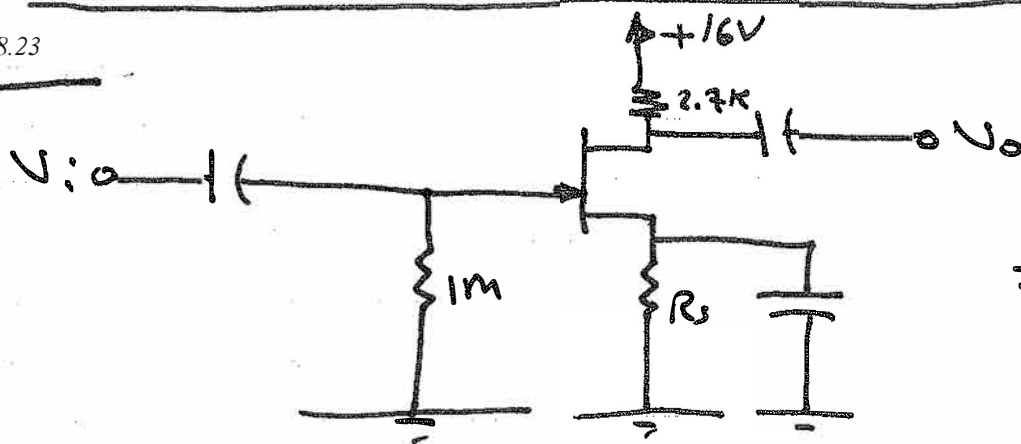



8.23



$$I_{DSS} = 9 \text{ mA}$$

$$V_P = -8 \text{ V}$$

ac small signal equivalent circuit:

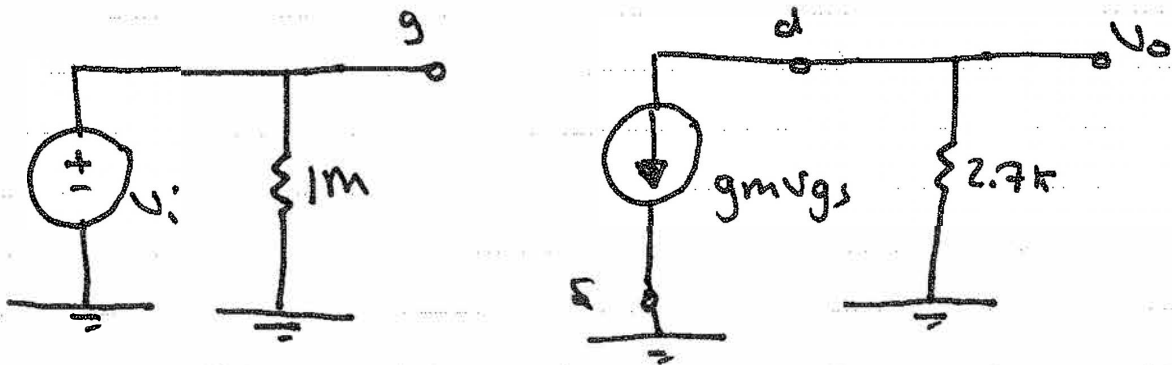

$$V_o = -g_m V_{gs} (2.7 \text{ k})$$

$$V_{gs} = V_o - V_s = V_i$$

$$\therefore A_v = \frac{V_o}{V_i} = -g_m (2.7 \text{ k}) = -2$$

$$\therefore g_m = 0.741 \text{ mA/V}$$

$$g_m = \frac{-2 I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P} \right)$$

$$\therefore V_{GS} = -5.37 \text{ V}$$

-1-

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$

$$\therefore I_{DS} = 0.973 \text{ mA}$$

$$\therefore V_{GS} = V_G - V_S = 0 - R_S I_{DS} = -5.37 \text{ V}$$

$$\therefore R_S = \frac{5.37}{0.973} = 5.5 \text{ k}$$

b) if $r_{ds} = 30 \text{ k}$

$$A_{vo} = -g_m r_{gs} (2.7 \text{ k} \parallel 30 \text{ k}) = -2$$


$$\therefore g_m = 0.8 \text{ mA/V}$$

$$\therefore V_{GS} = -5.129 \text{ V}$$


$$\therefore I_{DS} = 1.159 \text{ mA}$$

$$\therefore R_S = 4.425 \text{ k}$$

8.46

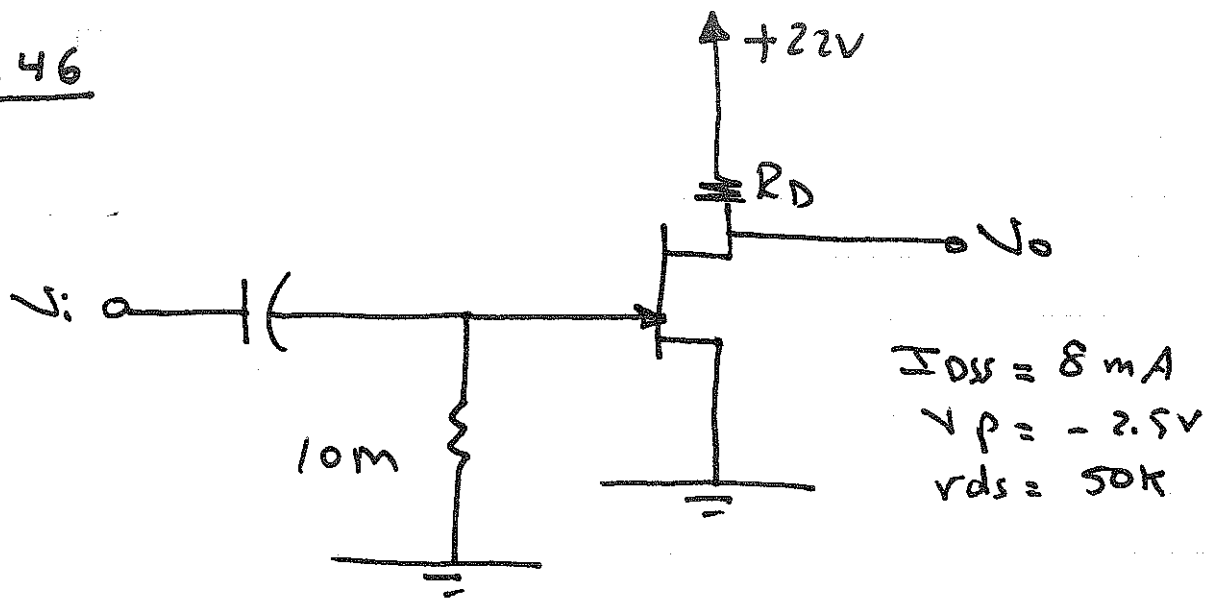

ac small signal equivalent circuit:

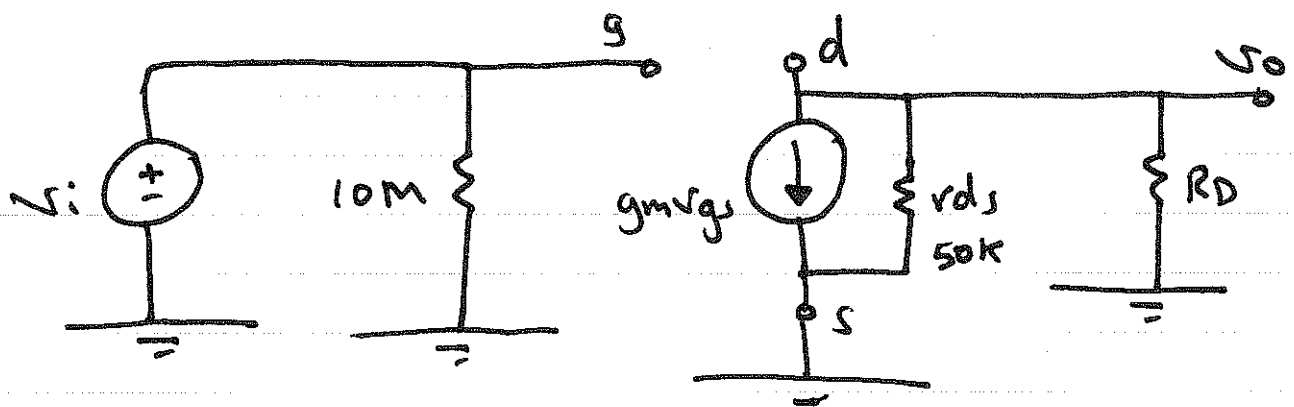

$$V_o = -g_m v_{gs} (50k \parallel R_D)$$

$$g_m = \frac{-2 I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p} \right)$$


$$\nabla G_s = 0$$

$$\therefore g_m = 6.4 \text{ mA/V}$$

$$A_v = -8 = -g_m (50k \parallel R_D)$$

$$\therefore R_D = 1.28 \text{ k}$$

8.47

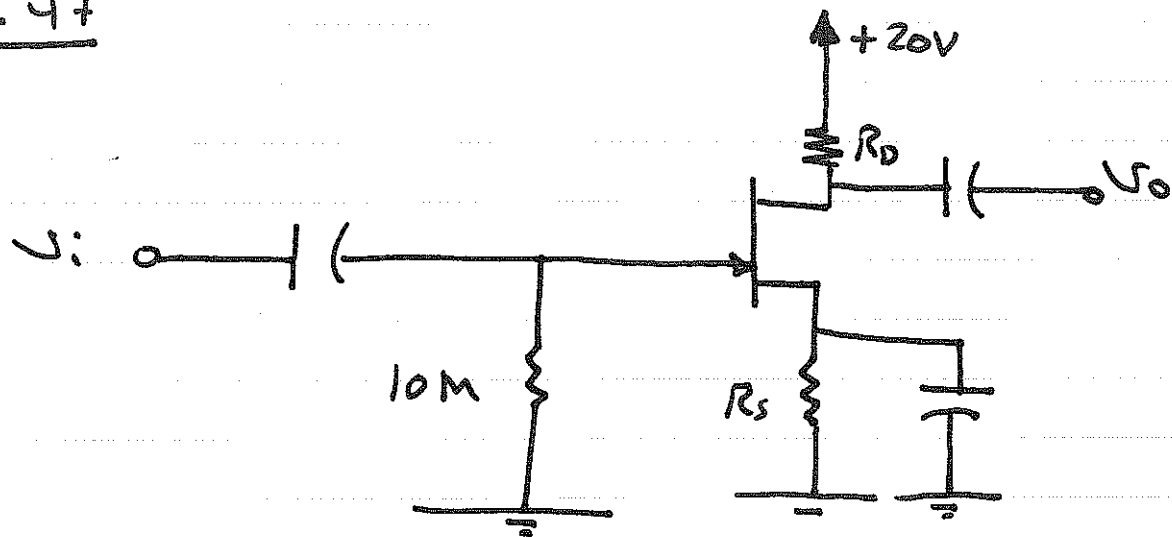


$$I_{DSS} = 12\text{mA}$$

$$V_p = -3\text{V}$$

$$r_{ds} = 40\text{k}\Omega$$

$$V_{GS} = -1\text{V}$$

ac small signal equivalent circuit:

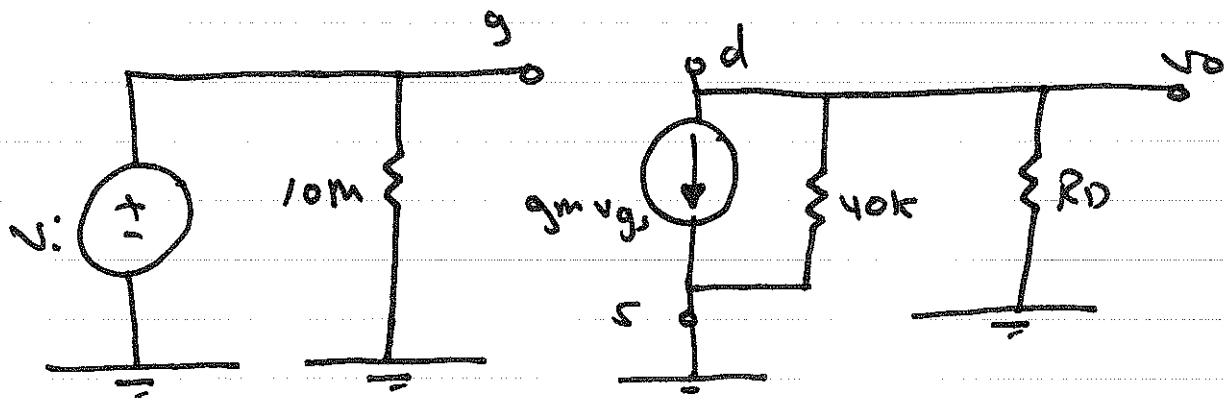

$$A_v = -g_m (R_D \parallel 40\text{k}) = -10$$

$$g_m = \frac{-2 I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p} \right)$$

$$V_{GS} = -1\text{V}$$

$$\therefore g_m = 5.33\text{mA/V}$$

\therefore for $A_v = -10$

$$R_D = 1.97 \text{ k}$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_P} \right)^2$$


$$\therefore I_{DS} = 5.77 \text{ mA}$$

$$V_{GS} = -1 = V_G - V_S = 0 - R_S I_{DS}$$

$$\therefore R_S = \frac{1 \text{ V}}{5.77 \text{ mA}} = 0.187 \text{ k}$$

8.56

DC Analysis :

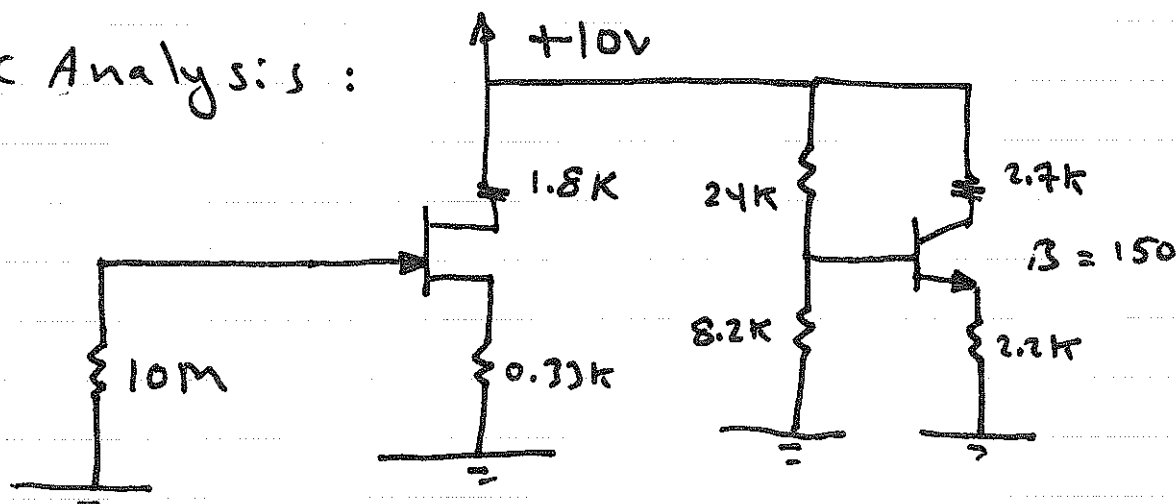

$$I_{DSS} = 6 \text{ mA} , V_p = -3 \text{ V}$$

$$I_{DS} = I_{DSS} \left(1 - \frac{V_{GS}}{V_p} \right)^2$$

$$V_{GS} = V_G - V_S = (-0.33 \text{ K}) I_{DS}$$

Solving for I_{DS} , we get

$$I_{DS} = 2.84 \text{ mA}$$

$$R_{TH} = 24 \text{ K} \parallel 8.2 \text{ K} = 6.11 \text{ K}$$

$$V_{TH} = \frac{8.2 \text{ K}}{8.2 \text{ K} + 24 \text{ K}} (+10) = 2.55 \text{ V}$$

$$\therefore I_E = \frac{2.55 - 0.7}{2.2 \text{ K} + \frac{6.11 \text{ K}}{151}} = 0.824 \text{ mA}$$

$$V_{CE} = 10 - 2.7 \text{ K} I_C - 2.2 \text{ K} I_E \approx 5.96 \text{ V}$$

$$V_{DS} = 10 - (1.8 \text{ K} + 0.33 \text{ K}) I_{DS} = 3.95 \text{ V}$$

$$V_D = 10 - (1.8k)(2.84mA) = 4.89V$$

$$V_S = (0.33k)(2.84mA) = 0.937V$$

$$\therefore V_{DS} = 3.95V ; V_G = 0$$

$$|V_{DS}| > |V_P| - |V_G|$$

$$|V_{DS}| > 3 - 0.937 = 2.063 \quad \checkmark$$


$$\frac{8.57}{h_{ie}} = \frac{(\beta+1) V_T}{I_E} = 4.71k$$

$$g_m = \frac{-2 I_{DSS}}{V_P} \left(1 - \frac{V_{GS}}{V_P} \right)$$

$$g_m = 2.75 \text{ mA/V}$$

$$V_{GS} = -0.33k I_{DS} = -0.937V$$

ac small signal equivalent circuit:

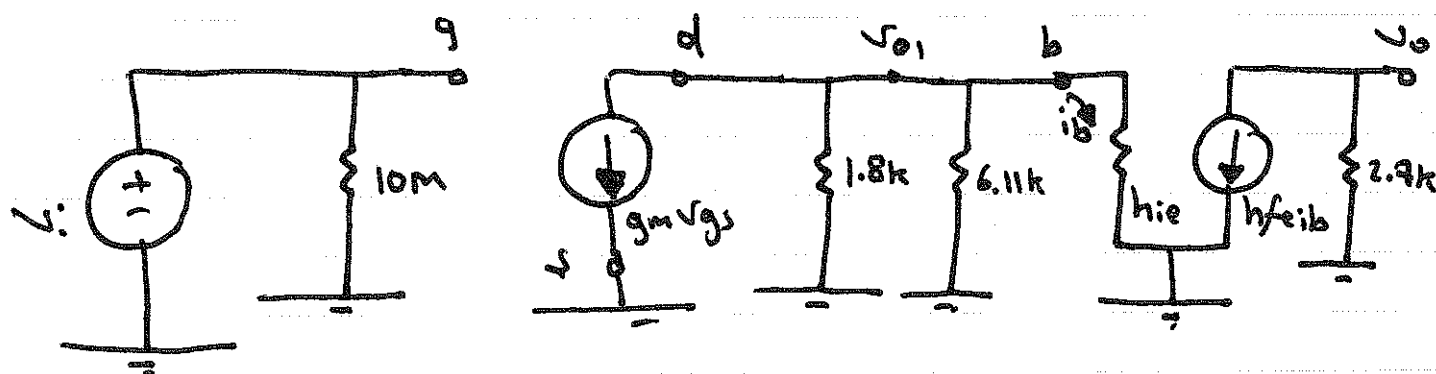

$$A_{v1} = \frac{V_{o1}}{V_i} ; V_{o1} = -g_m V_{gs} (1.8k \parallel 6.11k \parallel h_{ie})$$

$$V_{gs} = V_g - V_s = V_g = V_i$$

$$\therefore A_{v1} = -2.75$$

$$A_{v2} = \frac{V_o}{V_{i2}} = \frac{V_o}{V_{o1}} ; V_o = -h_{feib} (2.7k)$$

$$i_b = \frac{V_{o1}}{h_{ie}}$$

$$\therefore A_{v2} = -85.98$$

$$A_{vt} = A_{v1} \cdot A_{v2} = 236.5$$

8.58

$$Z_i = 10 \text{ M}\Omega$$

$$Z_o = 2.7 \text{ K}\Omega$$