

Circuit Analysis

By

Jibreel Bornat

Chapter 7

Birzeit University

2025

Chapter 7

Natural and Step Response of RL and RC Circuits

In this chapter our goal is to find V and I that shows when energy is either released or acquired on the **conductor (L)** and the **capacitor (C)** in response to the sudden change in a DC voltage or current source

Important Notes :

$t = 0^+$ \rightarrow After the sudden change

$t = 0$ \rightarrow At the sudden change

$t = 0^-$ \rightarrow Before the sudden change

$t(0^-) = t(0^+)$ (VERY IMPORTANT)

What are we going to work on ?

1 - Natural Response :

Find I and V when we don't have a current or voltage source in the circuit , so the is released to a resistance network

2 - Step Response :

Find I and V when we have a current or voltage source in the circuit so the energy is being acquired by L and C

3 - General Case :


We use it to solve both cases above and get the complete response

* هايه الطريقة نعمل وأخذ من يليه فوقه , لذن يليه فوقه لحزم
نتفقه القانون في كل ذال , بالتاليه رح استخدم هايه الطريقة في
كل جميع الخ سلة على القانون العام .

The Rule : $X(t) = X(\infty) + [X(0^+) - X(\infty)] e^{-t/\tau}$

first - The Inductor (L):
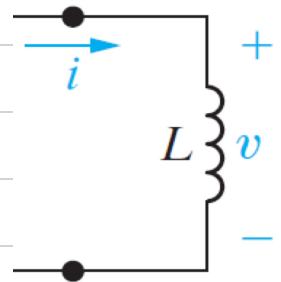
$$V_L = L \frac{di}{dt} \Rightarrow \text{the value of } L \times I \text{ prime}$$



$$I_L(t) = I_L(0) + \frac{1}{L} \int_0^t V_L(t) dt, \quad t \geq 0$$


1 - There is no voltage across the inductor if the current through it is not changing with time, so we convert it into short circuit

2 - a finite amount of energy can be stored in the. Inductor even if the voltage across it is zero, according to the following law


Energy of the inductor:
$$W_L(t) = \frac{1}{2} L I_L^2(t)$$

3 - the inductor never dissipate energy, it only stores energy

$t = 0^+$

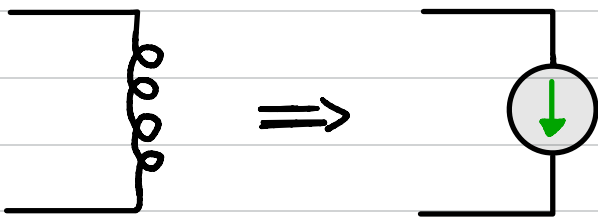

$t = \infty$ AND $t = 0^-$

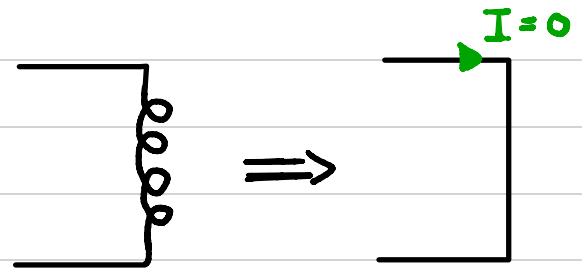


* At $t = 0^+$ the inductor can be considered as a Current source.

* At $t = \infty$ And $t = 0^-$, the inductor can be considered as a short circuit

* The inductor stores Current

Second - The Capacitor :
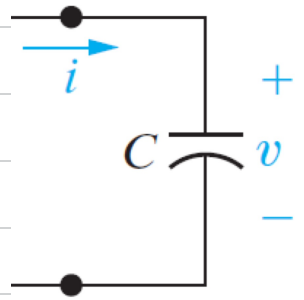
$$I_c = C \frac{dV}{dt} \Rightarrow C \text{ value} * V \text{ prime}$$



$$V_c(t) = V_c(0) + \frac{1}{C} \int_0^t I_c(t) dt, \quad t \geq 0$$

1 - There is no current across the capacitor if the voltage across it is not changing with time, so we convert it into open circuit

2 - a finite amount of energy can be stored in the capacitor even if the current across it is zero, according to the following law

Energy of the Capacitor :
$$W_c(t) = \frac{1}{2} C V_c^2(t)$$

3 - the capacitor never dissipate energy, it only stores energy

$t = 0^+$



$t = \infty$ AND $t = 0^-$



* At $t = 0^+$ the Capacitor can be considered as a Voltage Source.

* At $t = \infty$ And $t = 0^-$, the Capacitor can be considered as a open Circuit

* The Capacitor Stores Voltage


Series parallel combination of inductors and capacitors

1.1 - series inductors :




$$L_{eq} = L_1 + L_2 + L_3$$

1.2 - parallel inductors :

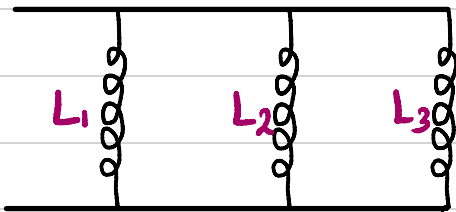


$$\frac{1}{L_{eq}} = \frac{1}{L_1} + \frac{1}{L_2} + \frac{1}{L_3}$$

2.1 - series capacitors :

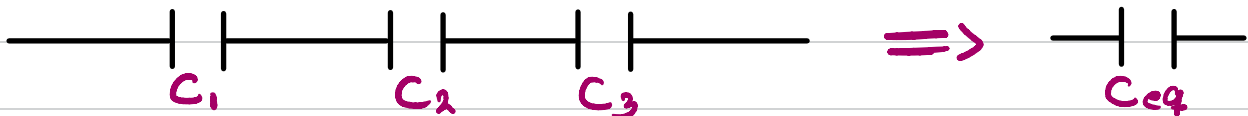

$$\frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2} + \frac{1}{C_3} \Rightarrow C_{eq}$$

2.1 - parallel capacitors :

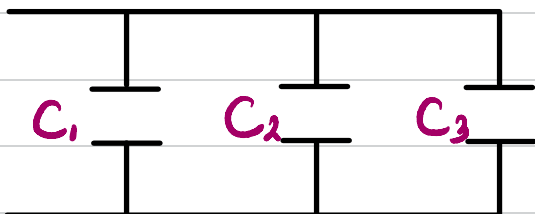

$$C_{eq} = C_1 + C_2 + C_3$$

First Order Circuits (RL and RC)


- * The circuits that include inductor or capacitor BUT not both
- * First order circuit = first order differential equation

1 - Natural Response (discharging):


It happens when we switch from the battery to a resistive network
And it can be RL or RC circuit

① RL circuit

- $I_L(0^+) = I_L(0^-) = \frac{V_s}{R_{eq}} = I_{\text{Current Source}}$
- time constant: $\tau = L / R$
- $i(t) = i(\infty) + [i(0^+) - i(\infty)] e^{-t/\tau}$

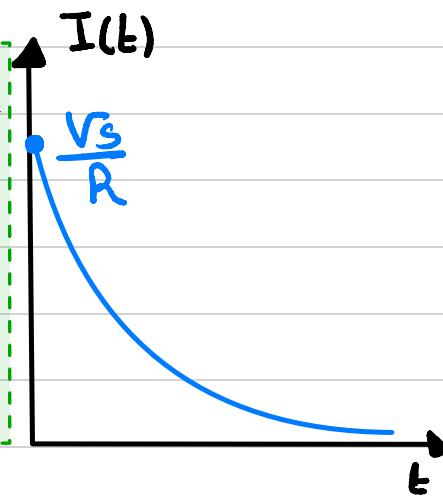

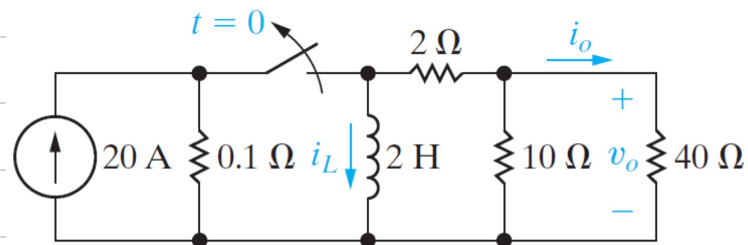Example 1
after switching it out find
1- $I_L(t)$ for $t \geq 0$




Step 1 :-

find $I(0^-)$, from the circuit directly or on the law
Since we have a current source $\Rightarrow I_L(0^-) = 20 \text{ A}$

Step 2 :-

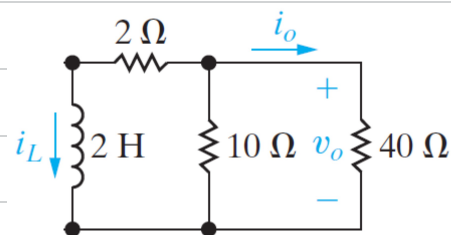After switching we get a natural response circuit, then we find:



1. τ $\tau = L / R$, $R: 10 \parallel 40 + 2 \Rightarrow R = 10 \Omega$
 $\tau = 2 / 10 \Rightarrow \tau = 0.2 \text{ s}$


2. $i(\infty)$ You have to find i when the Capacitor became open circuit or the inductor became short circuit :

We don't have any sources $\Rightarrow i(\infty) = 0$

$$i(t) = i(\infty) + (i(0^+) - i(\infty)) e^{-t/\tau}$$

$$i(t) = 0 + (20 - 0) e^{-5t}$$

$$i(t) = 20 e^{-5t}$$

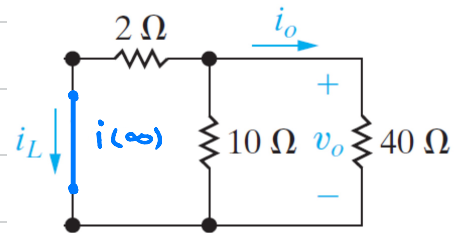

Note : Usually $i(\infty)$ in the natural response is equal to zero because we don't have any source to supply the circuit


2- $I_o(t)$ for $t \geq 0^+$

We use Current divider rule

$$\frac{10}{10 + 40} * (-I_L(t))$$

سالب لأنها
على الذقبة
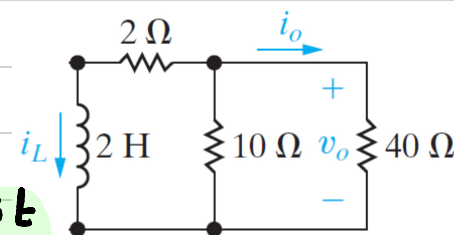
$$= 0.2 * -20 e^{-5t} \Rightarrow I_o(t) = -4 e^{-5t}$$



3- $V_o(t)$ for $t \geq 0^+$

$$V_o = I_o * R_{40} \Rightarrow V_o = -4 e^{-5t} * 40$$


$$\Rightarrow V_o = -160 e^{-5t}$$

② RC circuit

- $V_c(0^-) = V_c(0^+) = V_s$

- time constant : $\tau = RC$

- $V(t) = V(\infty) + [V(0^+) - V(\infty)] e^{-t/\tau}$

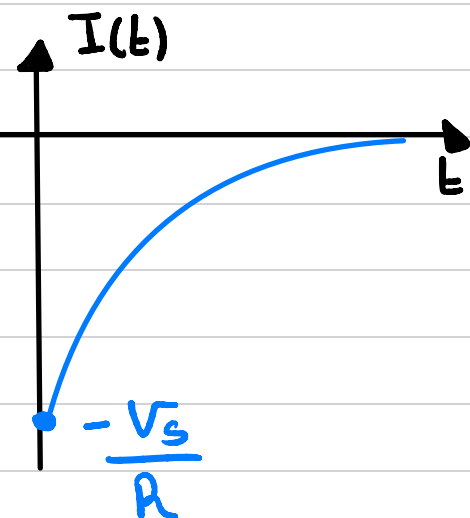


Example 2

After switching $x \rightarrow y$ find

1- $V_C(t)$ for $t \geq 0$

like the steps above
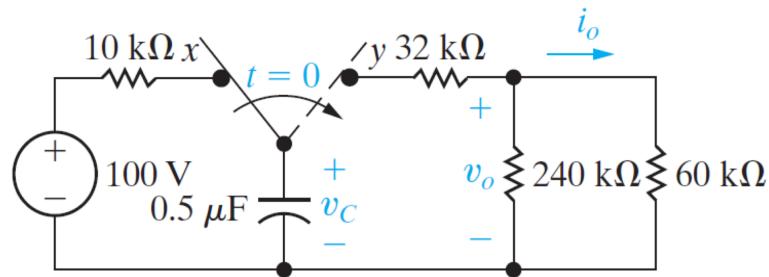
$$V_C(0^-) = V_s \Rightarrow V_C(0^-) = 100$$



$$\tau = RC, R: (240 \parallel 60) + 32 \Rightarrow R = 80 \text{ k}\Omega$$

$$\tau = 0.5 \times 80 \Rightarrow \tau = 40 \text{ ms}$$

$$V(\infty) = 0$$

$$V(t) = 0(100 - 0)e^{-25t} \Rightarrow V(t) = 100e^{-25t}$$

2- $V_o(t)$ for $t \geq 0^+$

by voltage divider rule, $\frac{48}{48+32} \times 100e^{-25t}$

$$V_o(t) = 60e^{-25t} \text{ for } t \geq 0^+$$

3- $I_o(t)$ for $t \geq 0^+$

$$I_o(t) = \frac{60e^{-25t}}{60} \Rightarrow I_o(t) = e^{-25t} \text{ mA}$$

4- Total energy dissipated by 60 k Ω

step 1

find the power at 60 k $\Omega \Rightarrow P = I_o^2 \times R$

$$P = (e^{-25t})^2 \times 60 \text{ k} \Rightarrow P = 60e^{-50t} \text{ mW}$$

Step 2

do integration from ZERO to ∞

$$W = \int_0^{\infty} 60e^{-50t} dt = 0 - (-60/50) \Rightarrow W = 1.2 \text{ mJ}$$

Example 3 for Step response

1- find $i(t)$


we do source transformation to get $V_s = IR \Rightarrow V_s = 80$

$$i(0^-) = \frac{V_s}{R} \Rightarrow i(0^-) = -8A$$

$$i(\infty) = \frac{V}{R} = \frac{24}{2} \Rightarrow i(\infty) = 12A$$

$$\tau = L/R \Rightarrow \tau = (200 \times 10^{-3})/2 \Rightarrow \tau = 0.1$$
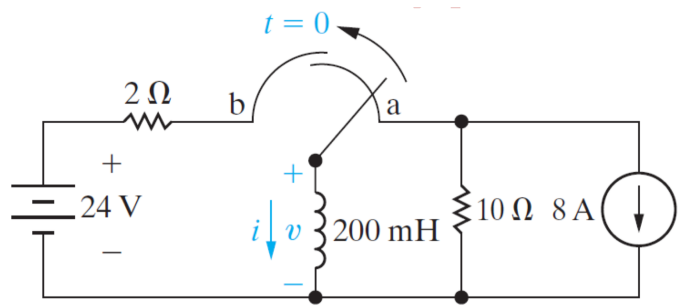
$$i(t) = 12 + (-8 - 12)e^{-\frac{t}{0.1}} \Rightarrow i(t) = 12 - 20e^{-10t}$$



2- V at inductor after switching to b

$$V = L \frac{di}{dt} \Rightarrow V = 0.2 \times 200 e^{-10t} \Rightarrow V = 40 e^{-10t}$$


3- t when the Voltage of the inductor = 25V

from the law above $V = 40 e^{-10t}$

$$25 = 40 e^{-10t} \Rightarrow \frac{25}{40} = e^{-10t} \Rightarrow \ln\left(\frac{25}{40}\right) = \ln e^{-10t}$$

$$-0.47 = -10t \Rightarrow t = 0.047 \text{ s}$$

*** Note :** $i(0^+) = i(0^-)$ Just for the inductor
 $V(0^+) = V(0^-)$ Just for the Capacitor

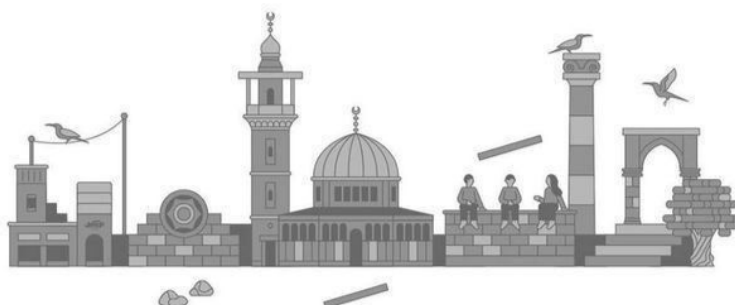

Example 4 : Dependent Source


1- find $V(t)$

Step 1

Normally find i at $t=0^-, \infty$


$$i(0^-) = 10/5 \Rightarrow i(0^-) = 2$$

$$V(\infty) = 0$$

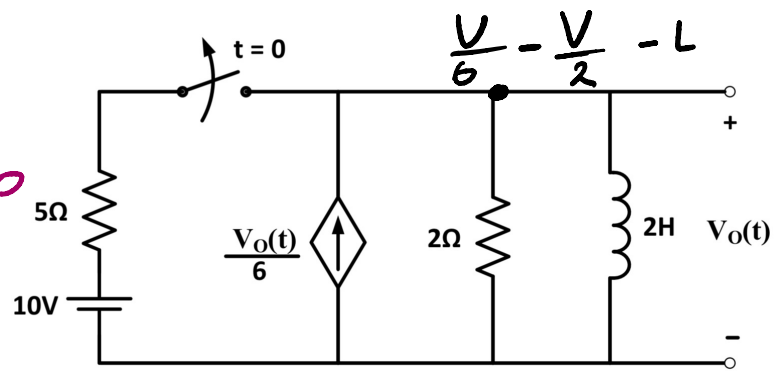

Step 2

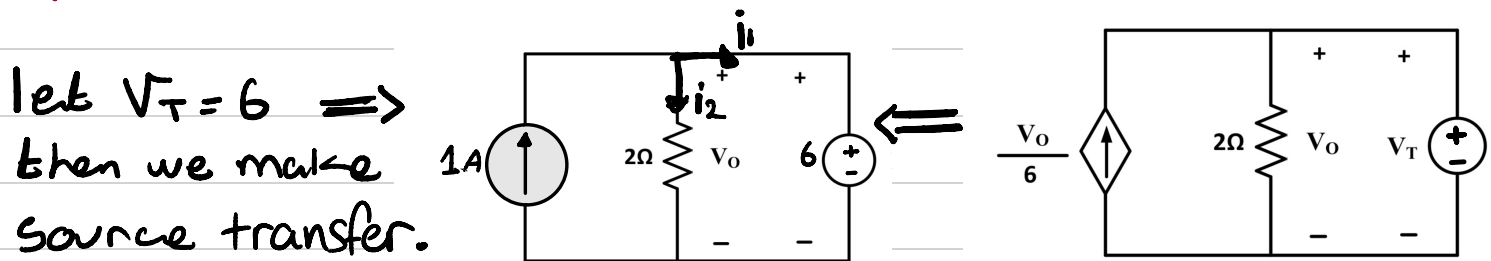Since we have dependent source we find Thevenin equivalent circuit at $t = \infty$



let $V_T = 6 \Rightarrow$
then we make
source transfer.

and apply KVL

$$-6 + 2i_T + 2 = 0 \Rightarrow 2i_T = 4 \Rightarrow i_T = 2A$$

$$R_{th} = \frac{V_T}{i_T} \Rightarrow R_{th} = \frac{6}{2} \Rightarrow R_{th} = 3\Omega$$


$$\tau = L / R_{th} \Rightarrow \tau = \frac{2}{3}$$

Step 3

find V or i at $t=0^+$ Using KCL

- Capacitor \rightarrow Voltage source

- Inductor \rightarrow Current source

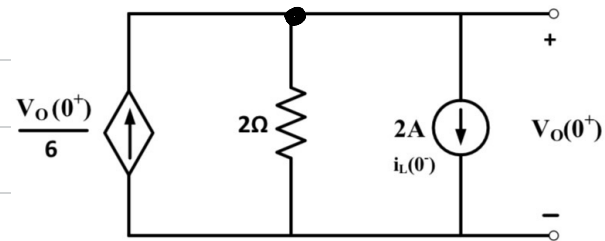

$$\frac{V_O}{6} - \frac{V_O}{2} - 2 = 0 \Rightarrow V_O = V(0^+) = -6V$$

$$V(t) = 0 + (-6 - 0)e^{-\frac{3t}{2}} \Rightarrow V(t) = -6e^{-\frac{3t}{2}}$$