



## ENEE236 CH4 Homework Problems

10. Given the information provided in Fig. 4.123, determine:

- a.  $R_C$ .
- b.  $R_E$ .
- c.  $R_B$ .
- d.  $V_{CE}$ .
- e.  $V_B$ .

11. Given the information provided in Fig. 4.124, determine:

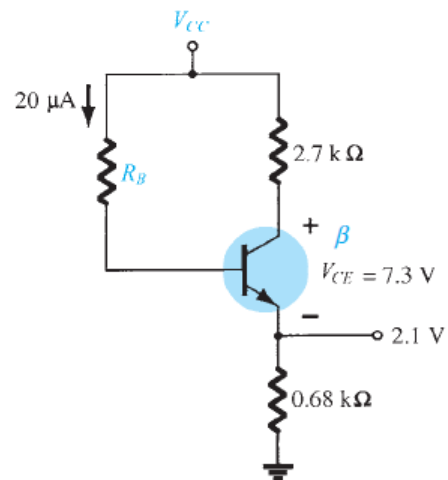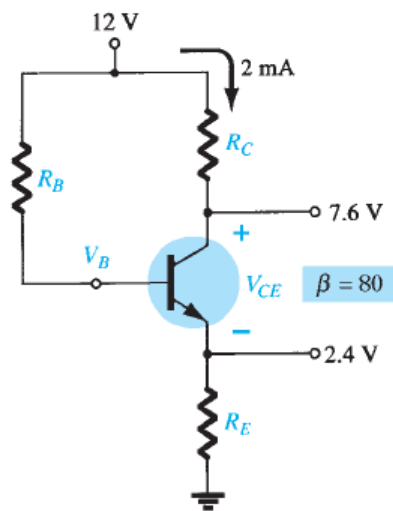- a.  $\beta$ .
- b.  $V_{CC}$ .
- c.  $R_B$ .



18. Given the information appearing in Fig. 4.127, determine:

- a.  $I_C$ .
- b.  $V_E$ .
- c.  $V_{CC}$ .
- d.  $V_{CE}$ .
- e.  $V_B$ .
- f.  $R_1$ .


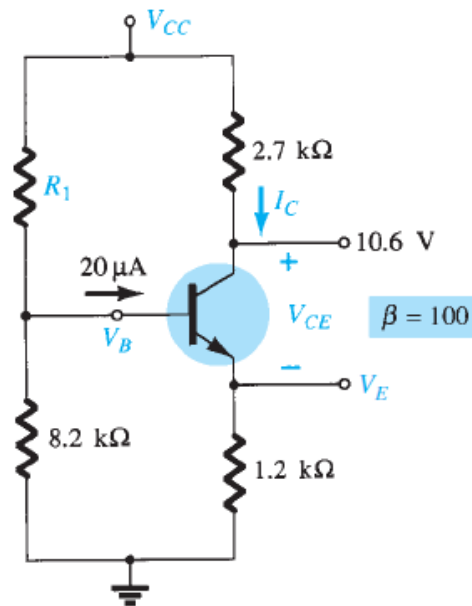


FIG. 4.127


\*33. Given  $V_B = 4\text{ V}$  for the network of Fig. 4.133, determine:

- a.  $V_E$ .
- b.  $I_C$ .
- c.  $V_C$ .
- d.  $V_{CE}$ .
- e.  $I_B$ .
- f.  $\beta$ .

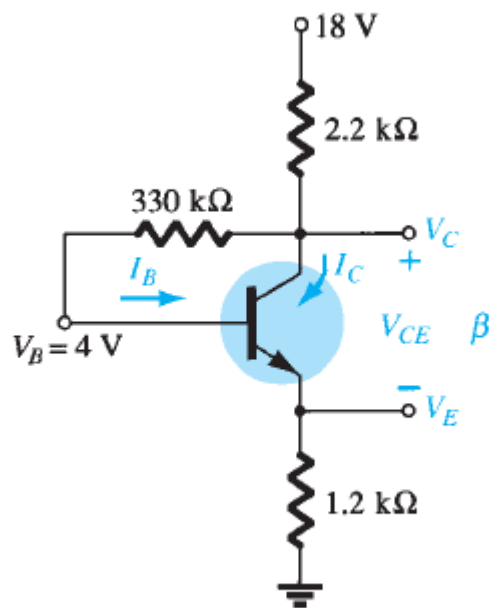

**FIG. 4.133**

\*34. Determine the level of  $V_E$  and  $I_E$  for the network of Fig. 4.134.

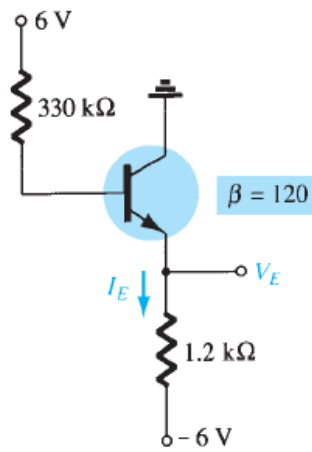

**FIG. 4.134**

43. Design a voltage-divider bias network using a supply of 24 V, a transistor with a beta of 110, and an operating point of  $I_{CQ} = 4 \text{ mA}$  and  $V_{CEQ} = 8 \text{ V}$ . Choose  $V_E = \frac{1}{8}V_{CC}$ . Use standard values.

46. For the Darlington amplifier of Fig. 4.142 determine
- the level of  $\beta_D$ .
  - the base current of each transistor.
  - the collector current of each transistor.
  - the voltages  $V_{C1}$ ,  $V_{C2}$ ,  $V_{E1}$ , and  $V_{E2}$ .

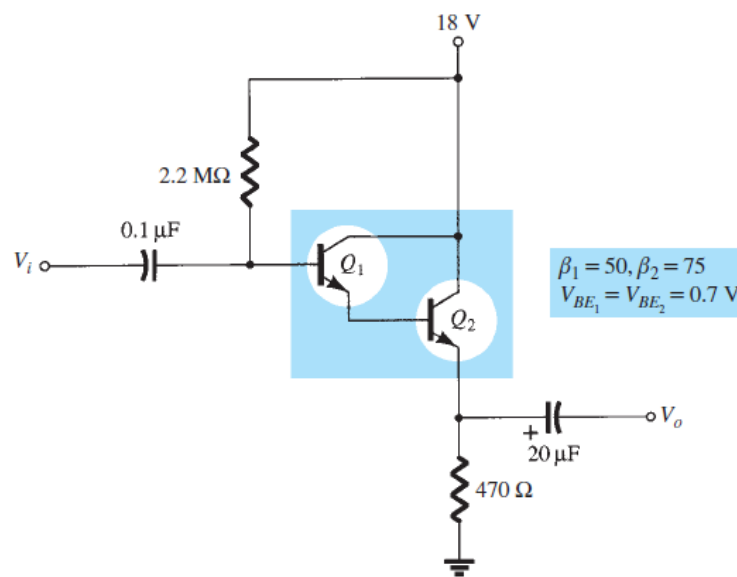


FIG. 4.142

56. Determine  $I_E$  and  $V_C$  for the network of Fig. 4.152.

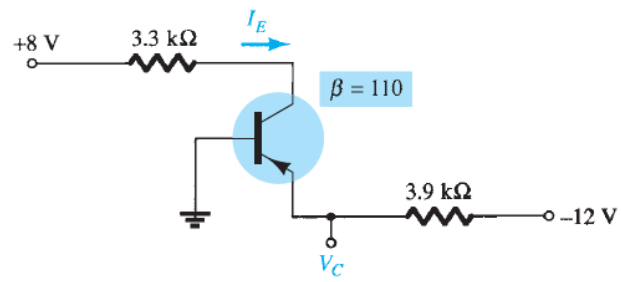


FIG. 4.152