



BERZIET UNIVERSITY
FACULTY OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND COMPUTER ENGINEERING

ENEE 2110

Circuits Laboratory

Experiment #7 Pre-lab

Impedance and sinusoidal steady state

Prepared by:

AbdulAziz Safi

1211258

Supervised by:

Dr. Muhammad Abu-Khaizaran

Teaching Assistance:

Eng. Mohammad Deek

Aug.2025

Part A: Impedance Measurement

1. For the circuits shown in Figures 7.7 - 7.10 **calculate the magnitude of the impedances** Z_R , Z_C , Z_L , and Z_{RC} respectively, for the following frequencies: 250, 500, 1000 and 2000 Hz.

1. Connect the circuit in Figure 7.7, set V_{in} to sinusoidal voltage at $8 V_{PP}$, $f = 250$ Hz

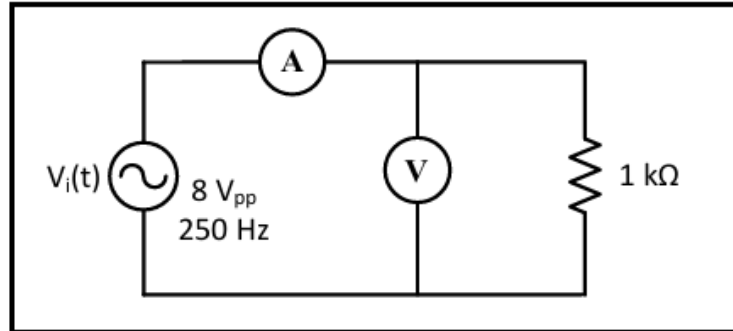


Figure 7.7

$Z_R = 1k\Omega$ at any frequency(constant)

2. Connect the circuit in Figure 7.8, set V_{in} to sinusoidal voltage at $8 V_{PP}$, $f = 250$ Hz.

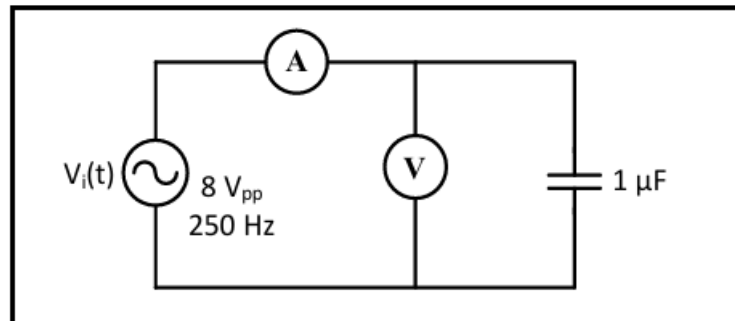


Figure 7.8

$$Z_C = 1/\omega C = 1/(250 * 2 * \pi * 1 * 10^{-6}) = 636.6 \, \Omega \quad f = 250 \, \text{Hz}$$

$$Z_C = 1/(500 * 2 * \pi * 10^{-6}) = 318.3 \, \Omega \quad f = 500 \, \text{Hz}$$

$$Z_C = 1/(1000 * 2 * \pi * 10^{-6}) = 159.2 \, \Omega \quad f = 1000 \, \text{Hz}$$

$$Z_C = 1/(2000 * 2 * \pi * 10^{-6}) = 79.6 \, \Omega \quad f = 2000 \, \text{Hz}$$

3. Connect the circuit in Figure 7.9, set V_{in} to sinusoidal voltage at $8 V_{pp}$, $f = 250$ Hz.

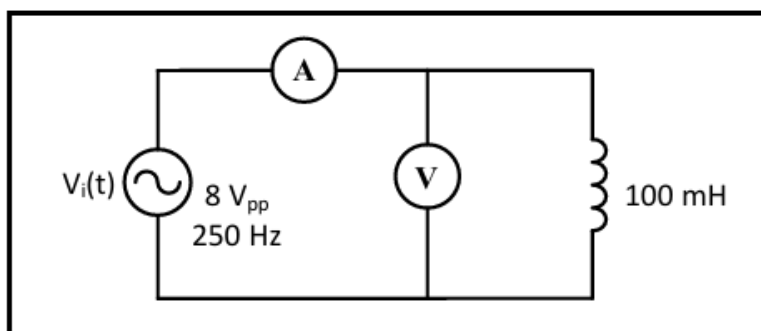


Figure 7.9

$Z_L = \omega * L = 2 * \pi * 250 * 0.1 = 157 \Omega$	$f = 250$ Hz
$Z_L = \omega * L = 2 * \pi * 500 * 0.1 = 314 \Omega$	$f = 500$ Hz
$Z_L = \omega * L = 2 * \pi * 1000 * 0.1 = 628 \Omega$	$f = 1000$ Hz
$Z_L = \omega * L = 2 * \pi * 2000 * 0.1 = 1256 \Omega$	$f = 2000$ Hz

4. Connect the circuit in Figure 7.10, set V_{in} to sinusoidal voltage at $8 V_{pp}$, and $f = 250$ Hz.

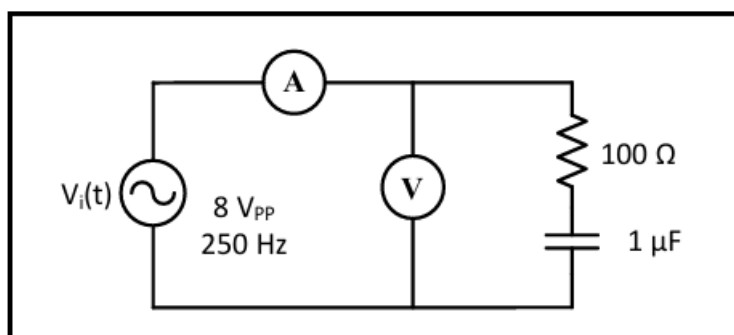


Figure 7.10

$Z_R = 100 \Omega$ (do not be affected by frequency)

$Z_{RC} = \sqrt{(Z_R^2 + Z_C^2)}$

$Z_{RC} = \sqrt{(100^2 + 636.62^2)} = 644 \Omega$	$f = 250$ Hz
$Z_{RC} = \sqrt{(100^2 + 318.32^2)} = 333.6 \Omega$	$f = 500$ Hz
$Z_{RC} = \sqrt{(100^2 + 159.12^2)} = 188 \Omega$	$f = 1000$ Hz
$Z_{RC} = \sqrt{(100^2 + 79.52^2)} = 127 \Omega$	$f = 2000$ Hz

Part B: Phase Measurement

1. For the circuit shown in Figure 7.11

a. Use PSPICE to do transient analysis of the circuit, show $V_{in}(t)$ and $V_R(t)$ on one plot



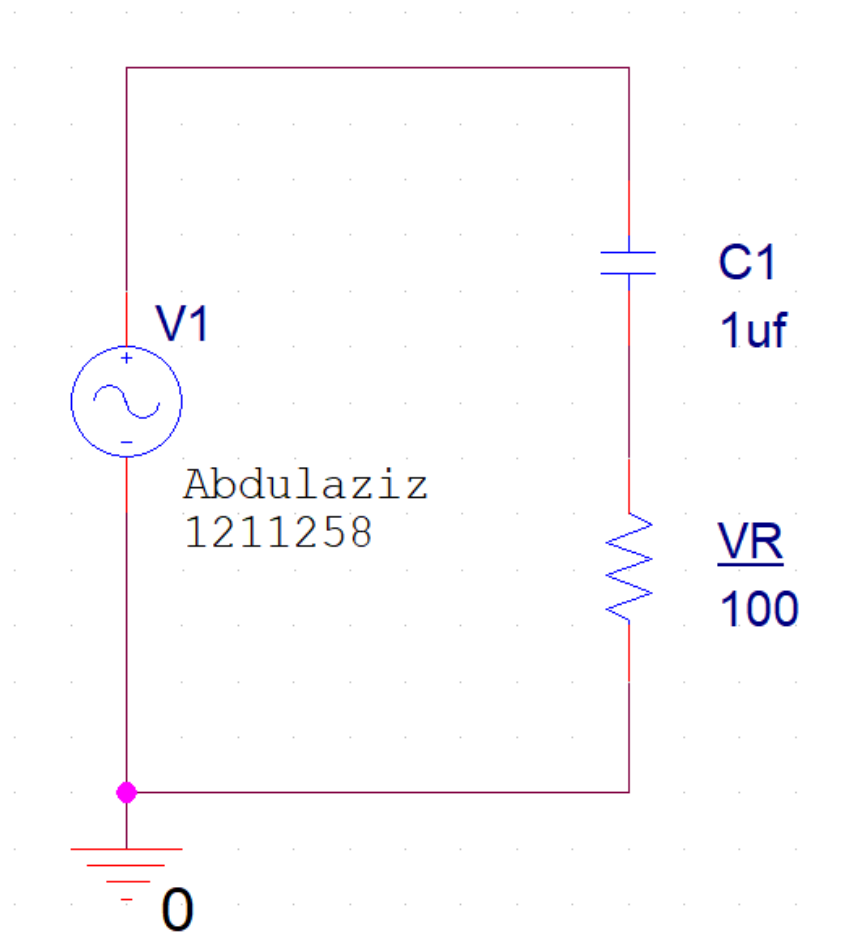


Figure 7.11

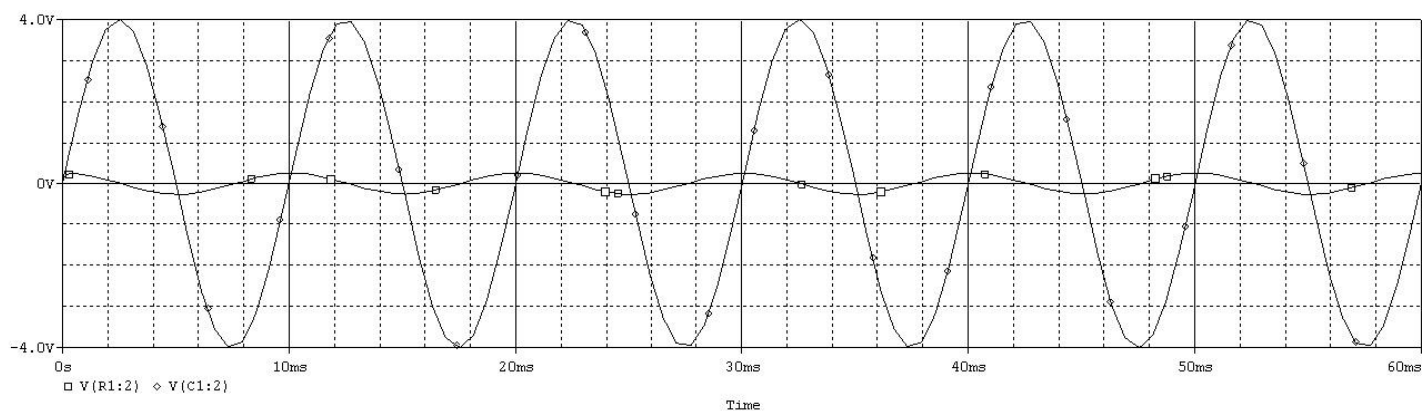

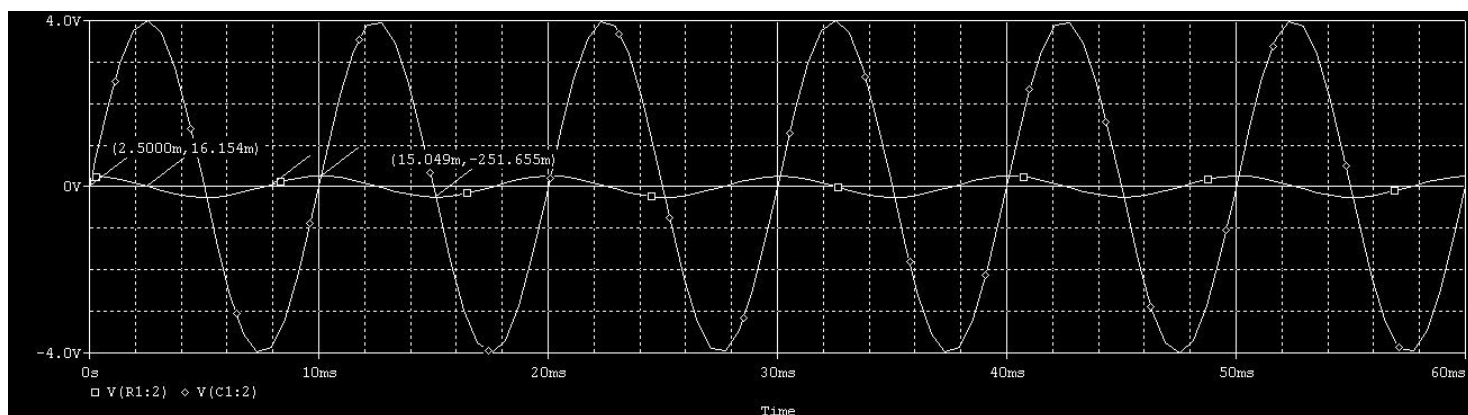B- Use cursors to measure the time difference between the peaks of the two signals, then use the following relationship to calculate the phase shift using the measured time $\{\Delta\theta = 360^\circ \times f \times \Delta t\}$.



From the figure above

$$\Delta t = (5 - 7.5)\text{ms} = -2.5\text{ms}$$

$$\Delta\theta = 360 \times f \times \Delta t = 360 \times 100 \times 2.5 \times 10^{-3} = -90^\circ$$

1. For the circuit shown in Figure 7.12

2. Connect the circuit in Figure 7.12, set V_{in} to sinusoidal voltage at 8 VPP and $f = 1$ KHz


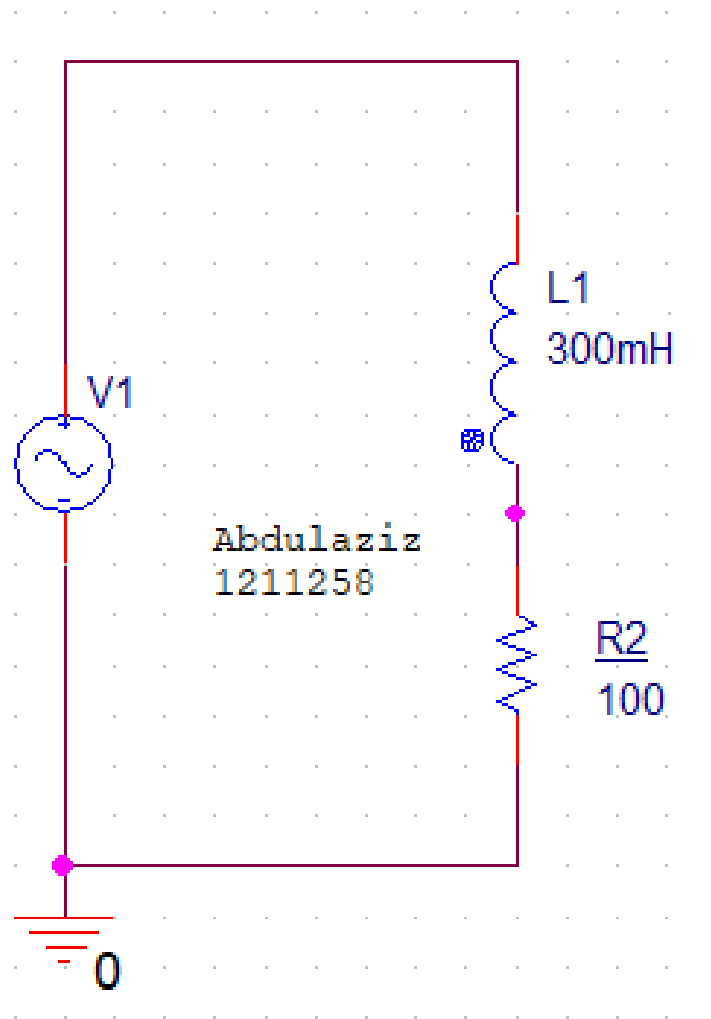
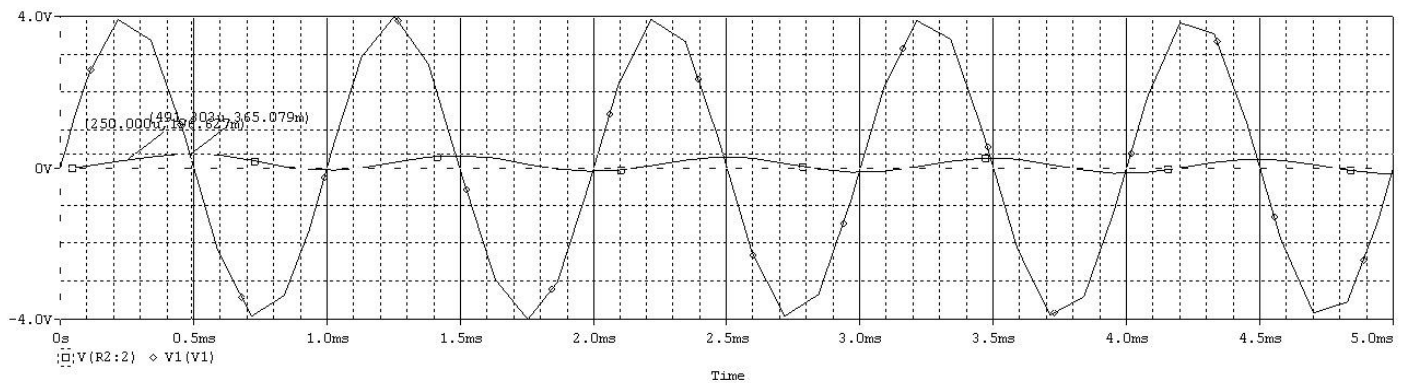


Figure 7.12

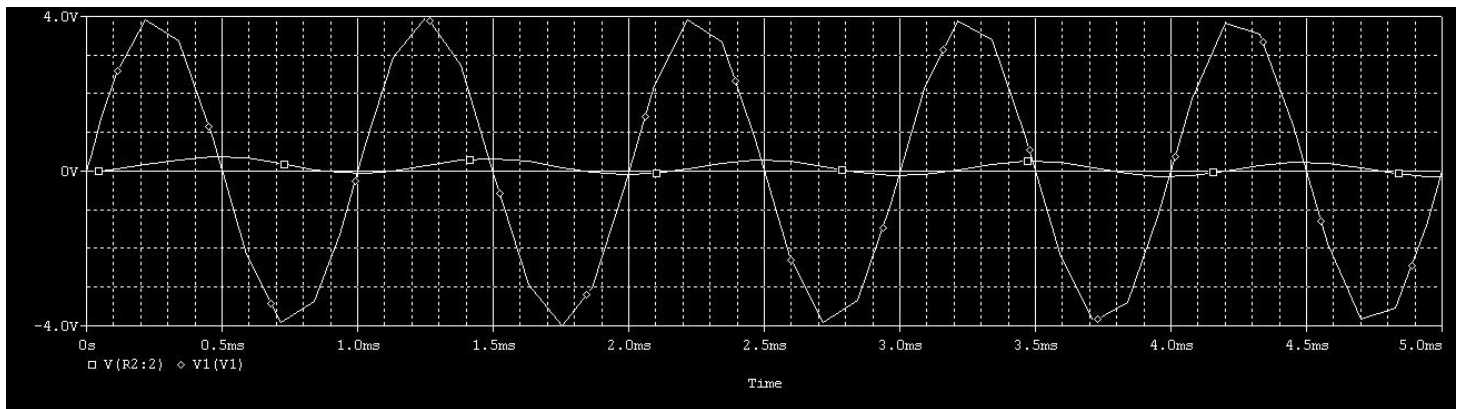

b. Use cursors to measure the time difference between the peaks of the two signals, then use the following relationship to calculate the phase shift using the measured time $\{\Delta\theta = 360^\circ \times f \times \Delta t\}$.

From the figure above

$$\Delta t = (0.5 - 0.25) \text{ms} = 0.25 \text{ms}$$

$$\Delta\theta = 360 \times f \times \Delta t = 360 \times 1000 \times 0.25 \times 10^{-3} = 90^\circ$$