

T12:

Amplifier Frequency Response

Instructor : Nasser Ismail

1

Instructor Nasser Ismail First_2021-2022 Uploaded By: anonymous

Amplifier Frequency Response

- Audio frequency signals such as speech and music are combination of many different sine waves, occurring simultaneously with different amplitude and frequency in the following range (20Hz-20kHz (audible noise), other types of signals have their own range.
- In order for the output to be an amplified version of the input, the amplifier must amplify each and every component in the signal by the same amount
- The Bandwidth must cover the entire range of frequency components if considered amplification is to be achieved

















Series Capacitance and low frequency response

1) let $\omega_{c1} = 616$ rad/sec and $\omega_{c2} = 17.86$ rad/sec here $\omega_{c1} >> \omega_{c2}$ $\omega_{L} = 616.5$ rad/sec 2) let $\omega_{c1} = 200$ rad/sec and $\omega_{c2} = 750$ rad/sec here $\omega_{c2} >> \omega_{c1}$ $\omega_{L} = 798$ rad/sec In both cases and in general if $\omega_{c1} >> \omega_{c2}$ $\omega_{c1} < \omega_{L} < \omega_{c1} + \omega_{c2}$ Biggest $\omega_{c1} < \omega_{L} < \text{sum of all } \omega_{c} 's$

Low Frequency Response Example

• Calculate the low frequency corner frequencies due to C1,C2, Cs and estimate ω_L ?



Effect of each Capacitor at ω

• We Calculate the low frequency corner frequencies due to each cap acting alone while all others are considered as short circuit

1) consider C1 (while C2 and Cs are shorted) $\omega_{c_{1}} = \frac{1}{C1.Rth1} = 45.45 \text{ rad/sec};$ Rth1 is the thevenin impedance seen by C1 while all independant sources are set to zero Rth1 = Ri + (R1//R2) 2) consider C2 (while C1 and Cs are shorted) $\omega_{c_{2}} = \frac{1}{C2.Rth2} = 100 \text{ rad/sec};$ Rth1 is the thevenin impedance seen by C1 Rth2 = R_{D} + R_{L}











Design of ωι

- Previous method explained how to estimate value of <u>on</u> in an analysis problem where all capacitor values are given, but what happens if it was desired to design an amplifier with certain <u>on</u> and the task was to find capacitor values ?
- Design criteria to be used is:

 $\omega_{\rm CE} = (0.7 - 0.8)\omega_{\rm L}$

 $\omega_{c_1} = \omega_{c_2} = (0.1 - 0.15)\omega_{L}$

C1,C2 are input and output coupling capacitors

 $C_{\rm E}$ is bypass capacitor // to $R_{\rm E}$ emitter stabilizing

resistor or Rs source resistor

make sure that $\omega_{CE} + \omega_{C1} + \omega_{C3} = \omega_{L}$



