

Solution Key



BIRZEIT UNIVERSITY

Electrical and Computer Engineering Department

Electrical Machines ENEE 2408

Short Exam # 5 (10mins)

Student Name:

ID:

January 8, 2025

A 10hp, 300V, shunt DC motor has an $R_A = 0.5 \Omega$. When loaded, the motor was found to draw an armature current of 30A and to have a speed of 2000rpm. If the rotational losses were 500W then:

- Calculate the induced torque
- Calculate the efficiency of the motor

Solution

a)


$$n = 2000 \text{ rpm}$$

$$I_A = 30 \text{ A}$$

$$P_{FW} = 500 \text{ W}$$

$$\omega = \frac{2000 \times 2\pi}{60} = 209.4 \text{ rad/s}$$

1.5

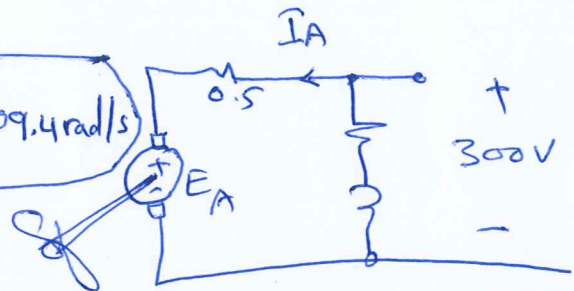

$$T_{ind} = \frac{P_{conv}}{\omega} = \frac{E_A I_A}{\omega}$$

1.5

$$\text{But } E_A = 300 - R_A I_A \Rightarrow E_A = 300 - 0.5(30) = 285 \text{ V} = E_A$$

$$\therefore P_{conv} = 285 \times 30 = 8550 \text{ W} = P_{conv}$$

2

$$\therefore T_{ind} = \frac{8550}{209.4} = 40.83 \text{ N.m}$$

2

STUDENTS-HUB.com

Uploaded By: anonymous

$$b) \eta = \frac{P_{out}}{P_{in}} \times 100\%$$

1

$$P_{out} = P_{conv} - P_{FW} = 8550 - 500 = 8050 \text{ W} = P_{out}$$

$$P_{in} = V_T I_A = 300(30) = 9000 \text{ W} = P_{in}$$

1

$$\therefore \eta = \frac{8050}{9000} \times 100\% = 89.44\% = \eta$$

1