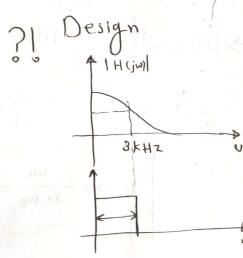



* Choose values for Rg@ that will yield a low-pass filter with a cutoff frequency of 3 KHz.


$$C = IMF$$


$$L = w_c = 2\pi(3\times70) = \frac{1}{R*1\times10^6}$$

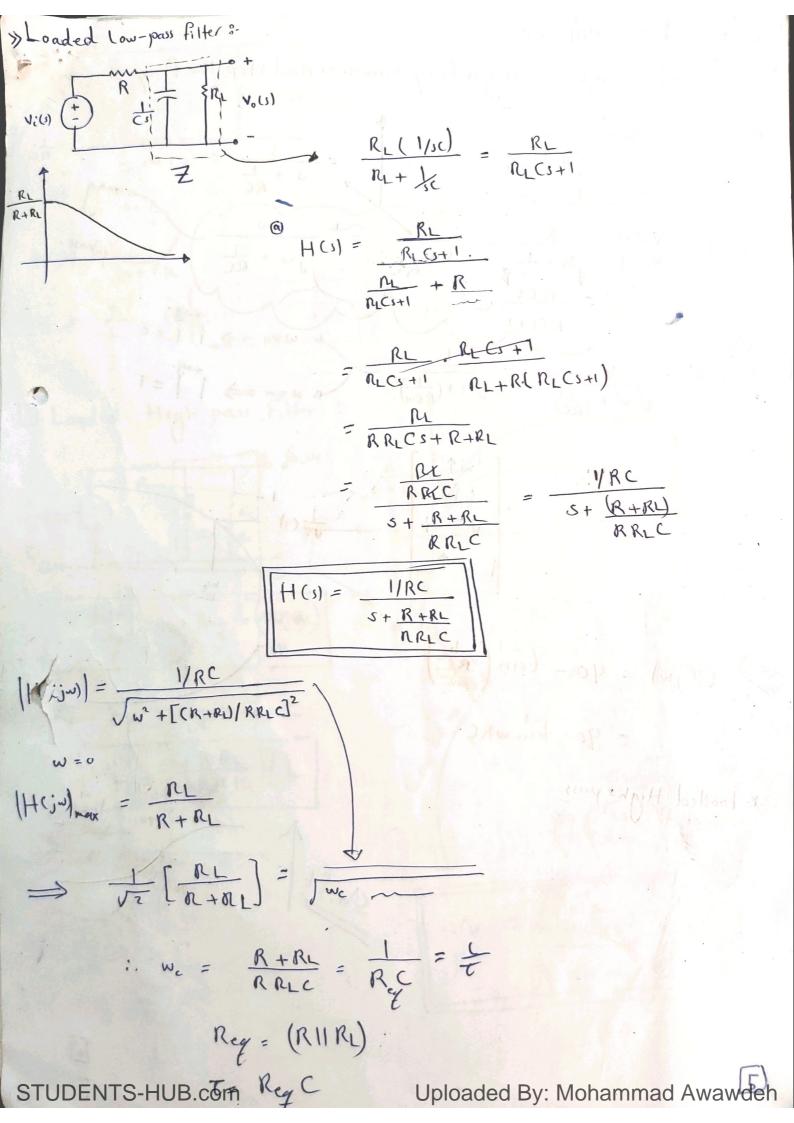
$$R = \frac{1}{10^6*2\pi*3*10^3} = 53 \text{ T}$$





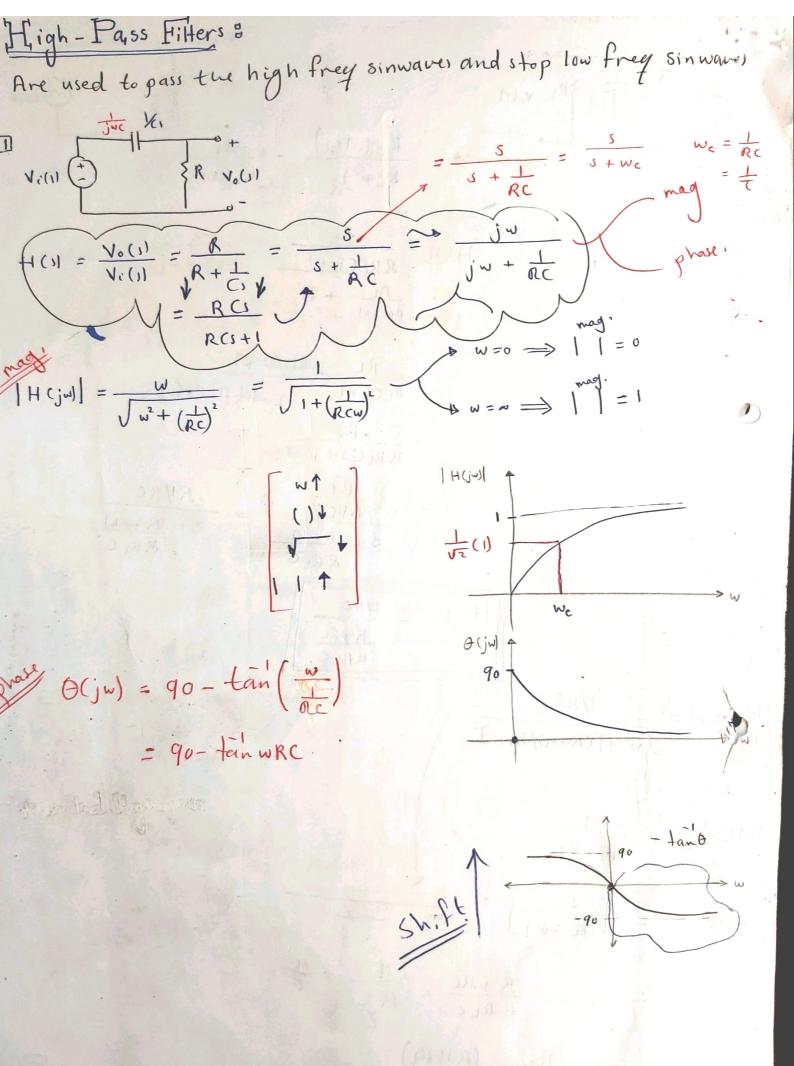

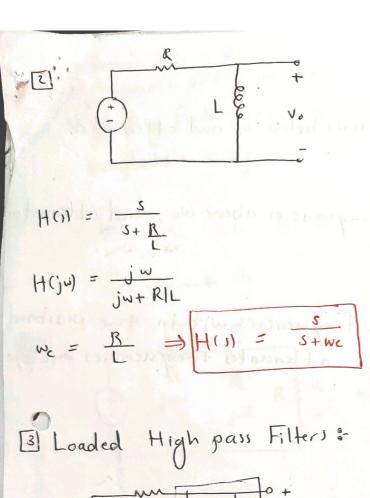

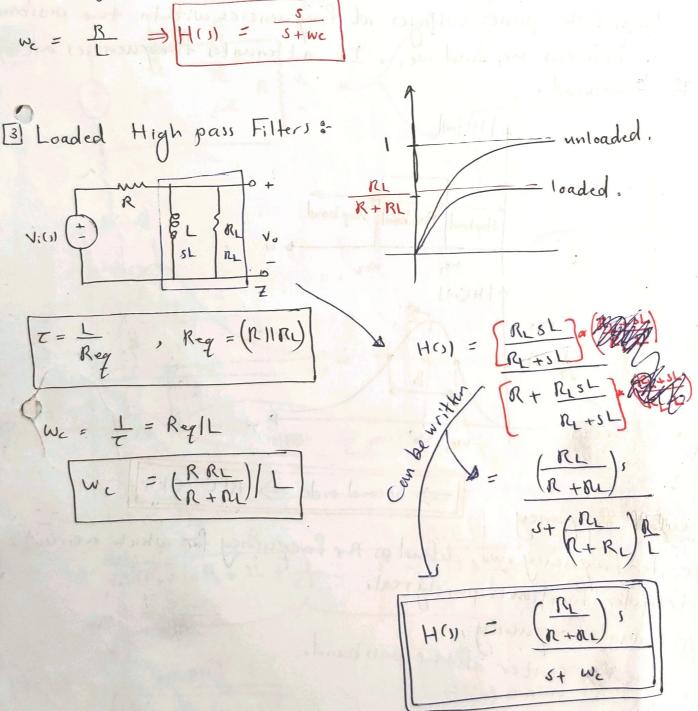


Bandpass Filters &

» A low-pass filter passes voltages at frequencies below we and attenuates frequencies above we.

» A high-pass filter passes voltages at frequencies above we, and attenuates voltages at frequencies below we.
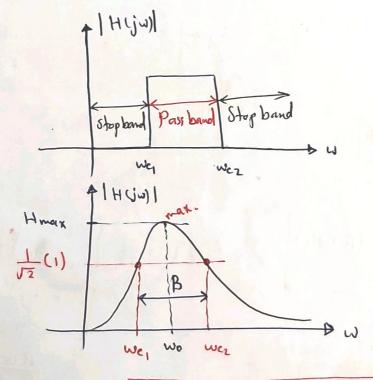
>> A bandpass filter passes voltages at frequencies within the passband which is between we, and wer. It attenuates frequencies outsided the passband.



We = cutoff frequency

⇒ Second orde ⇒ RLC, CKT

wo = center friquency, wo, defind as the frequency for which a circuit's transfer function is purely real.

= resonant frequency,

= geometric center at the pass band.

= Jwg wcz

Hmax = [H(jwo)] For bandpass Filters
STUDENTS-HUB.com Up

Filters

Uploaded By: Mohammad Awaweeh

B & Bandwidth = B = the width at the passband. I Q = quality factor, which is the ratio of the center frequency to the bandwidt = wo Wez, wo, B, Q SL Juc $H(s) = \frac{V_0(s)}{V_1(s)} = \frac{\frac{1}{2} \times R}{100} = \frac{(R | L)^s}{S^2 + (\frac{R}{L})^s + \frac{1}{Lc}} = \frac{R}{-\omega^2 + \frac{R}{L}} \frac{1}{3\omega + \frac{1}{Lc}}$ » (tc-w)+ Rwj $\Theta(jw) = 90 - tan \left[\frac{w(RLL)}{(1/LC) - w^2} \right]$

STUDENTS-HUB Com We, , Wez , Brupidaded By: Mohammad Awawdeh

$$j w_{0}L + \frac{1}{j w_{0}C} = 0$$


$$j w_{0}L = \frac{1}{j w_{0}C} \implies w_{0}^{2}LC = 1$$

$$w_{0} = \int LC$$

$$+1 = w_c \frac{L}{R} - \frac{1}{w_c RC} \Rightarrow w_c^2 + w_c \frac{R}{L} - \frac{1}{cL} = 0$$

$$w_{c_1} = -\frac{R}{2L} + \int \left(\frac{R}{2L}\right)^2 + \left(\frac{L}{Lc}\right)^2$$
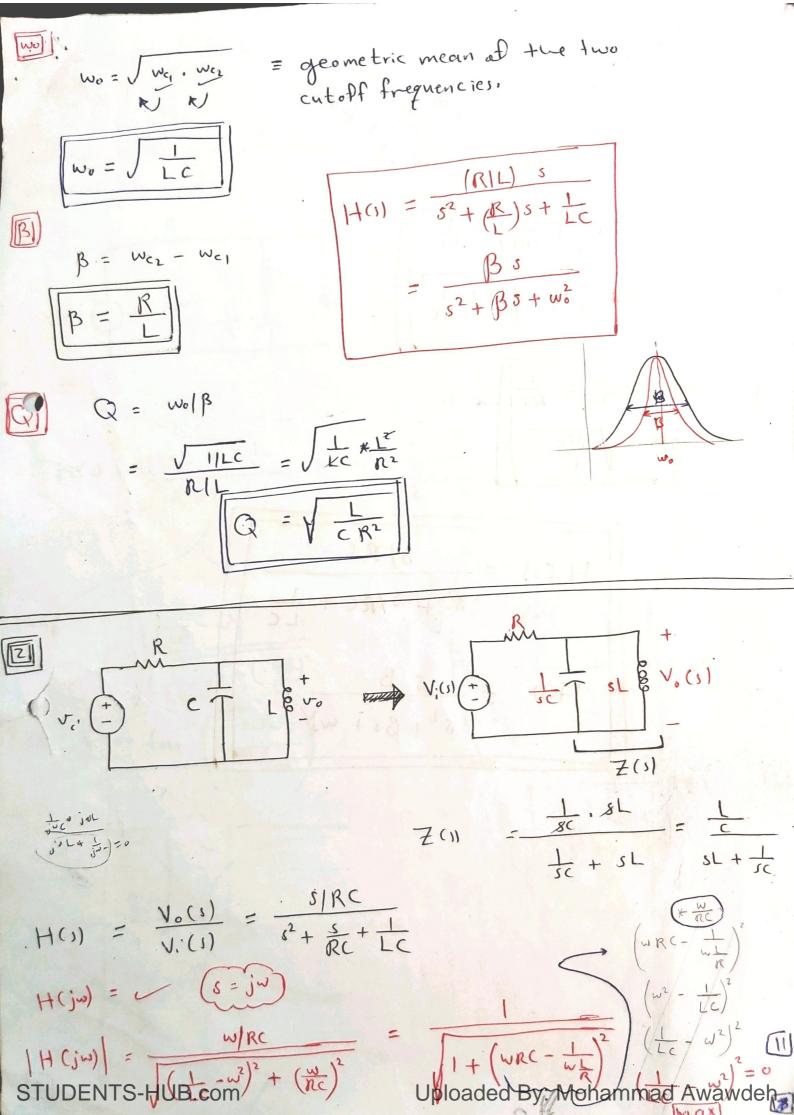
$$w_{c2} = \frac{R}{2L} + \int \left(\frac{R}{2L}\right)^2 + \left(\frac{L}{Lc}\right)^2$$



$$W_{0} = \sqrt{\frac{1}{Lc}}$$

$$H_{max} = |H(jw_{0})| = |$$

$$\sqrt{\frac{1}{2}} H_{max} = |H(jw_{0})|$$

$$W_{c_{1}} = -\frac{1}{2Rc} + \sqrt{(\frac{1}{2Rc})^{2} + \frac{1}{Lc}}$$


$$W_{c_{2}} = \frac{1}{2Rc} + \sqrt{(\frac{1}{2Rc})^{2} + \frac{1}{Lc}}$$

$$H(s) = \frac{s/RC}{s^2 + s/RC + \frac{1}{LC}}$$

$$H(s) = \frac{s}{s^2 + \beta s + \omega_0^2}$$

· Band reject Filter & Band Stop Filter

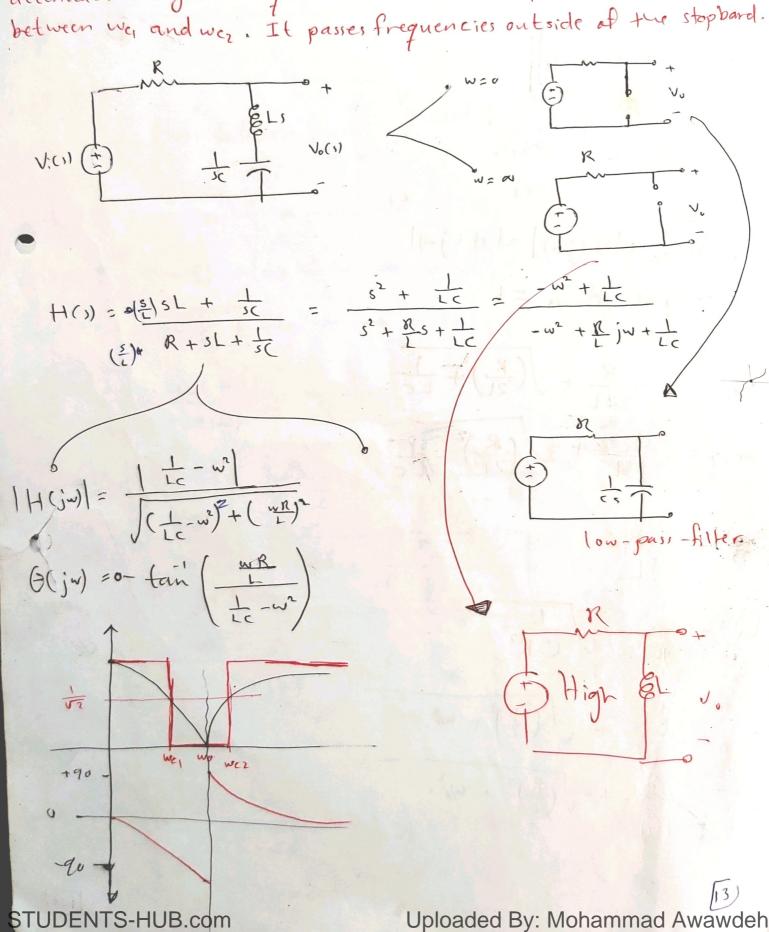attenuates voltages at frequencies within the stopband, which is



$$W_{0} = \text{center frequency} = \text{resconent freq}$$

$$Jw_{0}L + J_{0} = 0$$

$$W_{0} = J_{0}LC$$


$$|H(jw_{0})| = 0 \text{ (min)}|$$

$$|H(jw_{0})| = |H(j_{0})| = |H(j_{0})|$$

$$|H(jw_{0})| = |H(jw_{0})|$$

$$|H(jw_{0})| = |H(jw_{0}$$

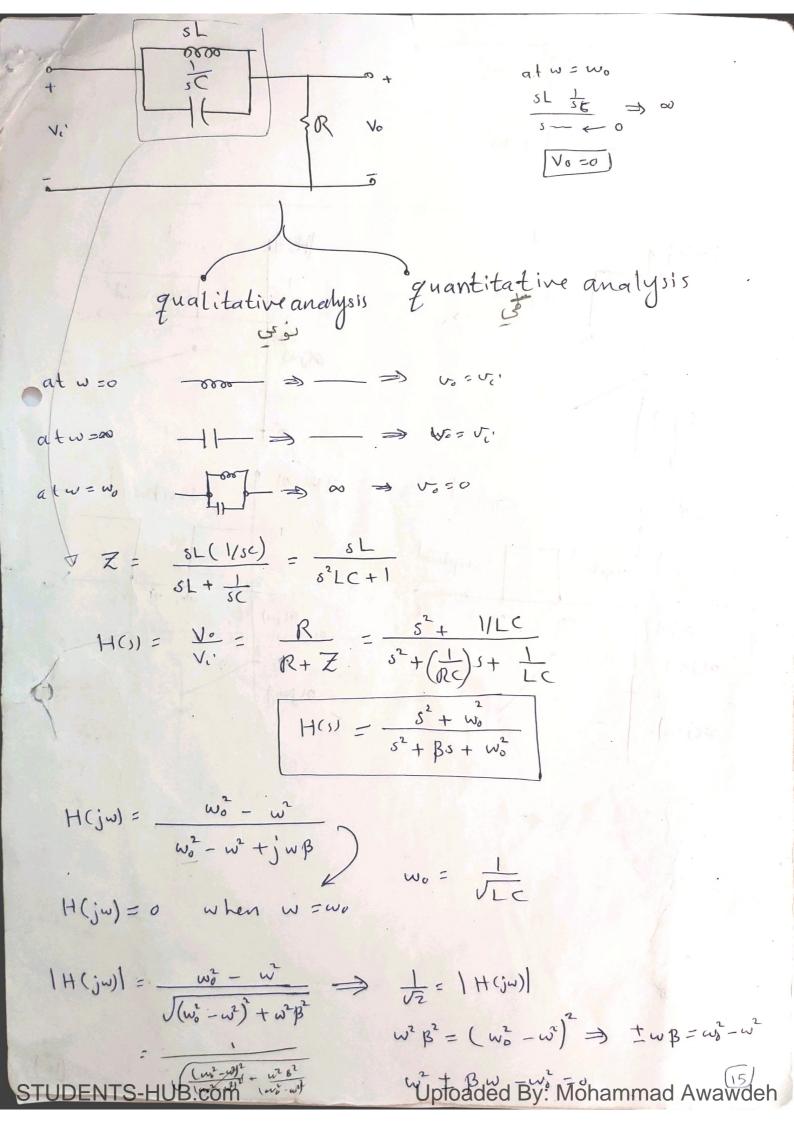Wer = \frac{B}{2} + \sqrt{\left(\frac{B}{2}\right)^2 + w_0^2}.



$$w_{c_1} = \frac{-\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + w_o^2}$$
 $w_{c_2} = \frac{\beta}{2} + \sqrt{\left(\frac{\beta}{2}\right)^2 + w_o^2}$

