

Experiment 4: Network Analysis II


The Thevenin and Norton Techniques

Thevenin: "any network of resistors and supplies having two output terminals and supplies having two output terminals can be replaced by a series combination of E_{eq} & R_{eq} By three steps:- starting by R_3

Step 1:- you consider that E_1, E_2 does not exist:-

$$R_{eq} = R_1 + R_2$$


$$R_{eq_3} = \frac{R_1 R_2}{R_1 + R_2}$$

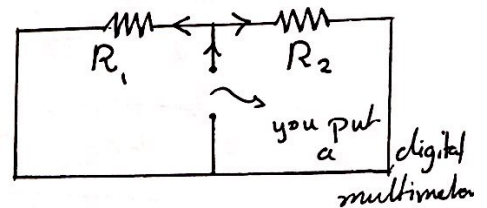

Step 2:- you consider that E_1, E_2 exist


$$E_{eq} = E_1 - I R_1 \quad \text{--- ①}$$

you find I --- ②

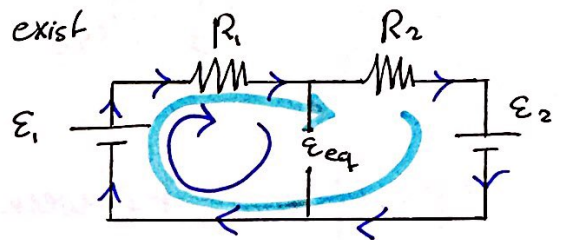

Step 3:- you find I_{eq_3}
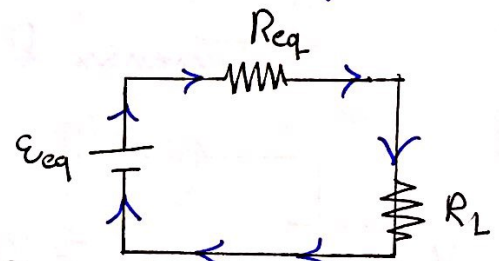
$$I_{eq_3} = \frac{E_{eq}}{R_{eq} + R_L}$$




• You do the same for R_1 and R_2 and you find I_{eq_1} and I_{eq_2}

2- **Norton's** for R_3

Step 1:- The same

$$\begin{aligned} \text{Step 2:- } I_{eq_3} &= I_1 + I_2 \\ &= \frac{E_1}{R_1} + \frac{E_2}{R_2} \end{aligned}$$

Step 3 get rid of E_1, E_2

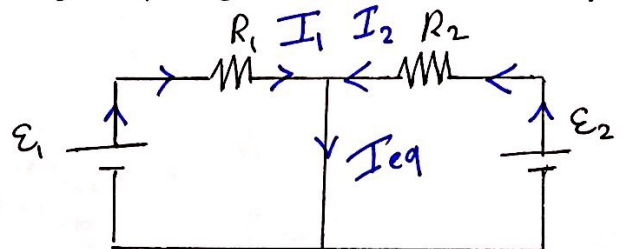


Alaa Etawneh

• you replace R_1, R_2 with R_{eq3}

• $I_{L3} R_3 = (I_{eq3} - I_{L3}) R_{eq3}$

على مصدر الجهد عند التحويل
على التوازي

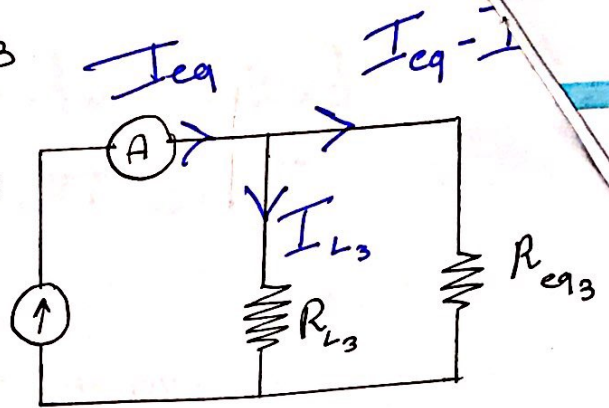


$$I_{L3} (R_3) = I_{eq3} R_{eq3} - I_{L3} R_{eq3}$$

$$I_{L3} (\underbrace{R_3 + R_{eq3}}_{\text{you have it}}) = \underbrace{I_{eq3} R_{eq3}}_{\text{you have it}}$$


you have it

$$I_{L3} = \frac{I_{eq3} R_{eq3}}{R_3 + R_{eq3}}$$

Difference between
Theremin & Norton

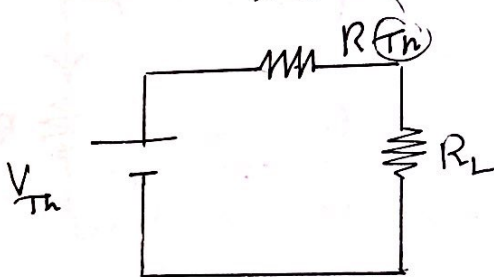

$$R_{Th} = R_L$$

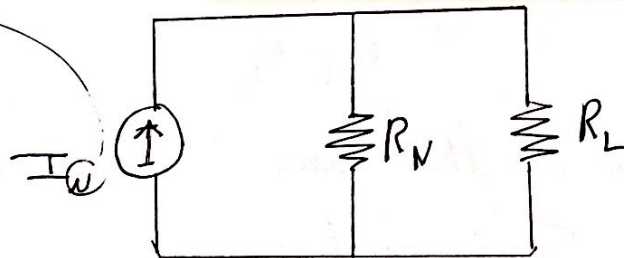

• in Theremin's

$$I_{L3} = \frac{E_{eq}}{R_{eq} + R_L}$$

if you dont
calculate

Then I_{L3}

Alaa Itaiwi

• what we use

- 2 voltage sources
- 3 carbon Resistances
- Circuit board
- digital Multimeter

• DMM: digital Multimeter

• Procedure


Theremin :-

There are 3 currents to measure each one we have 3 steps:- let's say we want to measure I_3

Step 1:- Calculate R_{eq} :-

• first circuit :-

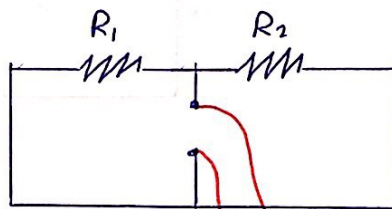- Take E_1 and E_2 off
- Put a DMM in the place of R_3




$$I_L = I_3$$

$$R_L = R_3$$

Step 2:- Calculate E_{eq} :-

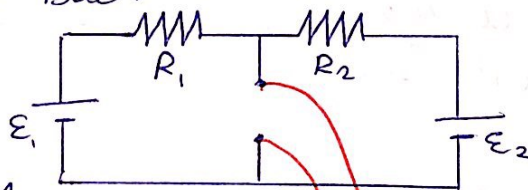- second circuit:-
- Take R_3 off and put E_1 and E_2 back




Step 3:-

- Connect the Circuit

$$R_L = R_3$$

R_{eq} = you get it from the box

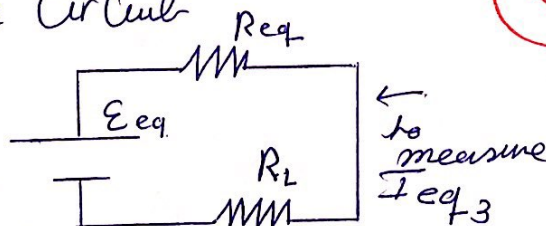


to a DMM
to measure
 E_{eq3}

E_{eq} = Power supply
Alaa Ffaini

• هذه الخطوات الثلاث هي لتقريب التيار I_3 في المقاومة R_3 في الدارة الأولى.
1- إزالة المقاومة R_3 من الدارة وإدخال دMM في مكانها لقياس المقاومة المكافئة R_{eq} .
2- إعادة تركيب الدارة مع مصدر الجهد E_1 و E_2 وقياس الجهد المكافئ E_{eq} بين طرفي المقاومة R_3 .
3- توصيل الدارة مع المقاومة R_3 وقياس التيار I_3 الذي يمر فيها.

Norton :-

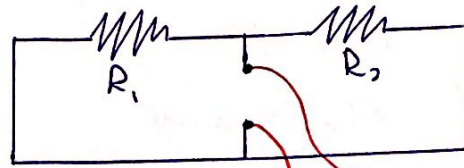
Step 1 :- The same as Thevenin's first step



نفس الخطوة
Thevenin is

DMM to find R_{eq3}


Step 2 :- measure I_{eq3} :-

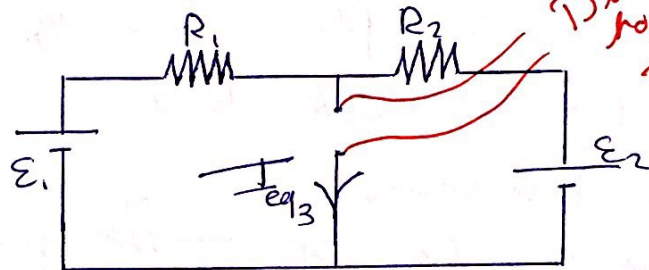

I_{eq3} is

DMM to find I_{eq3}

Step 3 :- Connect this circuit

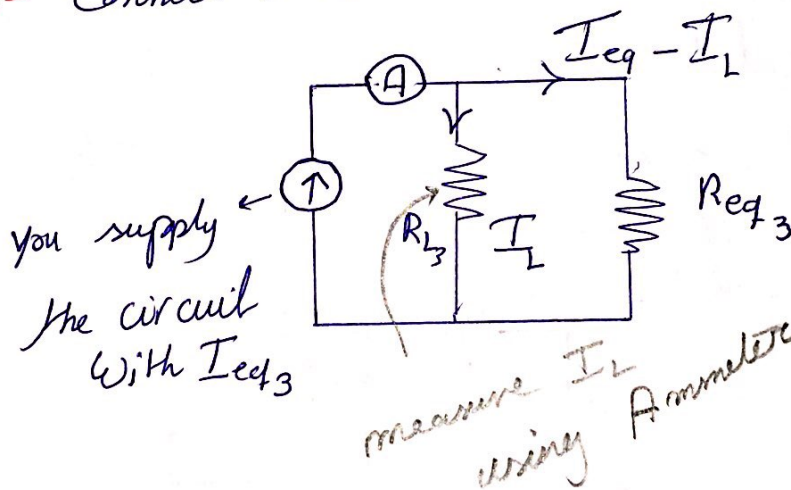

In Norton's

$$R_{eq} = \text{جميع المقاومات المتصلة في التوازي}$$

$R_1 = R_2 + R_3$ is the total Resistance

Alaa Etaiwi