

ENEE2360 CH5 Homework Problems

12. For the network of Fig. 5.152, determine V_{CC} for a voltage gain of $A_v = -160$.

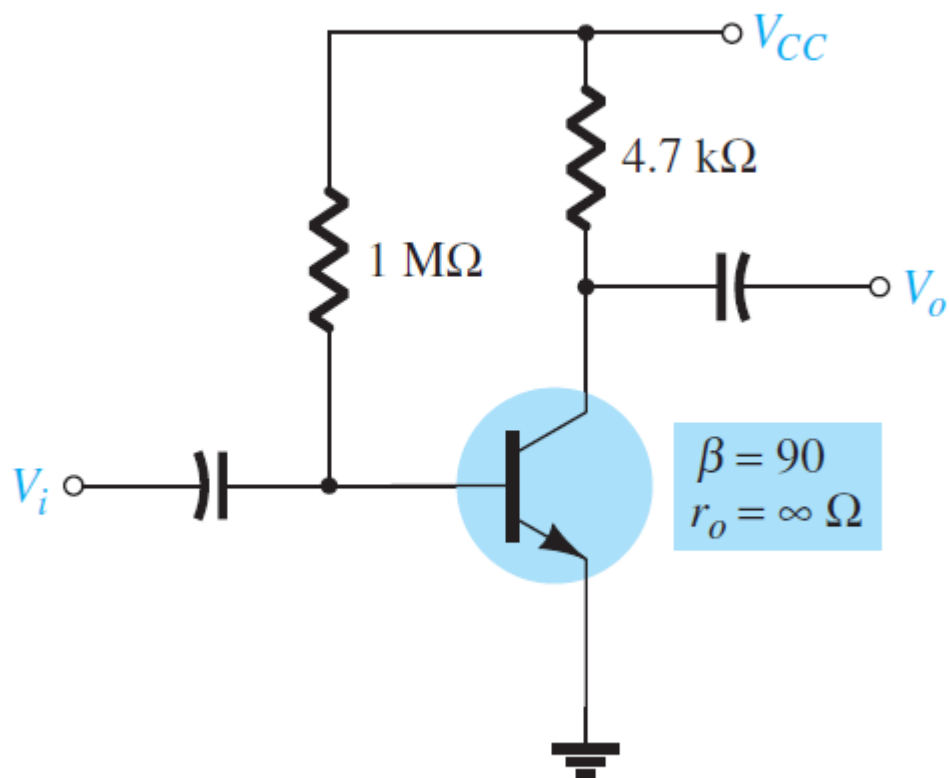


FIG. 5.152

Note that $\frac{1}{h_{oe}} = \infty$

- *25. For the network of Fig. 5.163:
- Determine Z_i and Z_o .
 - Find A_v .
 - Calculate V_o if $V_i = 1$ mV.
- *26. For the network of Fig. 5.164:
- Calculate I_B and I_C .
 - Determine r_e .
 - Determine Z_i and Z_o .
 - Find A_v .

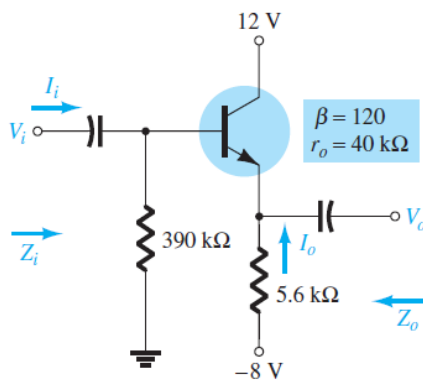


FIG. 5.163

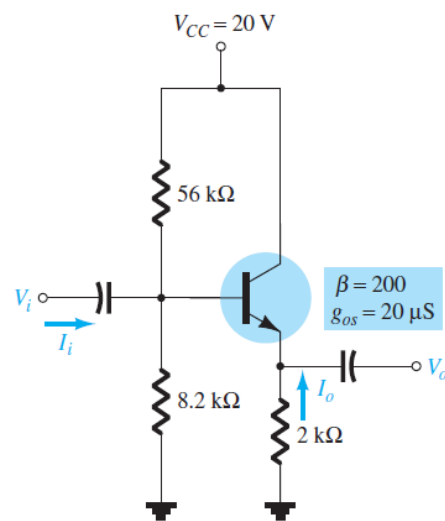


FIG. 5.164

$$\frac{1}{h_{oe}} = 40K \quad \text{for FIG5.163}$$

$$\frac{1}{h_{oe}} = 50K \quad \text{for FIG5.164}$$

40. For the emitter-stabilized network of Fig. 5.174:
- Determine $A_{v_{NL}}$, Z_i , and Z_o .
 - Sketch the two-port model of Fig. 5.63 with the values determined in part (a).
 - Determine A_{v_L} and A_{v_s} .
 - Change R_s to $1\text{ k}\Omega$. What is the effect on $A_{v_{NL}}$, Z_i , and Z_o ?
 - Change R_s to $1\text{ k}\Omega$ and determine A_{v_L} and A_{v_s} . What is the effect of increasing levels of R_s on A_{v_L} and A_{v_s} ?
 - Determine $A_i = I_o/I_i$.

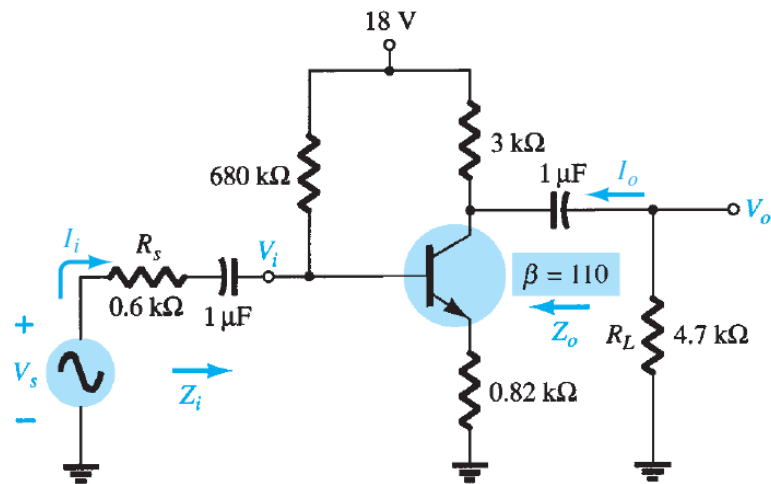


FIG. 5.174