


Problem#1 :

Design an Op Amp phase - shift oscillator to produce a 1KHz sinusoidal wave.

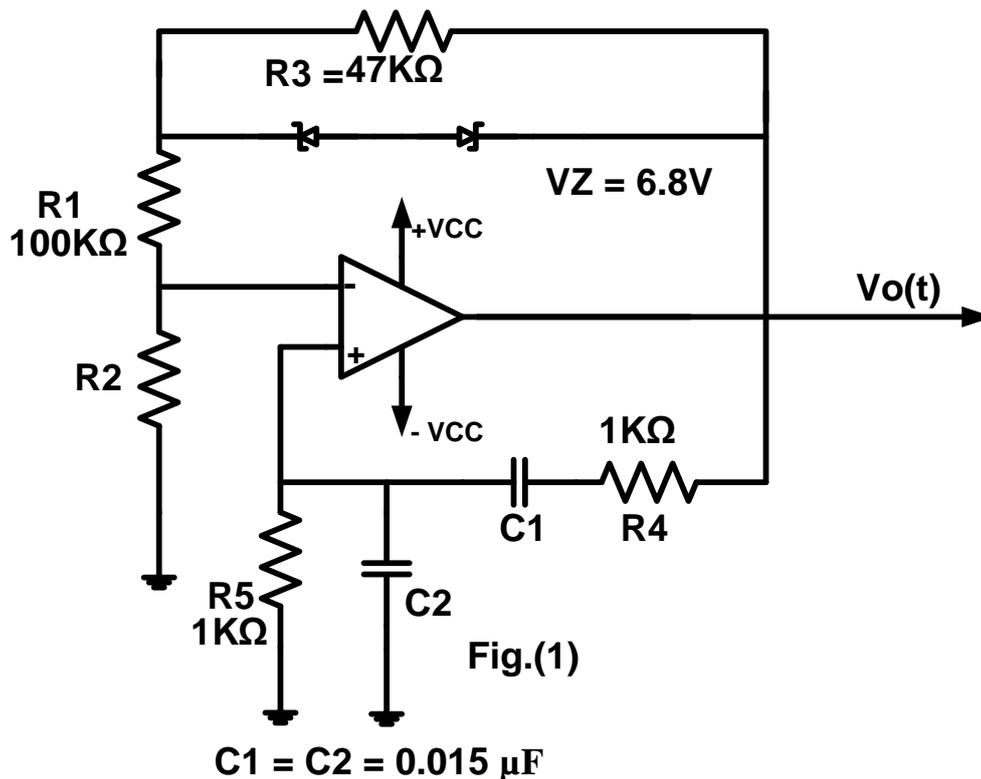Problem #2 :


For the Wien – bridge oscillator shown in Fig .(1)

- Find the frequency of oscillation.
- Determine the necessary value of R2 so that the circuit will oscillate.
- Explain the purpose of R3.



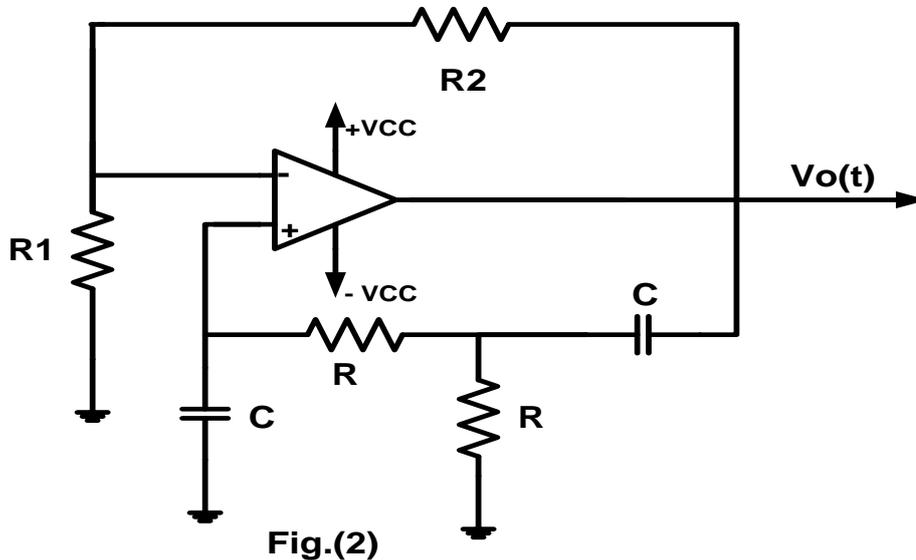
**Problem #3 :**

For the circuit in Fig.(2) , find the expression of the frequency of oscillation.



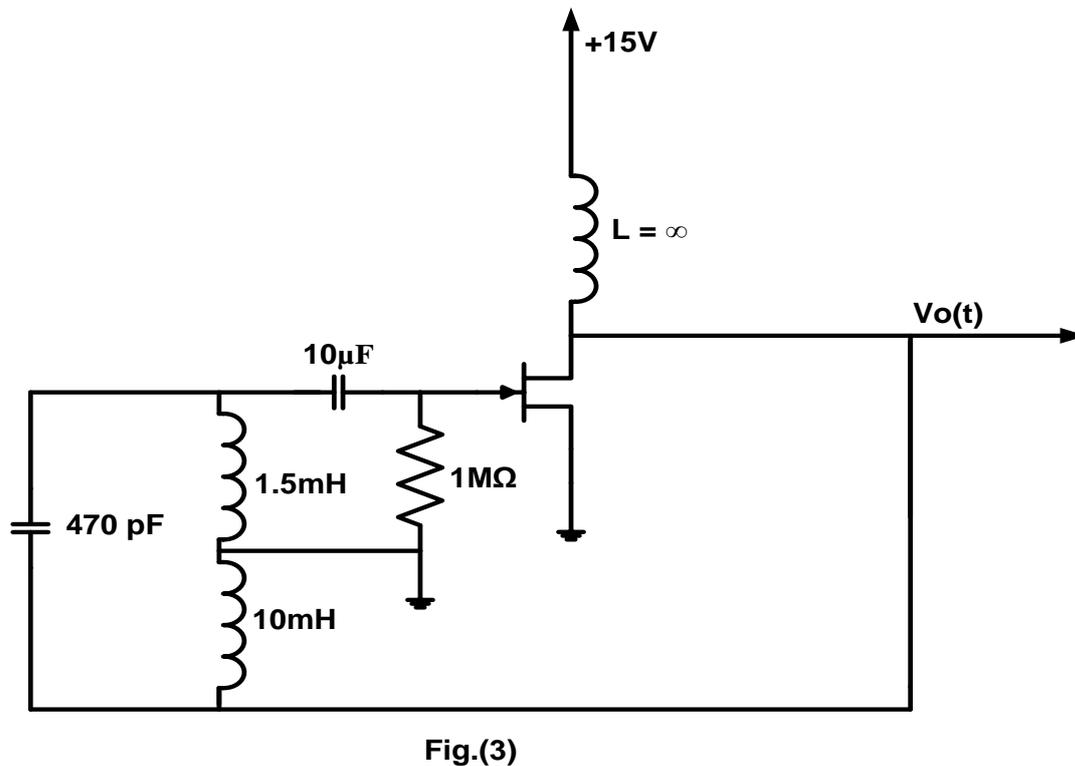
**Problem #4 :**

Calculate the frequency of oscillation and the minimum open circuit voltage gain of the oscillator shown in Fig.(3).



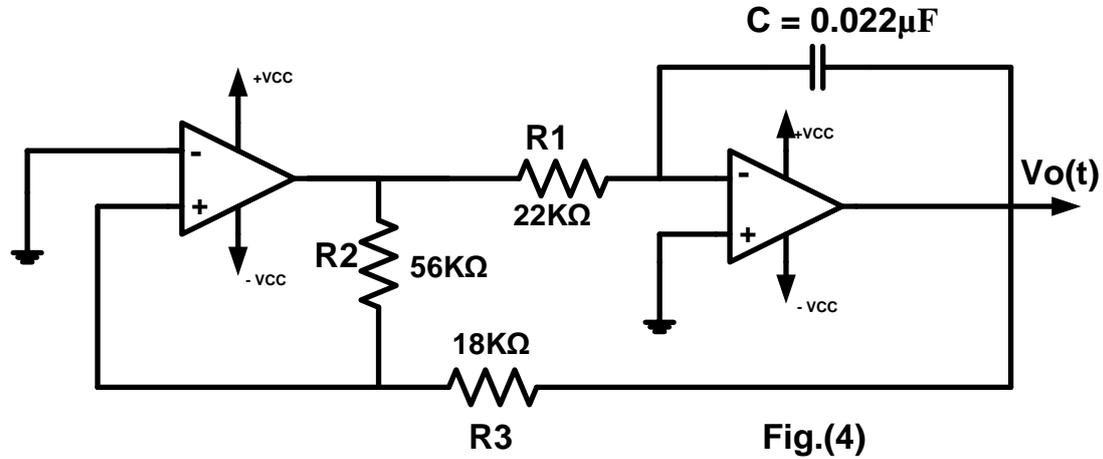**Problem #5 :**

What type of signal does the circuit in Fig.(4) produce ?. Determine the amplitude and the frequency of the output  $V_o(t)$ .



**Problem #6 :**

For the circuit shown in Fig (5)

- a) Determine  $C_{ext}$  so that the frequency of oscillator is 25KHz .
- b) With the values of  $C_{ext}$  found in a), what will be the duty cycle.

