



ANSWER BOOKLET

Student: <u>Digital</u>	Number: <u>9</u> <u>GP</u>
Course: Department: _____	Number: _____
Division: _____	Instructor: _____
Date: <u>chapter 7</u> <u>(PLDs)</u>	_____
Day	Month Year

For Instructor's Use

Question	Grade
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	
Total	

Chapter 7: Memory and Programmable Logic

① memory unit: it is a device to which binary information is stored.

② Two types of memories:

① RAM (Random access memory): ~~access for~~

- Same access time for ~~any~~ accessing any location (opposite to sequential access).
- Read and write
- information will be lost when power down.
- many types (e.g. SRAM, DRAM)
↳ volatile memory


② ROM (Read Only Memory)

- Read only (no write operation)
- nonvolatile memory
- many types (EPROM, PROM, EEPROM, Flash).
- ROM is a programmable logic device (PLD).

⊗ RAM

- random access memory (vs sequential access memory)
Same access time.
- Read & write operations
- volatile memory
- many types (SRAM, DRAM)
- memory unit stores binary information in groups of bits called words (word: is a group of bits. (~~15 and 20~~))
e.g. 8-bit byte
16-bit 2 byte (word - int.)
32-bit 4 byte (double word)
- Capacity of a memory unit: either in bit or byte

- block diagram of RAM

 

- address lines (k lines $\rightarrow 2^k$ locations)

④ memory unit is specified by the number of words it contains and the number of bits in each word (e.g. $2^k \times 8$) $\rightarrow$ 2k byte or 16k bit

⑤ each word has an address range of addresses $(0 - (2^k - 1))$.

⑥ $1k = 2^{10}$ $1M = 2^{20}$ $1G = 2^{30}$
 $4k = 2^{12}$ $2G = 2^{31}$... etc.

⑦ Example 1k words $\times$ 16 bit each

$\Rightarrow$ no. of address lines = 10

Capacity = 2k byte
or 16k bit


10 lines

0
1

⑧ 16 bit as single unit.

$2^k \geq m$ (k no. of address lines)
 m no. of locations

10 lines
1023

 

Write and Read Operations

- write : transfer ~~out~~ data to memory location,
- read : $\downarrow$, $\downarrow$ out from $\downarrow$, $\downarrow$,

④ Write operation:

- 1) Apply the binary address of the desired word to address lines,
- 2) apply the data bits to the data input lines
- 3) activate the ~~memory~~ chip and write inputs

④ Read operation:

1. Apply the binary address of the desired word to the address lines
2. activate the ~~chip~~ read input.

④ Some memories have memory enable input ^(chip select) pin, and Read/write inputs are in the same pin

memory enable (CS)	Read/write	Memory operation
0	X	None
1	0	write operation
1	1	Read operation

④ Memory Description in HDL

Memory is modeled in Verilog HDL by an array of registers

```
reg [15:0] memword [0:1023]; // 2 dimension array
```


④ this is 2k x 16 memory.

(1024 registers, each containing 16 bits).

now memword[7] refers to the 16-bit memory word at address 7.

 Example

```
module memory(Enable, ReadWrite,
  Address, DataIn, DataOut);
  input Enable, ReadWrite;
  input [3:0] DataIn;
  input [5:0] Address;
  output [3:0] DataOut;
  reg [3:0] DataOut;
  reg [3:0] memword [0:63];
```



```
always @ ( Enable, or ReadWrite)
```

```
if (Enable == 0)
```

```
  DataOut = 4'bZ;
```

```
else
```

```
  if (ReadWrite)
```

```
    DataOut = memword [ Address];
```

```
  else
```

```
    mem[Address] = DataIn;
```

* Error Detection and Correction

- ① Some errors may occur in storing and retrieving the binary information.
- ② employ error detecting and correcting codes. (e.g. Parity bit is the most common).

③ Hamming Code:

- In Hamming Code, k parity bits are added to an n -bit data word, forming a new word of $n+k$ bits.
- The bit positions are numbered in sequence from 1 to $n+k$.
- Those positions numbered a power of 2 are reserved for the parity bits. The remaining bits are the data bits.

~~- for n bits of data, we need~~

- The following relationship between n and k

$$2^k - 1 - k \geq n$$

e.g. for $k = 3$ (check bits (parity bits))

$$n \leq 2^3 - 1 - 3 = 4$$

for $k = 4$

$$n \leq 2^4 - 1 - 4 = 11$$

$$\Rightarrow 5 \leq n \leq 11$$

if $n < 5 \rightarrow k = 3$ bits is enough.

Example: Consider the 8-bit data word 11000100

⇒ we need 4 parity bits

⇒ new word size = $n + k = 8 + 4 = 12$

Bit positions:

Bit positions:	1	2	3	4	5	6	7	8	9	10	11	12
	P_1	P_2	d_1	P_4	1	0	0	P_8	0	1	0	0

$P_1 = \text{XOR of bits (3, 5, 7, 9, 11)}$

$$= 1 \oplus 1 \oplus 0 \oplus 0 \oplus 0 = 0$$

$P_2 = \text{XOR of bits (3, 6, 7, 10, 11)}$

$$= 1 \oplus 0 \oplus 0 \oplus 1 \oplus 0 = 0$$

$P_4 = \text{XOR of bits (5, 6, 7, 12)}$

$$= 1 \oplus 0 \oplus 0 \oplus 0 = 1$$

$P_8 = \text{XOR of bits (9, 10, 11, 12)}$

$$= 0 \oplus 1 \oplus 0 \oplus 0 = 1$$

(EVEN PARITY).

3	0	0	1	1
5	0	1	0	1
6	0	1	1	0
7	0	1	1	1
9	1	0	0	1
10	1	0	1	0
11	1	0	1	1
12	1	1	0	0

⊕ Now the 8-bit data word is stored in memory together with the 4 parity bits as a 12-bits composite words

Bit position:	1	2	3	4	5	6	7	8	9	10	11	12
	0	0	1	1	1	0	0	1	0	1	0	0

⊕ when the 12 bits are read from memory, they are checked again for possible errors.

⇒

$C_1 = \text{XOR of bits } (1, 3, 5, 7, 9, 11)$

$C_2 = \text{XOR of bits } (2, 3, 6, 7, 10, 11)$

$C_4 = \text{XOR of bits } (4, 5, 6, 7, 12)$

$C_8 = \text{XOR of bits } (8, 9, 10, 11, 12)$

if $C = 0 \Rightarrow$ Even parity $\Rightarrow$ no errors

$\Rightarrow C = C_8 C_4 C_2 C_1 = 0000$ indicates that no error in the stored word.

if $C \neq 0 \Rightarrow$ ^{an} error has occurred

eg: 0 0 1 1 1 0 0 1 0 1 0 0 no error

$\Rightarrow C_1 = 0 \quad C_2 = 0 \quad C_4 = 0 \quad C_8 = 0$

$\Rightarrow$ No error.

1 0 1 1 1 0 0 1 0 1 0 0 error in bit 1

$\Rightarrow C_1 = 1 \quad C_2 = 0 \quad C_4 = 0 \quad C_8 = 0$

$\Rightarrow$ error in bit 1 (the parity bit).

0 0 1 1 0 0 0 1 0 1 0 0 error in bit 5

$\Rightarrow C_1 = 1 \quad C_2 = 0 \quad C_4 = 1 \quad C_8 = 0$

$\Rightarrow$ error in bit $(4+1) = 5$

Ⓐ C is called the syndrome ~~vector~~.

Ⓑ The syndrome value C consists of k bits and has a range of 2^k values between 0 and $2^k - 1$.

- The value $C = 0$ indicates no error $\Rightarrow$

$2^k - 1$ are left to indicate which

of the $n+k$ bits was in error.

$$\Rightarrow 2^h - 1 \geq n+k$$

$$\Rightarrow \underline{\underline{2^h - 1 - k \geq n}}$$

④ Up to now we can detect one error and correct one error

④ Single error Correction, Double error Detection

- By adding another parity bit to the coded word, the hamming code can be used to correct a single error and detect double errors

- in the previous example

0011100100 P_{13}

$P_3 = \text{XOR of all previous bits}$

$\Rightarrow P_3 = 1$ (even parity).

- thus 13 bits are stored in memory

- when reading data $P = \text{XOR of the 13-bits}$

If $c = 0$ and $P = 0 \Rightarrow$ no error occurred


If $c \neq 0$, $P = 1$, a single error has occurred that can be corrected

If $c \neq 0$, $P = 0$, a double error has occurred that can not be corrected.

If $c = 0$, $P = 1 \Rightarrow$ An error occurred in the P_{13} bit.


⊛ ROM:

- Read only
- nonvolatile memory

 

⊛ internal block diagram

 Ex. 32 x 8 ROM (5 address lines
8 output lines)



⊛ 8 OR gates with 32 inputs for each

$\Rightarrow$ ^{this} ROM has $32 \times 8 = 256$ internal connections.

⊛ In general, $2^k \times n$ ROM will have an internal $k \times 2^k$ decoder and n OR gates. Each OR gate has 2^k inputs.

Inputs					Outputs							
I_4	I_3	I_2	I_1	I_0	A_7	A_6	A_5	A_4	A_3	A_2	A_1	A_0
0	0	0	0	0	1	0	1	1	0	1	1	0
0	0	0	0	1	0	0	0	1	1	1	0	1
0	0	0	1	0	1	1	0	0	0	1	0	1
0	0	0	1	1	1	0	1	1	0	0	1	0
⋮					⋮							
1	1	1	0	0	0	0	0	0	1	0	0	1
1	1	1	0	1	1	1	0	0	0	1	0	0
1	1	1	1	0	0	1	0	0	1	0	1	0
1	1	1	1	1	0	0	1	1	0	0	1	1

④ Combinational Circuit Implementation

④ ROM contains Decoder & OR gates.

⇒ ROM outputs can be programmed to represent the boolean functions.

④ ROM can be interpreted in two ways

- ① memory unit that contains a fixed pattern of stored word
- ② unit that implements a combinational circuit.

e.g. $A_7(I_4, I_3, I_2, I_1, I_0) = \sum (0, 2, 3, \dots, 29)$


Example :-

3-bit number, output equal the square of the input number. Implement this function using ROM

$\Rightarrow$ 6 outputs

Inputs			Outputs					
A_2	A_1	A_0	B_5	B_4	B_3	B_2	B_1	B_0
0	0	0	0	0	0	0	0	0
0	0	1	0	0	0	0	0	1
0	1	0	0	0	0	1	0	0
0	1	1	0	0	1	0	0	1
1	0	0	0	1	0	0	0	0
1	0	1	0	1	1	0	0	1
1	1	0	1	0	0	1	0	0
1	1	1	1	1	0	0	0	1

$$B_0 = A_0 \quad B_1 = 0$$



 


Types of ROM

   - 1) mask programming: programming done during the fabrication process according to a truth table by the user (customer)
- 2) PROM: programmed by the user for one time.
- 3) EPROM: Erasable PROM through a special device using ultraviolet radiation for a period of time
- 4) EEPROM: Electrically Erasable PROM.

⑥ Combinational PLD

- 3 main types: differ in the placement of the programmable connections in the AND OR array




⊗ Programmable Logic Array (PLA)

- no decoder $\rightarrow$ doesn't generate all minterms like PROM.

Example: PLA with 3 inputs and 2 outputs

$$F_1 = AB' + AC + A'BC'$$

$$F_2 = (AC + BC)'$$

 

* SynaptCAD

⑧ Programming Table

Product Term	Inputs			Outputs	
	A	B	C	$\overline{F_1}$	$\overline{F_2}$
AB'	1	0	-	1	-
AC	1	-	1	1	1
ABC	-	1	1	-	1
$A'Bc'$	0	1	0	1	-

↓
no need
for this

Example: Implement the following two Boolean functions with a PAL

$$F_1(A, B, C) = \sum (0, 1, 2, 4)$$

$$F_2(A, B, C) = \sum (0, 5, 6, 7)$$

A \ BC	00	01	11	10
0	1	1	0	1
1	1	0	0	0

$$F_1 = A'B' + A'C' + B'C'$$

$$\text{or } F_1 = (F_1')' = (AB + AC + BC)'$$

A \ BC	00	01	11	10
0	1	0	0	0
1	0	1	1	1

$$F_2 = AB + AC + A'B'C'$$

$$F_2 = (A'C + A'B + AB'C')'$$


$$F_1(T) \& F_2(T) \Rightarrow 6 \text{ terms}$$

$$F_1(T) \& F_2(C) \Rightarrow 6 \text{ terms}$$

$$F_1(C) \& F_2(T) \Rightarrow 4 \text{ terms}$$
 
$$F_1(C) \& F_2(C) \Rightarrow 6 \text{ terms}$$





⑤ Programming table

Product term		Inputs			outputs	
		A	B	C	(C) F1	(T) F2
AB	1	1	1	-	1	1
AC	2	1	-	1	1	1
BC	3	-	1	1	1	-
A'B'C'	4	0	0	0	-	1

- In general, For n inputs, k product terms and m outputs the internal logic of the PLA

consists of n -buffer-inverter gates,
 k AND gates, m OR gates, and m XOR gates.
There are $2n \times k$ connections between the
inputs and the AND array, $k \times m$ connections
between the AND and OR arrays and m
connections with the XOR gates.

SynaptCAD