

# **ENEE236**

## **Analog Electronics**

### **T2 Semiconductor Diodes**

**Instructor: Nasser Ismail**

## **Diode Operating Conditions**


**A diode has three operating conditions:**

- 1) No bias**
- 2) Reverse bias**
- 3) Forward bias**
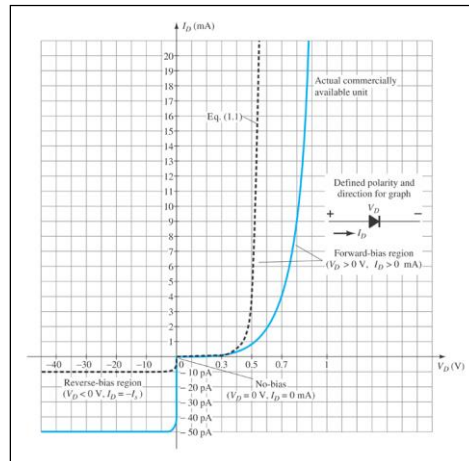
## Actual Diode Characteristics


Note the regions for no bias, reverse bias, and forward bias conditions.

Carefully note the scale for each of these conditions.


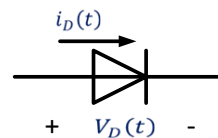
## Diode Equation

$$i_D(t) = I_S \left( e^{\frac{V_D(t)}{\eta V_T}} - 1 \right)$$



$I_S$ : Reverse saturation current

$$I_S = 10^{-12}, 10^{-14} \text{ A}$$

$\eta$ : eta

$$\eta = \begin{cases} 1 & \text{for Ge} \\ 2 & \text{for Si (small current)} \\ 1 & \text{for Si (large current)} \end{cases}$$

$V_T$  = Thermal Voltage

$$V_T = \frac{T}{11600} \quad ; T \text{ in kelvin}$$

At Room Temp.  $T=300$  k

$\therefore V_T = 25.69$  mv at Room Temp.

► The equation is a non linear equation



$\therefore$  The Diode is non linear Device

$$i_D(t) = I_S \left( e^{\frac{V_D(t)}{\eta V_T}} - 1 \right)$$

► For **positive**  $V_D(t)$ ,  $i_D(t) = I_S \left( e^{\frac{V_D(t)}{\eta V_T}} - 1 \right)$

► For **negative**  $V_D(t)$   $i_D(t) = -I_S$

## Diode V-I Characteristic curve

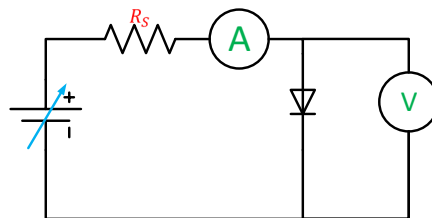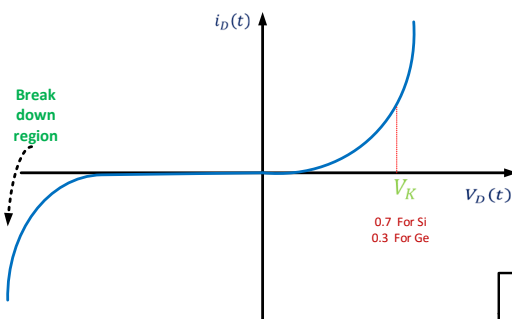

## Approaches to Diode Circuit Analysis


The rectifier diode is a non linear device .

There are essentially **three** basic approaches to the solution of such problem :

- 1- The use of non linear mathematics
- 2- The use of graphical techniques
- 3- The use of equivalent circuit (**models**)  
(piecewise linear models)
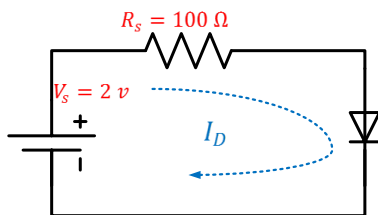
### 1)The use of non linear mathematic (shown , but not required)

► For the circuit shown, find  $I_D$  and  $V_D$



Silicon:

$\eta=1.1$

$I_S = 10^{-14} \text{ A}$

► KVL :  $V_S = R_S I_D + V_D$

$$I_D = I_S (e^{\frac{V_D}{\eta V_T}} - 1)$$

► Since the diode is **forward biased** , we could approximate

$$I_D = I_S (e^{\frac{V_D}{\eta V_T}})$$

► Solving for  $V_D = \eta V_T \ln \frac{I_D}{I_S}$

∴ We have two equations and two unknowns

$$V_S = R_S I_D + V_D \dots\dots\dots 1$$

$$V_D = \eta V_T \ln \frac{I_D}{I_S} \dots\dots\dots 2$$

$$\therefore V_S = R_S I_D + \eta V_T \ln \frac{I_D}{I_S}$$

● **non linear equation**

## Iterative Analysis

$$I_D = \frac{V_S - V_D}{R_S}$$

$$V_D = \eta V_T \ln \frac{I_D}{I_S}$$

1) Let  $V_D = 0.7\text{v}$

$$I_D = \frac{2 - 0.7}{0.1k} = 13 \text{ mA}$$

$V_D = 0.7882392\text{v}$       The error is large

2) Let  $V_D = 0.7882392\text{v}$

$$I_D = 12.117608 \text{ mA}$$

$V_D = 0.7862529\text{v}$       The error is small

3) Let  $V_D = 0.7862529\text{V}$

$$I_D = 12.137471\text{ mA}$$

$V_D = 0.7862991\text{ V}$  The error getting smaller

4) Let  $V_D = 0.7862991\text{ V}$

$$V_D = 0.786298066\text{ V}$$

$$I_D = 12.137009\text{ mA}$$

$$I_D = 12.137\text{ mA}$$

$$V_D = 0.7863\text{ V}$$

## 2) The use of graphical techniques

(Requires the V-I exact plot)


$$V_S = R_S I_D + V_D \quad \dots\dots\dots 1$$

$$I_D = I_S \left( e^{\frac{V_D}{\eta V_T}} - 1 \right) \quad \dots\dots\dots 2$$


- Using equation 1

$$I_D = -\frac{1}{R_S} V_D + \frac{V_S}{R_S}$$

**Dc Load Line Equation**

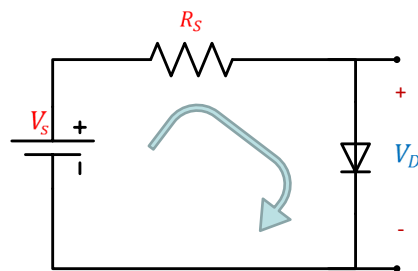


## Drawing the two equations

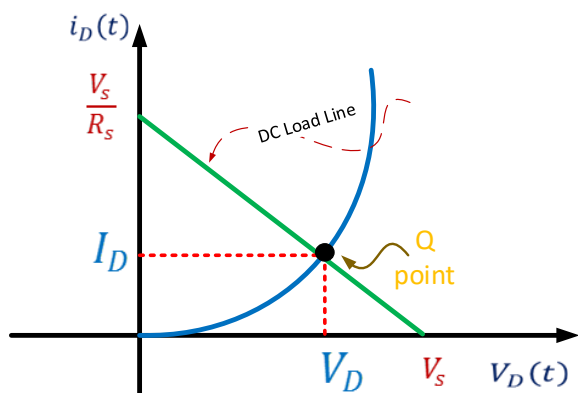

$$I_D = -\frac{1}{R_s}V_D + \frac{V_s}{R_s}$$


- $Q_{\text{point}} = (V_{DQ}, I_{DQ}) = Q_{\text{quiescent point}}$

## The effect of $R_s$ on the Qpoint

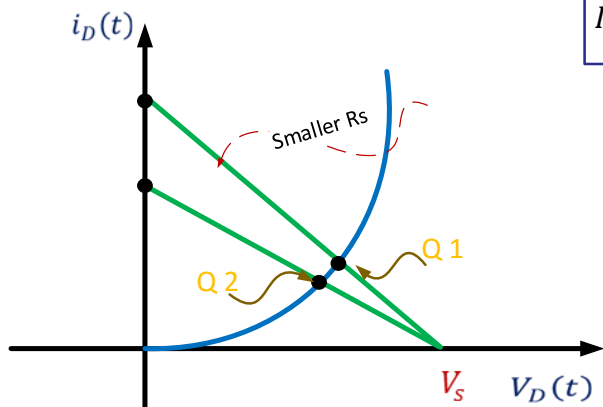

$$I_D = -\frac{1}{R_s}V_D + \frac{V_s}{R_s}$$

### The effect of Vs on Qpoint

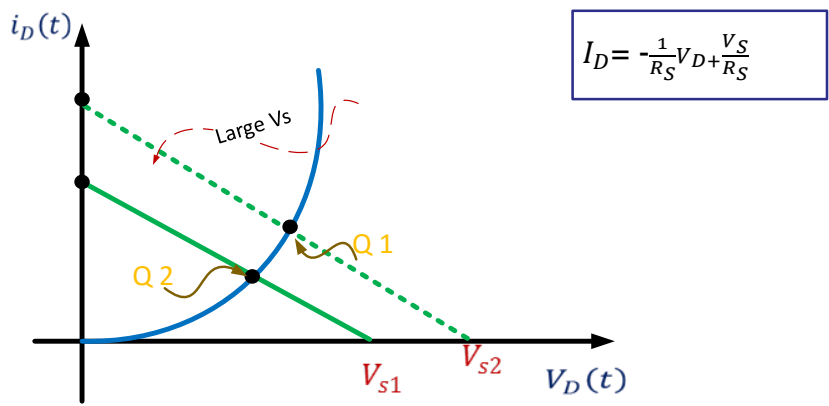


### The Use of Diode Model



## The use of Diode Models


- ▶ A piece wise linear models is an electrical equivalent circuit of a nonlinear electronic device
- It is composed of linear circuit elements arranged to approximate the characteristics of the electronic device
- 

### a) ideal diode model

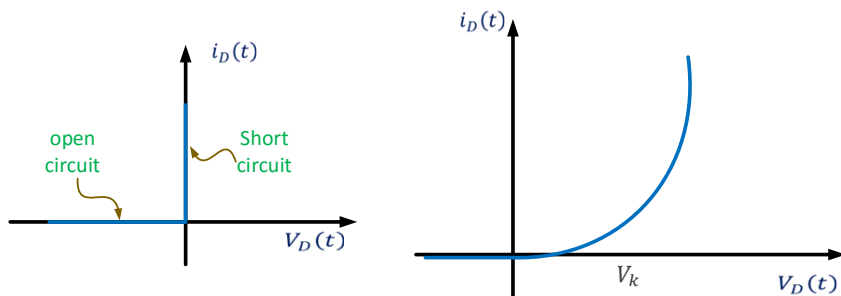



- When  $V_s < 0$  ; the Diode is off, and replaced with open circuit
- ▶ When  $V_s \geq 0$  ; the Diode is on, and replaced with short circuit

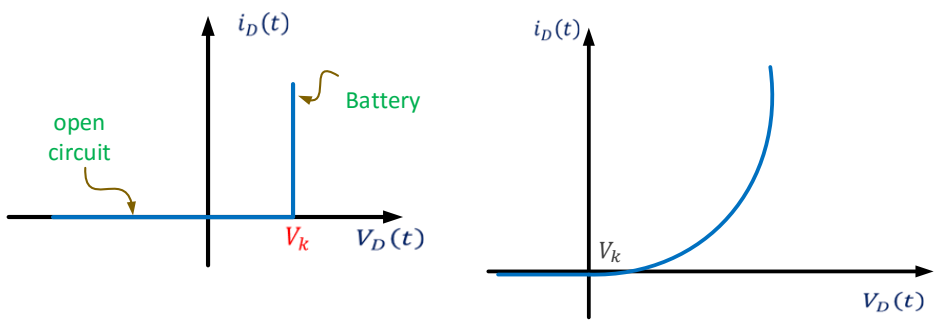**b) Knee Voltage model  
(simplified/practical model)**




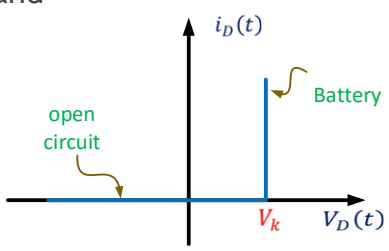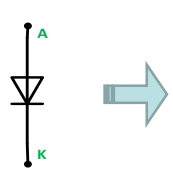**b) Knee Voltage model  
(simplified/practical model)**


► When  $V_s < V_k$ ; the Diode is off, and replaced with open circuit



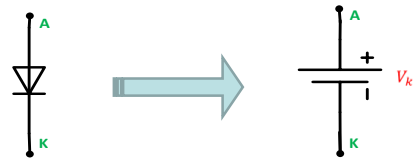► When  $V_s \geq V_k$ ; the Diode is on, and replaced with a constant voltage source



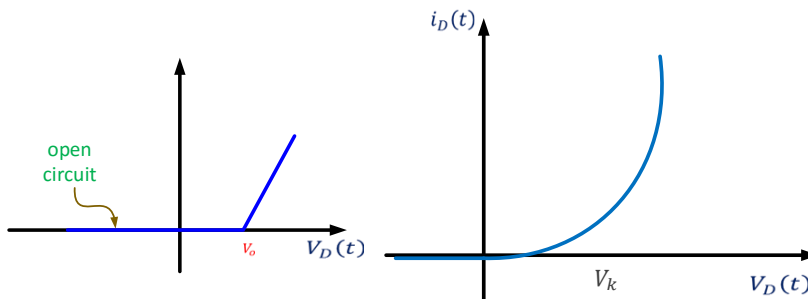
### c) Dynamic resistance model (complete model)




- When  $V_s \geq V_o$  ; the Diode is on, and replaced with a constant voltage source  $V_o$  and resistance  $R_o$
- When  $V_s < V_o$  ; the Diode is off, and replaced with open circuit
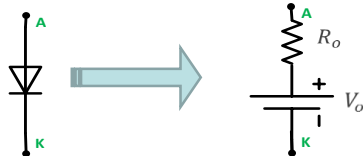
### c) Dynamic resistance model


- When  $V_s \geq V_o$  ; the Diode is on, and replaced with a constant voltage source  $V_o$  and resistance  $R_o$



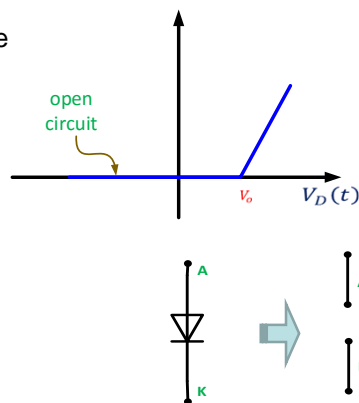- When  $V_s < V_o$  ; the Diode is off, and replaced with open circuit




To determine  $V_o$  and  $R_o$

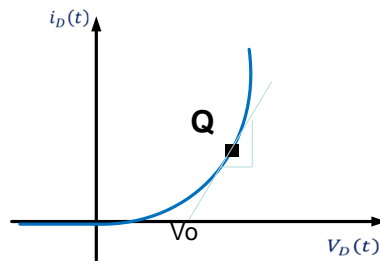

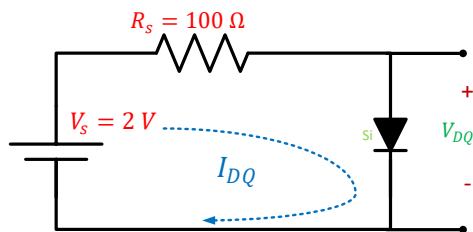
## Example

- Find the Q point ( $I_{DQ}$ ,  $V_{DQ}$ ) using
  - ideal diode model
  - knee voltage model




### a) using ideal diode model

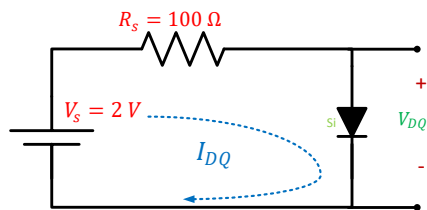

since  $V_s \geq 0$ , the diode is on and replaced with short circuit.

$$\therefore I_{DQ} = \frac{2}{100} = 20 \text{ mA}$$

$$\therefore V_{DQ} = 0 \text{ V}$$

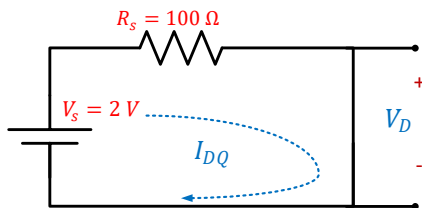



### b) Using knee voltage model

since  $V_s \geq 0.7$ , the diode is on and replaced with  $V_k = 0.7$ .

$$\therefore I_{DQ} = \frac{2-0.7}{100}$$

$$= 13 \text{ mA}$$

$$\therefore V_{DQ} = 0.7 \text{ V}$$

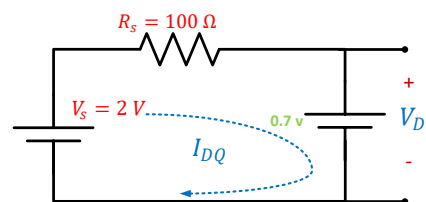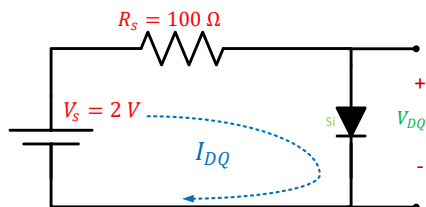

### c) using nonlinear mathematic

$$I_{DQ} = 12.137 \text{ mA}$$

$$V_{DQ} = 0.7863 \text{ V}$$

### Taking the knee voltage into a count

- If  $V_S \geq 10 V_k$ , we could use ideal diode model .

$$I_{DQ} = \frac{V_S - V_k}{100} \approx \frac{V_S}{100}$$

- If  $V_S < 10 V_k$ , we must use knee voltage model .

**Note:** If applied voltage is much higher than VAK ( at least 10 times) , then ideal diode model is recommended


## Example

- Find the Q point

Using thevenin's theorem , the circuit is simplified to

$$R_{th} = 10k + 10k \parallel 20k = 16.7k$$

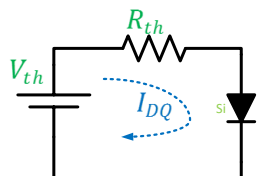
$$V_{th} = \frac{20k}{20k+10k} * 6 = 4V$$



since  $V_{th} \geq V_k$  , the diode is on

since  $V_{th} < 10V_k$  , we must use the knee voltage model

## Knee voltage model

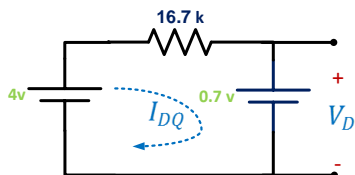


$$I_{DQ} = \frac{4 - 0.7}{16.7K} = 0.198 mA$$

$$V_{DQ} = V_K = 0.7V$$
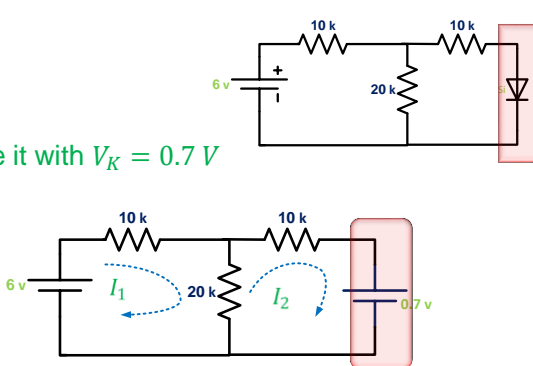
### Second method

assume the diode is on , replace it with  $V_K = 0.7\text{ V}$




**KVL:**

$$6 = 30 I_1 - 20 I_2$$
$$-0.7 = -20 I_1 + 30 I_2$$

Solve for:


$$I_2 = 0.198\text{ mA}$$
$$\therefore I_D = I_2 = 0.198\text{ mA}$$

Since  $I_D > 0$  ,  $\therefore$  our assumption is ok




ENEE236 – Analog Electronics

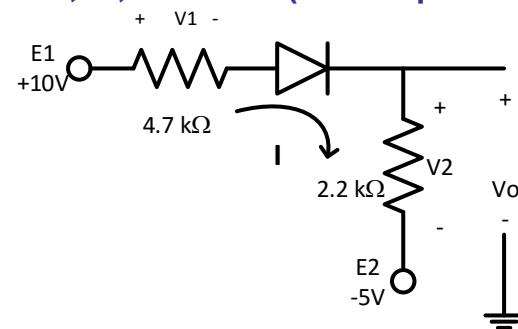Example: **Find  $I, V_1, V$  and  $V_o$**  (use simplified model)



**Solution:**

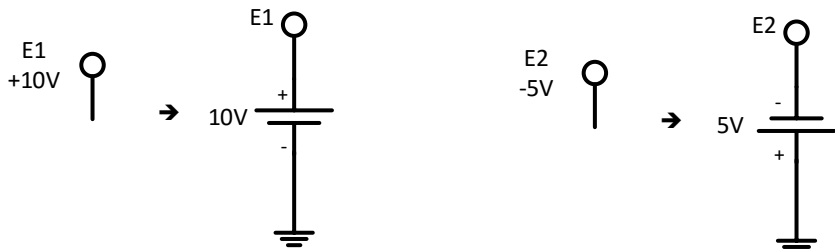



ENEE236 – Analog Electronics

Diagram showing a circuit with a 10V DC source (E1), a 4.7 kΩ resistor (R1), a diode, a 2.2 kΩ resistor (R2), and a 5V DC source. The output voltage  $V_o$  is measured across the 5V source. The current  $I$  flows through the diode and resistors. The voltage across the diode is  $V_1$ , and the voltage across  $R_2$  is  $V_2$ .

==> Diode is Forward biased

$$I = (10 + 5 - 0.7) \text{ V} / (4.7 + 2.2) \text{ k}\Omega$$

$$= 2.07 \text{ mA}$$

$$V_1 = I \cdot R_1 = 9.73 \text{ V}$$

$$V_2 = I \cdot R_2 = 4.55 \text{ V}$$

$$V_o = V_2 - 5 = -0.45 \text{ V}$$

ENEE236 – Analog Electronics

**Find  $I_1$ ,  $I_2$ ,  $I_{D2}$  (use practical diode model)**

**Solution:**

Applied voltage is suitable for forward biasing both diodes

$$I_1 = 0.7 \text{ V} / 3.3 \text{ k}\Omega$$

$$= 0.212 \text{ mA}$$

$$I_2 = (20 - 0.7 - 0.7) / 5.6 \text{ k}\Omega$$

$$= 3.32 \text{ mA}$$

$$I_2 = I_1 + I_{D2}$$

$$I_{D2} = I_2 - I_1 = 3.32 - 0.212$$

$$= 3.11 \text{ mA}$$