



FACULTY OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND COMPUTER
ENGINEERING

Basic Electrical Engineering Lab (ENEE 2101)

Report of Experiment 7
“Second Order Circuits”

Prepared by:

Name: Malak Qasem

Number: 1210484

Partners:

Name: Aya Badawi

Number: 1222065

Name: Leen Shawakha

Number: 1221826

Instructor: Dr. Jaser Sa'Ed

TA: Eng. Mohammad Deek

Date of experiment: November 7, 2024

Table of Contents

<i>Abstract:</i>	3
<i>Theory:</i>	3
<i>Procedure:</i>	6
<i>Data, calculations, and analysis of results:</i>	8
<i>Conclusion:</i>	15
<i>References</i>	16

List of figures:

<i>Figure 1:RLC circuit:</i>	3
<i>Figure 2: current equations</i>	5
<i>Figure 3: voltage equations</i>	5
<i>Figure 4:Parallel RLC circuit Equations</i>	5
<i>Figure 5: Part A circuit</i>	6
<i>Figure 6: Part B circuit:</i>	7
<i>Figure 7: Overdamped response</i>	8
<i>Figure 8: Critical response</i>	9
<i>Figure 9: Underdamped response</i>	10
<i>Figure 10: Underdamped response in detailed:</i>	10
<i>Figure 11: Question #2</i>	11
<i>Figure 12: Underdamped response</i>	12
<i>Figure 13: Underdamped response in detailed:</i>	13
<i>Figure 14: Question #3</i>	13
<i>Figure 15: Critical response</i>	14
<i>Figure 16: Overdamped response</i>	14
<i>Figure 17: Data sheet:</i>	16

List of tables:

<i>Table 1: inductor resistance</i>	8
<i>Table 2: 7.1 Table</i>	11
<i>Table 3: Inductor resistance</i>	12
<i>Table 4: 7.2 Table</i>	15

Abstract:

This experiment examines the behavior of second-order RLC circuits in series and parallel configurations, focusing on their responses to step and sinusoidal inputs.

Theory:

The process of determining the natural or step responses of a series RLC circuit follows the same steps as for a parallel RLC circuit, since both types of circuits are governed by differential equations with the same structure.

We start by adding up the voltages around the closed loop on the circuit shown

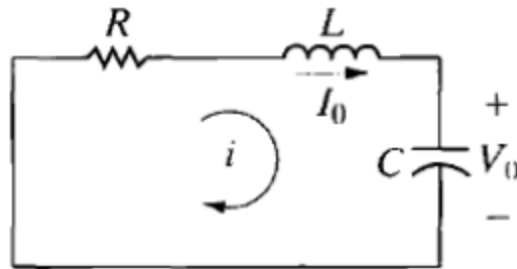


Figure 1:RLC circuit

The total voltage drop across each component in the loop:

$$Ri + L \frac{di}{dt} + \frac{1}{C} \int_0^t i d\tau + V_0 = 0.$$

We now differentiate the above equation with respect to t to get the following equation:

$$R \frac{di}{dt} + L \frac{d^2i}{dt^2} + \frac{i}{C} = 0.$$

After rearranging the equation, we get:

$$\frac{d^2i}{dt^2} + \frac{R}{L} \frac{di}{dt} + \frac{i}{LC} = 0.$$

The characteristic equation for a series RLC circuit can be expressed as follows:

$$s^2 + \frac{R}{L}s + \frac{1}{LC} = 0.$$

Since this is a quadratic equation, it will have two distinct solutions, as shown in the following equation:

$$s_{1,2} = -\frac{R}{2L} \pm \sqrt{\left(\frac{R}{2L}\right)^2 - \frac{1}{LC}}.$$

Assuming that $\alpha = \frac{R}{2L} \text{ Rad/s}$ and $\omega_0 = \frac{1}{LC} \text{ Rad/s}^2$

While α is the neper frequency for RLC circuits, ω_0 is the resonant radian frequency.

As a result, the equation will be:

$$s_{1,2} = -\alpha \pm \sqrt{\alpha^2 - \omega_0^2}.$$

The response will be overdamped when $\omega_0^2 < \alpha^2$

The response will be underdamped when $\omega_0^2 > \alpha^2$

The response will be critically damped when $\omega^2 = \alpha^2$

Therefore, the three possible solutions for the current are as follows:

$$\begin{aligned} i(t) &= A_1 e^{s_1 t} + A_2 e^{s_2 t} \text{ (overdamped),} \\ i(t) &= B_1 e^{-\alpha t} \cos \omega_d t + B_2 e^{-\alpha t} \sin \omega_d t \text{ (underdamped),} \\ i(t) &= D_1 t e^{-\alpha t} + D_2 e^{-\alpha t} \text{ (critically damped).} \end{aligned}$$

Figure 2: current equations

The three possible solutions for v_C are as follows:

$$\begin{aligned} v_C &= V_f + A'_1 e^{s_1 t} + A'_2 e^{s_2 t} \text{ (overdamped),} \\ v_C &= V_f + B'_1 e^{-\alpha t} \cos \omega_d t + B'_2 e^{-\alpha t} \sin \omega_d t \text{ (underdamped),} \\ v_C &= V_f + D'_1 t e^{-\alpha t} + D'_2 e^{-\alpha t} \text{ (critically damped),} \end{aligned}$$

Figure 3: voltage equations

Where V_f is the final value of V_C

Step response of second-order parallel RLC circuit

These equations are a helpful equation to calculate Decay time constant, Damping Coefficient, Damped radian frequency in underdamped response case:

Decay time constant	$\tau = \frac{t_b - t_a}{\ln \left(\frac{V_a - V_{o(\infty)}}{V_b - V_{o(\infty)}} \right)}$..
Damping Coefficient	$\alpha = \frac{1}{\tau}$
Damped radian frequency	$\omega_d = \frac{2\pi}{t_b - t_a}$

Figure 4: Parallel RLC circuit Equations

Procedure:

Part A: Step response of second-order Series RLC circuit

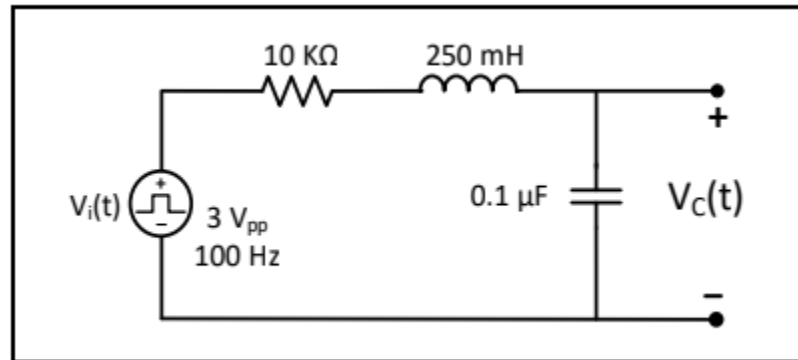


Figure 7.5

Figure 5: Part A circuit

To examine the step response of a second-order series RLC circuit, begin by connecting the circuit as shown in the provided diagram. Set up the function generator to output a square wave with a peak-to-peak voltage of 3 V, a frequency of 100 Hz, and a DC offset of 1.5 V. Use a decade box to adjust the resistor R as needed. Next, use a digital multimeter (DMM) to measure the DC resistance of the inductor and record this value in the data sheet. Connect Channel 2 (CH2) of the oscilloscope across the capacitor. Gradually adjust the variable resistor within its range (10 k Ω to 1 k Ω) while observing the changes in the output voltage $V_C(t)$ across the capacitor.

- ***Case A: Over damped response***

Set the variable resistor to 10 k Ω .

- ***Case B: Critically damped response***

Set the variable resistor to the critical resistance.

- ***Case C: Under damped response***

Set the variable resistor to 500 Ω .

After take a picture of resulting waveform we must use cursors to find the values V_a , t_a , V_b , t_b , $V(\infty)$. Then record the results in table 7.1.

Part B: Step response of second-order parallel RLC circuit

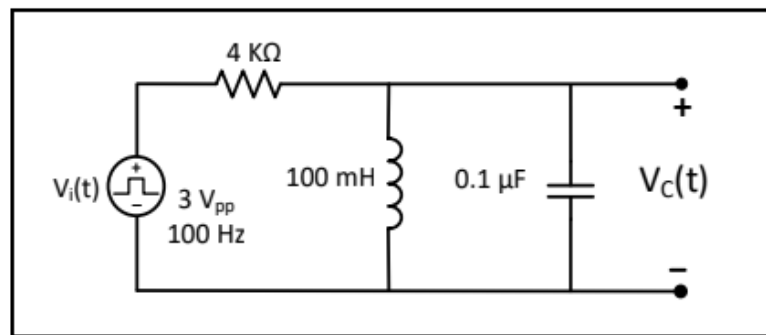


Figure 7.6

Figure 6: Part B circuit

In this procedure for studying the step response of a second-order parallel RLC circuit, Keep the function generator settings the same: an output square wave with a peak-to-peak voltage of 3 V, a frequency of 100 Hz, and a DC offset of 1.5 V. Use a decade box to adjust the resistor R as needed. Next, use a digital multimeter (DMM) to measure the DC resistance of the inductor and record this value in the data sheet. Connect Channel 2 (CH2) of the oscilloscope across the capacitor. Adjust the variable resistor (set to 4 k Ω initially) over its entire range, and observe how the output waveform $V_c(t)$ across the capacitor changes.

- ***Case A: Under damped response***

Set the variable resistor to 4 k Ω .

- ***Case B: Critically damped response***

Set the variable resistor to the critical resistance.

- ***Case C: Over damped response***

Set the variable resistor to 150 Ω .

After adjusting the variable resistor and observing the resulting waveform for each setting, capture a picture of the waveform in each case. Use the oscilloscope's cursors to measure the following values $V_a, t_a, V_b, t_b, V(\infty)$. Then record the results in table 7.1.

Data, calculations, and analysis of results

Part A: Step response of second-order Series RLC circuit

Use a digital multimeter (DMM) to measure the resistance of the inductor.

R inductor (Ω)	12.3 Ω
-------------------------	---------------

Table 1: inductor resistance

➤ Case A: Over damped response

Set the variable resistor to 10 k Ω .

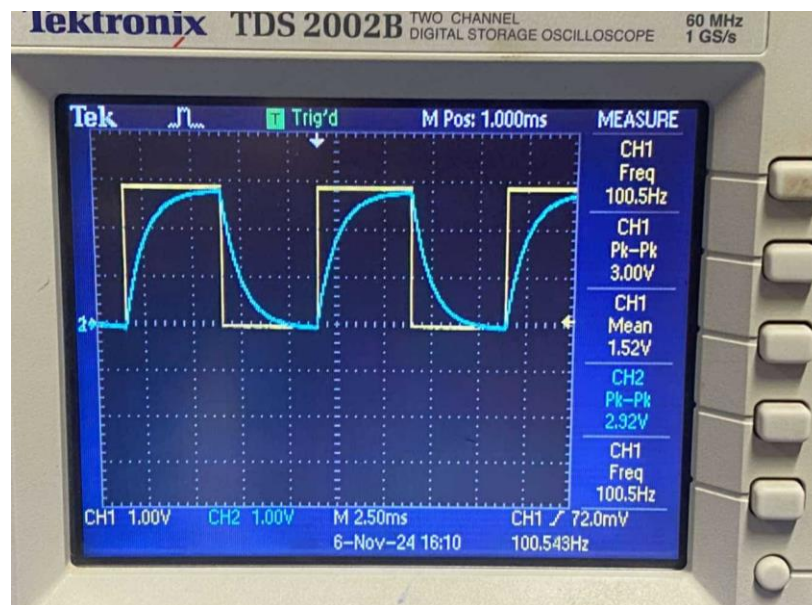


Figure 7: Overdamped response

➤ **Case B: Critically damped response**

Calculating R_{cr} critical using this equation $R_{cr} = \sqrt{\frac{4L}{C}}$ after calculate it we get $R_{cr} = 3.16k\Omega$

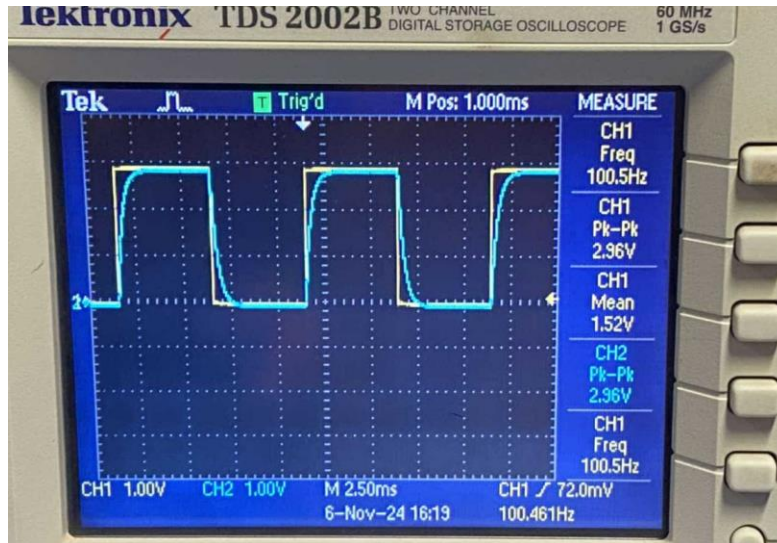


Figure 8: Critical response

As shown in the figures above, the overdamped curve rises more slowly than the critically damped one, as critical damping allows the system to reach its maximum value more quickly.

➤ **Case C: Under damped response**

Set the variable resistor to 500Ω .

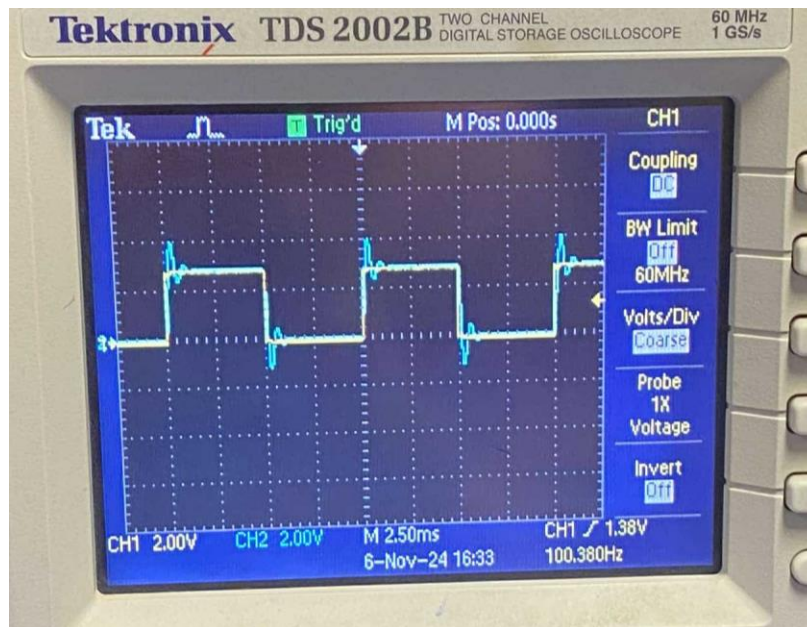


Figure 9: Underdamped response

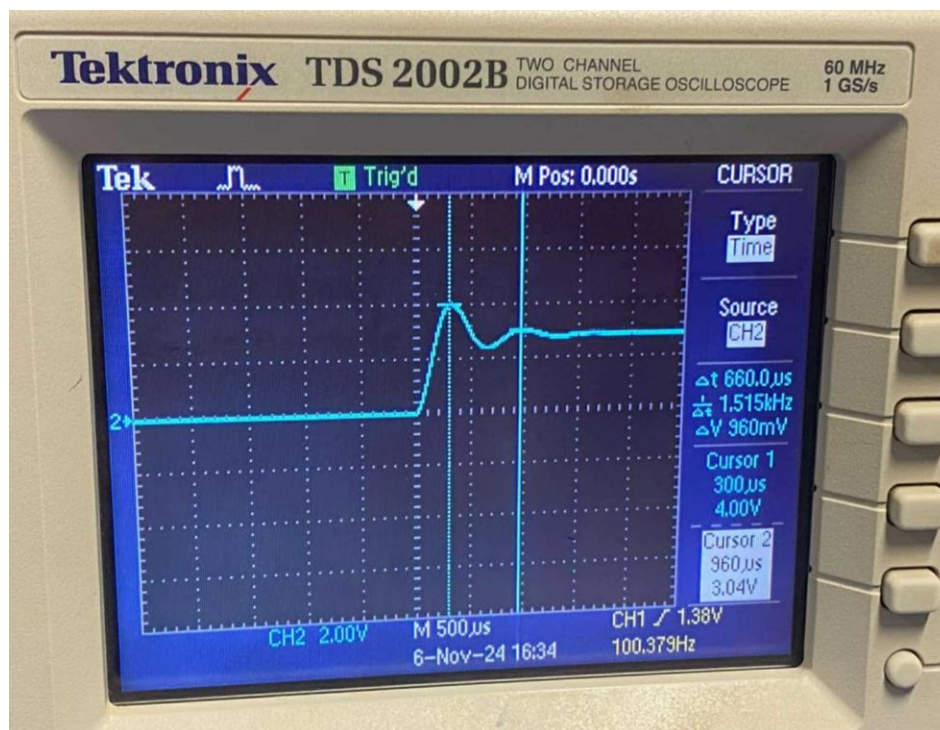


Figure 10: Underdamped response in detailed

The voltage (V_a) and time (t_a) at the greatest peak and the voltage (V_b) and time (t_b) at the lowest peak are measured in an underdamped response. The system's oscillatory nature is captured by these values. The voltage value $V(\infty)$ at which the system reaches equilibrium without varying, is measured in a Critical damped response.

V_a	t_a	V_b	t_b	$V(\infty)$
3.92V	300 μ s	3.04V	960 μ s	2.92V

Table 2: 7.1 Table

Calculate decay-envelope time constant (τ), the damping coefficient (α), and damped frequency (ω_d):

Question #2: Malak Qusem
1210484

- Decay time constant $\tau = \frac{t_b - t_a}{\ln \left(\frac{V_a - V_o(\infty)}{V_b - V_o(\infty)} \right)}$

$$\tau = \frac{960 \times 10^{-6} - 300 \times 10^{-6}}{\ln \left(\frac{3.92 - 2.92}{3.04 - 2.92} \right)}$$

$$\tau = \frac{660 \times 10^{-6}}{\ln 8.33} \Rightarrow \boxed{\tau = 3.113 \times 10^{-4} \text{ sec/rad}}$$
- Damping coefficient $\alpha = \frac{1}{\tau} = \frac{1}{3.113 \times 10^{-4}} \Rightarrow \boxed{\alpha = 3212.34 \text{ rad/sec}}$
- Damped Frequency $\omega_d = \frac{2\pi}{t_b - t_a} = \frac{2\pi}{960 \times 10^{-6} - 300 \times 10^{-6}}$

$$\omega_d = 9515.15 \text{ sec}^{-1}$$

Figure 11: Question #2

Part B: Step response of second-order parallel RLC circuit

Use a digital multimeter (DMM) to measure the resistance of the inductor.

R inductor (Ω)	12.3 Ω
-------------------------	---------------

Table 3: Inductor resistance

➤ *Case A: Under damped response*

Set the variable resistor to 4 k Ω .

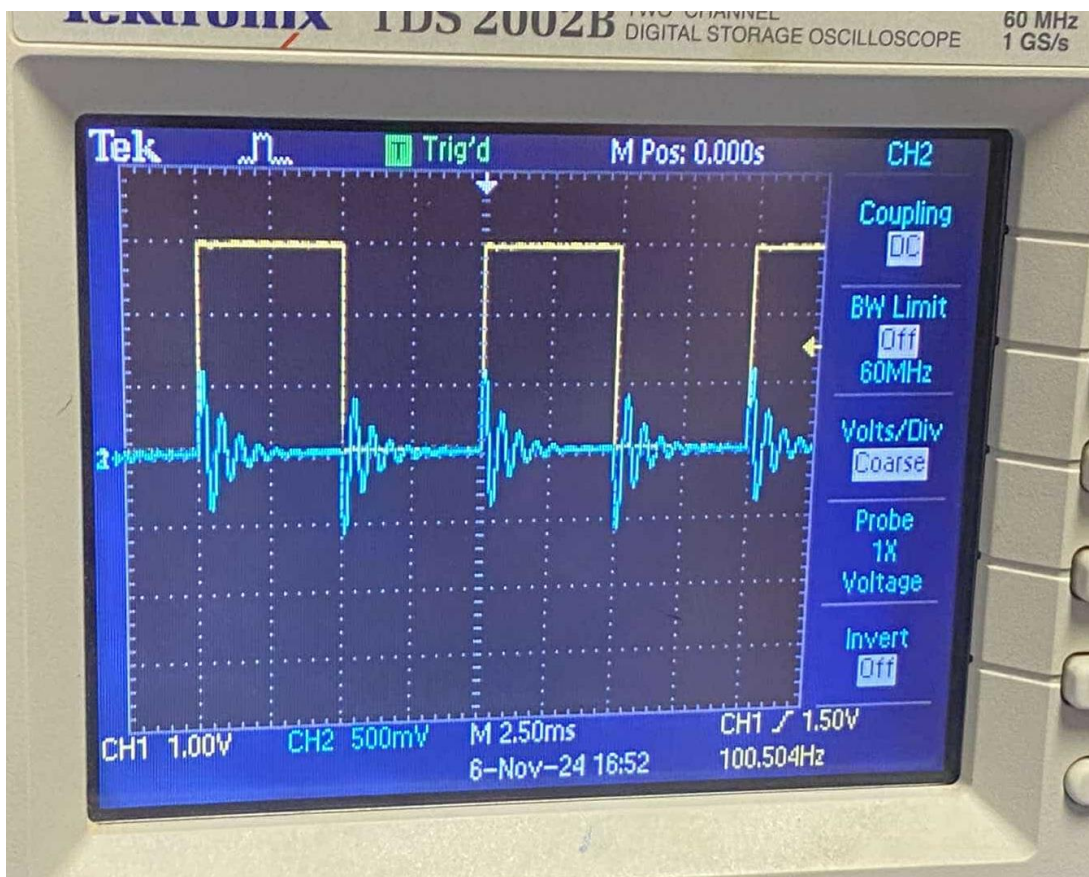


Figure 12: Underdamped response

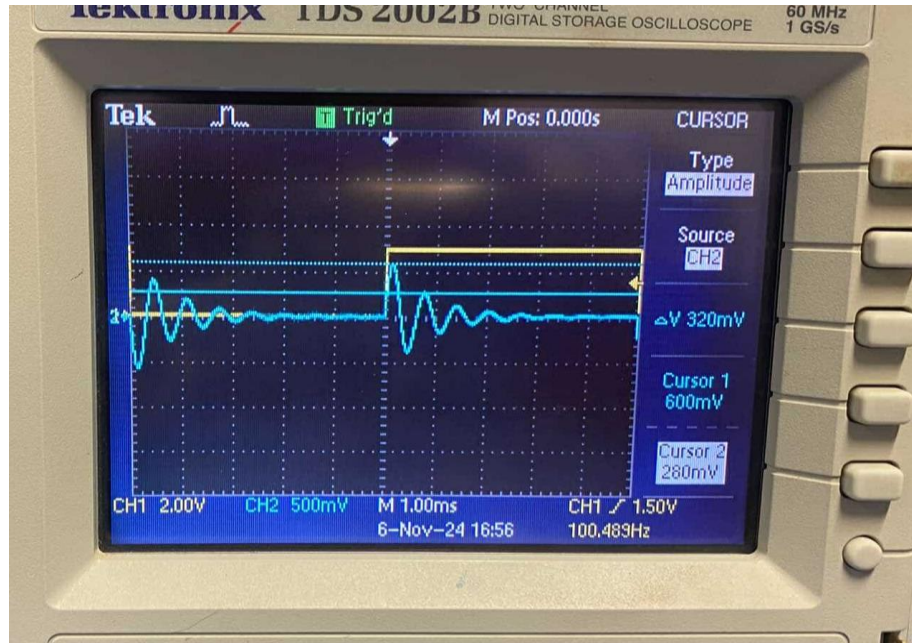


Figure 13: Underdamped response in detailed

Calculate decay-envelope time constant (τ), the damping coefficient (α), and damped frequency (ω_d):

Question #3

Malak Qasem
1210484

- Decay time constant $\tau = \frac{t_b - t_a}{\ln\left(\frac{V_a - V_o(\infty)}{V_b - V_o(\infty)}\right)}$

$$\tau = \frac{760 \times 10^{-6} - 40 \times 10^{-6}}{\ln\left(\frac{600 \times 10^{-3} - 0}{280 \times 10^{-3} - 0}\right)}$$

$$\therefore \tau = 9.447 \times 10^{-4} \text{ sec/rad}$$
- Damping coefficient $\alpha = \frac{1}{\tau} \Rightarrow \alpha = \frac{1}{9.447 \times 10^{-4}}$

$$\therefore \alpha = 1058.54 \text{ rad/sec}$$
- Damped frequency $\omega_d = \frac{2\pi}{t_b - t_a}$

$$\omega_d = \frac{2\pi}{760 \times 10^{-6} - 40 \times 10^{-6}}$$

$$\therefore \omega_d = 8.722.22 \text{ sec}^{-1}$$

Figure 14: Question #3

➤ **Case B: Critically damped response**

Calculating R_{cr} critical using this equation $R_{cr} = \sqrt{\frac{4L}{C}}$ after calculate it we get $R_{cr} = 500\Omega$



Figure 15: Critical response

➤ **Case C: Over damped response**

Set the variable resistor to 150Ω .

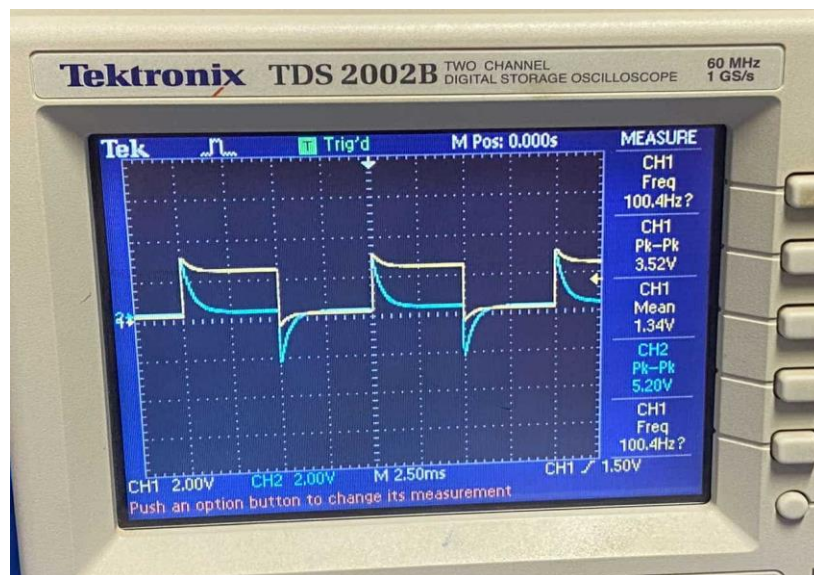


Figure 16: Overdamped response

The voltage (V_a) and time (t_a) at the greatest peak and the voltage (V_b) and time (t_b) at the lowest peak are measured in an underdamped response. The system's oscillatory nature is captured by these values. The voltage value $V(\infty)$ at which the system reaches equilibrium without varying, is measured in a Critical damped response.

V_a	t_a	V_b	t_b	$V(\infty)$
600mV	40 μ s	280mV	760 μ s	0V

Table 4: 7.2 Table

The critically damped response represents the circuit's quickest decay time without oscillating, while the overdamped response also avoids oscillation but decays at a slower rate.

Conclusion:

In conclusion the experiment provided clarity on the natural response of series and parallel RLC circuits, specifically analyzing the three damping cases: **overdamped**, **underdamped**, and **critical damped** responses. The practical analysis allowed for an understanding of the decay time constant, damping coefficient, and damped radian frequency, demonstrating how these factors influence the circuit's response. This Practical method helped clarify theoretical concepts by showing how damping conditions impact RLC circuit behavior and stability.

References:

-ENEE2101-Manual

-Data taken in the laboratory

Experiment 7 - Data Tables:

Part A: Step response of second-order Series RLC circuit

Case C: under damped response

$R_{\text{inductor}} [\Omega]$	0.22K 12.3 Ω
--------------------------------	--------------------------------

Table 7.1

V_a	t_a	V_b	t_b	$V(\infty)$
3.92V	300 μ s	3.04V	960 μ s	2.92V

Part B: Step response of second-order parallel RLC circuit

Case A: under damped response

$R_{\text{inductor}} [\Omega]$	6.9 Ω
--------------------------------	--------------

Mohammad
6/11/2024

Table 7.2

V_a	t_a	V_b	t_b	$V(\infty)$
600mV	400 μ s	280mV	760 μ s	0

Figure 17: Data sheet