

#### **FET Vs conventional Transistors**

#### **Advantages**

- 1- High input impedance ; 100 M  $\Omega$
- 2- fewer steps in manufacturing process.
- 3- more devices can be package into smaller area for integrated circuit IC

# **Disadvantages**

- 1- Low values of voltage gain.
- 2- Poor high frequency performance.









### **Junction Field Effect Transistor JFET**

#### **JFET construction:**

n-channel JFET



✓ If the channel width increases  $I_{DS}$  increases . STUDENTS-HUB.com

# Operation of a JFET



STUDENTS-HUB.com

#### JFET Circuit Symbol:

# 

# n-channel p-channel

STUDENTS-HUB.com

#### **JFET output characteristic:**





STUDENTS-HUB.com

# **JFET Characteristics: Pinch Off**

• If  $V_{GS} = 0$  V and  $V_{DS}$  continually increases to a more positive voltage, a point is reached where the depletion region gets so large that it pinches off the channel.

• This suggests that the current in channel ( $I_D$ ) drops to 0 A, but it does not: As  $V_{DS}$  increases, so does  $I_D$ . However, once pinch off occurs, further increases in  $V_{DS}$  do not cause  $I_D$  to increase.



#### Pinch of voltage V<sub>P</sub>:

For  $V_{GS} = 0$ , the value of  $V_{DS}$  at witch  $I_{DS}$  becomes essentially constant Is the absolute of the pinch of voltage



**JFET Transfer characteristic curve:** 

$$I_{DS}(\mathbf{t}) = I_{DSS} \left(1 - \frac{V_{GS}(t)}{V_P}\right)^2$$

In pinch off region:

 $V_P < V_{GS} \leq 0$ 

 $|V_{DS}| > |V_P| - |V_{GS}|$ 



STUDENTS-HUB.com

#### **P-channel JFET**

$$I_{DS}(\mathbf{t}) = I_{DSS} \left(1 - \frac{V_{GS}(t)}{V_P}\right)^2$$

In pinch off region:

$$|V_{DS}| > |V_P| - |V_{GS}|$$

 $V_P > V_{GS} \ge 0$ 



STUDENTS-HUB.com

# Summary

#### **Pinch off voltage:**

- ✓ The voltage that cusses the depletion region to touch and close the channel is called pinch off voltage
- ✓ For the n-channel JFET to be in the pinch off region:

 $V_P < V_{GS} \leq 0$ 

 $|V_{DS}| > |V_P| - |V_{GS}|$ 

✓ For the p-channel JFET to be in the pinch off region:

 $|V_{DS}| > |V_P| - |V_{GS}|$ 





# JFET Biasing Circuit

1) Fixed bias circuit

Find **Q**point

Since  $V_{GS}$  = -1.5 V , the JFET could be either in the ohmic or pinch off region



#### Assume that the JFET is in the pinch off region

$$\therefore I_{DS} = I_{DSS} (1 - \frac{V_{GS}}{V_P})^2$$

$$\boldsymbol{V}_{\boldsymbol{G}\boldsymbol{S}} = \boldsymbol{V}_{\boldsymbol{G}} - \boldsymbol{V}_{\boldsymbol{S}}$$

VGS = -1.5 - 0 = -1.5 V



∴ *I<sub>DS</sub>*= 3.9mA

STUDENTS-HUB.com



 $V_{DD} = R_D I_{DS} + V_{DS}$  $\therefore V_{DS} = 8.2 \vee$ 

For the JFET is in the pinch off region  $|V_{DS}| > |V_P| - |V_{GS}|$  > |-4| - |-1.5| $|V_{DS}| > 2.5 \vee$ 

since  $V_{DS} > 2.5 \text{ V}$ ;  $\therefore$  our assumption is ok



STUDENTS-HUB.com

2) Self – bias circuit

 Assume that the JFET is in the region

$$I_{DS} = I_{DSS} (1 - \frac{V_{GS}}{V_P})^2$$

$$V_{GS} = V_G - V_S$$

$$V_{GS}$$
= -(0.6K)  $I_{DS}$ 

STUDENTS-HUB.com







Sub 2 into 1

$$\therefore I_{DS} = 10 \times 10^{-3} (1 - \frac{-0.6 K I_{DS}}{-4})^{-2}$$

 $I_{DS} = 14.77 \text{ mA}, 3\text{mA}$ Since  $I_{DS} = 14.77\text{mA} > I_{DSS}$ 

$$\therefore I_{DS} = 3mA$$
$$V_{GS} = -1.8 V$$

 $V_{DD} = R_D I_{DS} + V_{DS} + R_S I_{DS}$  $V_{DS} = 8.7 V$ 



For the JFET to be in the pinch off

•  $|V_{DS}| > |V_P| - |V_{GS}|$ > |-4| - |-1.8|  $|V_{DS}| > 2.2 V$ 



 Since | V<sub>DS</sub> | > 2.2 V, the JFET is in the pinch off region and our

assumption is ok and

•  $I_{DS} = 3.0 \text{ mA}$  $V_{DS} = 8.7 \text{ V}$ STUDENTS HUB = 01.8 V



STUDENTS-HUB.com

*V<sub>DS</sub>*= -5.93 V

#### Metal Oxide Semiconductor Field Effect Transistor MOSFET

- 1) Depletion type MOSFET: DMOSFET
- 2) Enhancement type MOSFET: EMOSFET
- The MOSFET differs from the JFET in that it has no pn junction structure; instead, the gate of the MOSFET in insulated from the channel by a silicon dioxide ( $S_iO_2$ ) large.
- Due to this the input resistance of MOSFET is greater than JFET.

STUDENTS-HUB.com

## Depletion type MOSFET:

• Construction of n-channel DMOSFET:



STUDENTS-HUB.com

Operation, characteristic and parameters of DMOSFET



- On the application of  $V_{DS}$  and keeping  $V_{GS} = 0$  electrons from the n-channel are attracted towards positive potential of the drain terminal .
- This establishes current through the channel to be denotes as  $I_{DSS}$  at  $V_{GS} = 0$ .

STUDENTS-HUB.com



- The grater the negative voltage applied at the gate , the level of drain  $\mathcal{L}_{F}$  and  $\mathcal{L}$ 

- For positive value of  $V_{GS}$ , the positive gate will draw additional electrons from the ptype substrate and the drain current increases .





STUDENTS-HUB.com

#### Drain characteristics for an n-channel DMOSFET



# Transfer characteristics for an n-channel DMOSFET



STUDENTS-HUB.com

# Transfer characteristics for an p-channel DMOSFET



# In the pinch off region

$$i_{DS}(t) = I_{DSS} (1 - \frac{V_{GS}}{V_P})^2$$

#### ♦ For the n- channel

 $V_{GS} > V_P$ (negative)  $V_{DS} > V_{GS} - V_P$ 

For the p- channel

 $V_{GS} < V_P$  (positive)  $V_{DS} < V_{GS} - V_P$ STUDENTS-HUB.com

# Example

Suppose that the DMOSFET is in the pinch off region

$$I_{DS} = I_{DSS} (1 - \frac{V_{GS}}{V_P})^2 \dots 1$$

$$V_{GS} = V_G - V_S = V_G$$

$$V_G = \frac{11M}{11M + 100M}$$
 (12) = 1.19 V .....<sup>2</sup>  
sub 2 into 1 we obtain

 $I_{DS} = 6.13 \text{mA} > I_{DSS}$  !!

$$V_{DS} = V_{DD}$$
- 0.5K  $I_{DS} = 8.93$  V  
 $V_{DS} >^{?} V_{GS} - V_{P} = 6.19$  V  
STUDENTS-HUB.com



+12 V



# Enhancement type MOSFET

• Construction of n-channel EMOSFET:



STUDENTS-HUB.com



Construction of n-channel DMOSFET

Construction of n-channel EMOSFET

STUDENTS-HUB.com

# Operation , characteristic and parameters of EMOSFET

- On the application of  $V_{DS}$  and keeping  $V_{GS}$ =0 practically zero current flows .
- If we increase  $V_{GS}$  in the positive direction the concentration of electrons near the SiO<sub>2</sub> surface increases ,
- At particular value of  $V_{GS}$  there is a measurable current flow between drain and source ;  $I_{DS}$ .
- This value of  $V_{GS}$  is called threshold voltage denoted by  $V_T$
- A positive  $V_{GS}$  above  $V_T$  induce a channel and hence the drain current  $(I_{DS})$  by creating a thin layer of negative charges (electrons) in the substrait adjacent to the Si $O_2$  large.

STUDENTS-HUB.com

The conductivity of the channel is enhanced by increasing  $V_{GS}$  and thus pulling more electrons into the channel .



STUDENTS-HUB.com

# Drain characteristics for an n-channel EMOSFET



STUDENTS-HUB.com

# Transfer characteristics for an n-channel EMOSFET $I_{DS}(t)$ $V_T$ $V_{GS}(t)$ Uploaded By: anonymous STUDENTS-HUB.com
#### Drain characteristics for an p-channel EMOSFET



#### Transfer characteristics for an p-channel EMOSFET



#### In the pinch off region

$$i_{DS}(t) = K_n (V_{GS}(t) - V_T)^2$$

$$K_n = \frac{1}{2} K n \frac{W}{L}$$

$$K_n = \mu_n C_{ox}$$



$$|V_{DS}| > |V_{GS} - V_T|$$

$$V_{GS} > V_T$$
 ; n- channel  
 $V_{GS} < V_T$  ; p- channel

Uploaded By: anonymous

STUDENTS-HUB.com



STUDENTS-HUB.com

$$V_{S}$$
 = (0.5K)  $I_{DS}$ 

 $V_{GS} = 5.74 - (0.5 \text{K}) I_{DS}$ .....2

solving for *V<sub>GS</sub>*:

$$V_{GS} = 4.78V \quad \sqrt{}$$
  
= -8.78V X

 $I_{DS} = 1.92 \,\mathrm{mA}$ 

**STUDENTS-HUB.com** 

$$R_{1} \xrightarrow{47 \text{ M}} 2.2 \text{ k}$$

$$R_{2} \xrightarrow{22 \text{ M}} 5$$

$$R_{2} \xrightarrow{100}{3} \text{ M}$$

$$V_{DS} = 12.82 > |V_{GS} - V_T|$$

# Complementary MOS (cmos) inverter **1)** Let $V_{S}(t) = 10 V$ $V_{GS1} = V_{G1} - V_{S1} = 10 - 0 = 10 \text{ V} > V_{T1}$ $Q_1$ is on , replaced with short circuit +10V $V_{GS2} = V_{G2} - V_{S2} = 10 - 10 = 0 \text{ V} > V_{T2}$ **Q**<sub>z</sub> is eff, seplaced with open circuit



2) Let 
$$V_{S}(t) = 0 V$$

 $V_{GS1} = V_{G1} - V_{S1} = 0 = 0 V < V_{T1}$ 

 $Q_1$  is off , replaced with open circuit



$$V_{GS2} = V_{G2} - V_{S2} = 0.10 = -10 \text{ V} < V_{T2}$$

**Q**<sub>2</sub> is on , replaced with short circuit STUDENTS-HUB.com



STUDENTS-HUB.com

#### Ac small signal Equivalent for FET



STUDENTS-HUB.com

$$i_{g} = y_{11}v_{gs} + y_{12}v_{ds}$$
$$i_{ds} = y_{21}v_{gs} + y_{22}v_{ds}$$

$$y_{11} = \frac{i_g}{v_{gs}} |_{v_{ds=0}} = \frac{\Delta i_{G(t)}}{\Delta V_{GS(t)}} |_{V_{DS(t)}=V_{DSQ}}$$

$$i_{g}$$
 +  $v_{ds}$  -  $v_{gs}$  -

But 
$$i_{G(t)} = 0$$
  
STUDENTS-HUB.com

$$\therefore y_{11} = 0$$

#### (open circuit)

$$y_{12} = \frac{i_g}{v_{ds}} |_{v_{gs=0}} = \frac{\Delta i_{G(t)}}{\Delta V_{DS(t)}} |_{v_{GS(t)}=v_{GSQ}}$$
  
But  $i_{G(t)}=0$   
 $\therefore y_{12}=0$   
 $\therefore y_{12}v_{gs}=0$  (open circuit )

(open circuit )

STUDENTS-HUB.com



 $y_{21} = g_m$ ; Forward Trans conductance

STUDENTS-HUB.com

### 1) For JFET and DMOSFET

$$i_{DS}(t) = I_{DSS}(1 - \frac{V_{GS}(t)}{V_P})^2$$

$$g_{m} = \frac{-2I_{DSS}}{V_{p}} \left(1 - \frac{V_{GS}(t)}{V_{p}}\right) |_{Q}$$

$$g_m = \frac{-2I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p}\right)$$
STUDENTS-HUB.com

### 2) For EMOSFET

$$i_{DS} = K_n (V_{GS}(t) - V_T)^2$$

$$g_m = 2K_n(V_{GS} - V_T)$$

$$g_m = 2 \sqrt{K_n I_{DS}}$$
 proof !!

STUDENTS-HUB.com



#### ac small signal equivalent circuit of JFET



STUDENTS-HUB.com

### ac small signal equivalent circuit for MOSFET



Uploaded By: anonymous

STUDENTS-HUB.com

#### STUDENTS-HUB.com

#### FET Ac Small Signal Amplifiers

#### 1) Common Source Amplifier

$$g_m = \frac{-2I_{DSS}}{V_p} \left(1 - \frac{V_{GS}}{V_p}\right)$$
$$V_{GS} = -2v$$







STUDENTS-HUB.com

#### ac small signal equivalent circuit



#### **Impedance Reflection**

ac small signal equivalent circuit





let 
$$g_m r_{ds} = \mu$$

$$i_{ds} = \frac{v_3 + \mu v_{gs} - v_2}{R_d + R_s + r_{ds}}$$

$$v_{gs} = v_g - v_s$$

$$v_s = R_s i_{ds} + v_2$$

:. 
$$i_{ds} = \frac{\mu v_g + v_3 - (\mu + 1)v_2}{r_{ds} + R_d + (\mu + 1)R_s}$$





Uploaded By: anonymous

STUDENTS-HUB.com

### Drain equivalent circuit

$$i_{ds} = \frac{\mu v_g + v_3 - (\mu + 1)v_2}{r_{ds} + R_d + (\mu + 1)R_s}$$





Source equivalent circuit



### **Phase splitting circuit**

ac small signal equivalent circuit





To find 
$$v_{o1}$$
, and  $Z_{o1}$   
 $\rightarrow$  drain equivalent CKT  
 $v_{o1} = -\frac{R_d \mu v_g}{r_{ds} + R_d + (\mu + 1)R_s}$   
 $v_g = \frac{R_1 || R_2}{R_1 || R_2 + R_i} v_i$   
 $\therefore v_{o1} = -\frac{R_1 || R_2}{R_1 || R_2 + R_i} \cdot \frac{R_d \mu}{r_{ds} + R_d + (\mu + 1)R_s} v_i$   
 $Z_{o1} = R_d || (r_{ds} + (\mu + 1)R_s)$   
if  $r_{ds} = \infty$   
 $\therefore Z_{o1} = R_d$   
STUDENTS-HUB.com



#### To find $V_{o2}$ , and $Z_{o2}$ $\rightarrow$ source equivalent CKT

 $v_{o1}$ 

$$\boldsymbol{v_{o2}} = \frac{R_s \left(\frac{\mu}{\mu+1}\right) \boldsymbol{v_g}}{R_s + \frac{r_{ds} + R_d}{\mu+1}}$$

$$v_g = \frac{R_1 || R_2}{R_1 || R_2 + R_i} v_i$$

$$v_{o2} = \frac{R_1 || R_2}{R_1 || R_2 + R_i} \cdot \frac{R_s \left(\frac{\mu}{\mu + 1}\right) v_g}{R_s + \frac{r_{ds} + R_d}{\mu + 1}}$$

STUDENTS-HUB.com

$$Z_{o2} = R_{s} || \frac{R_{d} + r_{ds}}{\mu + 1}$$
  
If  $r_{ds} = \infty$   

$$\frac{R_{d} + r_{ds}}{\mu + 1} = \frac{R_{d} + r_{ds}}{g_{m}r_{ds} + 1}$$
  

$$\lim_{r_{ds} \to \infty} \frac{R_{d} + r_{ds}}{g_{m}r_{ds} + 1} = \frac{1}{g_{m}}$$
  

$$\therefore ||f || r_{ds} = \infty$$
  

$$Z_{o2} = ||R_{s}|| \frac{1}{g_{m}}$$
  
STUDENTS-HUB.com

### **Common Gate Amplifier**



Ac small signal equivalent circuit





STUDENTS-HUB.com

To find 
$$v_o$$
, and  $Z_o$ 

drain equivalent CKT

$$v_o = \frac{(10k || 10k)(\mu+1)\frac{1}{2}}{10k || 10k+r_{ds} + (\mu+1)*5k} v_i$$

$$Z_o = 10 \mathrm{K} \parallel [r_{ds} + (\mu + 1)5k]$$



STUDENTS-HUB.com

To find  $Z_i \rightarrow$  source equivalent CKT



 $Z_i = 10k || \frac{r_{ds} + 10k || 10k}{\mu + 1}$ 

STUDENTS-HUB.com

## **Common Source Amplifier : Design**

• Design a Common source MOSFET Amplifier to provide a voltage gain  $\left|\frac{V_o}{Vi}\right| = 10$ , between a small signal voltage source having a resistance  $10k\Omega$  and load  $R_L = 10k$ 

and  $Zi = 1M\Omega$ .

The MOSFET has rds = 20k , VT = 1.419 V , Kn =  $\frac{2 mA}{V^2}$  , and IDS = 5mA. Assume VDD = 24V.

STUDENTS-HUB.com

# **Solution**

Ac small signal equivalent circuit





$$v_{0} = -g_{m}v_{gs}(R_{D} \parallel r_{ds} \parallel 10K)$$

$$v_{gs} = v_{g} - v_{s}$$

$$v_{g} = \frac{R1/R2}{R1/R2 + Ri} V_{i} = \frac{Z_{i}}{Z_{i} + Ri} V_{i} = \frac{1000k}{1000k + 10k} V_{i}$$

$$v_{g} \cong V_{i} \qquad v_{s} = 0 \qquad \therefore A_{v} = -g_{m}(R_{D} \parallel 20K \setminus 10K)$$
Uploaded By: anonymous

$$\therefore A_{v} = -g_{m} (R_{D} \setminus 20K \setminus 10K)$$
Using  $gm = 2\sqrt{Kn IDS}$  gm = 6.23 $m$ ()  
For Av = -10 RD = 2.1K $\Omega$  VDS = 8.7V Pinch off region  
DC Analysis  
Let VS = VDD/5 = 4.8V RS = 0.96K  $\Omega$   
But  $I_{DS} = K_{n}(V_{GS} - V_{T})^{2}$   
For  $I_{DS} = 5mA$   $\therefore$  VGS = 3V  
 $V_{GS} = V_{G} - V_{S}$  Solving for R1 and R2, we get  
 $\therefore$  VG = 7.8V R1 = 3.1M  $\Omega$   
NOW R2 = 1.48M  $\Omega$   
 $V_{G} = \frac{R2}{R2+R1}(24) = 7.8V$   
 $Z_{i} = R1 \setminus R2 = 1M \Omega$  Uploaded By: anonymous





#### STUDENTS-HUB.com