


L4 - Part 2
13/7/2021

ENEE236

Analog Electronics

T3:

Diode Applications

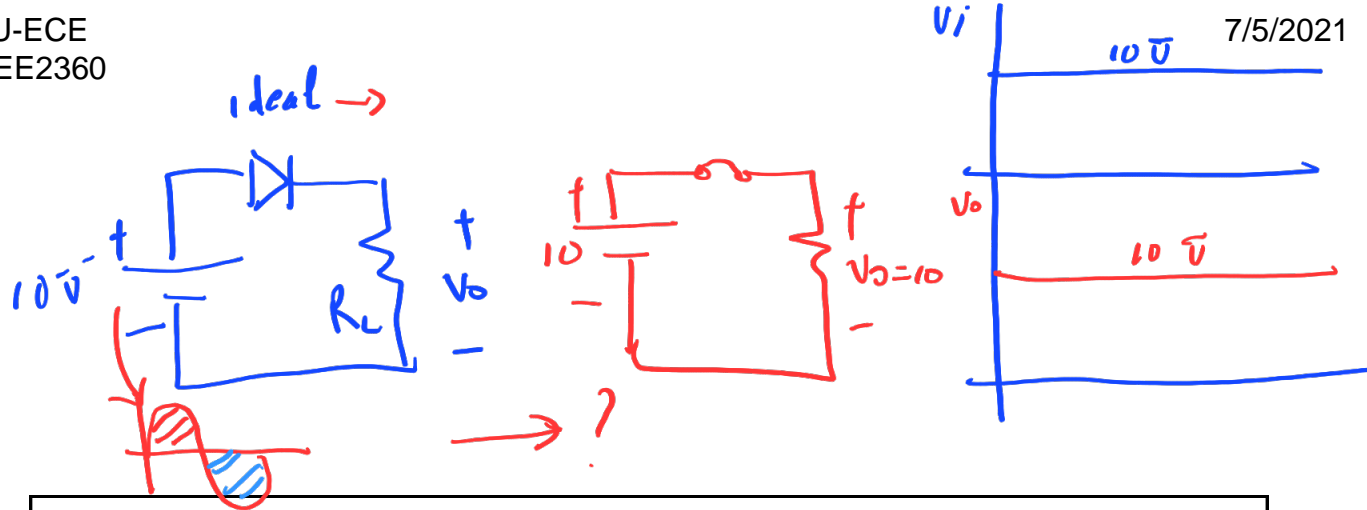

Diode large – signal application

1) Diode clipper circuit \equiv Limiter

a) assume the diode is on
replace it with short circuit


$$i_D(t) > 0$$

$$i_D(t) = \frac{V_i(t)}{R_L} > 0 \quad \checkmark$$


$$\therefore V_i(t) > 0$$

? always positive

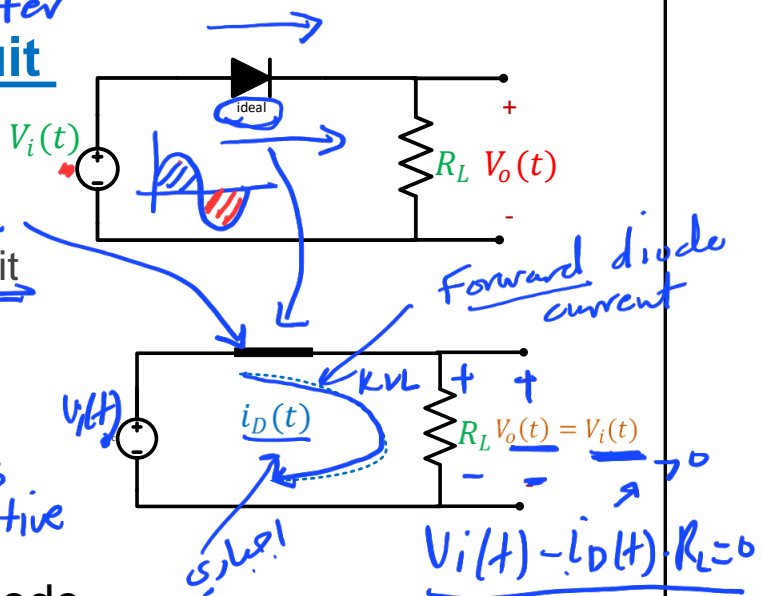\therefore when $V_i(t) > 0$, the diode is on and $V_o(t) = V_i(t)$





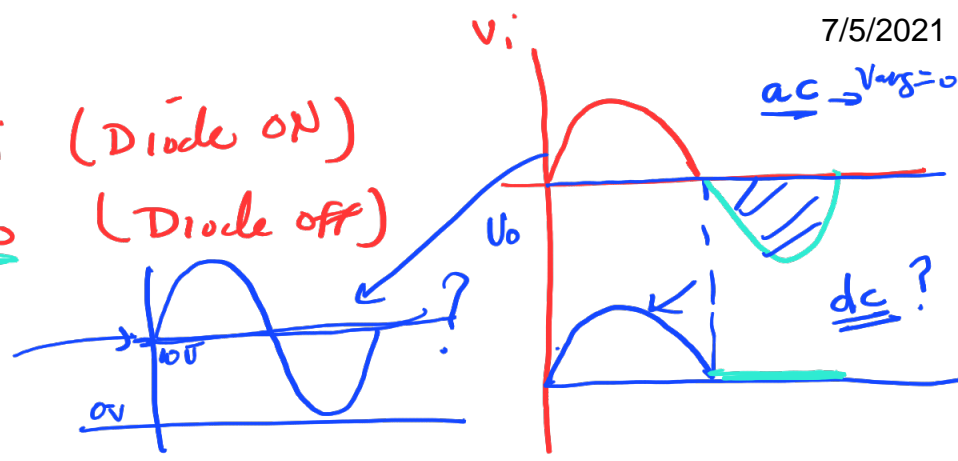$V_i(t) > 0 \rightarrow V_o = V_i$ (Diode ON)
 $V_i(t) < 0 \rightarrow V_o = 0$ (Diode OFF)



\therefore when $V_i(t) < 0$, the diode is off and $V_o(t) = 0$. $= i_D \cdot R_L$

$V_o(t) = 0$.

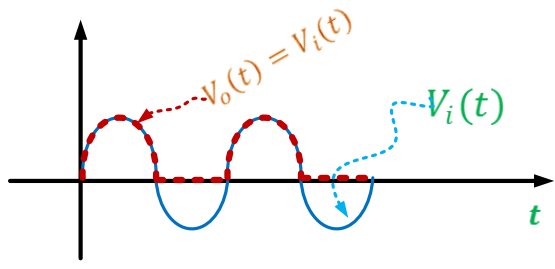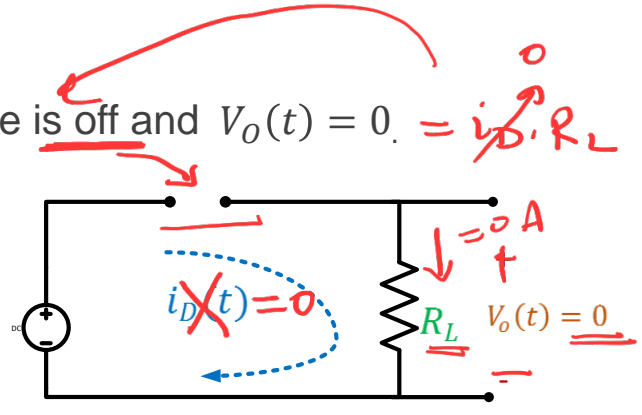




\therefore the clipper circuit used to eliminate portion of the input signal .

Example

a) assume that the diode is on

→ replace it with short circuit

$i_D > 0$

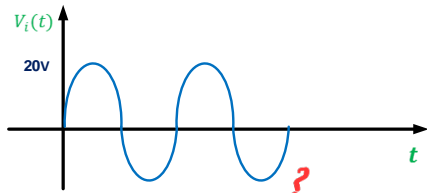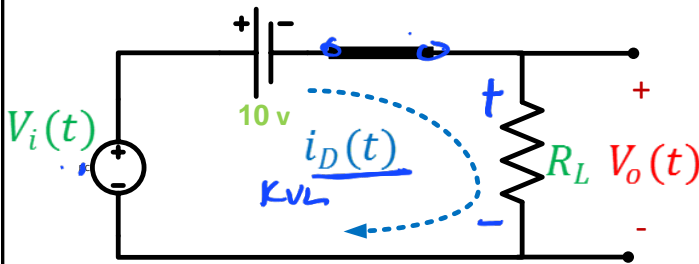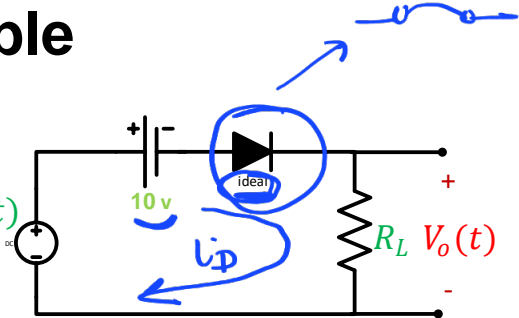

$$i_D(t) = \frac{V_i(t) - 10}{R_L} \geq 0$$

$$V_i(t) - 10 - i_D(t) \cdot R_L = 0$$

$$V_o(t) \leftarrow$$

$V_i - 10 > 0$ } → Diode ON
 $V_i > 10$ } → $V_o = V_i(t) - 10$

$$i_D(t) = \frac{V_i(t) - 10}{R_L} > 0$$



$$\therefore V_i(t) - 10 > 0$$

$$\therefore V_i(t) > 10$$


\therefore when $V_i(t) > 10\text{ V}$, the diode is on and $V_o(t) = V_i - 10$

and also we can prove that when $V_i(t) < 10\text{ V}$, the diode is off




$$\therefore V_o(t) = 0$$

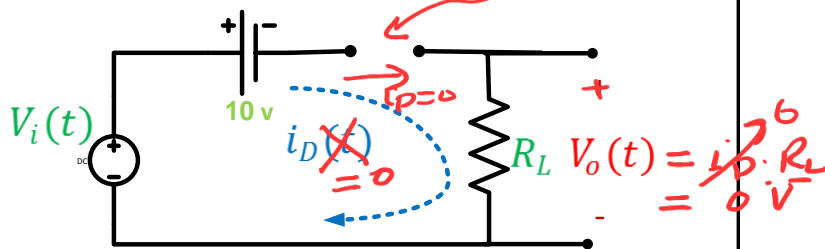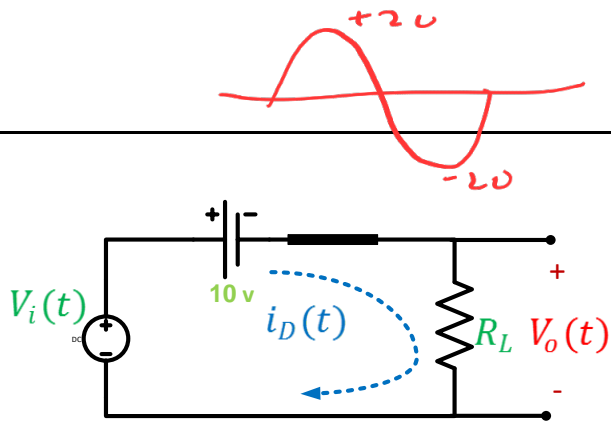

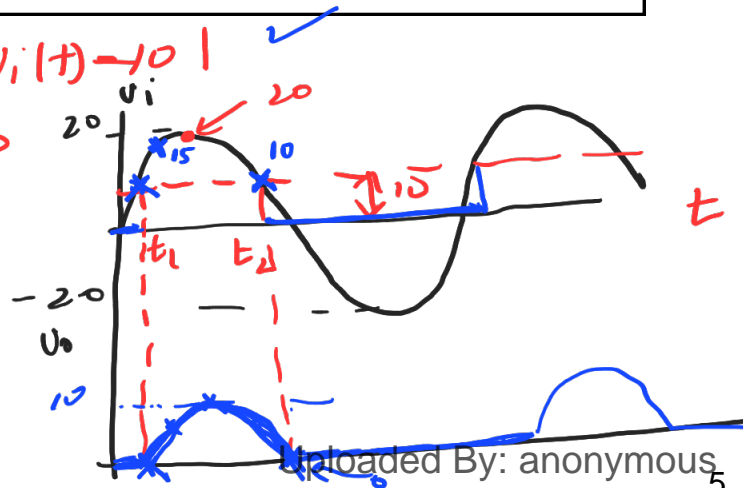$V_i(t) > 10$ Diode ON $\rightarrow V_o = V_i(t) - 10$ ✓
 $V_i(t) < 10$ Diode OFF $\rightarrow V_o = 0$



The output

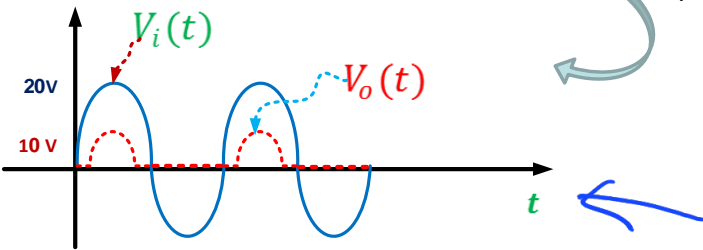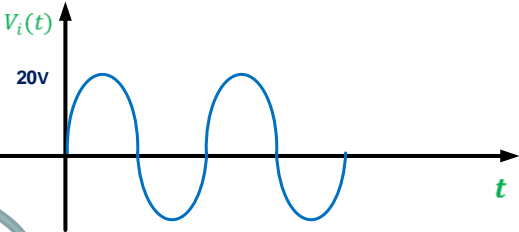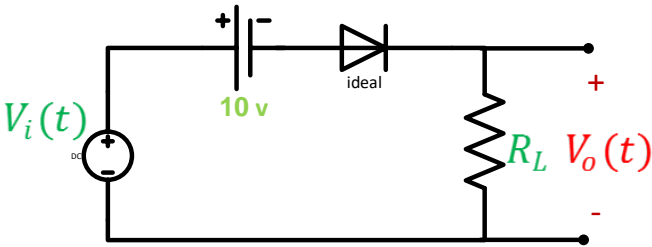


Second Method

assume that the diode is off, replace it with open circuit

$$V_D(t) < 0$$

$$V_D(t) = -10 + V_i$$

$$V_i(t) < 10 \text{ V}$$

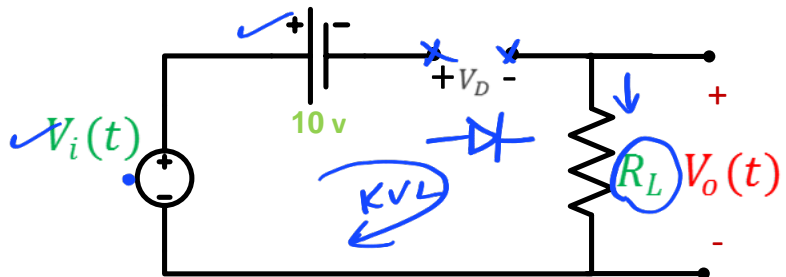

$$V_i - 10 - V_D = 0$$

$$V_D = V_i - 10$$

\therefore when $V_i(t) < 10 \text{ V}$, the diode is off and $V_o(t) = 0$

$$V_i > 10$$

, " ON



$$V_o = V_i - 10$$

← see previous solution

ENEE236 – Analog Electronics


Limiters (=Clipping circuits) (1)

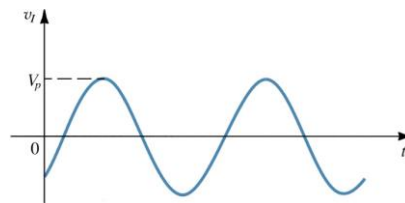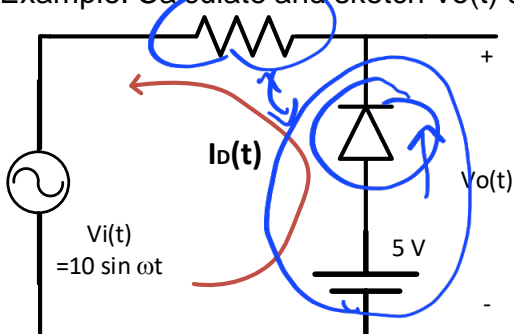Example: Calculate and sketch $V_o(t)$ using simplified diode model



$$5 = 0.7 + i_D R + V_i(t)$$

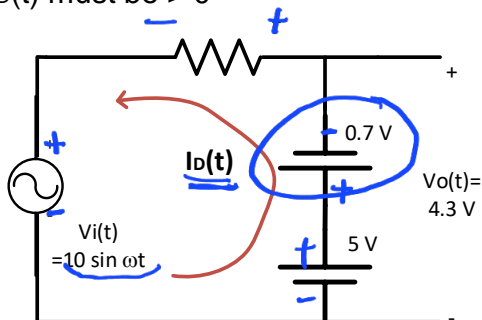1) Assume diode is ON, so we replace it by 0.7 V and $i_D(t)$ must be > 0




$$5V - 0.7V - i_D(t) \cdot R - V_i(t) = 0$$

$$i_D(t) \cdot R = 4.3V - V_i(t)$$

$$i_D(t) = \frac{4.3V - V_i(t)}{R} > 0$$

ENEE236 – Analog Electronics


Limiters (=Clipping circuits) (2)

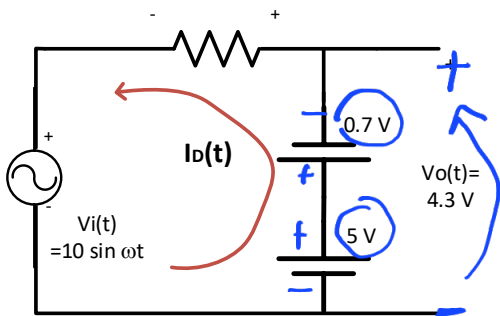

$\therefore 4.3\text{V} - V_i(t) > 0$
 $\Rightarrow V_i(t) < 4.3\text{V}$


when $V_i(t) < 4.3\text{ V}$ diode is ON and
 $V_o(t) = 4.3\text{V}$

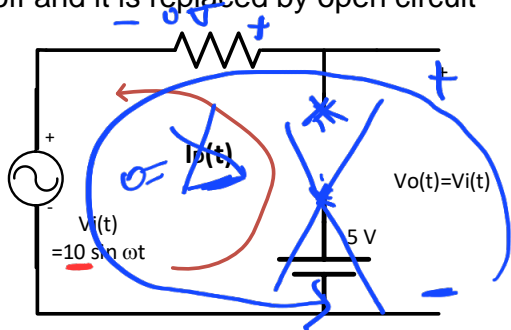2) Otherwise, When $V_i(t)$ is $> 4.3\text{ V}$, Diode will be off and it is replaced by open circuit



$\Rightarrow V_i(t) > 4.3\text{V}$
 $V_o(t) = V_i(t)$

$V_o(t) - V_i(t) = 0$
 $V_o(t) = V_i(t)$

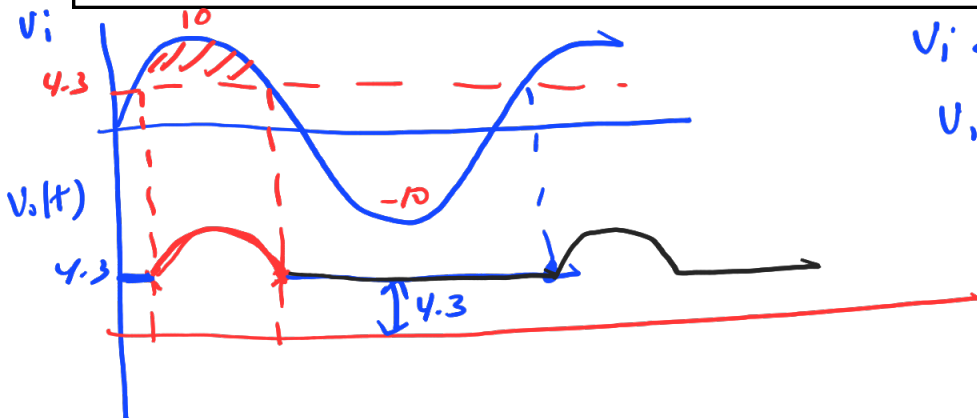


$V_i < 4.3 \rightarrow V_o = 4.3$
 $V_i > 4.3 \rightarrow V_o = V_i$

ENEE236 – Analog Electronics

Limiters (=Clipping circuits) (3)

when $V_i(t) < 4.3V$, diode is ON & $V_o(t) = 4.3V$

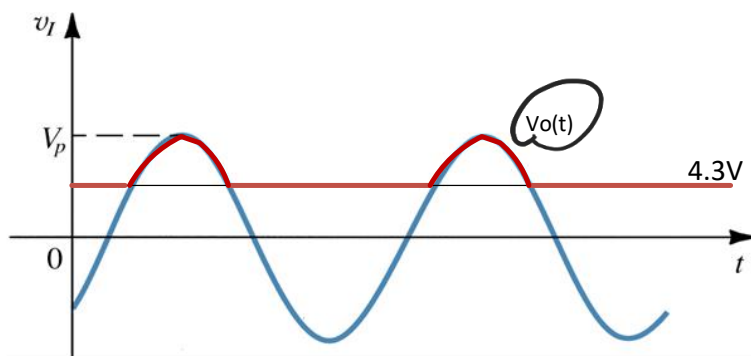when $V_i(t) > 4.3V$, diode is off & $V_o(t) = V_i(t)$





Summary

sketch

ENEE236 – Analog Electronics

Circuit Containing Two diodes

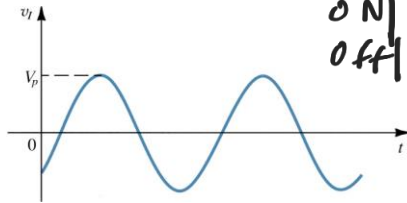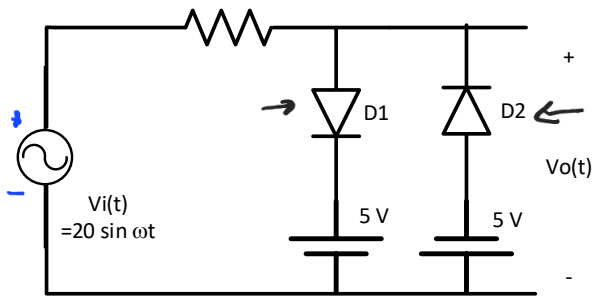Example: Calculate and sketch $V_o(t)$ using ideal diode model



D1	D2
ON	OFF
OFF	ON
ON	ON
OFF	OFF

Since the circuit contains two diodes, each of them can be either On or Off,
→ then there is 4 possible combinations for the states of D1 and D2


ENEE236 – Analog Electronics

- 1) Assume D1 is ON and D2 is OFF

$$i_{D1}(t) > 0$$

$$i_{D1}(t) = \frac{V_i(t) - 5}{R} > 0$$

when $V_i(t) > 5\text{ V}$, $V_o(t) = 5\text{ V}$

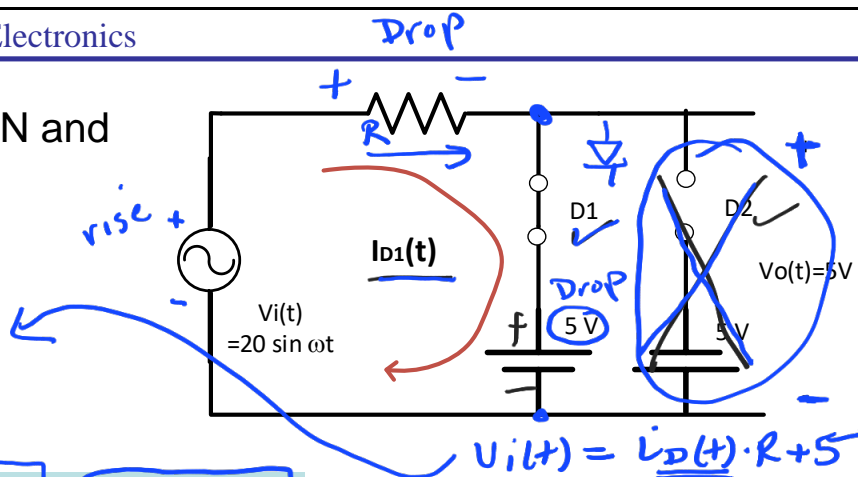


ENEE236 – Analog Electronics


2) Assume D2 is ON and D1 is OFF

$$i_{D2}(t) > 0$$

$$i_{D2}(t) = \frac{-V_i(t) - 5}{R} > 0$$

when $V_i(t) < -5V$, $V_o(t) = -5V$ ✓

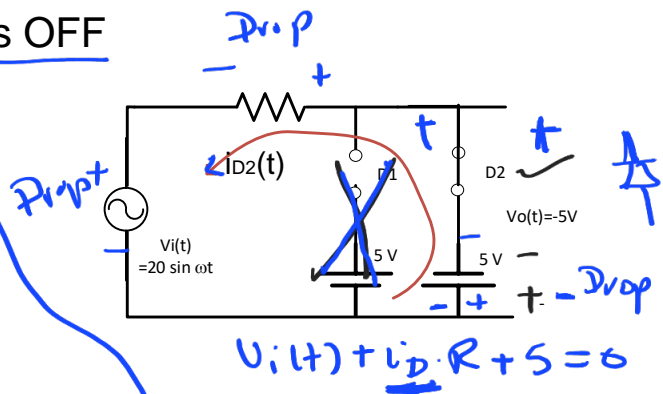

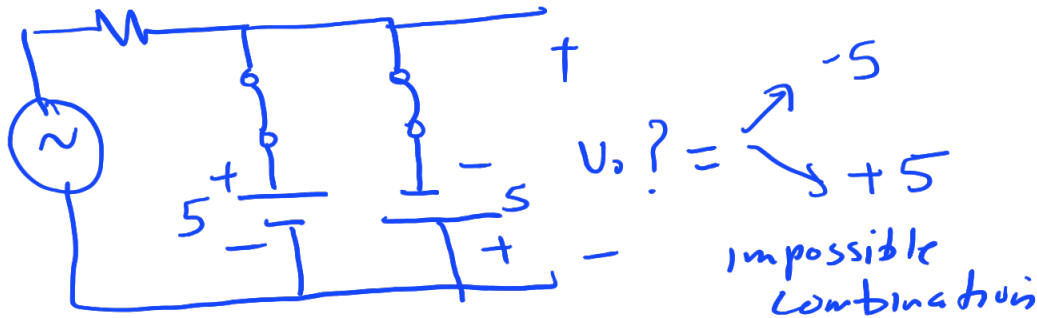


ENEE236 – Analog Electronics

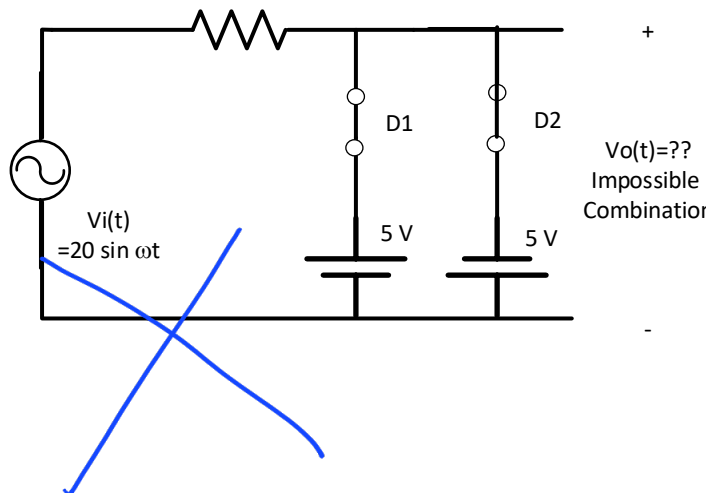3) Assume D1 & D2 are ON

$V_o = +5V$??
 $V_o = -5V$??





This is invalid configuration and impossible to occur



$V_i > 5 \rightarrow V_o = 5$
 $V_i < -5 \rightarrow V_o = -5$

$-5 < V_i < 5$?

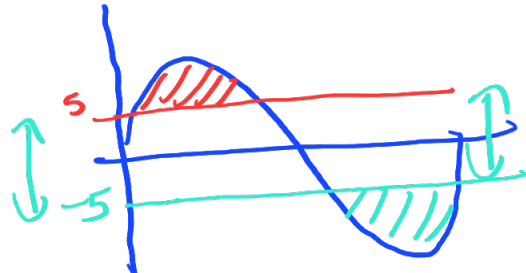


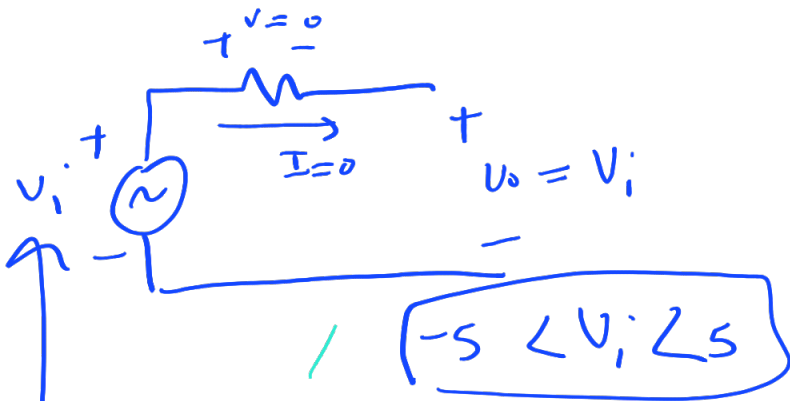

ENEE236 – Analog Electronics


4) Assume D1 & D2 are both OFF

$V_o(t) = V_i(t)$

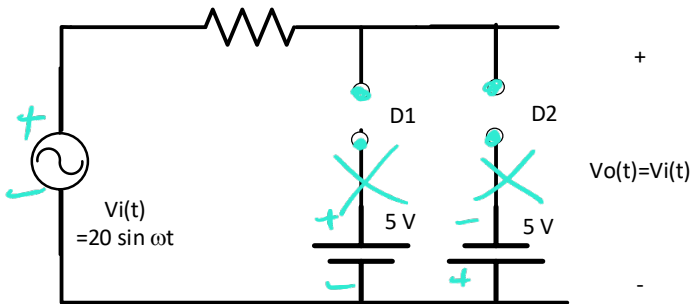



This occurs for the remaining part of the input voltage waveform:

$-5V < V_i(t) < 5V$

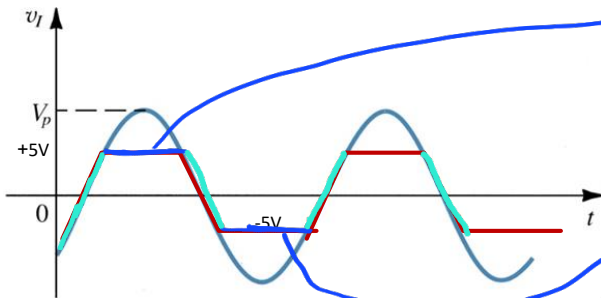

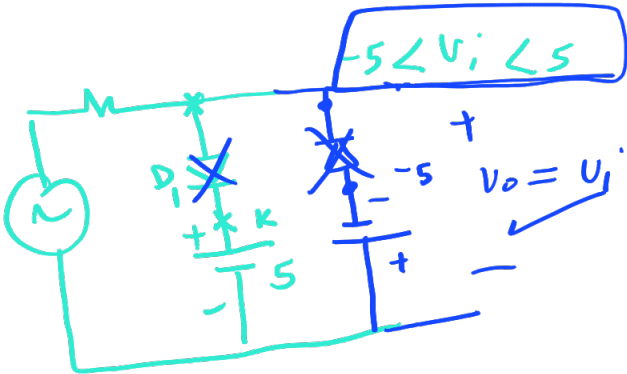
$V_o = 5, V_i > 5$
 $V_o = -5, V_i < -5$
 $V_o = V_i, -5 < V_i < 5$



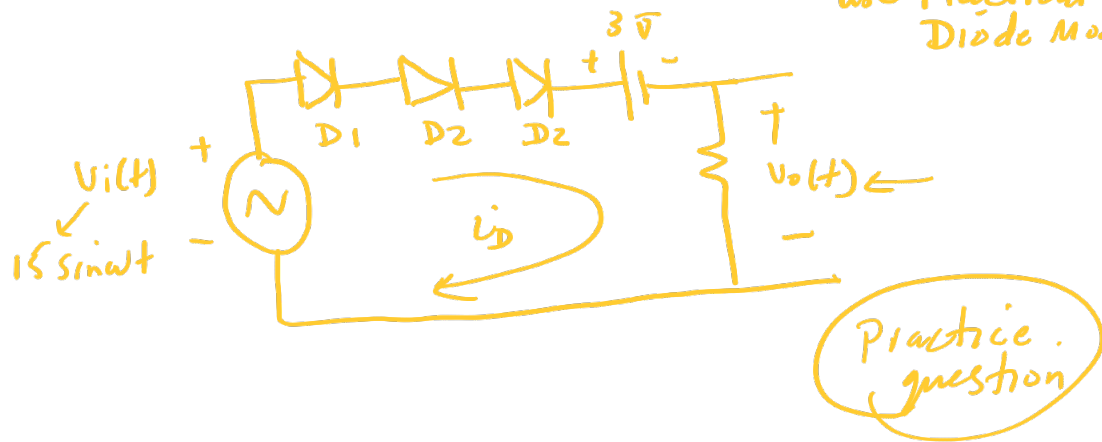


Summary of Clipper Circuits


HW for Practice

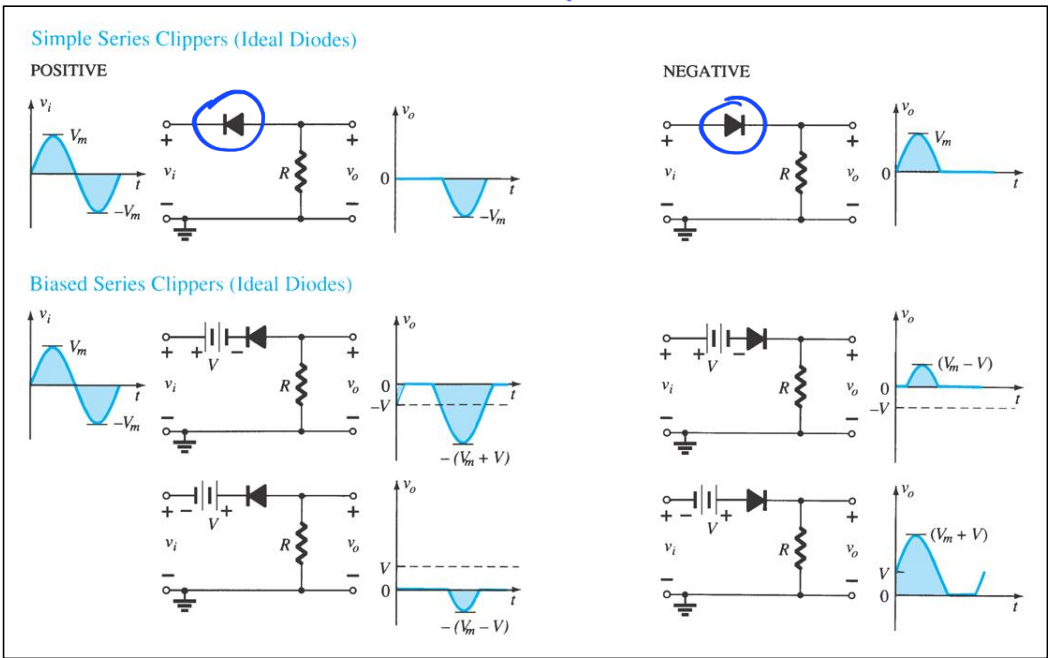

Summary of Clipper Circuits

HW for Practice

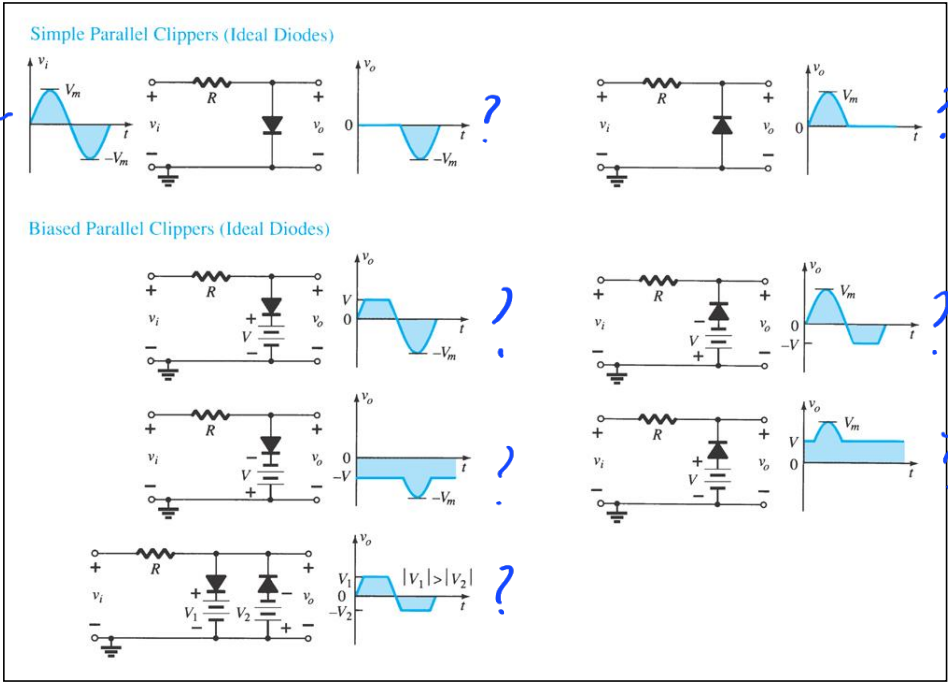

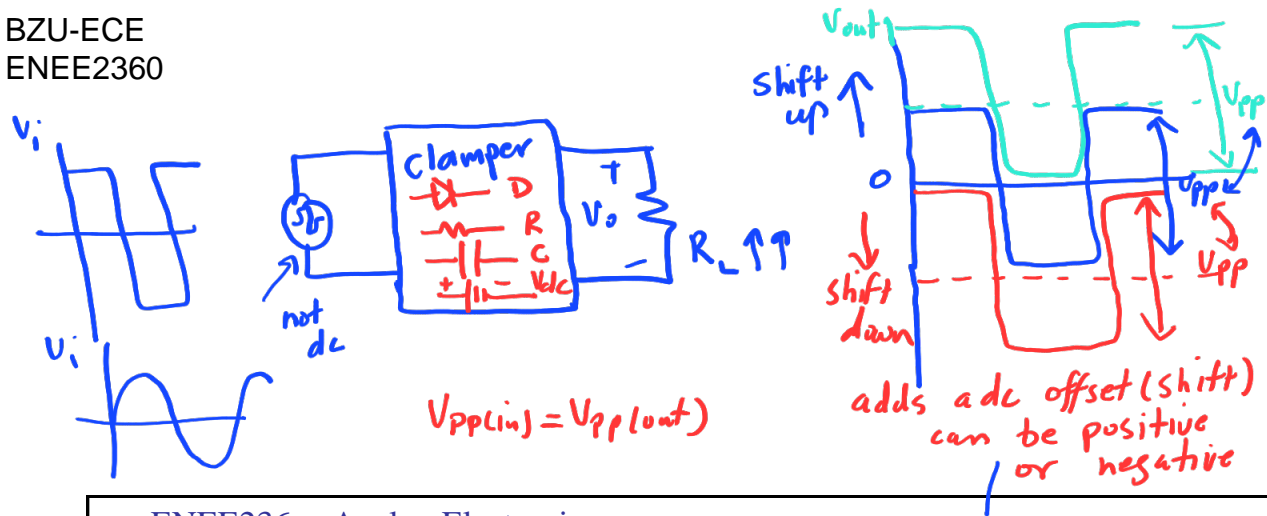



ENEE236 – Analog Electronics

Clampers

Function: A Clamper shifts the input waveform up or down (adds a dc offset) while keeping its shape and peak to peak value unchanged.

It consists of a diode and capacitor (and maybe a series dc source) that can be combined to “clamp” an AC signal to a specific DC level and supply it to the load R

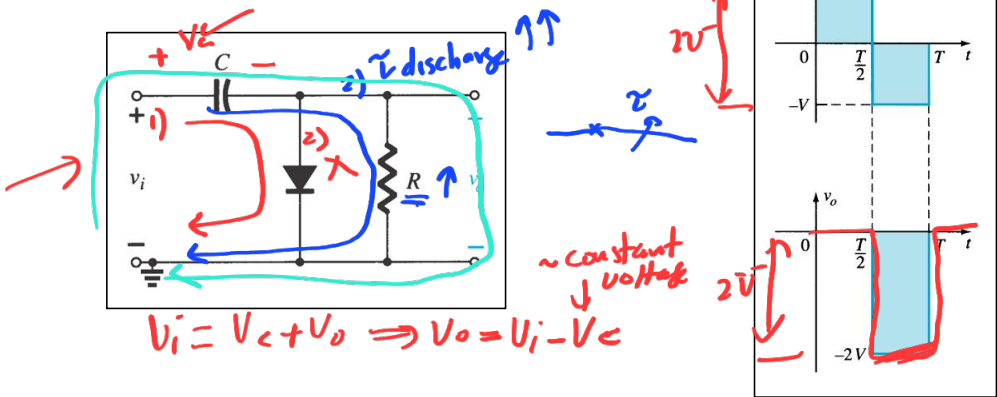


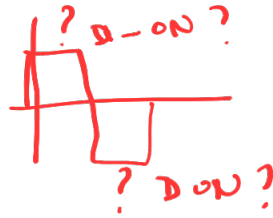

ENEE236 – Analog Electronics

Steps for Clamper Circuit Analysis



- ** 1) Start analysis by examining the portion of input that will forward bias the diode**
- 2) During diode On period, assume that the cap is charged instantaneously to a voltage level defined by surrounding network**
- 3) During OFF period, assume the cap holds the established voltage level (i.e. it behaves as constant dc voltage source)**
- 4) Consider value and polarity of V_o ←**
- * 5) Check that total swing (peak to peak) of output equal swing of input.**

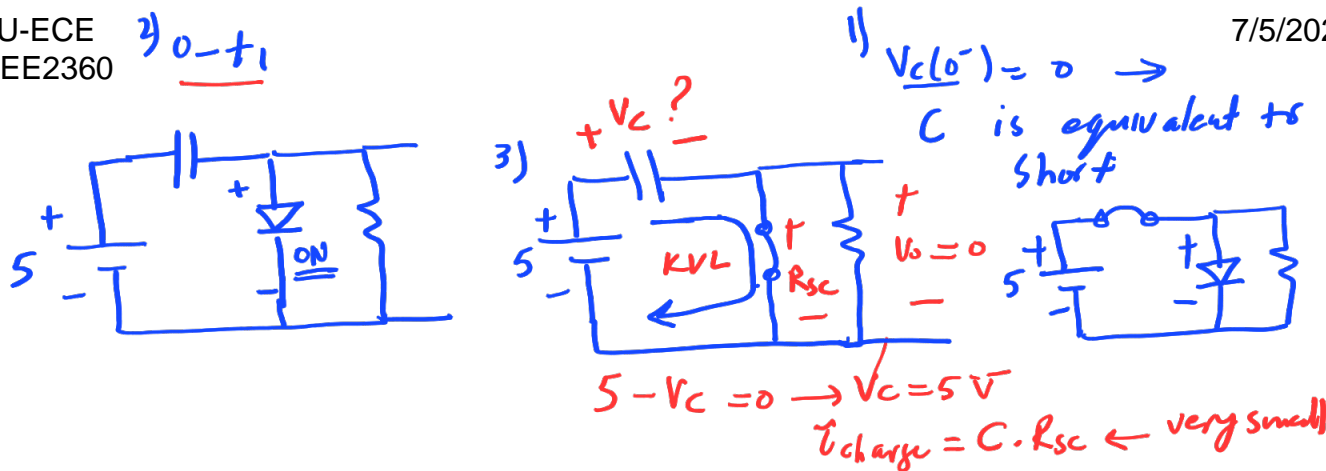

ENEE236 – Analog Electronics

Example

Find and sketch $V_o(t)$?

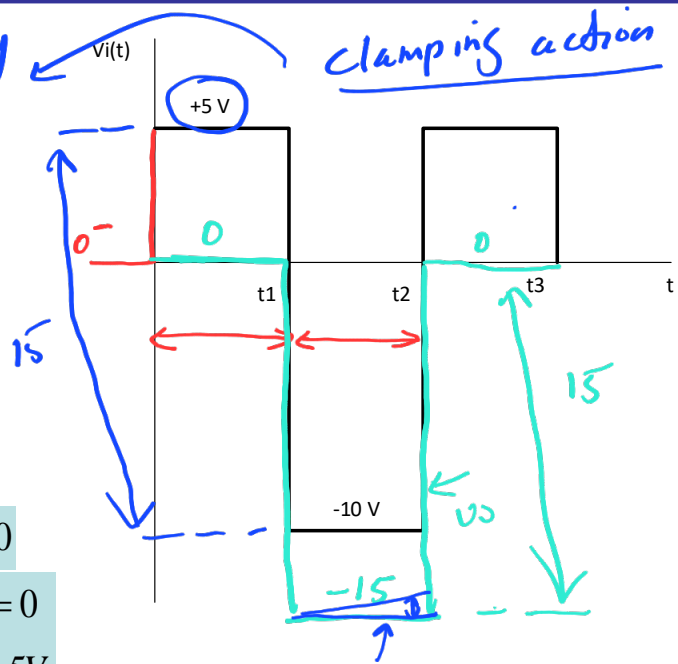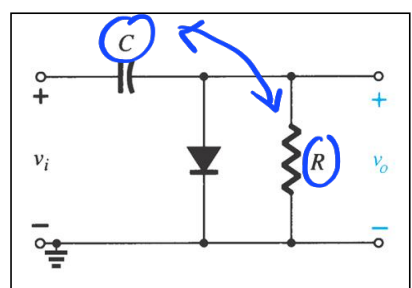


- 1) For $t < 0$ ($t = 0^-$) $V_C(0^-) = 0$
- 2) For $t > 0$ ($t = 0^+$) $V_C(0^+) = 0$
 $V_i(0^+) = 5V$
- $\Rightarrow D1$ is ON and it is replaced by short circuit
- 3) for $0^+ < t < t_1$ equivalent circuit is \Rightarrow see next page



4) $t_1 \rightarrow t_2 \rightarrow V_i = -10, V_C = 5V, \text{ Diode ?}$



$10 + 5 + V_D = 0$
 $V_D = -15 < 0 \rightarrow D$ is off

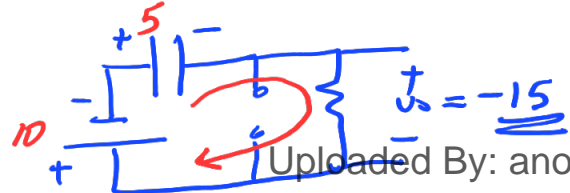


ENEE236 – Analog Electronics

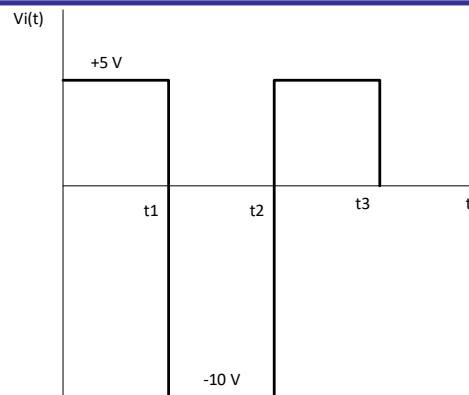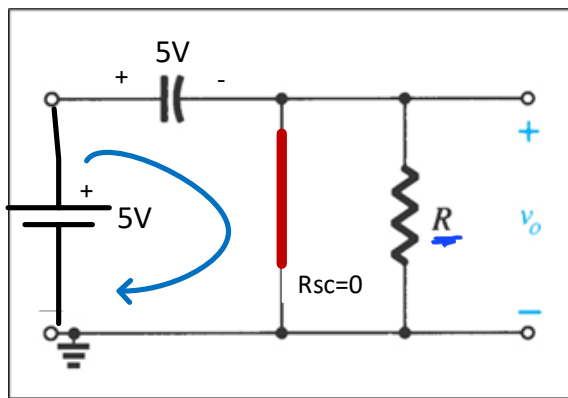


$\Rightarrow D1$ is ON, Cap charges instantously to +5V with shown polarity
since $\tau_{\text{charge}} = R_{sc} \cdot C \cong 0$ and $V_o(t) = 0 \text{ V}$ ✓

4) for $t_1 < t < t_2$ voltage source reverses polarity, $V_i(t) = -10\text{V}$
while Cap keeps its charge $V_c = 5\text{V}$ since $\tau_{\text{discharge}} = R \cdot C$ is large


ENEE236 – Analog Electronics

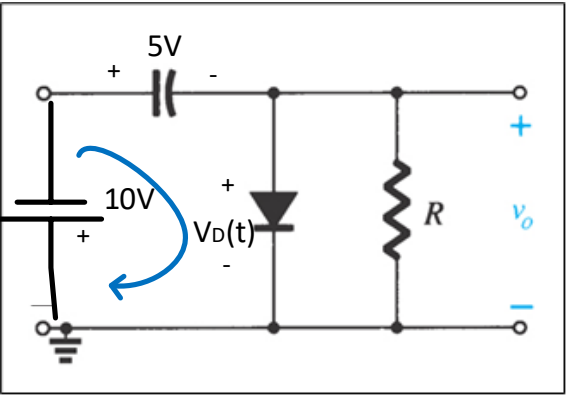

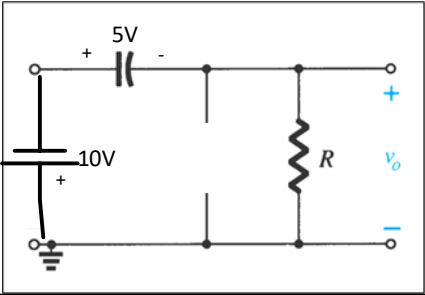KVL around the loop: $-10 - 5 - V_D(t) = 0$
 $\Rightarrow V_D(t) = -15\text{ V} < 0, \therefore$ diode is OFF




$V_o(t) = V_D(t) = -15\text{ V}$

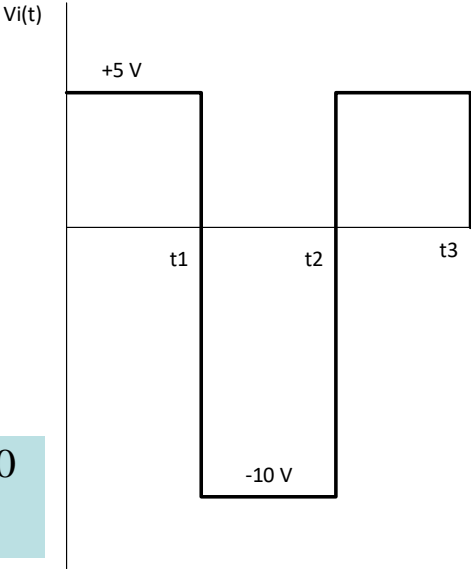


ENEE236 – Analog Electronics

5) for $t_2 < t < t_3$, $V_i(t) = 5V$
while $V_C = 5V$
 $V_D(t) = 5 - 5 = 0$

Diode is OFF and it will
remain always off
no matter what happens to $V_i(t)$
 $V_o(t) = V_D(t) = V_i(t) - 5$


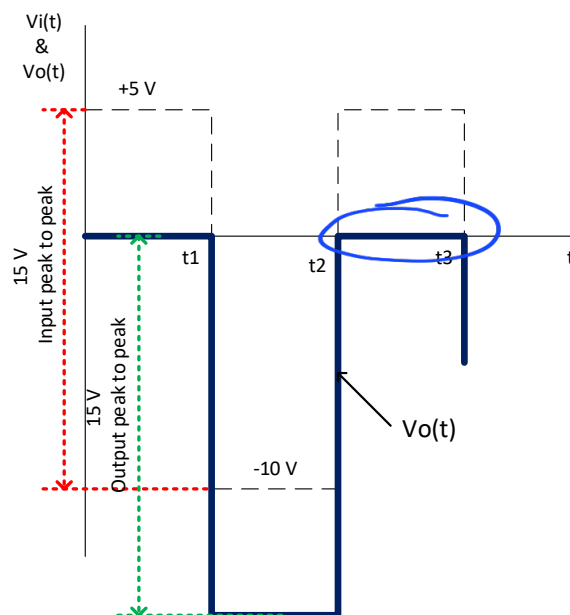


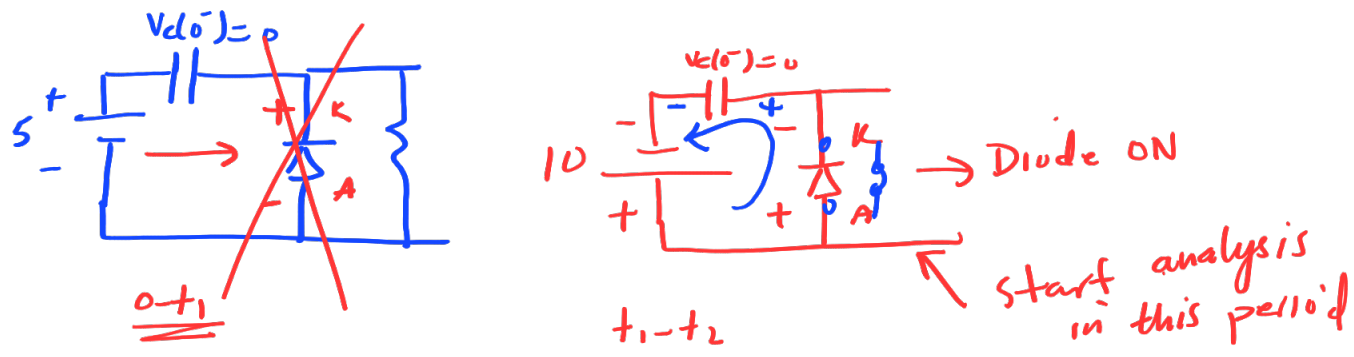

ENEE236 – Analog Electronics




Example


What happens if the diode was inversed

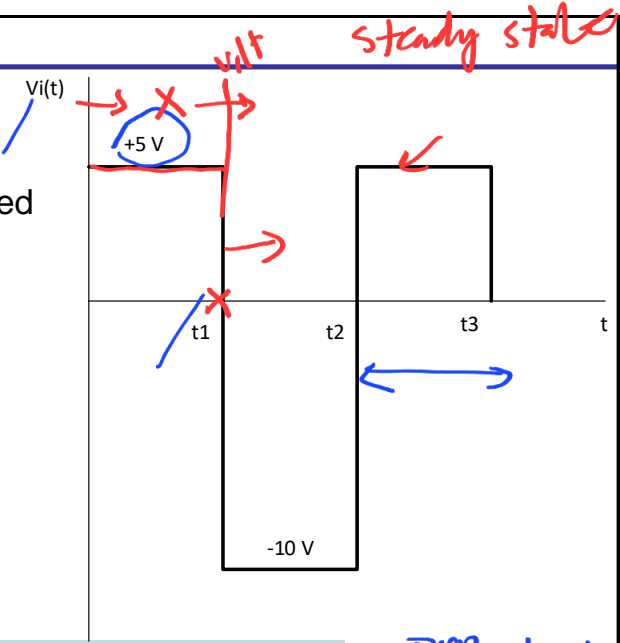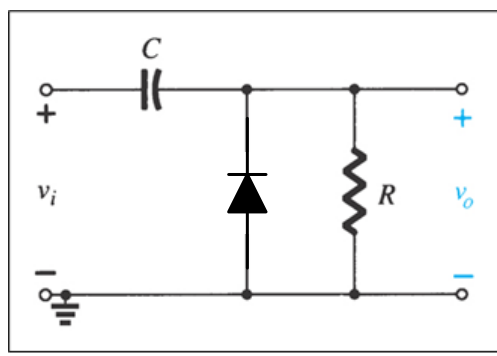

1) Consider $t_1 < t < t_2$ which makes the diode ON



$\Rightarrow D$ is ON and it is replaced by short circuit
 $V_o(t) = 0V$

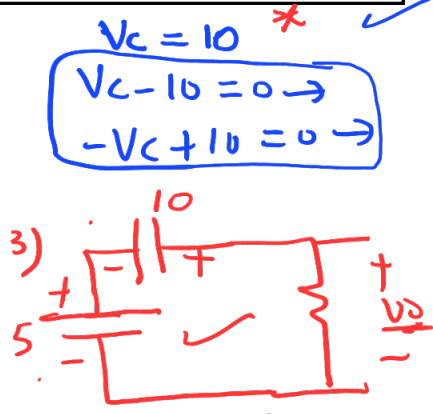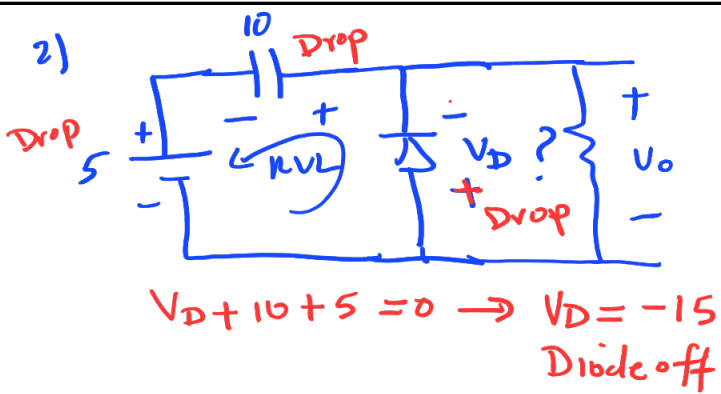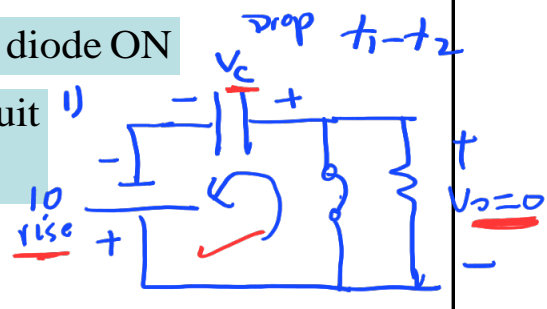

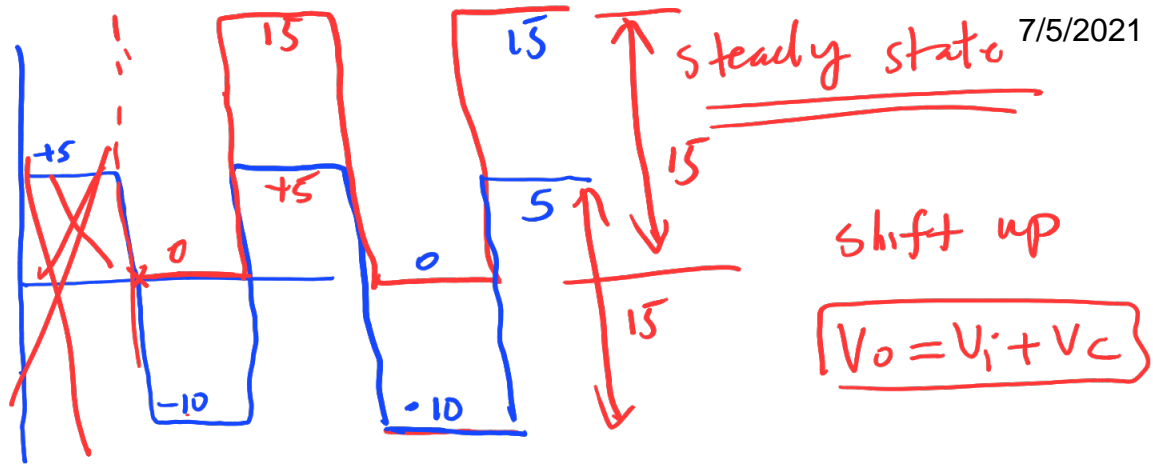


ENEE236 – Analog Electronics

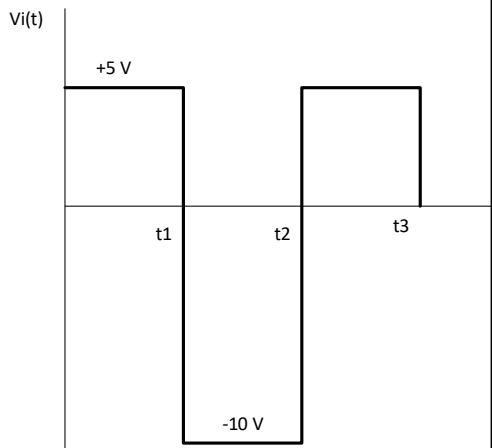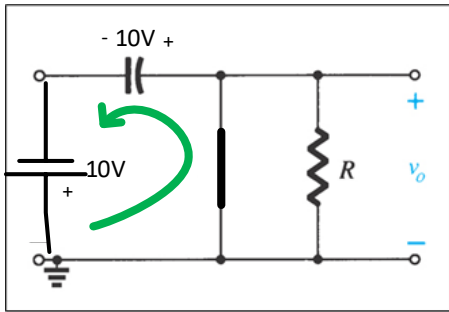Cap is charged to 10V with shown polarity due to diode forward current $V_o(t) = 0$ V




2) for $t_2 < t < t_3$ voltage source reverses polarity, $V_i(t) = +5$ V while Cap keeps its charge $V_c = 10$ V


ENEE236 – Analog Electronics

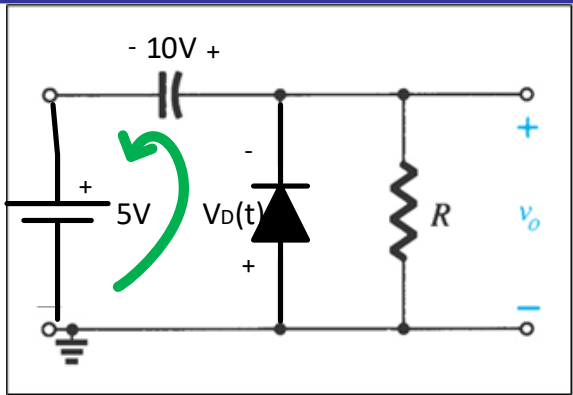

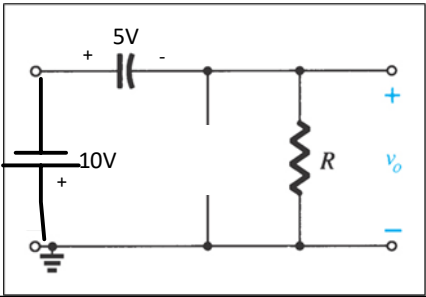KVL around the loop: $10 + 5 + V_D(t) = 0$
 $\Rightarrow V_D(t) = -15\text{ V} < 0, \therefore \text{diode is OFF}$



$V_o(t) = -V_D(t) = 15\text{ V}$

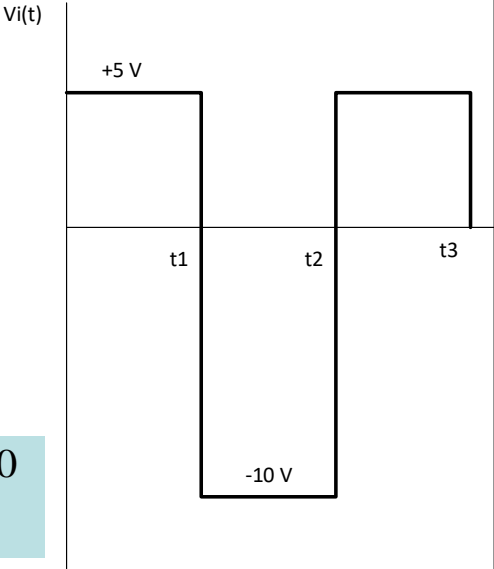

ENEE236 – Analog Electronics



Afterwards for any value of the given $V_i(t)$ diode remains OFF and $V_o(t) = V_i(t) + 10$


∴ the clamper charges a cap and uses this charge to add up to the input to shift it up or down (i.e. add dc offset)

Important Note *

For Proper Clamping action , $\tau_{discharge}$ must be large enough (at least 10 times the period of the input waveform)



$$\tau_{discharge} = R.C > 10 (t_1 + t_2)$$

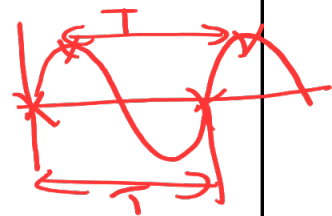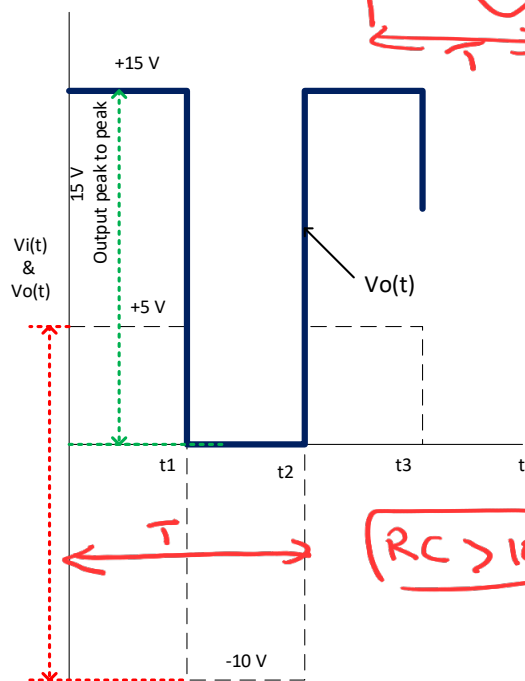

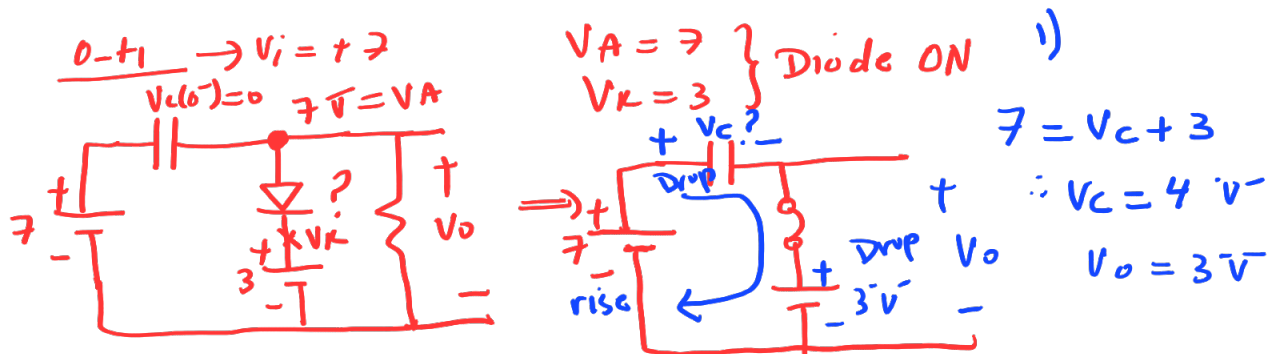

ENEE236 – Analog Electronics

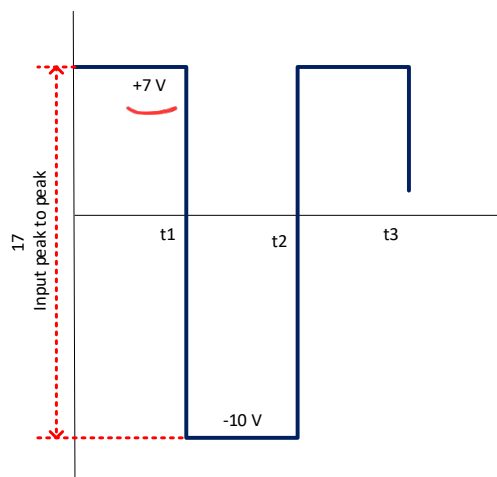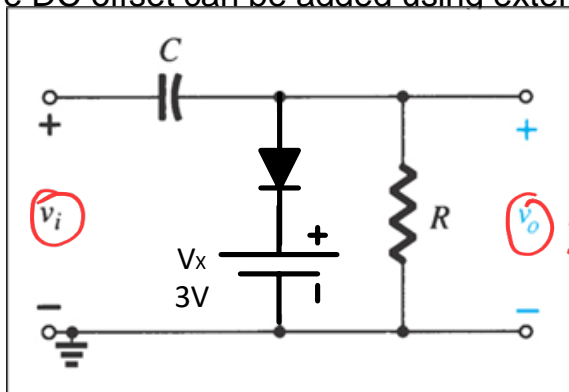More DC offset can be added using external voltage source



1) When $V_i = +7V$

$$7 - V_C(t) - V_X = 0$$

$$\therefore V_C(t) = 7 - 3 = 4V$$



$$\Rightarrow V_O(t) = V_X = 3V$$

2) for $V_i = -10V$



$$-10 - 4 - V_D(t) - 3 = 0$$

$$\Rightarrow V_D(t) = -17V < 0 \text{ and diode is OFF}$$

$$\begin{aligned} \Rightarrow V_O(t) &= V_i(t) - V_C(t) \\ &= V_i(t) - 4 \\ &= -10 - 4 = -14V \end{aligned}$$

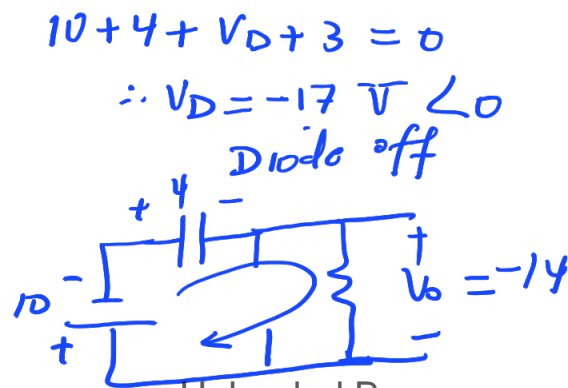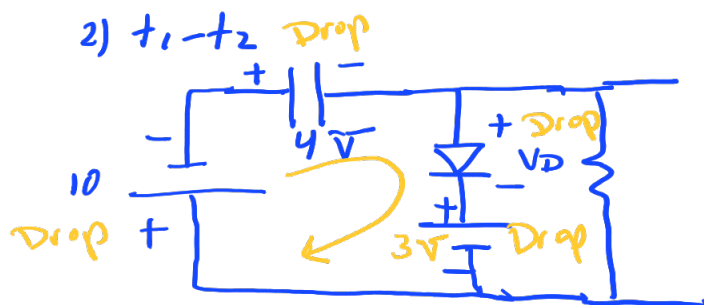

ENEE236 – Analog Electronics

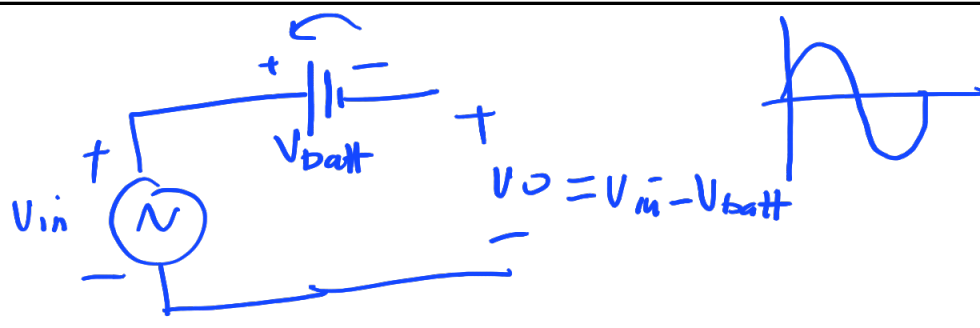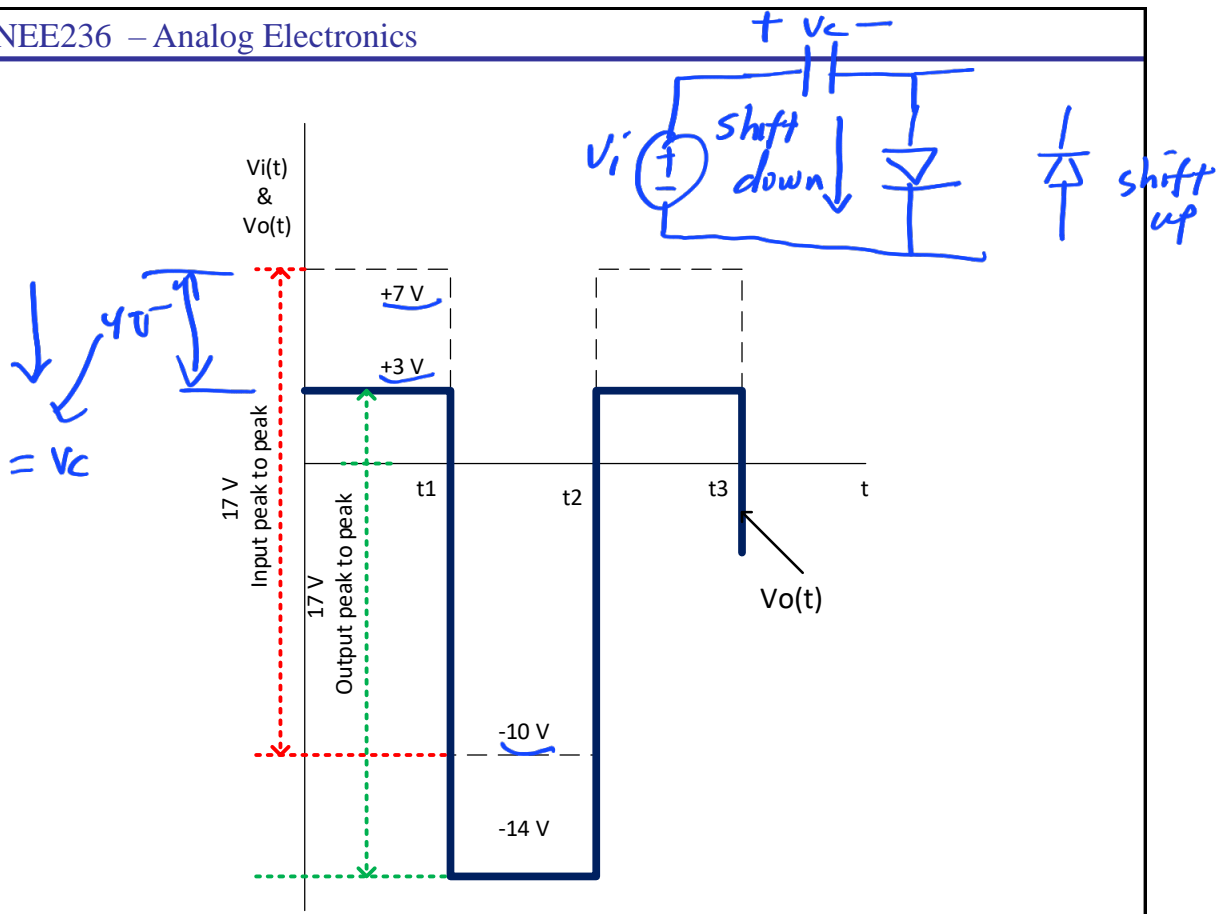


//

ENEE236 – Analog Electronics


For Self study

Biased Clamper Circuits

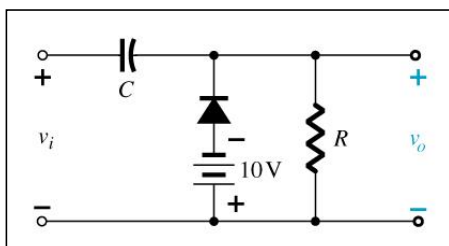The input signal can be any type of waveform such as a sine, square, or triangle wave.




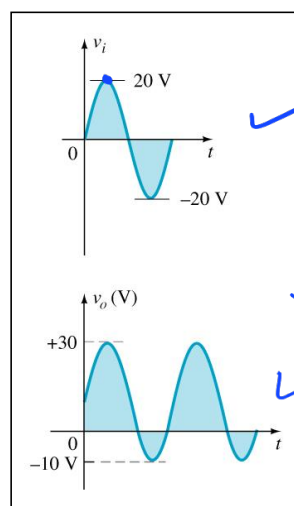The DC source lets you adjust the DC clamping level.



Practice solve

Summary of Clamper Circuits

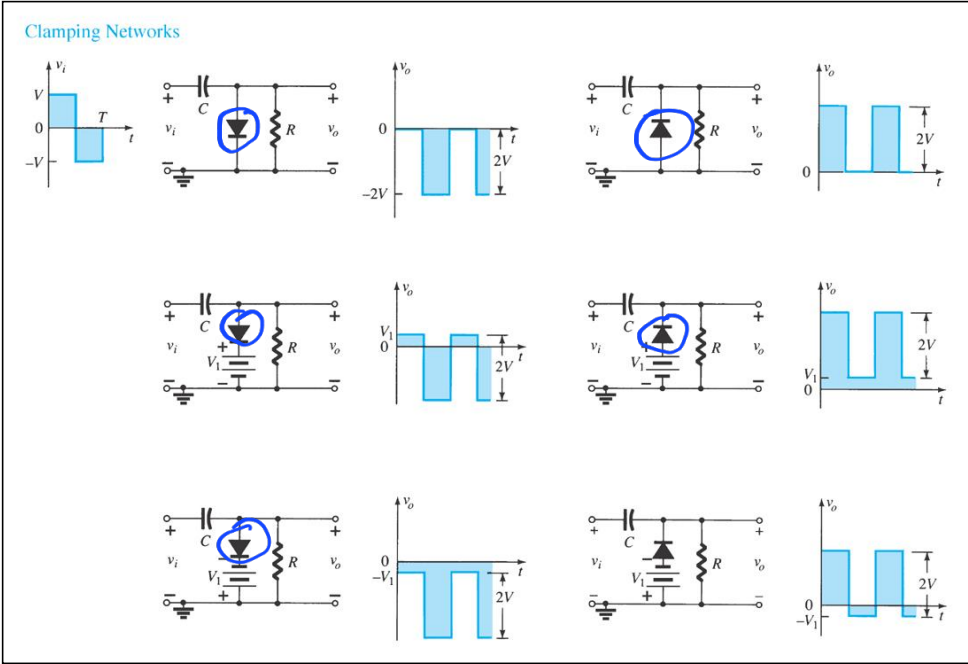

*End of L5
End of T3*

*عاده الكور لغايه هنا
يوم السبت*