

Exp 4: DC circuits

Resistance of a metallic conductor $R = \frac{\text{Voltage}}{\text{Current}} = \frac{V}{I}$ = potential difference / Current flowing

Materials $\rightarrow$ ohmic : V depends linearly on I
 $\rightarrow$ non-ohmic : V does not depend linearly on I

Equivalent Resistance of 2 Resistors

I is the same for R_1 & R_2

$R_{\text{series}} = R_1 + R_2$

$\frac{1}{R_{\text{parallel}}} = \frac{1}{R_1} + \frac{1}{R_2}$

V is the same for R_1 & R_2

$\Rightarrow \frac{\Delta R}{R} = \frac{\frac{\Delta V}{V}}{1} + \frac{\frac{\Delta I}{I}}{1}$

V
volts


I (mA)

non ohmic material

ohmic material


slope = $R = \frac{\Delta V}{\Delta I}$

Color code

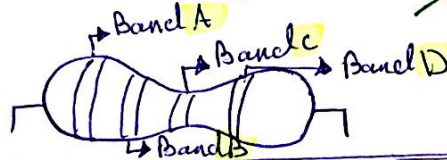

$R \text{ (Theoretically)} = AB \times 10^C \pm (D \times \% R)$

Exp 5: focal length of a convex lens

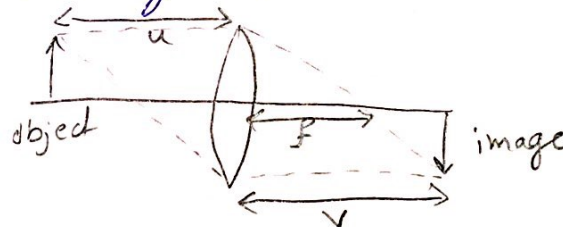

focal length:

The distance between the lens and the point of convergence of the light rays coming from the infinity

focal length $\frac{1}{f} = \frac{1}{u} + \frac{1}{v}$

$\Rightarrow \frac{1}{f} = \frac{1}{f_x} + \frac{1}{f_y}$

$\frac{\Delta f}{f^2} = \frac{\Delta u}{u^2} + \frac{\Delta v}{v^2}$

$f_x = f_y$ (theoretically)

$\frac{1}{x \text{ intercept}} = \frac{1}{y \text{ intercept}}$

Alaa Etarwi

