




IC NOTES

References:

1. Digital Integrated Circuits
2. CMOS VLSI Design

Prepared By: Ghazi Haj Qassem


MOS Transistor Theory

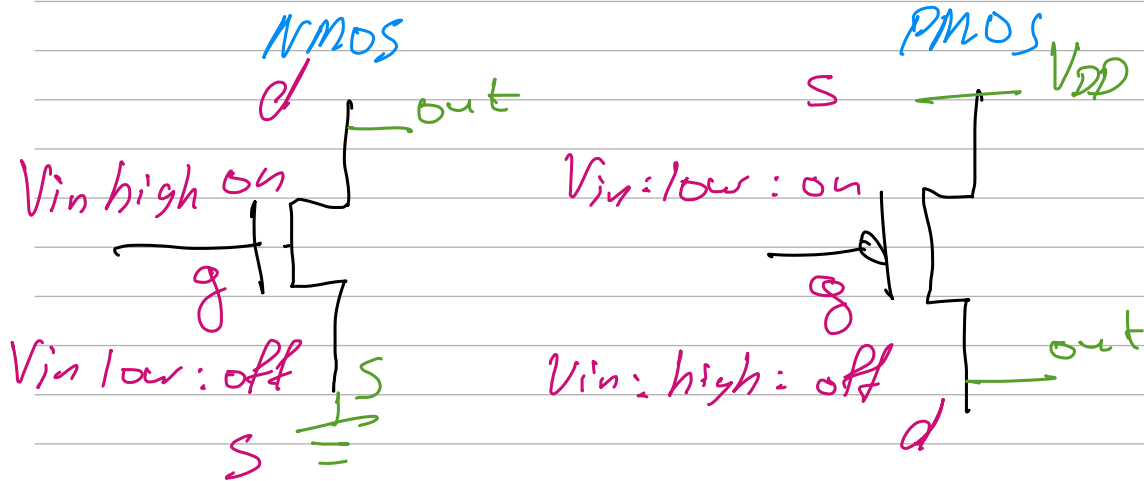

$$I_{DS} = \begin{cases} 0 & , V_{gs} < V_{tn} \\ \beta (V_{gs} - V_{tn} - V_{ds}/2) V_{ds} & , V_{gs} > V_{tn} , V_{ds} \leq V_{gs} - V_{tn} \\ \frac{\beta}{2} (V_{gs} - V_{tn})^2 & , V_{gs} > V_{tn} , V_{ds} > V_{gs} - V_{tn} \end{cases}$$

\rightarrow off (cutoff)
 \rightarrow linear
 \rightarrow on
 \rightarrow satur.

$$\beta = \mu_n C_{ox} \frac{W}{L}$$

 

$$C = \frac{e \cdot A}{d}$$

$$C_{gb} = \frac{\epsilon_{ox} W L}{t_{ox}}$$

0.3 μm process

$$\lambda = \frac{L}{2}$$

$$C_{db} = \frac{\epsilon L (\mu m)}{t}$$

$$C_{db} \text{ (1/}\mu m) \quad [C = C_{db} W]$$

$$C_{gb} \text{ (1/}\mu m^2)$$

$$C_{sb} \text{ (1/}\mu m) \quad [C = C_{sb} W]$$

$$C = C_{gb} W L$$

$$W/L$$

$$C_{ox}$$

Example:


Consider the NMOS inverter given.

$V_{DD} = 5V$, $R_D = 22\text{ k}\Omega$

$V_{th} = 1.5V$, $K_N = 100\text{ }\mu\text{A/V}^2$

Determine $V_{OL(min)}$ when $V_i = V_{DD}$

 Example for answer to be written $V_{OL(min)} = 0.3V$




$$R_{on} = \frac{1}{2K_N(V_{DD} - V_{th})} = \frac{1}{2(0.1)(5 - 1.5)} = \frac{1}{0.2(3.5)} = 1.43\text{ k}\Omega$$

$$V_{OL} = \frac{R_{on}}{R_D + R_{on}} V_{DD} = 0.3V$$

$$0.3V < V_{GS} - V_{th} = 3.5V$$

$$V_{DS} > V_{GS} - V_{th} = 3.5V$$

 

Example:


In the following circuit, the capacitance of C_L is 50 fF .

C_L is initially charged to $2.5V$. At time zero, its gate is attached ground, as shown in the figure. $V_{TP} = -0.5V$.

1) If we replace the PMOSFET with a $2\text{ k}\Omega$ resistor, how long does it take for the capacitor to discharge to $1.25V$? Your answer should be like this (1) 120 ps

 
2) If we consider the transistor cut-off, what is the final voltage of the capacitor?

Your answer should be like this (2) 200 v



PMOSFET with grounded gate.

 - ☐ A. 2) 2.0 v
- ☐ B. 2) 2.25 v
- ☒ C. 1) 69 ps
- ☐ D. 1) 0.69 ps
- ☒ E. 2) 0.5 v
- ☐ F. 1) 9 ps
- ☐ G. 2) 2.5 v



$$t = \ln 2 \tau$$

$$V = V_0 e^{-\frac{t}{\tau}}$$

$$\frac{1}{2} V_0 = V_0 e^{-\frac{t}{\tau}}$$

$$t = \ln 2 \tau$$

$$= \ln 2 RC$$

$$= \ln 2 (2\text{ k}\Omega) (50\text{ fF})$$

$$= 0.69 (100 \times 10^{-12})$$


$$= 69 \times 10^{-12} = 69\text{ ps}$$

$$V_{GS} > V_{tp} \quad V_G - V_S > V_{tp} \Rightarrow -V_S > V_{tp} \Rightarrow V_S < -V_{tp} = 0.5V$$

CMOS Inverter Operation

TABLE 2.2 Relationships between voltages for the three regions of operation of a CMOS inverter

	Cutoff	Linear	Saturated
nMOS	$V_{gsn} < V_{tn}$ $V_{in} < V_{tn}$	$V_{gsn} \geq V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} < V_{gsn} - V_{tn}$ $V_{out} < V_{in} - V_{tn}$	$V_{gsn} > V_{tn}$ $V_{in} > V_{tn}$ $V_{dsn} > V_{gsn} - V_{tn}$ $V_{out} > V_{in} - V_{tn}$
pMOS	$V_{gsp} > V_{tp}$ $V_{in} > V_{tp} + V_{DD}$ $V_g - V_s > V_{tp}$ $V_g > V_{tp} + V_s$ $V_{in} > V_{tp} + V_{DD}$	$V_{gsp} \leq V_{tp}$ $V_{in} < V_{tp} + V_{DD}$ $V_{dsp} > V_{gsp} - V_{tp}$ $V_{out} > V_{in} - V_{tp}$	$V_{gsp} < V_{tp}$ $V_{in} < V_{tp} + V_{DD}$ $V_{dsp} < V_{gsp} - V_{tp}$ $V_{out} < V_{in} - V_{tp}$

 


V_{in}	V_{out}
V_{DD} "1"	GND "0"
GND "0"	V_{DD} "1"

VTC of CMOS Inverter

TABLE 2.3 Summary of CMOS inverter operation

Region	Condition	p-device	n-device	Output
A	$0 \leq V_{in} < V_{tn}$	linear	cutoff	$V_{out} = V_{DD}$
B	$V_{tn} \leq V_{in} < V_{DD}/2$	linear	saturated	$V_{out} > V_{DD}/2$
C	$V_{in} = V_{DD}/2$	saturated	saturated	V_{out} drops sharply
D	$V_{DD}/2 < V_{in} \leq V_{DD} - V_{tp} $	saturated	linear	$V_{out} < V_{DD}/2$
E	$V_{in} > V_{DD} - V_{tp} $	cutoff	linear	$V_{out} = 0$

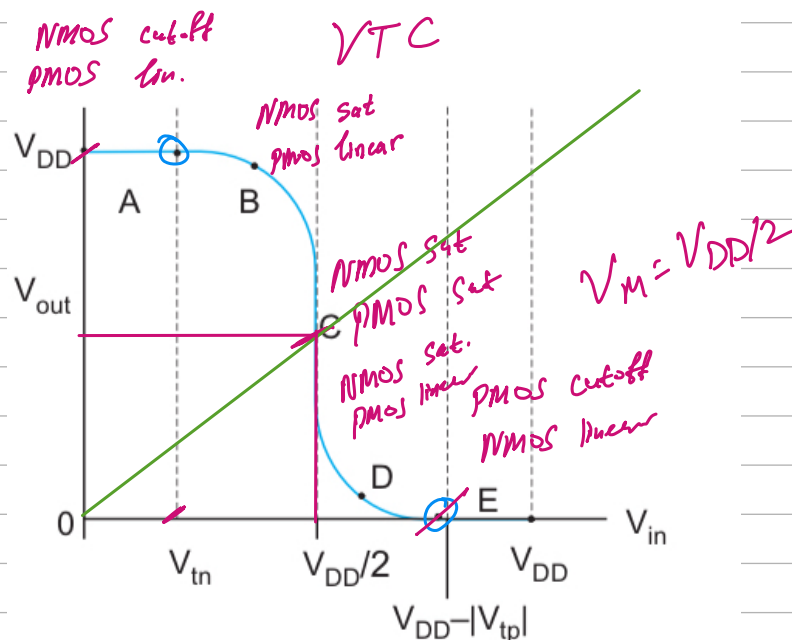

① Switching Threshold (V_M): defined as the point where $V_{in} = V_{out}$.

→ V_M is desired to be around the middle of the voltage swing ($V_M = V_{DD}/2$ for inverter)

→ This results in comparable high and low noise margins.

→ $W_p \uparrow$: $V_M \uparrow$, $W_n \uparrow$: $V_M \downarrow$

② Noise Margins

* V_{IH} , V_{IL} are defined when $\frac{dV_{out}}{dV_{in}} = -1$ (slope = -1).

V_{OH} , V_{OL}


V_{OH} : min output voltage

V_{IH} : min input voltage


V_{IL} : max lower input voltage

V_{OL} : max output voltage

 $W_n \uparrow$ $V_M \downarrow$
 $W_p \uparrow$ $V_M \uparrow$



$$NM_H = V_{OH} - V_{IH}$$

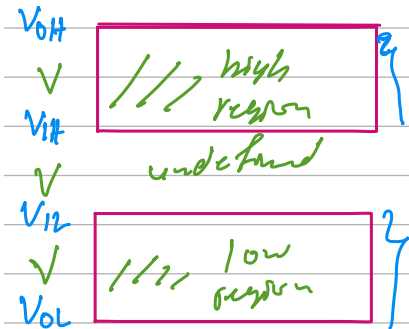

$$NM_L = V_{IL} - V_{OL}$$

C. arrange the terms V_{OHmin} , V_{IHmin} , V_{ILmax} and V_{OLmax} , and arrange them from lowest value to highest value. (2 pts)

$$V_{OLmax} \leq V_{ILmax} \leq V_{IHmin} \leq V_{OHmin}$$

FIGURE 2.30 CMOS inverter noise margins

Example:

Question 6

Not answered

Marked out of 1.00

Flag question


Consider the following transfer curve

What are its NMH and NML?

What is VM

* gain in buffer ($\frac{V_{out}}{V_{in}} = 1$). Hence, slope = 1.

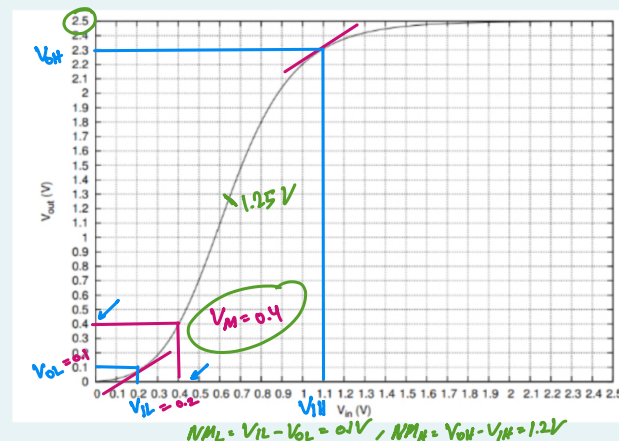On the other hand, inverter gain = slope = -1.



NML ≈ Choose...

VM ≈ Choose...

NMH ≈ Choose...

The correct answer is: NML ≈ → 0.25 V, VM ≈ → 0.77 V, NMH ≈ → 1.5 V

??

Extra:




4- In this problem, the circuits are implemented in 0.25 μ m technology, and all the transistors have the minimum channel lengths .a. Consider the CMOS circuit from Fig. 2.a. If the NMOS transistor has channel width W_n and the PMOS transistor has channel width, W_p , label and sketch the voltage transfer characteristics from FIG. 2.b that correspond to following device sizes assuming V_{tn} and V_{tp} are threshold voltages for n and p devices :**(8 points)**


A: $W_n = 5\mu\text{m}$, $W_p = 5\mu\text{m}$

B: $W_n = 1\mu\text{m}$, $W_p = 5\mu\text{m}$

 C: $W_n = 5\mu\text{m}$, $W_p = 1\mu\text{m}$



Sol.

 

2

3. Given three different ways to design inverter. Match the right VTC curve to the right figure for each one. [8 marks]

Fig. A

 


Fig. B



 


Fig. C

 


Sol.

 

Pass Transistor DC Characteristics (Strong & Weak Signals)

* PMOS passes strong "1" (V_{DD}), and weak "0" = $|V_{tp}|$.

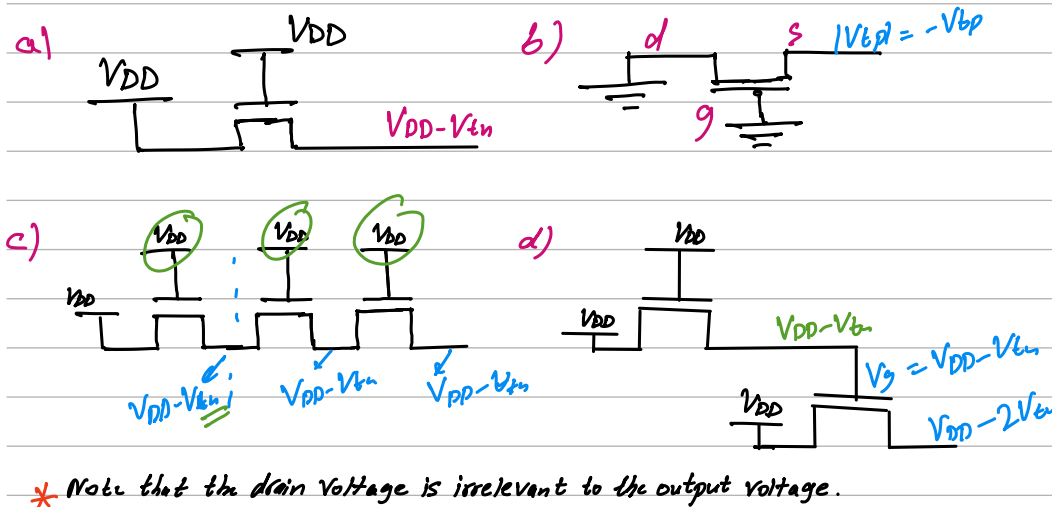* NMOS passes strong "0" (GND), and weak "1" = $V_{DD} - V_{tn}$.



Recall:

* NMOS ON:

$$V_{gs} > V_{tn} \Rightarrow V_g - V_s > V_{tn}$$

$$V_s < \underline{V_g - V_{tn}}$$

* PMOS ON:

$$V_{gs} < V_{tp} \Rightarrow V_g - V_s < V_{tp}$$

$$V_s > V_g - V_{tp} \text{ or } V_s > V_g + |V_{tp}|$$

* Note that the drain voltage is irrelevant to the output voltage.

$$V_s < V_g - V_{tn}$$

$$< (V_{DD} - V_{tn}) - V_{tn}$$

$$= V_{DD} - 2V_{tn}$$

2.20 Give an expression for the output voltage for the pass transistor networks shown in Figure 2.35. Neglect the body effect.

 


FIGURE 2.35 Pass transistor networks

2.21 Suppose $V_{DD} = 1.2$ V and $V_t = 0.4$ V. Determine V_{out} in Figure 2.36 for the following. Neglect the body effect.

- a) $V_{in} = 0$ V $\Rightarrow V_o = 0$
- b) $V_{in} = 0.6$ V $\Rightarrow V_o = 0.6$ V
- c) $V_{in} = 0.9$ V $\Rightarrow V_o = 0.8$ V
- d) $V_{in} = 1.2$ V $\Rightarrow V_o = 0.8$ V

 


FIGURE 2.36


Single pass transistor

$$V_g - V_t = 0.8$$



Device Sizing:

Example #1:

21

 


 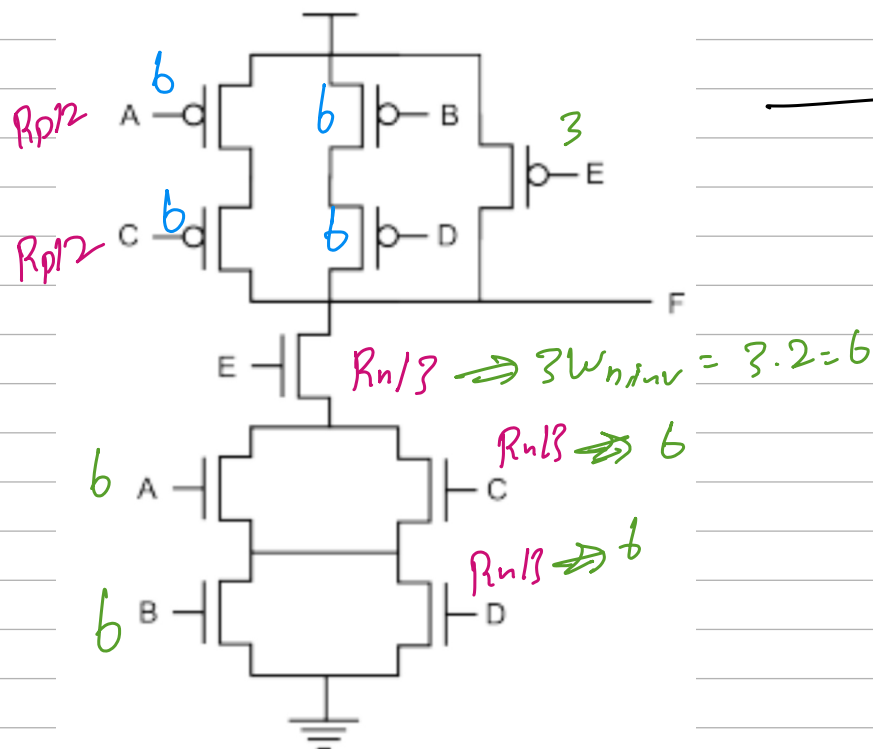Example #2: Inverter: 3 (PMOS), 2 (NMOS).



Extra:

 - c. What are the device sizes if it is going to match inverter with ratio of 2 for p and 1 for n (10 points)




Elmore Delay

$$R_{ik} = \sum R_j, \quad R_j \in [\text{path}(s \rightarrow i) \cap \text{path}(s \rightarrow k)] \quad (\text{path resistance})$$

$$\tau_{Di} = \sum_{k=1}^N C_k R_{ik}$$

 Example: compute the Elmore delay for node i .



$$\sum_{k=1}^N \text{path resistance} \times C_k$$

$$s \rightarrow i: R_1, R_2, R_i$$

$$s \rightarrow 1: R_1$$

$$\tau_D = R_1 C_1 + R_1 C_2 + (R_1 + R_2) C_3 + (R_1 + R_2) C_4 + (R_1 + R_2 + R_i) C_i$$

Example: compute the Elmore delay for node N .


 



Figure 4.13 RC chain.

$$\tau_{DN} = \sum_{i=1}^N C_i \sum_{j=1}^i R_j = \sum_{i=1}^N C_i R_{ii}$$
 
$$\tau_D = R_1 C_1 + (R_1 + R_2) C_2 + \dots + (R_1 + \dots + R_N) C_N$$



 Example: Find the delay of a wire of length L , resistance r , capacitance c , partitioned into N identical segments.



$$\begin{aligned} \tau_D &= \frac{L}{N} \cdot \frac{1}{N} r c + \frac{L}{N} \cdot \frac{1}{N} (r+r) c + \dots + \frac{L}{N} \cdot \frac{1}{N} (Nr) c \\ &= \left(\frac{L}{N}\right)^2 (1+2+\dots+N) r c = \left(\frac{L}{N}\right)^2 \frac{N(N+1)}{2} r c = \frac{L^2}{N} \frac{(N+1)}{2} r c \end{aligned}$$

$$\tau_D = \frac{r c L^2}{2} \cdot \frac{N+1}{N} \Big|_{N \rightarrow \infty} = \underline{\underline{\frac{r c L^2}{2}}}$$

$$\tau_D = \frac{r c L^2}{2}$$

* If the length of the wire is doubled, its delay will be quadrupled.

Exercises:

①


Question 10

Not answered

Marked out of 1.00

Flag question

 Determine the Elmore delay from Node a to Node b in the following circuit



- ☐ A. delay = $(R1 + R2 + R3 + R4)(C4 + C5)$
- ☐ B. delay = $R1(C1 + C2 + C3) + R2(C2 + C3 + C4) + R4(C4 + C5)$
- ☐ C. delay = $R1(C1 + C2 + C3 + C4) + R2(C2 + C3 + C4) + R4(C4 + C5)$
- ☐ D. delay = $R1(C1 + C2 + C3 + C4 + C5) + R2(C2 + C3 + C4 + C5) + R4(C4 + C5)$

The correct answer is: delay = $R1(C1 + C2 + C3 + C4 + C5) + R2(C2 + C3 + C4 + C5) + R4(C4 + C5)$

C2, C3 in parallel at node 2 ⇒ add them.

$$\begin{aligned} \text{delay} &= \overset{\text{node 1}}{R_1 C_1} + \overset{\text{node 2}}{(R_1 + R_2) C_2} + \overset{\text{node 3}}{(R_1 + R_2) C_3} + \overset{\text{node 4}}{(R_1 + R_2 + R_4) C_4} + \overset{\text{node 5}}{(R_1 + R_2 + R_4) C_5} \\ &= R_1(C_1 + C_2 + C_3 + C_4 + C_5) + R_2(C_2 + C_3 + C_4 + C_5) + R_4(C_4 + C_5) \end{aligned}$$

②


Question 11

Not answered

Marked out of 1.00

Flag question

 Derive an expression for the time constant when driving node d. Vs changes from 0 V to 2.5 V at time zero. (delay from s to d)



- ☐ A. $\tau_d = r_2(c1 + c3 + c4 + c5 + c6) + (r_2 + r_3) c_7$
- ☐ B. $\tau_d = r_2(c2 + r_3 + c4 + c5 + c6) c_7$
- ☐ C. $\tau_d = r_2(c1 + c3) + (r_2 + r_3 + c4 + c5 + c6) c_7$
- ☐ D. $\tau_d = r_2(c1 + c3 + c4) + (r_2 + r_3 + c5 + c6) c_7$




The correct answer is: $\tau_d = r_2(c1 + c3 + c4 + c5 + c6) + (r_2 + r_3) c_7$

$$\begin{aligned} \text{delay} &= \overset{\text{node 1}}{r_2 c_1} + \overset{\text{node 3}}{r_2 c_3} + \overset{\text{node 4}}{r_2 c_4} + \overset{\text{node 5}}{r_2 c_5} + \overset{\text{node 6}}{r_2 c_6} + \overset{\text{node 7}}{(r_2 + r_3) c_7} \\ &= r_2(c1 + c3 + c4 + c5 + c6) + (r_2 + r_3) c_7 \end{aligned}$$


** What happened to node 2? $[\text{path}(s \rightarrow 2) = \emptyset \cap \text{path}(s \rightarrow d) = r_2, r_3] = \emptyset$
The path resistance from a node to itself is zero, since there is no intersection.*

Propagation Delay

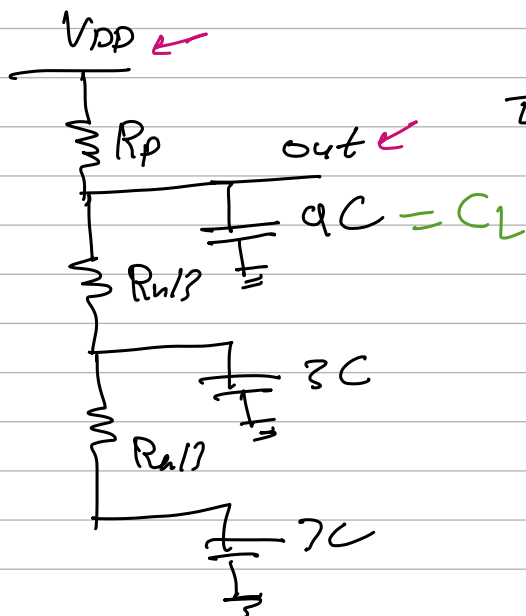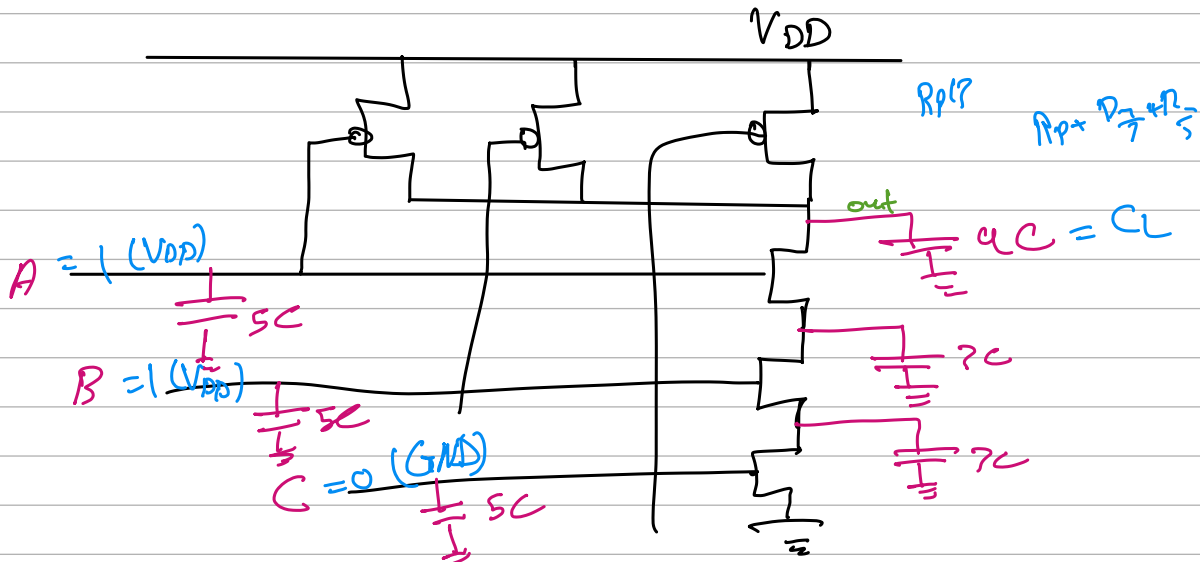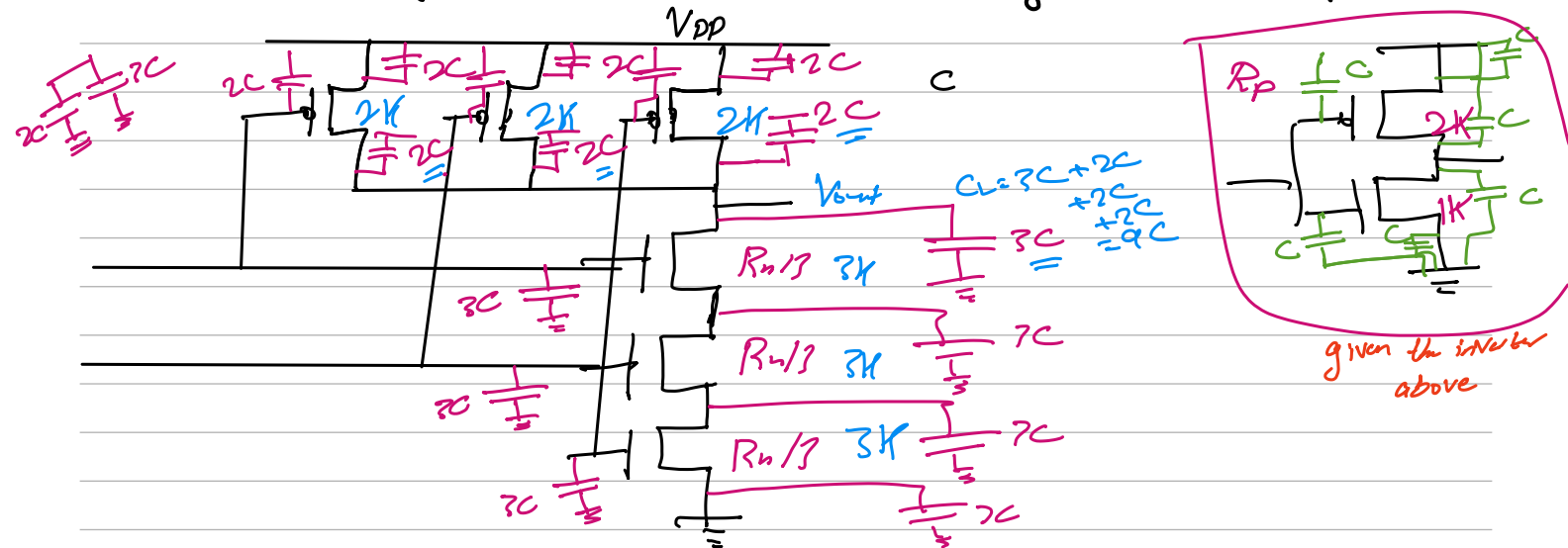Example: Sketch a 3-input NAND gate with transistor widths to achieve effective fall and rise time equal to that of an inverter. Annotate gate & diffusion capacitances.



 
$$T_p = R_p(9C) + R_p(3C) + R_p(2C) = 15C R_p$$





$$T_n = R_n/3(2C) + (R_p + R_n/3)3C + (R_p + R_n/3 + R_n/3)9C = 12C R_n$$

 Example: Estimate t_{pdf} t_{par} for the previous 3-input NAND gate loaded with h identical NAND gates.



$$C_L = 9C + 5hC = \underline{(9+5h)C}$$

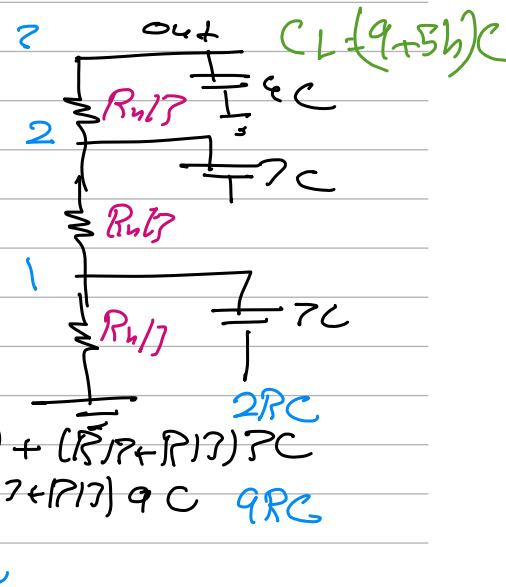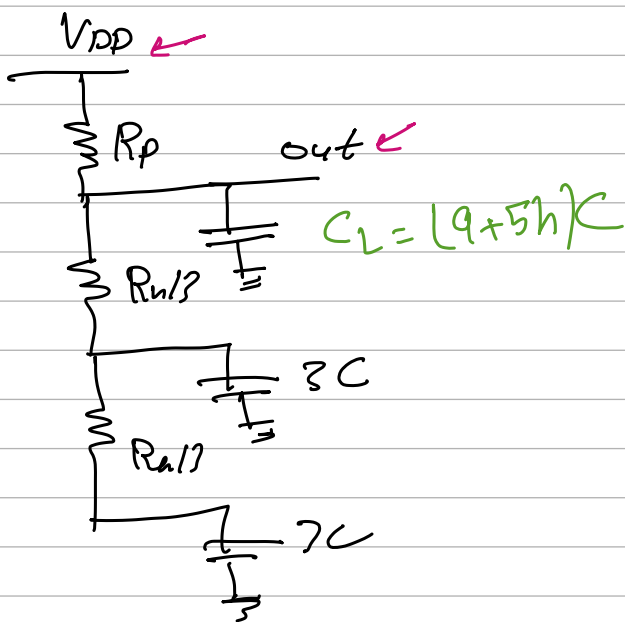

$$t_w = R_{n/3}(3C) + (R_{n/3} + R_{n/3})3C + (R_{n/3} + R_{n/3} + R_{n/3})(9+5h)C = 12RC$$


$$t_r = R_p(9+5h)C + R_p(3C) + R_p(3C) = (15+5h)R_pC$$

$$t_f = \frac{R_n}{3}(3C) + \left(\frac{R_n}{3} + \frac{R_n}{3}\right)(3C) + \left(\frac{R_n}{3} + \frac{R_n}{3} + \frac{R_n}{3}\right)(9+5h)C = R_nC + 2R_nC + (9+5h)R_nC = (12+5h)R_nC$$

Similar Example:

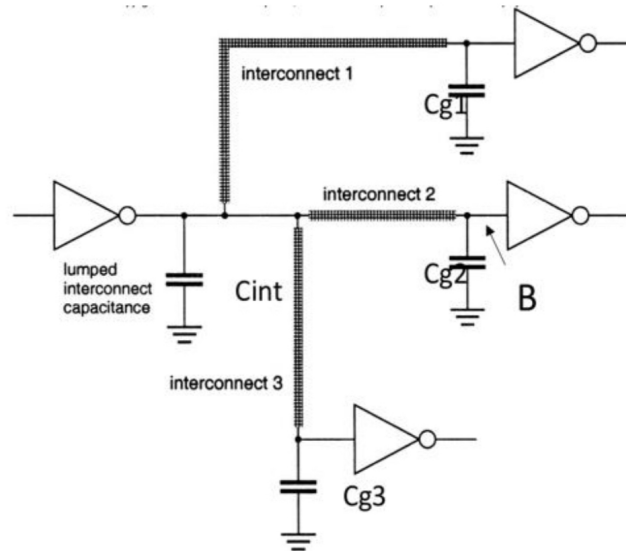- B) Compute the worst-case rising and falling RC time constants at point B of the circuit below using the Elmore delay method. Assume all transistors **are unit sized** and wire **capacitance is lumped**. (7 pts)

Assume $R_{chn} = 2000$ ohms. $R_{chp} = 8604$ ohms, $C_{g(n+p)} = 20$ ff, $C_{d(n+p)} = 20$ ff, and $C_{int} = 10$ ff. R_{int} for interconnect1 is 10 ohms, interconnect2 is 5 ohms, and interconnect3 is 7 ohms. Hint: Note that interconnect **capacitance is lumped at the beginning**, so we don't need to consider it separately for the 3 wires



Recall that channel resistance is inversely proportional to beta. So:

$$\frac{R_{chp}}{R_{chn}} = \frac{\beta_n}{\beta_p}$$

Page 6


Note that interconnect **capacitance is lumped at the beginning**, so we don't need to consider it separately for the 3 wires.

Following is the circuit for falling delay at B:

Falling Elmore delay at B = $2000 \times 20 + 10 + 20 + 20 + 5 \times 20 = 0.1801$ ns

For rising delay at B, the circuit is the same except that R_{chn} is replaced with R_{chp} and the leftmost Gnd symbol is replaced with Vdd.

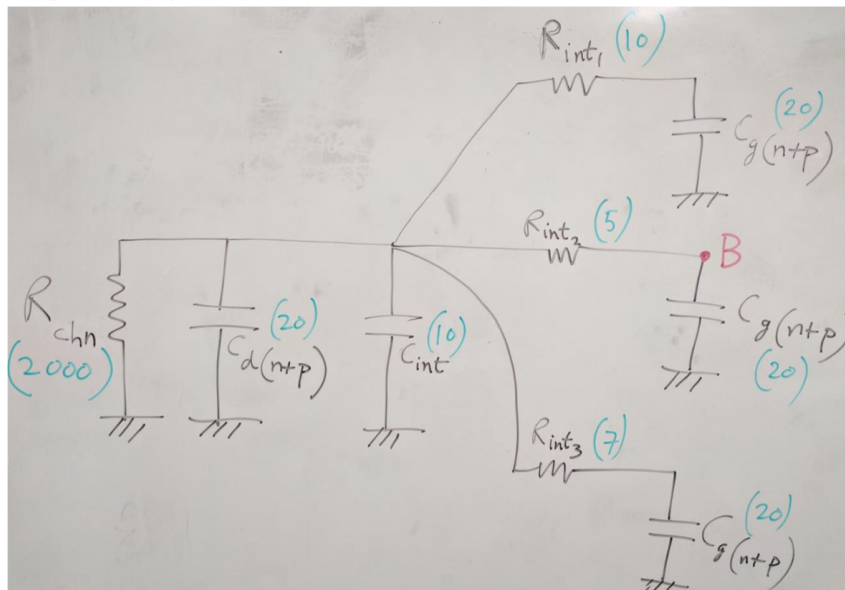Rising Elmore delay at B = $8604 \times 20 + 10 + 20 + 20 + 20 + 5 \times 20 = 0.77446$ ns




Q) List the steps required for creating a PMOS transistor. Draw a cross-section of the PMOS transistor, labelling each layer/feature in the order fabricated.

C. List the steps required for creating a PMOS transistor, and draw a cross-section of the PMOS transistor, labeling each layer/feature in the order fabricated. (5 pts)

The steps below assume that a p-type substrate and positive photoresist is used.

1. Expose the substrate to oxygen (and hydrogen) at very high temperatures to form silicon dioxide (SiO_2) layer. This is thick oxide.
2. Deposit photoresist.
3. Cover the photoresist with a mask which exposes those areas where n-well is to be created.
4. Expose to UV light.
5. Remove the exposed photoresist by dissolving.
6. Etch the surface to remove the portions of SiO_2 not covered by photoresist.
7. Strip off remaining photoresist.
8. Use n ion implantation to form n-wells in the areas without SiO_2 .
9. Cover the whole surface with thin oxide and polysilicon.
10. Selectively remove thin oxide and poly from everywhere except for transistor gates.
11. Use p^+ ion implantation to form sources and drains of PMOS transistors.
12. Use n^+ ion implantation to form n-taps.
13. Cover the whole surface with thick oxide.
14. Selectively remove thick oxide from the source, drain and body (n-tap). This forms contact cuts.

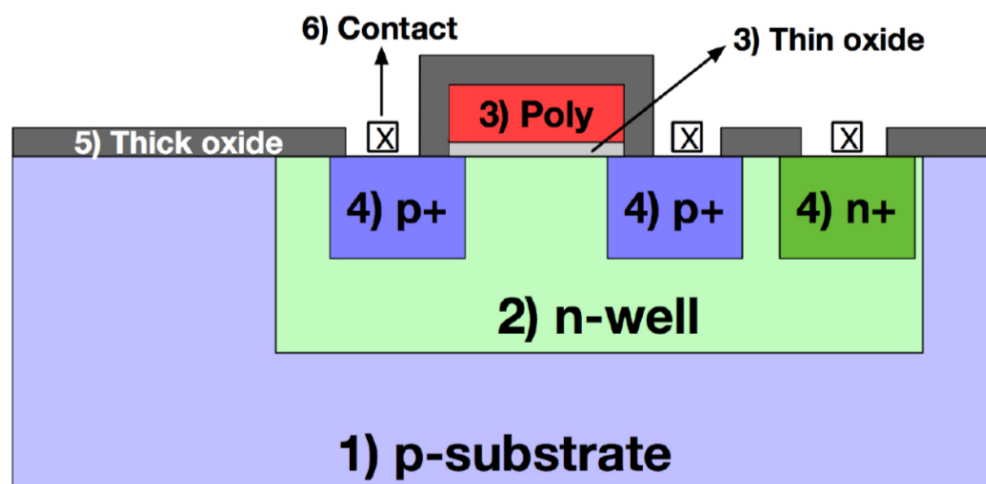

Question 4

Complete

Mark 0.20 out of 1.00

Flag question

List the following interconnect fabrication steps in chronological order:

- 5) • Etch metal. • Expose photoresist using mask. • Remove all photoresist. • Deposit photoresist. • Deposit metal everywhere.

- 5) Deposit photoresist. ⚡
- 3) Remove all photoresist. ⚡
- 1) • Expose photoresist using mask. ⚡
- 4) Etch metal ⚡
- 2) Deposit metal everywhere ⚡

The correct answer is: 5) → Remove all photoresist., 3) → • Expose photoresist using mask., 1) → Deposit metal everywhere, 4) → Etch metal, 2) → Deposit photoresist.