 


ENCS2340 | Section 2 | Fall 2024/2025
Chapter 3-4
Extra Exercises - 01

1. Show logic diagrams for implementing the logic circuit shown (without any modification) using each of the following:



- a. NAND gates Only
b. NOR gates Only

Assume that both the variables and their complements are readily available.

2. Given $F(w, x, y, z) = \Sigma(0, 2, 5, 7, 8, 10, 13, 15)$
- a. Using K-maps, verify that the following are optimized SOP implementations of F and F'
- $$F = xz + \bar{x}\bar{z} \quad , \quad F' = xz + \bar{x}z$$
- b. Use the results in (a) to implement F in each of the following 2-level forms (Give a logic diagram in each case, assuming that both the variables and their complements are readily available):
- i. NAND-AND
 - ii. NOR-OR
 - iii. NAND-NAND
 - iv. NOR-NOR
 - v. AND-OR
 - vi. AND-NOR
 - vii. OR-NAND
 - viii. OR-AND
3. We would like to design a combinational circuit that counts the number of 0s in a 4-bit binary input X (=X₃X₂X₁X₀). The output representing the number of 0s is Y (=...Y₁Y₀). X₀ and Y₀ are the LSBs.
- a. Give the truth table for the circuit
- b. Give an optimized SOP expression for each of circuit outputs using K-maps if required.

4. In the full adder (FA) circuit shown opposite, let propagation delays for the various gates be as follows: OR: 2.5 ns, AND: 2 ns, XOR: 5.5 ns.

4.1. We would like to use the FA given as a building block to implement:


- a. A 1-bit adder
b. A 2-bit ripple-carry adder

The two inputs to an adder are A= ...A₁A₀ and B= ...B₁B₀ and an input carry C_{in} = 0. The Outputs are sum S=...S₁S₀ and an end carry C_{out}.


For each of the two cases above:

- Mark the critical propagation delay path on a circuit diagram of the adder.
- Calculate the time delay for the adder in ns (based on the critical path).

 - 4.2. Calculate the throughput rate (= number of additions per second) for the 2-bit adder.



 5. For the 4-bit 2's complement adder/subtractor circuit shown opposite:



Show all work required to perform the following operations in the 2's complement notation and then complete the missing information in the table below:

	Inputs			Output		Overflow Occurred? (Yes/No)	Is the result correct? (Yes/No)
	A	B	Subtract/Add [O/P = (A-B) or (A+B)]	C4	S (binary)		
a	0010	0101	0				
b	1100	1011	1				
c	0111	1101	0				
d	1100	0110	1				