

Exp3: Network Analysis I


Kirchhoff's Laws & Superposition principle

① Kirchhoff's laws:

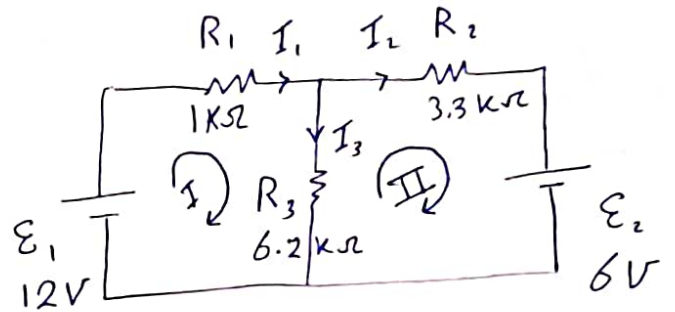i) Junction theorem

$$\sum_i I_i = 0$$

$$I_1 = I_2 + I_3 \quad \dots \textcircled{1}$$



ii) Loop theorem:

$$\sum_i V_i = 0 \quad (\text{in a closed loop})$$

$$\text{loop I: } E_1 - R_1 I_1 - R_3 I_3 = 0 \quad \dots \textcircled{2}$$

$$I_3 R_3 - I_2 R_2 - E_2 = 0 \quad \dots \textcircled{3}$$

To solve for I_1, I_2, I_3 ??

sub. ① in ②

$$E_1 - R_1 (I_2 + I_3) - R_3 I_3 = 0 \quad \dots \textcircled{2}$$

$$\begin{aligned} 12 - (I_2 + I_3) - 6.2 I_3 &= 0 \quad \dots \textcircled{2} \\ 6.2 I_3 - 3.3 I_2 - 6 &= 0 \quad \dots \textcircled{3} \end{aligned}$$

حل بالكند

$$\text{eq ②: } (12 - I_2 - 7.2 I_3 = 0) \times (-3.3) \quad \dots \textcircled{2}$$

$$\begin{aligned} + / \quad & -39.6 + 3.3 I_2 + 23.76 I_3 = 0 \quad \dots \textcircled{2} \\ & -6 - 3.3 I_2 + 6.2 I_3 = 0 \quad \dots \textcircled{3} \end{aligned}$$

$$-45.6 + 29.96 I_3 = 0$$

$$I_3 = 1.52 \text{ mA}$$

Find I_1, I_2 ??

Some Rules :


$$\begin{array}{c} I \rightarrow \text{---} \overset{R}{\text{---}} \text{---} \\ \rightarrow \end{array} \quad - IR$$

$$\begin{array}{c} I \rightarrow \text{---} \overset{R}{\text{---}} \text{---} \\ \leftarrow \end{array} \quad + IR$$

$$\begin{array}{c} \text{---} \overset{\varepsilon}{|} \text{---} \\ \rightarrow \end{array} \quad + \varepsilon$$

$$\begin{array}{c} \text{---} \overset{\varepsilon}{|} \text{---} \\ \leftarrow \end{array} \quad - \varepsilon$$

② Superposition principle :

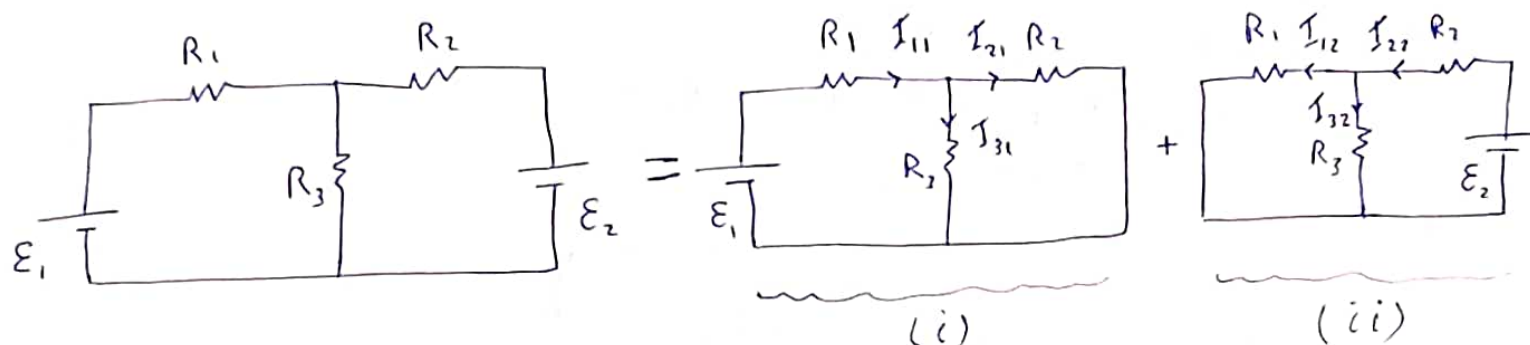

To find I_1, I_2, I_3 using the superposition principle we must find :

$$I_1 = I_{11} + I_{12} \quad (\text{الاتجاهات للاتجاهات})$$

$$I_2 = I_{21} + I_{22}$$

$$I_3 = I_{31} + I_{32}$$


← نفس الاتجاه جمع
← عكس الاتجاه طرح

* Finding I_1 :


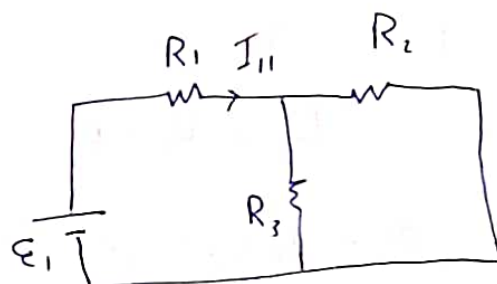
(i) $R_2 \parallel R_3$

$$I_{11} = \frac{\epsilon_1}{R_1 + R_2 \parallel R_3}$$

$$= \frac{\epsilon_1}{R_1 + \frac{R_2 R_3}{R_2 + R_3}} = \frac{12}{1 + \frac{3.3 \times 6.2}{3.3 + 6.2}} = 3.8 \text{ mA } (\rightarrow)$$


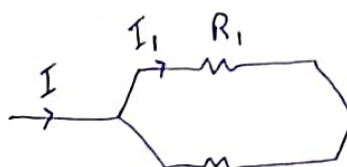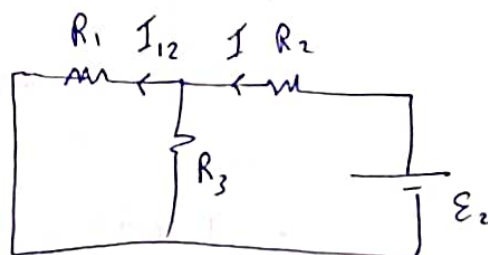
$$(ii) I = \frac{\epsilon_2}{R_2 + R_1 \parallel R_3}$$



جهد الفرع = الجهد قبل التفرع

$$I, R_1 = I (R_1 \parallel R_3)$$


$$R_1 I_{12} = I (R_1 \parallel R_3)$$

$$\begin{aligned} I_{12} &= \frac{\varepsilon_2}{R_2 + \frac{R_1 R_3}{R_1 + R_3}} \cdot \frac{R_1 R_3}{R_1 + R_3} \left(\frac{1}{R_1} \right) \\ &= \frac{6}{3.3 + \frac{1 \times 6.2}{1 + 6.2}} \times \frac{1 \times 6.2}{1 + 6.2} (1) \\ &= 1.24 \text{ mA } (\leftarrow) \end{aligned}$$

$$\begin{aligned} I_1 &= I_{11} - I_{12} \\ &= 3.8 - 1.24 = 2.55 \text{ mA } (\rightarrow) \end{aligned}$$

Finding I_3 :
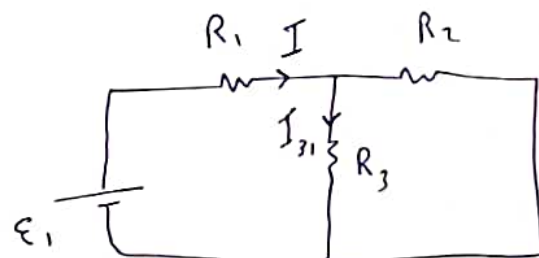
$$(i) \quad I = \frac{\varepsilon_1}{R_1 + R_2 \parallel R_3}$$



جهد التفرع R_3 = الجهد بين التفرع


$$I_{31} R_3 = I (R_2 \parallel R_3)$$

$$\begin{aligned} I_{31} &= \frac{\varepsilon_1}{R_1 + R_2 \parallel R_3} \cdot \frac{(R_2 \parallel R_3)}{R_3} \\ &= \frac{12}{1 + \frac{3.3 \times 6.2}{3.3 + 6.2}} \left(\frac{3.3 \times 6.2}{3.3 + 6.2} \right) \left(\frac{1}{6.2} \right) \\ &= 1.32 \text{ mA } (\downarrow) \end{aligned}$$

$$(ii) \quad I = \frac{\varepsilon_2}{R_2 + R_1 // R_3} = \frac{6}{3.3 + \frac{1 \times 6.2}{1 + 6.2}} = 1.44 \text{ mA}$$

$$I_{32} R_3 = I (R_1 // R_3)$$
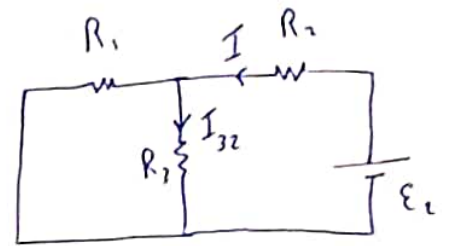
$$I_{32} = \frac{1.44}{6.2} \left(\frac{1 \times 6.2}{1 + 6.2} \right) = 0.2 \text{ mA} (\downarrow)$$



$$I_3 = I_{31} + I_{32} \\ = 1.32 + 0.2 = 1.52 \text{ mA} (\downarrow)$$

In the same way find I_2 !!