

L3  
part 2  
sec 2  
8/7/2021

# **ENEE2360**

## **Analog Electronics**

### **T2:**

### **Semiconductor**

### **Diodes and Diode**

### **Models**

**Instructor: Nasser Ismail**

# Diode Operating Conditions/Modes

A diode has three operating Modes:

- 1) No bias
- 2) Reverse bias
- 3) Forward bias


→ external  
voltage  
source

ENEE236 – Analog Electronics

# Diode Operating Modes

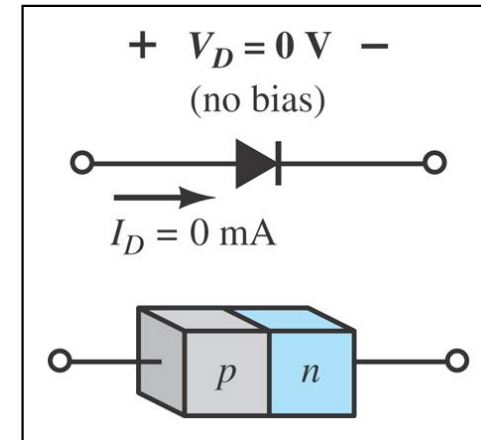
## 1) No Bias Condition

- No external voltage is applied:  $V_D = 0 \text{ V}$
- There is no diode current:  $I_D = 0 \text{ A}$
- Only a modest depletion region exists



## 2) Reverse Bias Condition

- External voltage is applied across the  $p$ - $n$  junction in the opposite polarity of the  $p$ - and  $n$ -type materials.

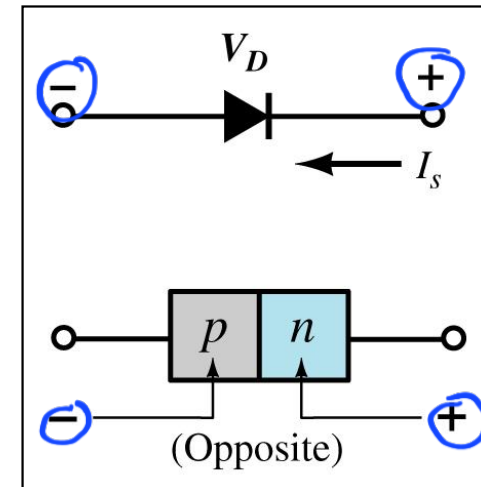


ENEE236 – Analog Electronics

# Diode Operating Modes

## Reverse Bias

- The reverse voltage causes the depletion region to widen.
- The electrons in the  $n$ -type material are attracted toward the positive terminal of the voltage source.
- The holes in the  $p$ -type material are attracted toward the negative terminal of the voltage source.


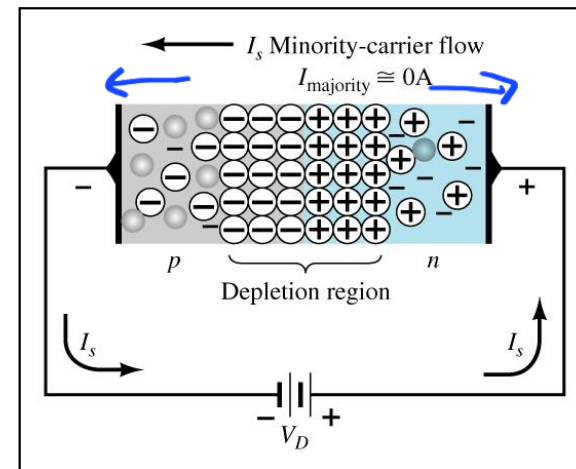


ENEE236 – Analog Electronics

# Diode Operating Modes
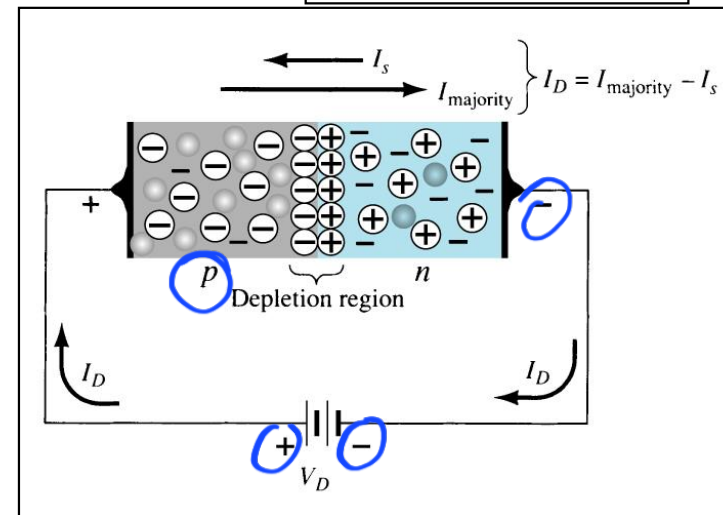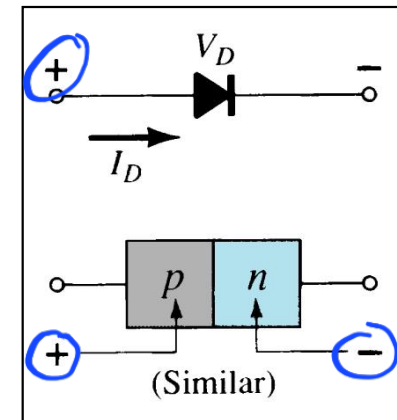
## 3) Forward Bias Condition


- External voltage is applied across the  $p$ - $n$  junction in the same polarity as the  $p$ - and  $n$ -type materials.
- The forward voltage causes the depletion region to narrow.
- The electrons and holes are pushed toward the  $p$ - $n$  junction.
- The electrons and holes have sufficient energy to cross the  $p$ - $n$  junction.



## Actual Diode Characteristics

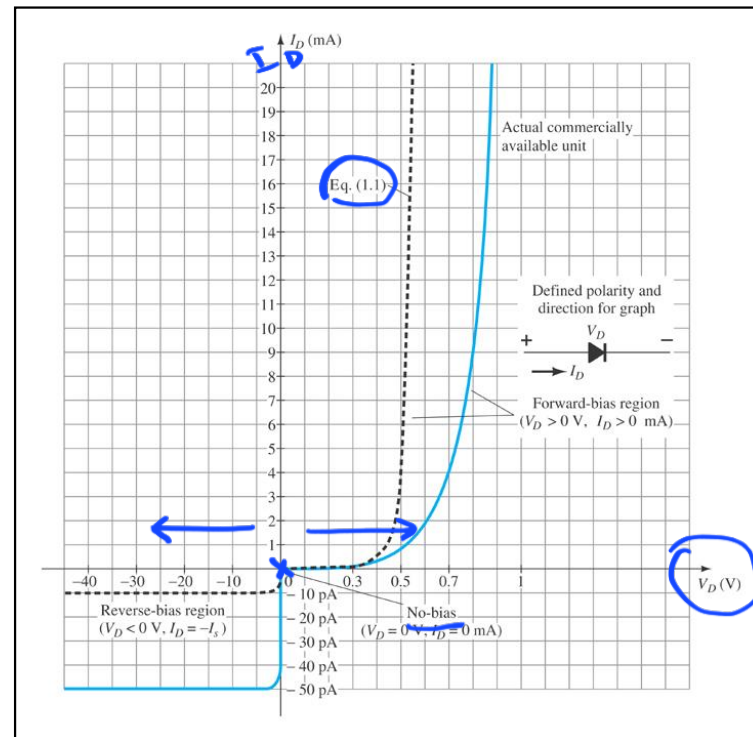**Note the regions for no bias, reverse bias, and forward bias conditions.**

Carefully note the scale for each of these conditions.



## ENEE236 – Analog Electronics


# Zener Region (Breakdown Region)

The Zener region is in the diode's reverse-bias region.

At some point the reverse bias voltage is so large the diode breaks down and the reverse current increases dramatically.

The maximum reverse voltage that won't take a diode into the zener region is called the **peak inverse voltage** or **peak reverse voltage**.

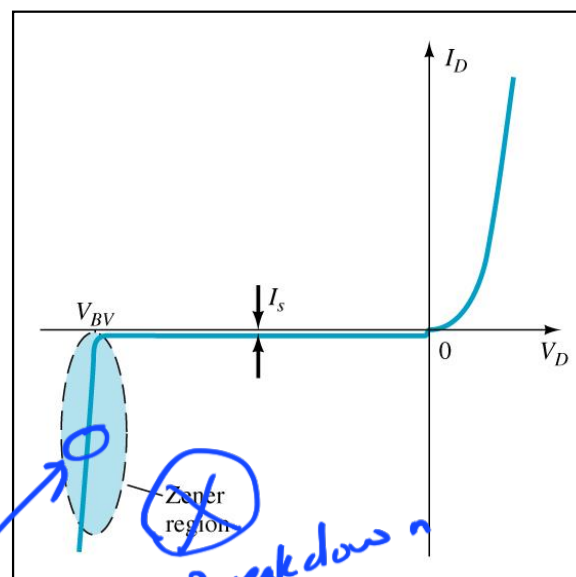The voltage that causes a diode to enter the zener region of operation is called the **zener voltage ( $V_Z$ )** or **reverse breakdown voltage ( $V_{BV}$ )**.



$I \uparrow$

$I^2 R \uparrow$ , heat, damage of Diode

# Forward Bias Voltage

The point at which the diode changes from no-bias condition to forward-bias condition occurs when the electrons and holes are given sufficient energy to cross the p-n junction. This energy comes from the external voltage applied across the diode.

The forward bias voltage required for a:

**gallium arsenide diode  $\cong 1.2\text{ V}$**

\*  $\rightarrow$  **silicon diode  $\cong 0.7\text{ V}$**

**germanium diode  $\cong 0.3\text{ V}$**






ENEE236 – Analog Electronics

# Temperature Effects

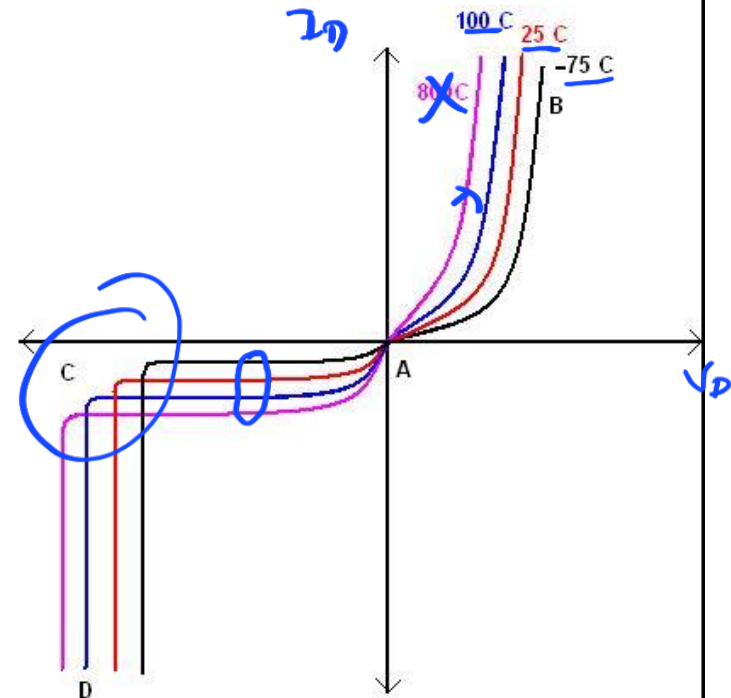**As temperature increases it adds energy to the diode.**

- It reduces the required forward bias voltage for forward-bias conduction.
- It increases the amount of reverse current in the reverse-bias condition.
- It increases maximum reverse bias avalanche voltage.



$$P = I^2 R$$

***Germanium diodes are more sensitive to temperature variations than silicon or gallium arsenide diodes.***

# Diode Internal Resistance




Semiconductors react differently to DC and AC currents.

*There are three types of resistance:*

**DC (static) resistance**

**AC (dynamic) resistance** ✓✓

**Average AC resistance**

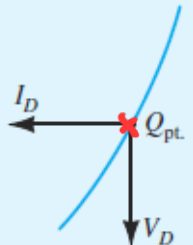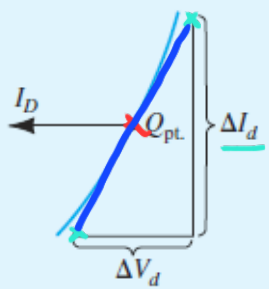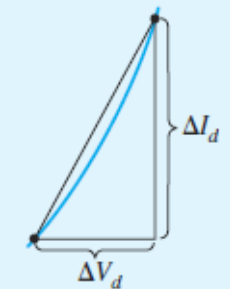Resistance Levels			
Type	Equation	Special Characteristics	Graphical Determination
DC or static	$R_D = \frac{V_D}{I_D}$	Defined as a point on the characteristics	
AC or dynamic	$r_d = \frac{\Delta V_d}{\Delta I_d} = \frac{26\text{ mV}}{I_D} = V_T$	Defined by a tangent line at the Q-point	
Average ac	$r_{av} = \frac{\Delta V_d}{\Delta I_d} \Big _{\text{pt. to pt.}}$	Defined by a straight line between limits of operation	

# Diode Equation

$$i_D(t) = I_S \left( e^{\frac{V_D(t)}{\eta V_T}} - 1 \right)$$


$I_S$ : Reverse saturation current

$I_S = 10^{-12}, 10^{-14} \text{ A}$

$\eta$  : eta       $1 \leq \eta \leq 2$

for example
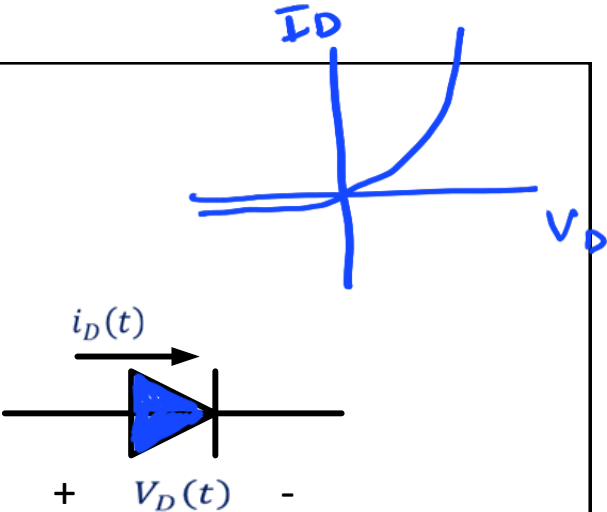
$$\eta = \begin{cases} 1 & \text{for Ge} \\ 2 & \text{for Si (small current)} \\ 1 & \text{for Si (large current)} \end{cases}$$



$V_T$  = Thermal Voltage

$V_T = \frac{T}{11600}$  ; T in kelvin

At Room Temp.  $T = 300\text{ k}$   
*Handwritten: 25°C, 298*

$\therefore V_T = 25.69\text{ mv}$  at Room Temp.

- The equation is a non linear equation
- $\therefore$  The Diode is non linear Device


► For positive  $V_D(t)$ ,

$i_D(t) = I_S(e^{\frac{V_D(t)}{\eta V_T}})$


► For negative  $V_D(t)$

$i_D(t) = -I_S$

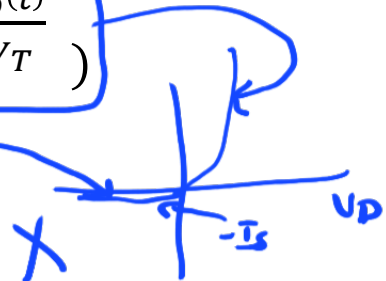
~~$i_D(t) = I_S(e^{\frac{V_D(t)}{\eta V_T}} - 1)$~~   
*Handwritten: < 1*



# Diode V-I Characteristic curve

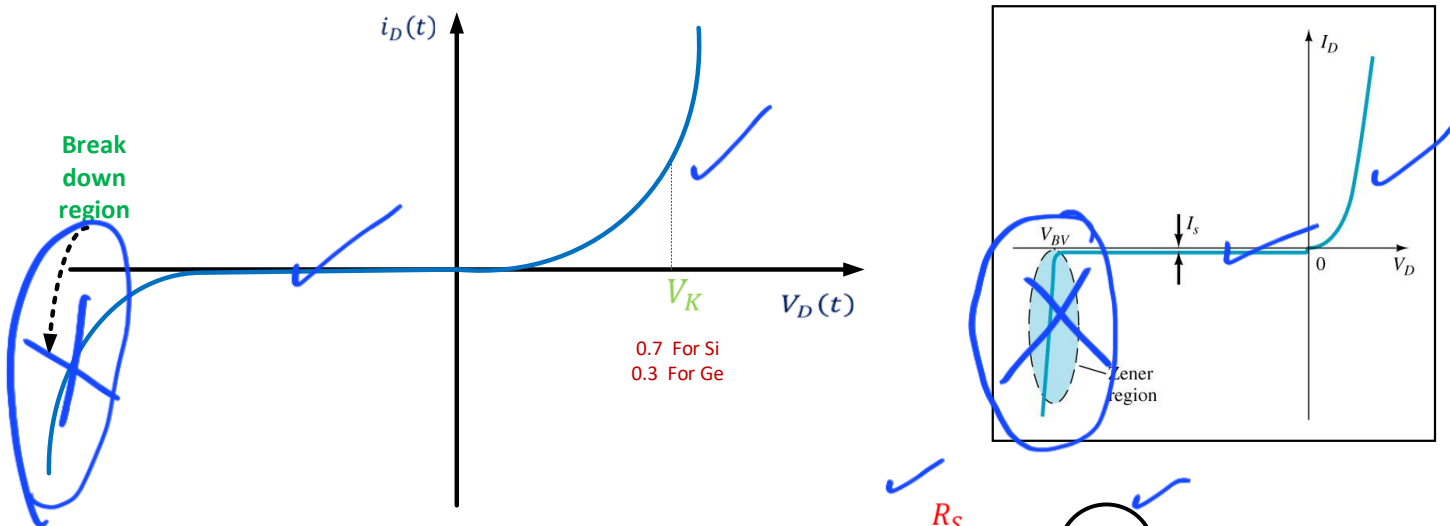

Practical circuit to measure diode curve

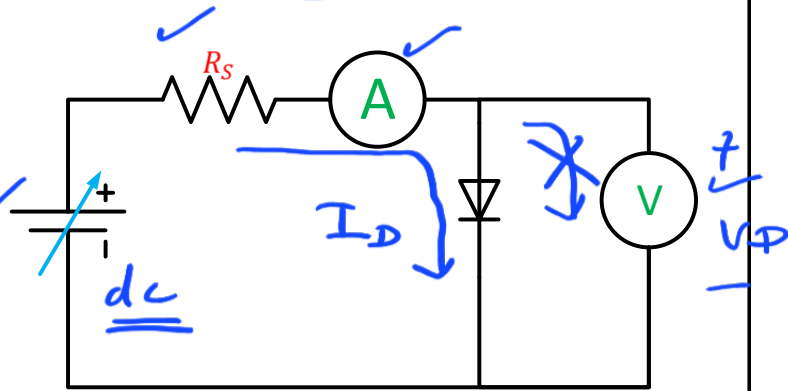

## Approaches to Diode Circuit Analysis

The rectifier diode is a non linear device.


Find  $I_D$  ?  
 $V_D$  ?

There are essentially **three** basic approaches to the solution of such problem :

- 1- The use of non linear mathematics ✗
- 2- The use of graphical techniques ✓
- 3- The use of equivalent circuit (models) ✓✓✓ \*

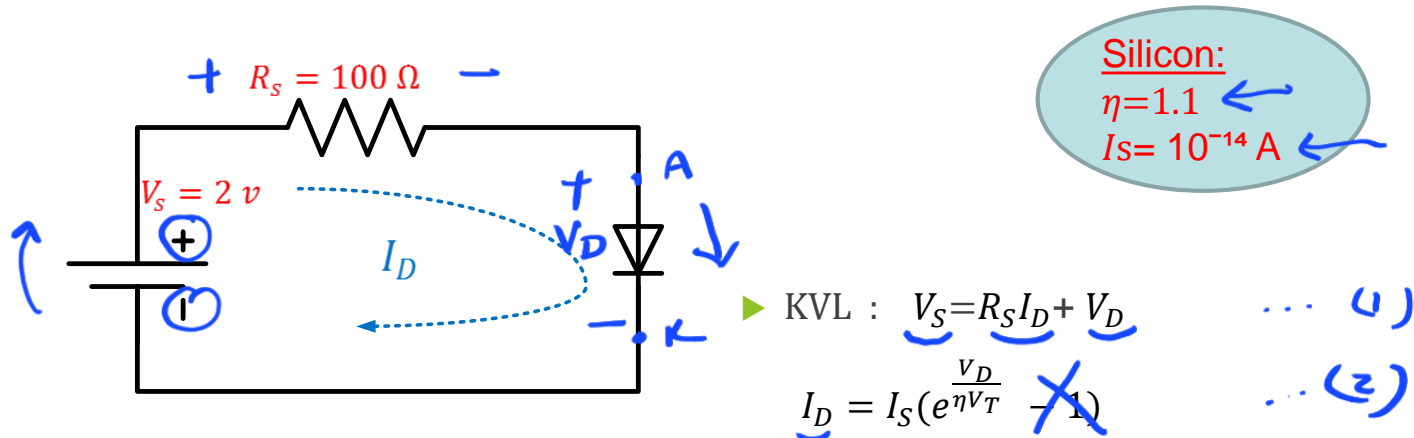1)The use of non linear mathematic (shown , but not required)

► For the circuit shown, find  $I_D$  and  $V_D$



► Since the diode is **forward biased** , we could approximate


$$I_D = I_S (e^{\frac{V_D}{\eta V_T}}) \rightarrow \frac{I_D}{I_S} = e^{\frac{V_D}{\eta V_T}}$$
$$\ln \frac{I_D}{I_S} = \frac{V_D}{\eta V_T}$$

► Solving for  $V_D = \eta V_T \ln \frac{I_D}{I_S}$  ...



∴ We have two equations and two unknowns

$$V_S = R_S I_D + V_D \dots\dots\dots 1$$

$$V_D = \eta V_T \ln \frac{I_D}{I_S} \dots\dots\dots 2$$


$$\therefore V_S = R_S I_D + \eta V_T \ln \frac{I_D}{I_S} \quad \checkmark$$

● **non linear equation**

# Iterative Analysis

1) Let  $V_D = 0.7\text{V}$

$$I_D = \frac{2 - 0.7}{0.1k} = 13\text{ mA}$$

$V_D = 0.7882392\text{V}$       The error is large

→ 2) Let  $V_D = 0.7882392\text{V}$

$$I_D = 12.117608\text{ mA}$$

$V_D = 0.7862529\text{V}$       The error is small

2)

$$I_D = \frac{V_S - V_D}{R_S}$$

3)

$$V_D = \eta V_T \ln \frac{I_D}{I_S}$$

$$\frac{0.088}{0.7}$$

$$\frac{0.0020}{0.788}$$

3) Let  $V_D = 0.7862529\text{V}$

$$I_D = 12.137471 \text{ mA}$$

$V_D = 0.7862991 \text{ V}$       The error getting smaller

4) Let  $V_D = 0.7862991 \text{ V}$

$$V_D = 0.786298066 \text{ V}$$

$$I_D = 12.137009 \text{ mA}$$

$$I_D = 12.137 \text{ mA}$$

$$V_D = 0.7863 \text{ V}$$

للعلم فقط

# 2) The use of graphical techniques



(Requires the V-I exact plot)\*\*

✓ ✓ ? ?  
 $V_S = R_S I_D + V_D$

$I_D = I_S \left( e^{\frac{V_D}{\eta V_T}} - 1 \right)$

- Using equation 1
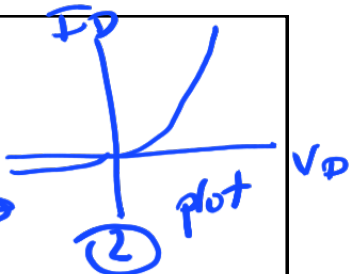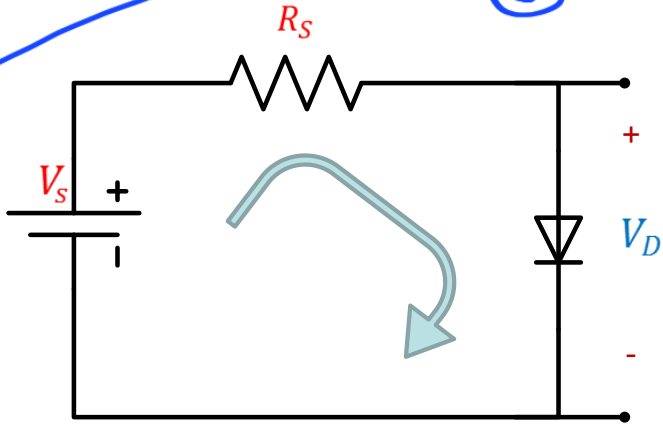
$$I_D = -\frac{1}{R_S} V_D + \frac{V_S}{R_S}$$




$I_D = f(V_D) \dots$  plot

$$I_D = \frac{V_S - V_D}{R_S}$$
$$= \frac{V_S}{R_S} - \frac{V_D}{R_S}$$

$I_D = f(V_D)$


$$I_D = -\frac{1}{R_S} V_D + \frac{V_S}{R_S}$$

Drawing the two equations

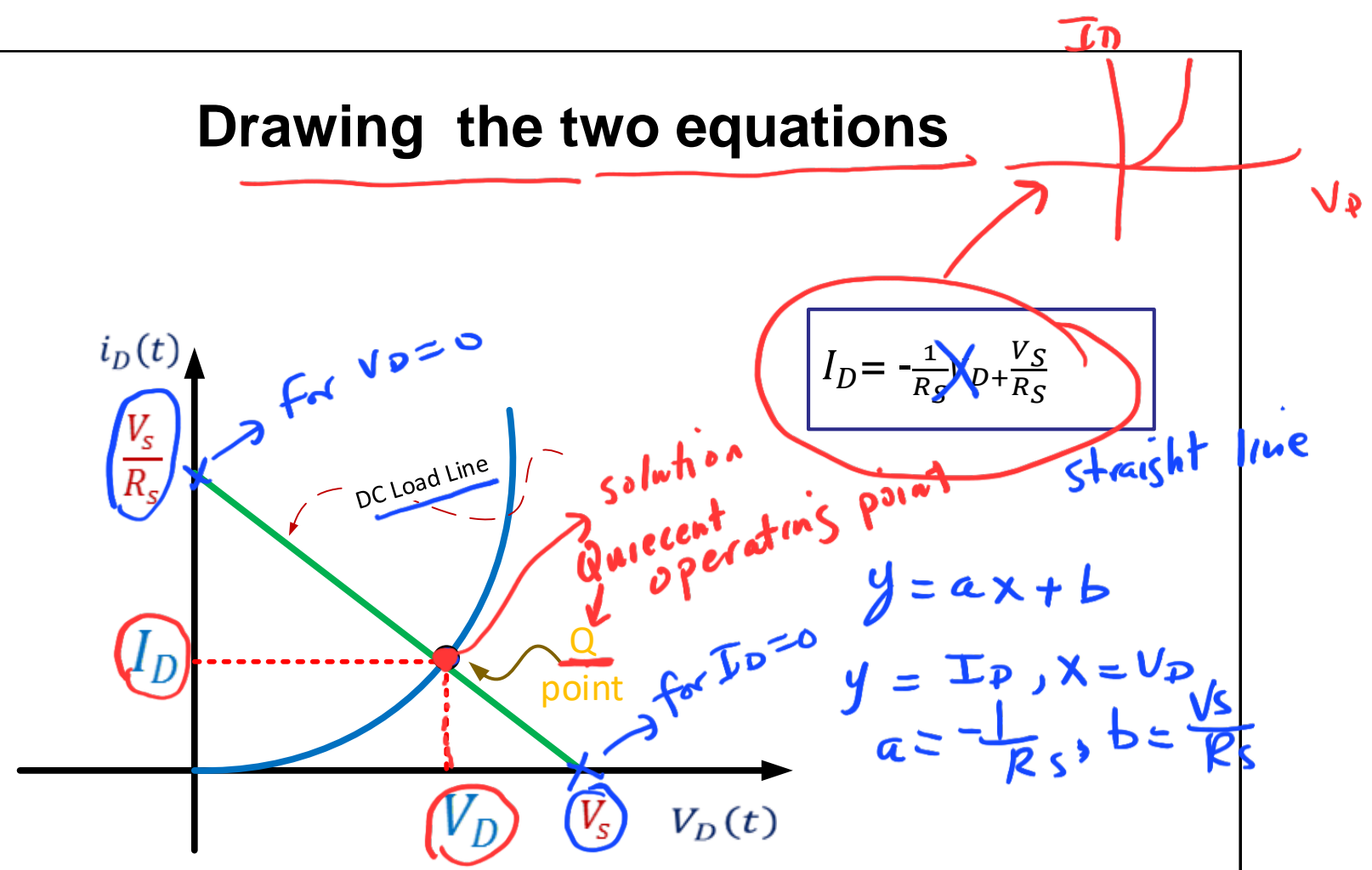


•  $Q_{\text{point}} = (V_{DQ}, I_{DQ}) = Q_{\text{uiacent point}}$

The effect of Rs on the Qpoint

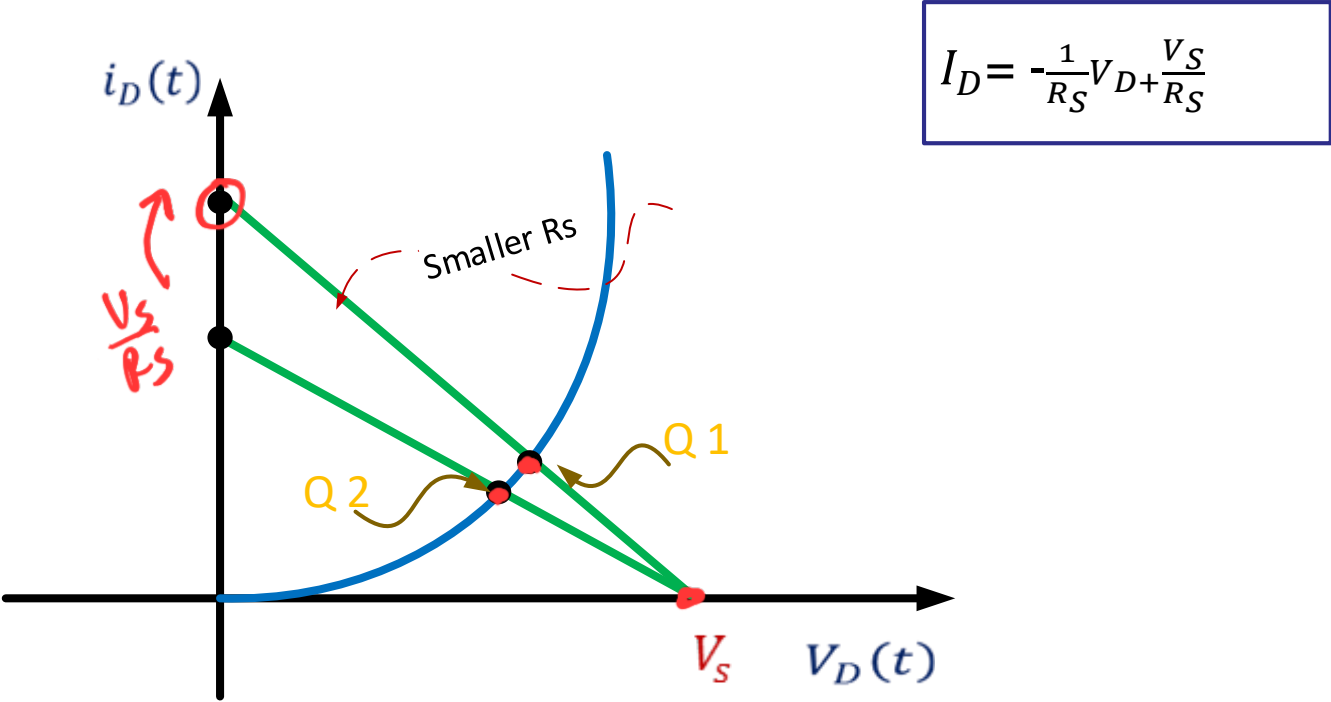



# The effect of Vs on Qpoint

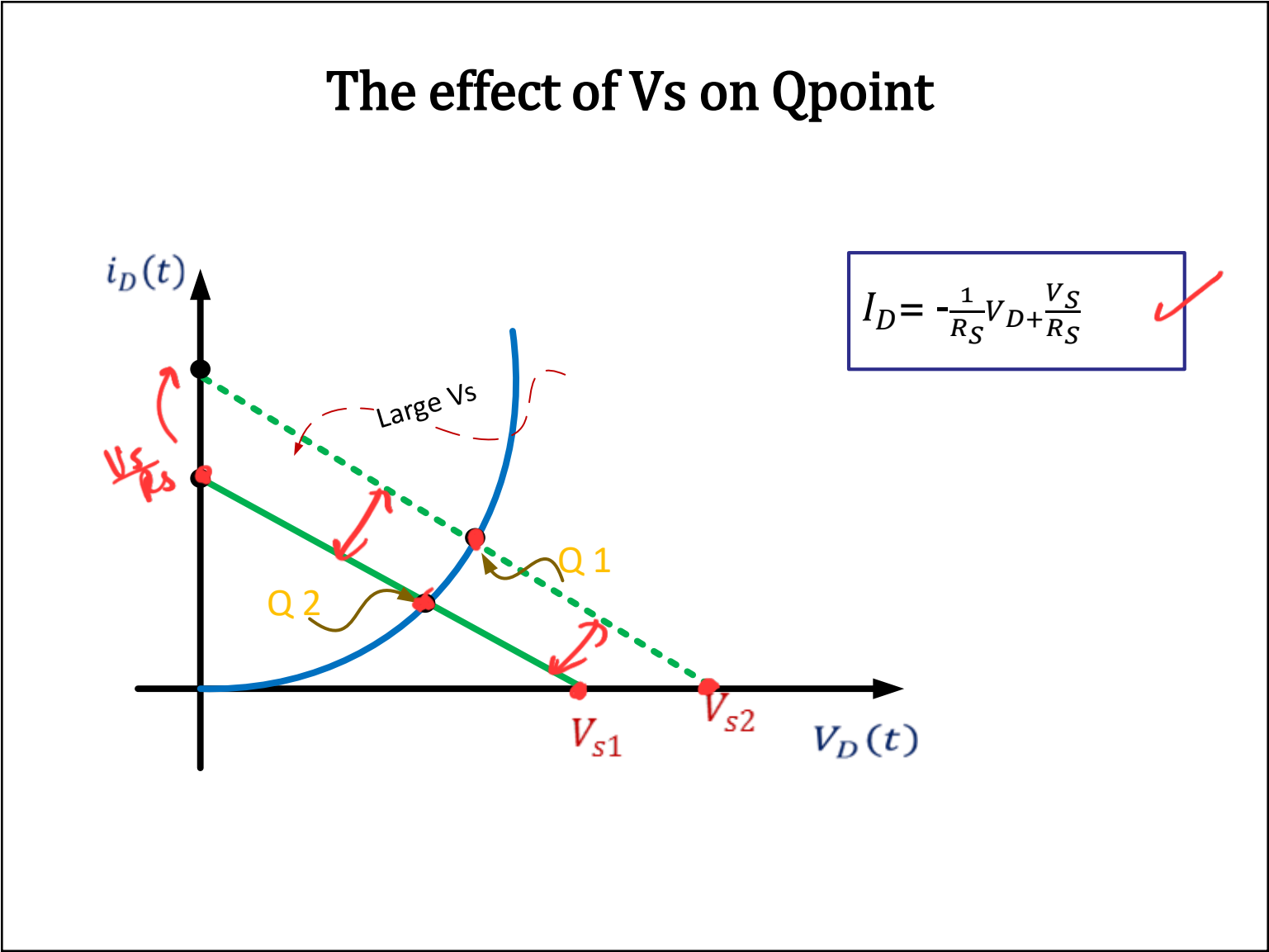

ENEE236 – Analog Electronics

## Diode (Models) \*\*\*

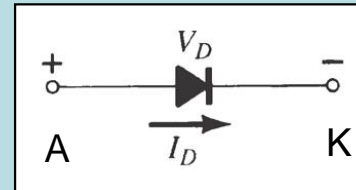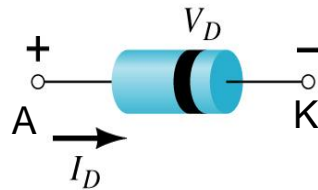- 1) Ideal Diode Model ✓✓
- 2) Simplified/piecewise/ knee model ✓✓  
*Linear*
- 3) Complete diode model ✗ *practical Model*




- Forward  
- Reverse

?




# Ideal Diode Model

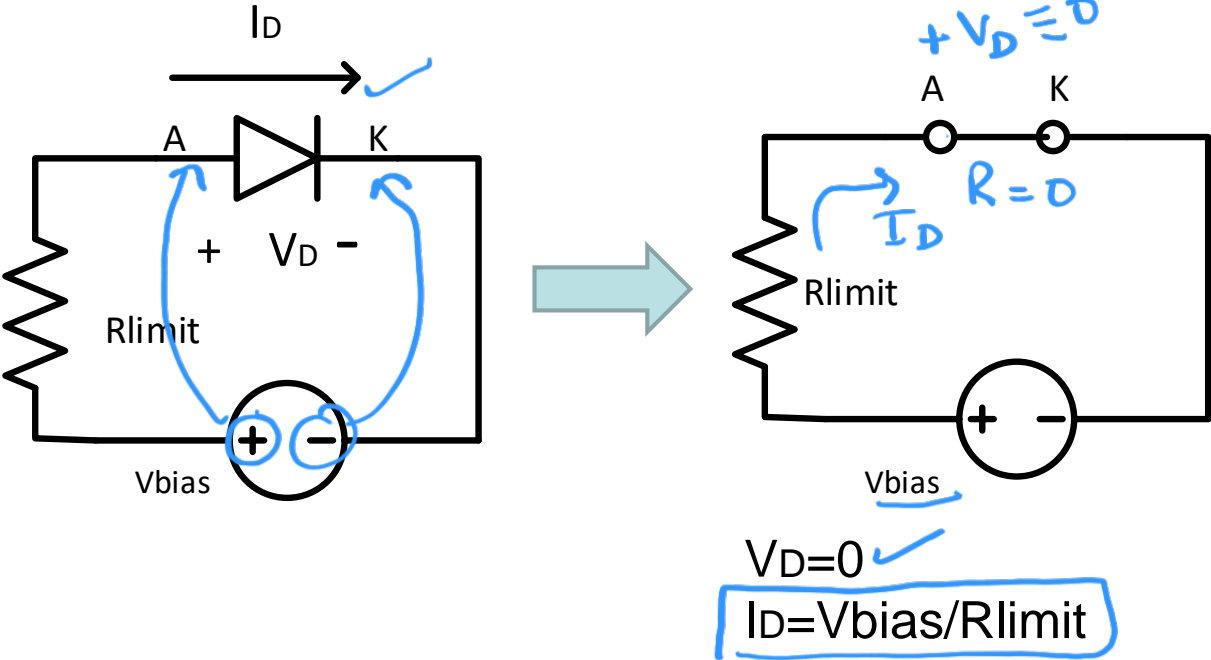- 1) if the diode is forward biased ==> diode is replaced by short circuit




# Ideal Diode Model

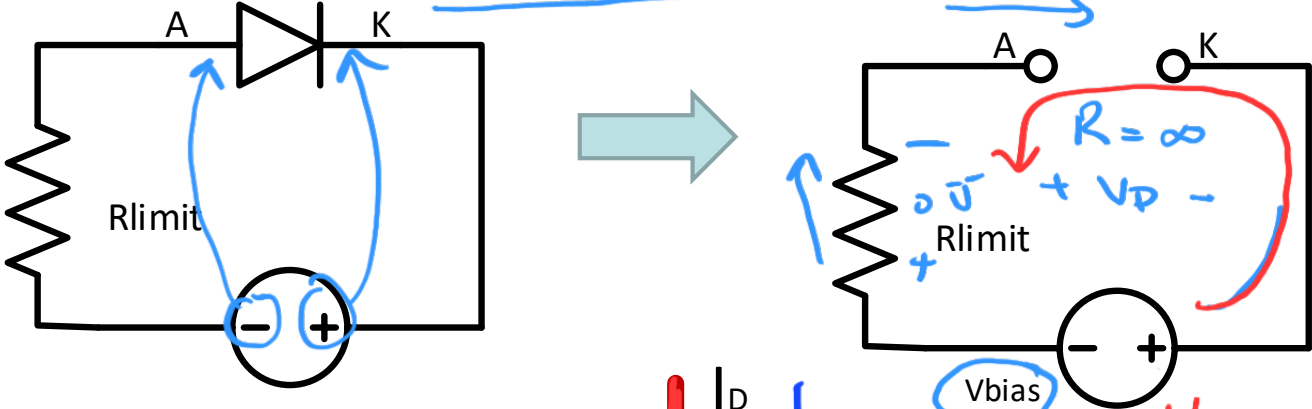- 2) if the diode is Reverse biased ==> diode is replaced by open circuit



$V_{Bias} + V_D = 0$

$V_D = -V_{bias}$   
 $I_D = 0$

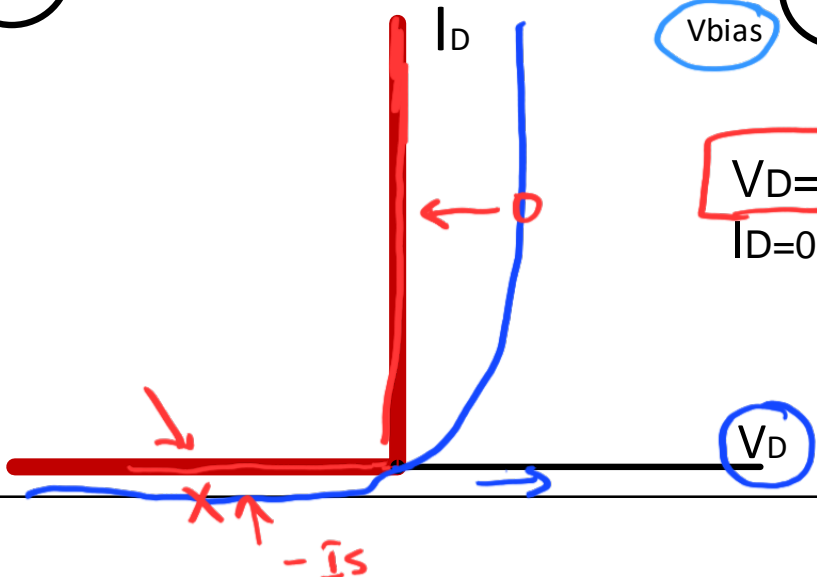


ENEE236 – Analog Electronics

# Simplified / knee model

*Practical*

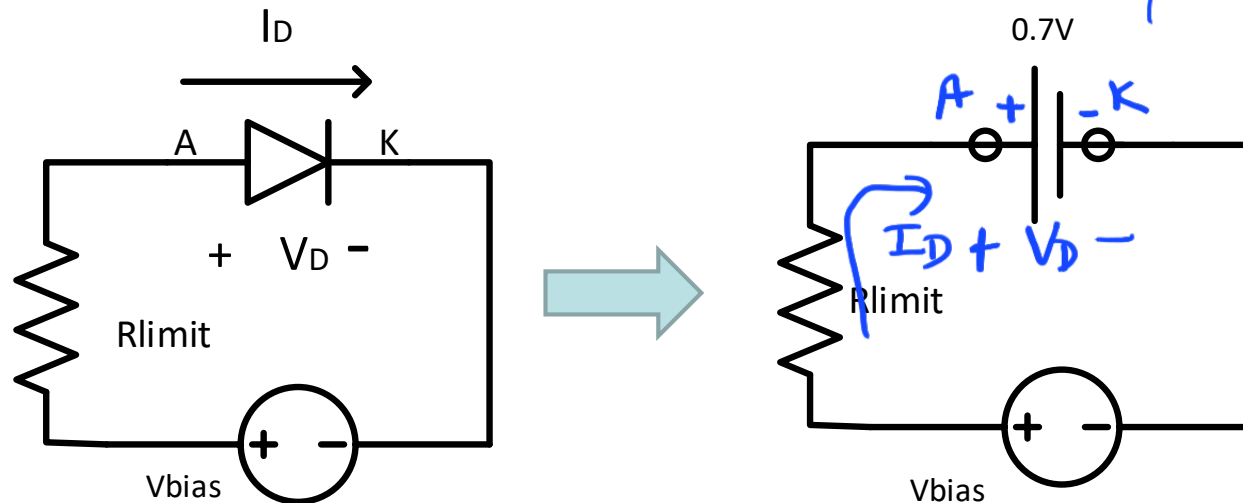- 1) if the diode is forward biased ==> diode is replaced by a 0.7V battery (for Si)




$$V_D = 0.7 \text{ V}$$

$$I_D = (V_{bias} - 0.7) / R_{limit}$$

ENEE236 – Analog Electronics


# Simplified/ knee model

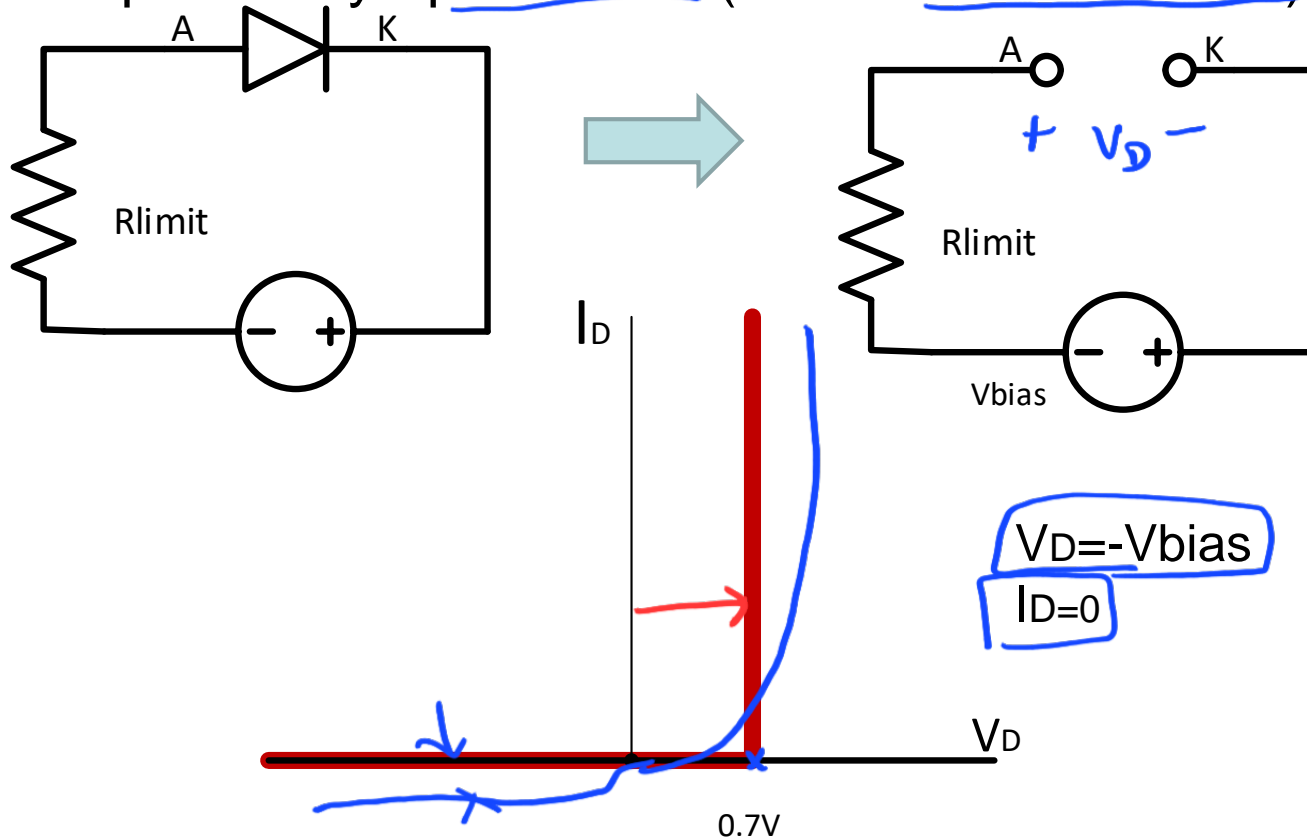- 2) if the diode is Reverse biased ==> diode is replaced by open circuit (same as ideal model)



## Complete Diode model

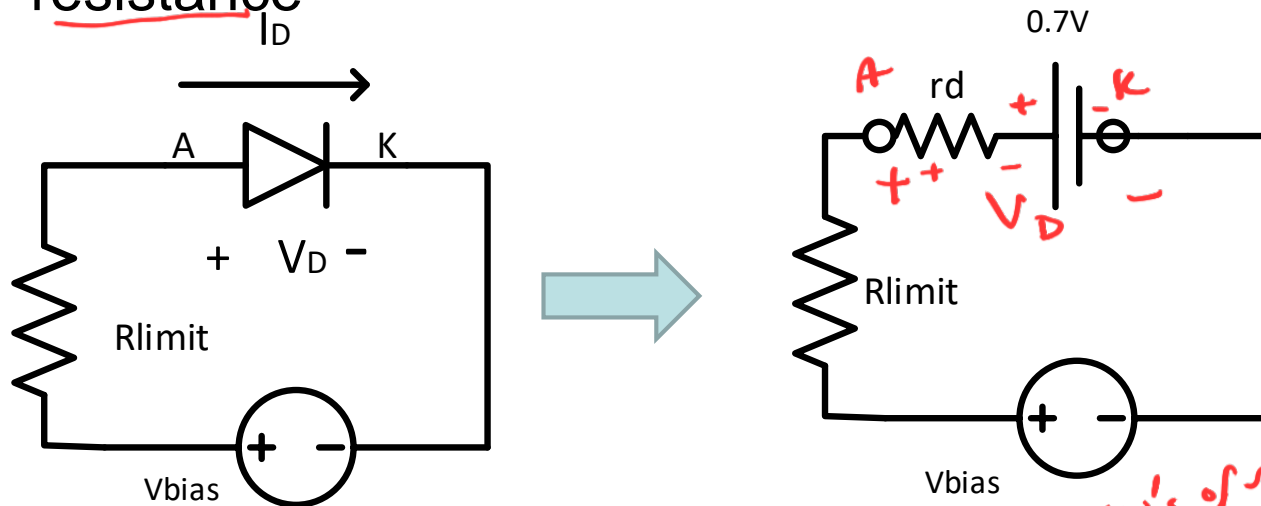- 1) if the diode is forward biased ==> diode is replaced by a 0.7V battery and forward dynamic resistance






$$V_D = 0.7 + I_D \cdot r_d$$

$$I_D = (V_{bias} - 0.7) / (R_{limit} + r_d)$$

100's of  $\Omega$ 's  
small  $\Omega$ 's

# Complete Diode model

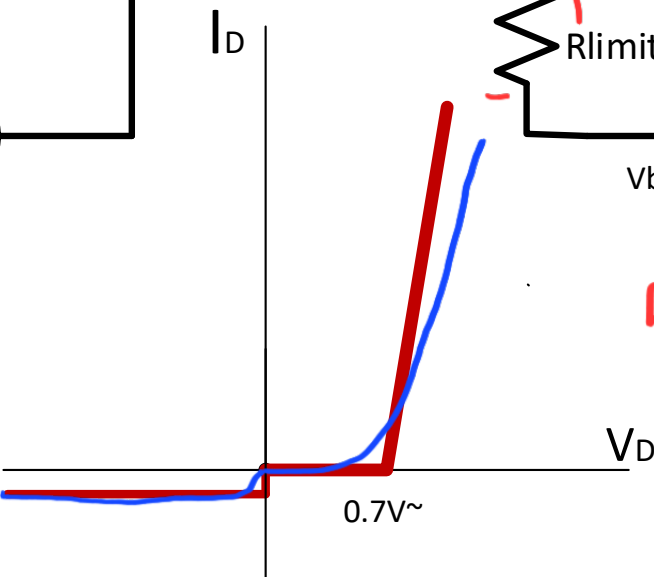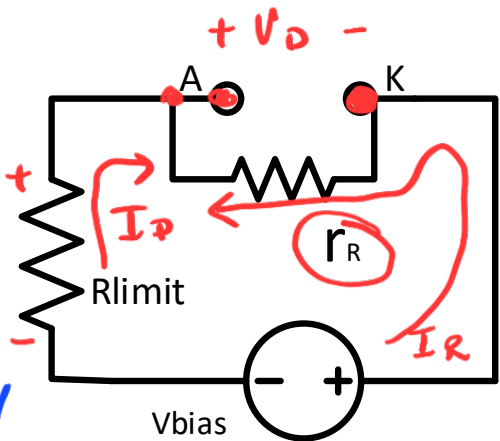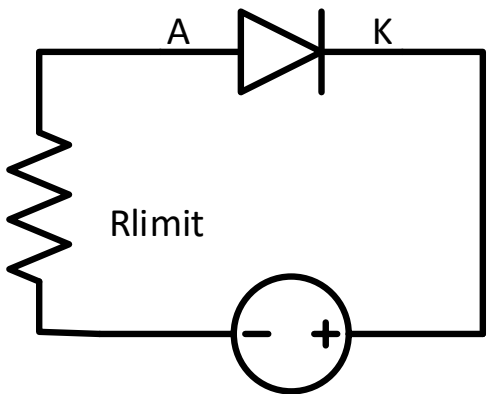- 2) if the diode is Reverse biased ==> diode is replaced by open circuit // to reverse resistance  $r_R$



$+V_D -$

not  $r_d$

$r_R$

$V_{bias}$

$V_D \approx -V_{bias}$

$I_D = -I_R$

$r_R \gg R_{limit}$

Mos

$V_{bias} + V_D - I_R \cdot R_{limit} = 0$

ENEE236 – Analog Electronics

Example:

Find the Q-point ( $I_{DQ}$  and  $V_{DQ}$ )



- a) Use ideal diode model
- b) Use practical diode model
- c) Use exact model

Solution

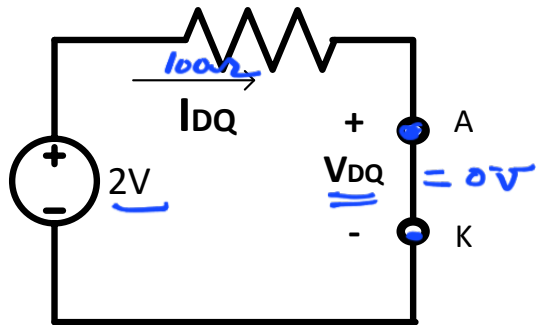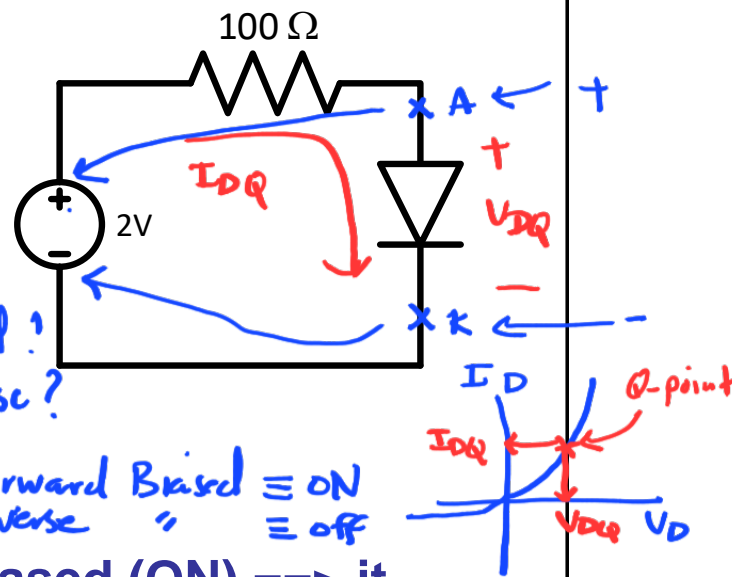a) Since  $V_A > V_K$ , diode is forward biased (ON) ==> it can be replaced by a short circuit

$V_{DQ} = V_{AK} = 0\text{ V}$

$I_{DQ} = 2\text{V} / 100\ \Omega = 20\text{ mA}$




# ENEE236 – Analog Electronics

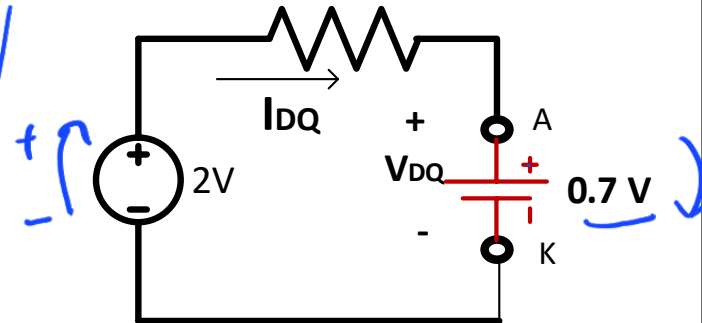b) When using practical model, diode is replaced by a 0.7 V battery

$$V_{DQ} = V_{AK} = 0.7 \text{ V}$$

$$I_{DQ} = (2 - 0.7) / 100 = 13 \text{ mA}$$



c) Exact solution yields

$$V_{DQ} = V_{AK} = 0.786 \text{ V}$$

$$I_{DQ} = 12.14 \text{ mA}$$

$\sim 0.7 \text{ V}$

Note: If applied voltage is much higher than  $V_{AK}$  ( at least 10 times), then ideal diode model is recommended



ENEE236 – Analog Electronics

Example:

Find the Q-point  
( $I_{DQ}$  and  $V_{DQ}$ )

Solution



It is better to convert the two loop circuit to a single loop circuit by finding Thevenin's equivalent circuit

$V_{TH}=6V. \frac{20k}{(20k+10k)}=4 V$

$R_{TH}=(10k+(\frac{20k}{10k}))=16.67 k\Omega$


$V_{DQ}=V_{AK}=0.7 V$

$I_{DQ}= \frac{(4-0.7)}{16.67 k\Omega} = 0.198 mA$

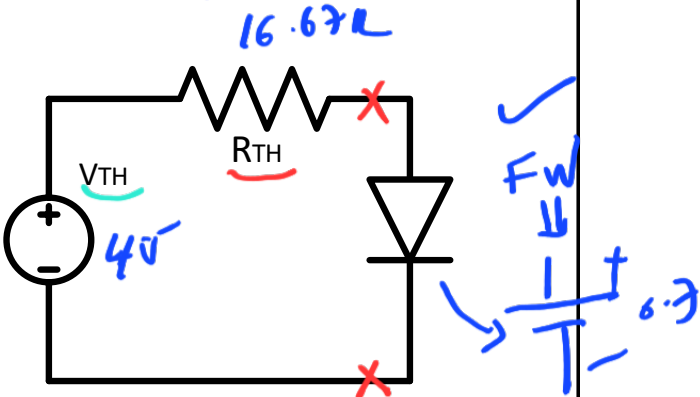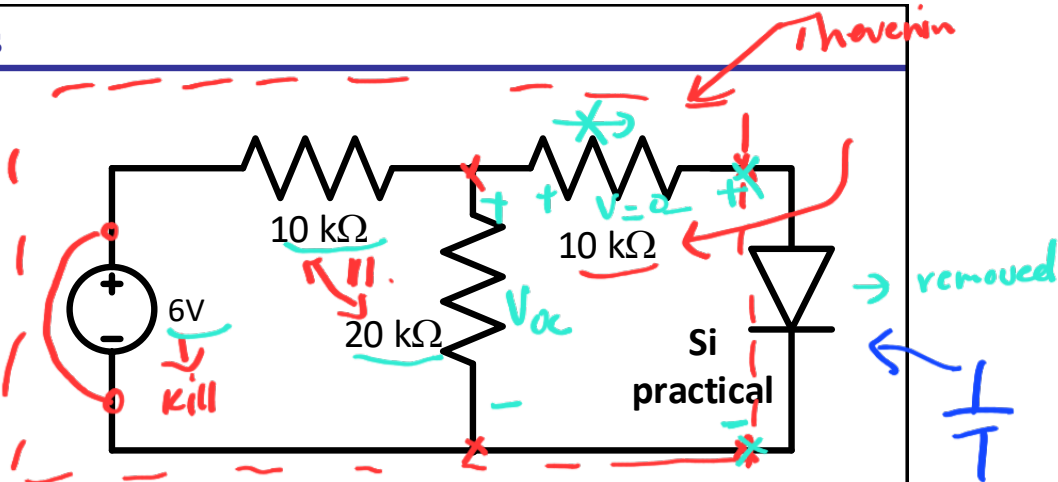


ENEE236 – Analog Electronics

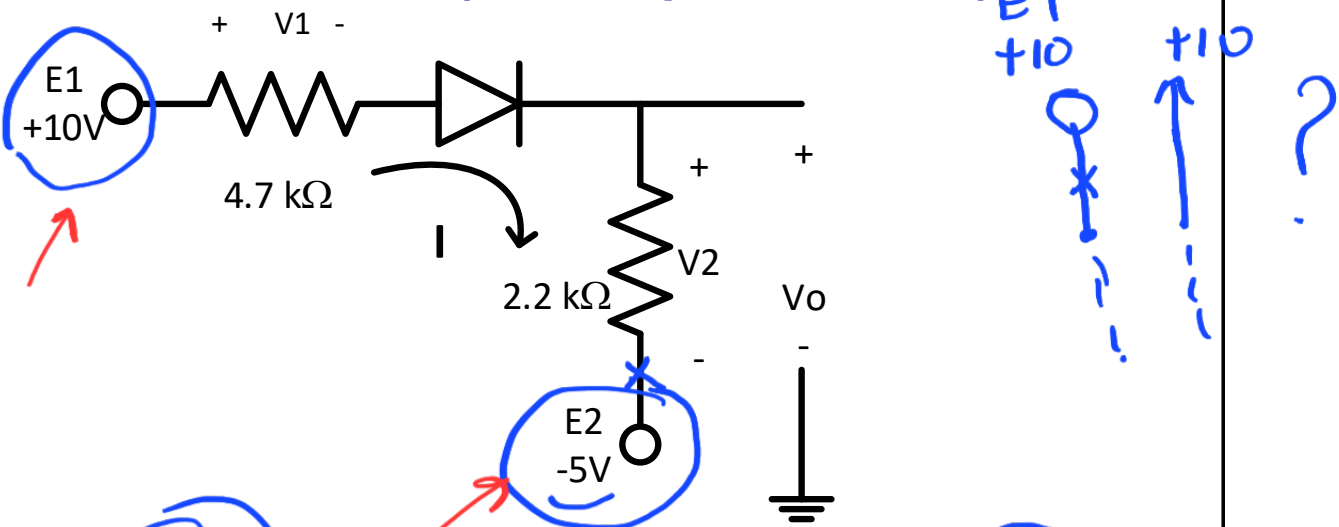Example: Find  $I, V_1, V$  and  $V_o$  (use simplified model)



Solution:

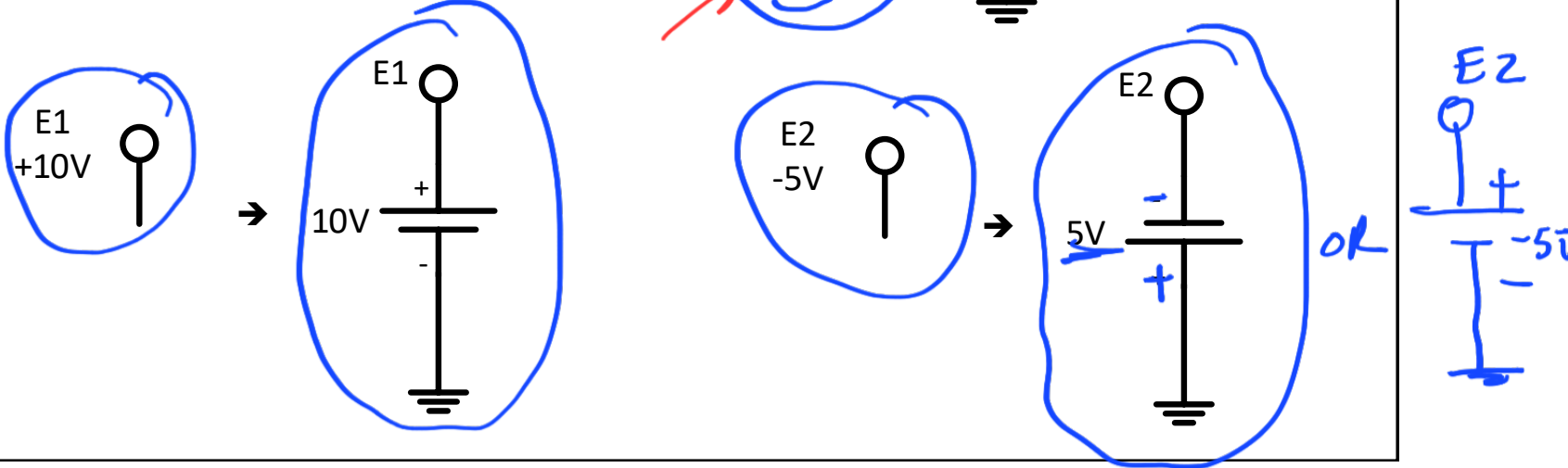

ENEE236 – Analog Electronics


Handwritten notes on the diagram:

- ? → forward Biased
- Diode is Forward biased
- Since  $V_A > V_K$
- $10 + 5 = I \cdot 4.7k + 0.7 + I \cdot 2.2k$
- $I = \frac{15 - 0.7}{6.9k} = 2.07mA$
- $V_1 = I \cdot R_1 = 9.73V = 2.07m \times 4.7k$
- $V_2 = I \cdot R_2 = 4.55V = 2.07m \times 2.2k$
- $V_o = V_2 - 5 = -0.45V$


**Find  $I_1$ ,  $I_2$ ,  $I_{D2}$  (use practical diode model)**

Applied voltage is suitable for forward biasing both diodes

$$= 3.11 \text{ mA}$$

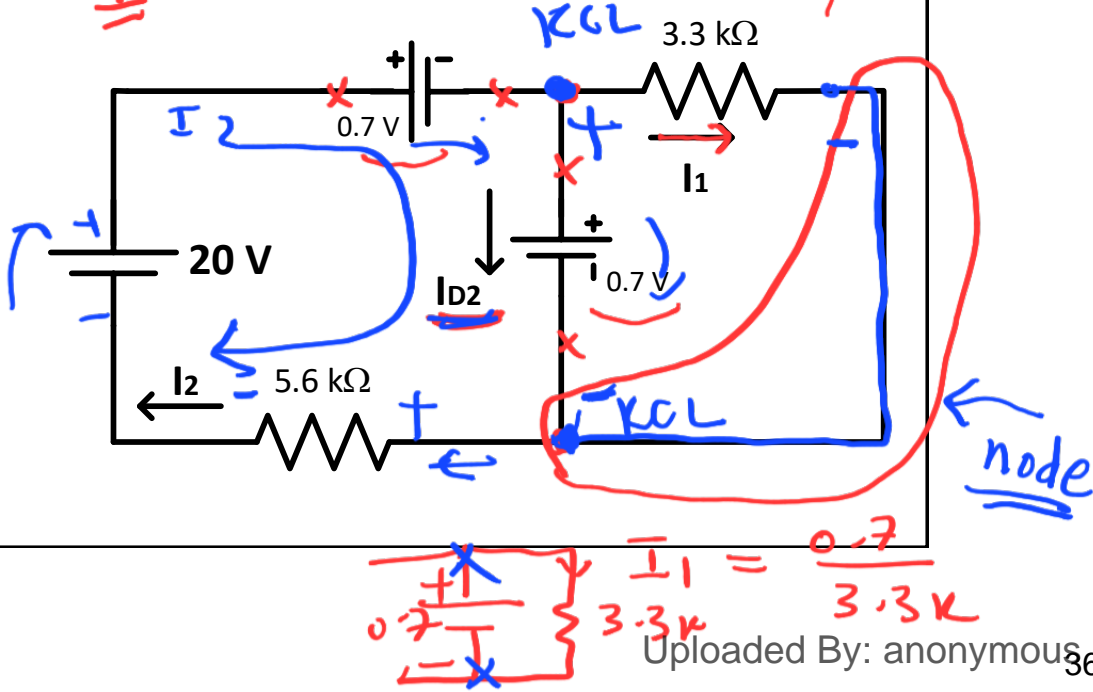


# Diode Specification Sheets

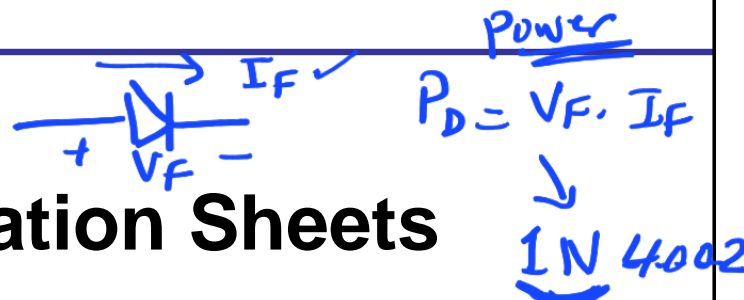

*Diode data sheets contain standard information, making cross-matching of diodes for replacement or design easier.*

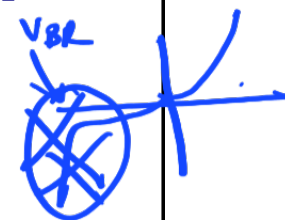1. Forward Voltage ( $V_F$ ) at a specified current and temperature
2. Maximum forward current ( $I_F$ ) at a specified temperature
3. Reverse voltage rating, PIV or PRV or  $V_{(BR)}$ , at a specified temperature  
*peak inverse voltage*  
*reverse*
4. Maximum power dissipation at a specified temperature
5. Reverse saturation current ( $I_R$ ) at a specified voltage and temperature
6. Capacitance levels
7. Reverse recovery time,  $t_{rr}$
8. Operating temperature range



## Other Types of Diodes

There are several types of diodes besides the standard  $p$ - $n$  junction diode. Three of the more common are:

Zener diodes

Light-emitting diodes


## ENEE236 – Analog Electronics

# Zener Diode (explained in 45) <sup>T5</sup>

A **Zener diode** is one that is designed to safely operate in its zener region; i.e., biased at the Zener voltage ( $V_Z$ ).


Common zener diode voltage ratings are between 1.8 V and 200 V

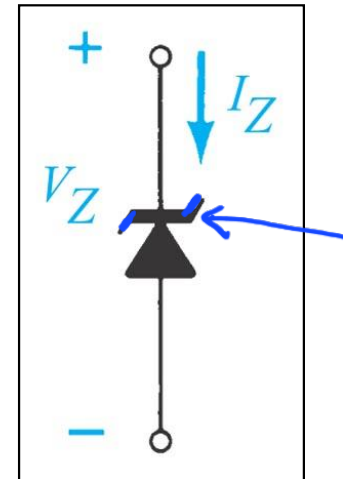The **Zener diode** is used mainly for voltage regulation, details will be discussed later


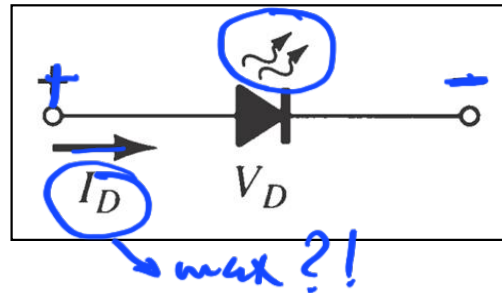
# Light-Emitting Diode (LED)

An **LED** emits light when it is forward biased,  
which can be in the infrared or visible spectrum.



The forward bias voltage is usually  
in the range of 2 V to 3 V. ←



End of T3

L4 - part 1

13/7/2021