

1. L PF

RL

$$H(s) = \frac{R/L}{s + R/L}$$

$$s = j\omega$$

$$\omega_c = \frac{R}{L} = 2\pi f$$


$$H(j\omega) = \frac{\omega_c}{j\omega + \omega_c}$$

$$|H(j\omega)| = \frac{R/L}{\sqrt{\omega^2 + (R/L)^2}}$$

$$R/L = \omega_c$$

$$\theta = -\tan^{-1}\left(\frac{\omega L}{R}\right) = -\tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

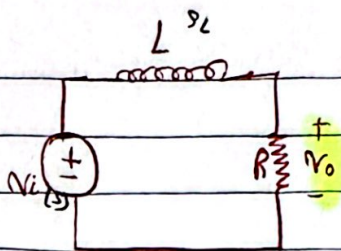

2. RC

$$H(s) = \frac{1}{cs} \cdot \frac{1}{R + \frac{1}{cs}}$$

$$H(s) = \frac{1}{RC} \cdot \frac{1}{s + \frac{1}{RC}}$$

$$s = j\omega$$

$$\omega_c = \frac{1}{RC} = 2\pi f$$


$$H(j\omega) = \frac{\omega_c}{j\omega + \omega_c}$$

$$|H(j\omega)| = \frac{1/RC}{\sqrt{\omega^2 + (1/RC)^2}}$$

$$\frac{1}{RC} = \omega_c$$

$$\theta = -\tan^{-1}\left(\frac{\omega}{\omega_c}\right)$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega}{\omega_c}\right)^2}}$$

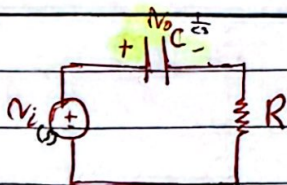

3. HP

RL

$$H(s) = \frac{s}{s + R/L}$$

$$s = j\omega$$


$$\omega_c = \frac{R}{L} = 2\pi f$$

$$H(j\omega) = \frac{j\omega}{j\omega + \omega_c}$$

$$|H(j\omega)| = \frac{j\omega}{\sqrt{\omega^2 + \omega_c^2}}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega_c}{\omega}\right)^2}}$$
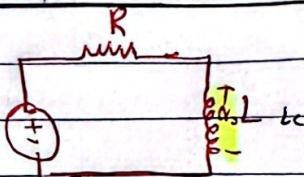
$$\theta = 90^\circ - \tan^{-1}\left(\frac{\omega_c}{\omega}\right)$$



4. RC

$$H(s) = \frac{R}{R + \frac{1}{cs}} = \frac{s}{s + \frac{1}{RC}}$$


$$s = j\omega$$

$$\omega_c = \frac{1}{RC} = 2\pi f$$

$$H(j\omega) = \frac{j\omega}{j\omega + \omega_c}$$

$$|H(j\omega)| = \frac{1}{\sqrt{1 + \left(\frac{\omega_c}{\omega}\right)^2}}$$
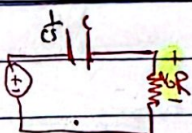
$$\theta = 90^\circ - \tan^{-1}\left(\frac{\omega_c}{\omega}\right)$$






## BPF
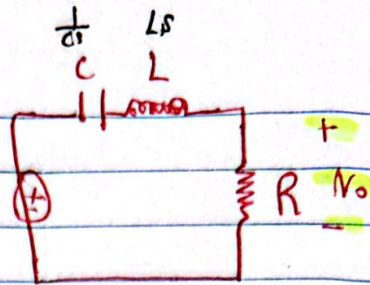
### 1) series RLC

$$H(s) = \frac{R}{R + sL + \frac{1}{sC}} = \frac{s(\frac{R}{L})}{s^2 + s(\frac{R}{L}) + \frac{1}{LC}}$$



$$H(j\omega) = \frac{1}{\sqrt{1 - \frac{\omega^2}{\omega_0^2}}}$$

$$s = j\omega$$

$$\beta = \omega_{c1} - \omega_{c2} = \frac{R}{L}$$

$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

$$\omega_{c1} = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}} = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{\omega_0}{\beta} = \sqrt{\frac{L}{CR^2}}$$

Remember:  $\frac{R}{L} = \beta, \frac{1}{LC} = \omega_0^2$

### 2) Parallel RLC

$$Z_{eq} = \frac{1}{\frac{1}{R} + \frac{1}{sL} + sC}$$

$$H(s) = \frac{Z_{eq}}{Z_{eq} + R}$$

$$H(s) = \frac{\frac{R}{s^2 + \frac{s}{RC} + \frac{1}{LC}}}{\frac{R}{s^2 + \frac{s}{RC} + \frac{1}{LC}} + R}$$

$$H(s) = \frac{\beta s}{s^2 + \beta s + \omega_0^2}$$

$$\omega_{c1} = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\beta = \omega_{c1} - \omega_{c2} = \frac{1}{RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$


$$Q = \frac{\omega_0}{\beta} = \frac{R^2 C}{L}$$

Rem:  $\frac{1}{RC} = \beta, \frac{1}{LC} = \omega_0^2$

## BPF
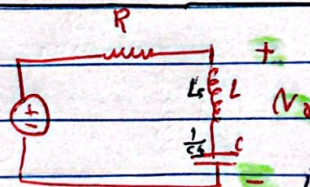
### 1) series RLC

$$H(s) = \frac{s^2}{s^2 + s(\frac{R}{L}) + \frac{1}{LC}}$$



$$H(s) = \frac{s^2}{s^2 + \beta s + \omega_0^2}$$

$$\omega_{c1} = \frac{-R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{R}{2L} + \sqrt{\left(\frac{R}{2L}\right)^2 + \frac{1}{LC}}$$

$$\beta = \frac{R}{L} = \omega_{c1} - \omega_{c2}$$

$$\omega_0 = \sqrt{\omega_{c1}\omega_{c2}} = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{\omega_0}{\beta} = \sqrt{\frac{L}{CR^2}}$$

Rem:  $\frac{R}{L} = \beta, \frac{1}{LC} = \omega_0^2$

### 2) Parallel RLC



$$\omega_{c1} = \frac{-1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$\omega_{c2} = \frac{1}{2RC} + \sqrt{\left(\frac{1}{2RC}\right)^2 + \frac{1}{LC}}$$

$$H(s) = \frac{s^2 + \omega_0^2}{s^2 + s(\frac{1}{RC}) + \frac{1}{LC}}$$

$$\beta = \omega_{c1} - \omega_{c2} = \frac{1}{RC}$$

$$\omega_0 = \frac{1}{\sqrt{LC}}$$

$$Q = \frac{\omega_0}{\beta} = \frac{R^2 C}{L}$$

Rem:  $\frac{1}{RC} = \beta, \frac{1}{LC} = \omega_0^2$



$$\begin{bmatrix} V_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} Z_{11} & Z_{12} \\ Z_{21} & Z_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix}, [Z] \text{ is the impedance matrix}$$

$$\begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} Y_{11} & Y_{12} \\ Y_{21} & Y_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}, [Y] = [Z]^{-1} \text{ is the admittance matrix.}$$

$$\begin{bmatrix} V_1 \\ I_1 \end{bmatrix} = \begin{bmatrix} a_{11} & -a_{12} \\ a_{21} & -a_{22} \end{bmatrix} \begin{bmatrix} V_2 \\ I_2 \end{bmatrix}, [A] \text{ is a transmission matrix.}$$

$$\begin{bmatrix} V_2 \\ I_2 \end{bmatrix} = \begin{bmatrix} b_{11} & -b_{12} \\ b_{21} & -b_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_1 \end{bmatrix}, [B], [A]^{-1} \text{ is a transmission matrix.}$$

$$\begin{bmatrix} V_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} h_{11} & h_{12} \\ h_{21} & h_{22} \end{bmatrix} \begin{bmatrix} I_1 \\ V_2 \end{bmatrix}, [H] \text{ is a hybrid matrix.}$$

$$\begin{bmatrix} I_1 \\ V_2 \end{bmatrix} = \begin{bmatrix} g_{11} & g_{12} \\ g_{21} & g_{22} \end{bmatrix} \begin{bmatrix} V_1 \\ I_2 \end{bmatrix}, [G] = [H]^{-1} \text{ is a hybrid matrix.}$$

$$Z_{11} = \frac{V_1}{I_1} \Big|_{I_2=0 \text{ o.c.}}$$

$$Z_{12} = \frac{V_1}{I_2} \Big|_{I_1=0 \text{ o.c.}}$$

$$Y_{11} = \frac{I_1}{V_1} \Big|_{V_2=0}$$

$$Y_{12} = \frac{I_1}{V_2} \Big|_{V_1=0}$$

$$Z_{21} = \frac{V_2}{I_1} \Big|_{I_2=0 \text{ o.c.}}$$

$$Z_{22} = \frac{V_2}{I_2} \Big|_{I_1=0 \text{ o.c.}}$$

$$Y_{21} = \frac{I_2}{V_1} \Big|_{V_2=0}$$

$$Y_{22} = \frac{I_2}{V_2} \Big|_{V_1=0}$$

$$a_{11} = \frac{V_1}{V_2} \Big|_{I_2=0}$$

$$a_{12} = -\frac{V_1}{I_2} \Big|_{V_2=0}$$

$$b_{11} = \frac{V_2}{V_1} \Big|_{I_1=0}$$

$$b_{12} = -\frac{V_2}{I_1} \Big|_{V_1=0}$$

$$a_{21} = \frac{I_1}{V_2} \Big|_{I_2=0}$$

$$a_{22} = -\frac{I_1}{I_2} \Big|_{V_2=0}$$

$$b_{21} = \frac{I_2}{V_1} \Big|_{I_1=0}$$

$$b_{22} = -\frac{I_2}{I_1} \Big|_{V_1=0}$$

$$h_{11} = \frac{V_1}{I_1} \Big|_{V_2=0}$$

$$h_{12} = \frac{V_1}{V_2} \Big|_{I_1=0}$$

$$g_{11} = \frac{I_1}{V_1} \Big|_{I_2=0}$$

$$g_{12} = \frac{I_1}{I_2} \Big|_{V_1=0}$$

$$h_{21} = \frac{I_2}{I_1} \Big|_{V_2=0}$$

$$h_{22} = \frac{I_2}{V_2} \Big|_{I_1=0}$$

$$g_{21} = \frac{V_2}{V_1} \Big|_{I_2=0}$$

$$g_{22} = \frac{V_2}{I_2} \Big|_{V_1=0}$$