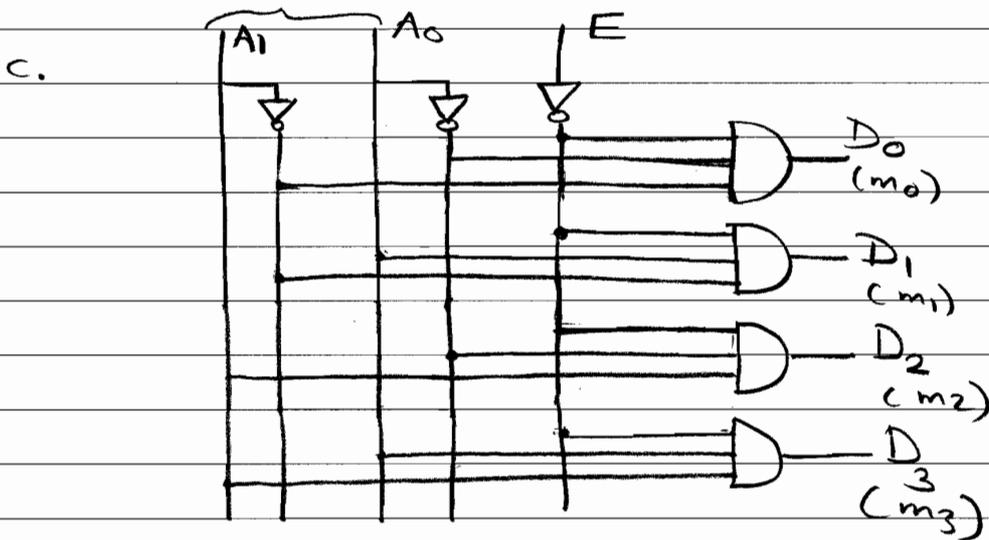


1. a. With $E=0$, the decoder is Enabled


A_1	A_0	D_0	D_1	D_2	D_3
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

b. with $E=1$, the decoder is disabled and all outputs = 0




d.

i. 1-to-4 DeMux

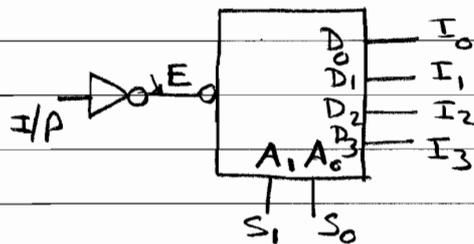


ii. 4-to-Mux

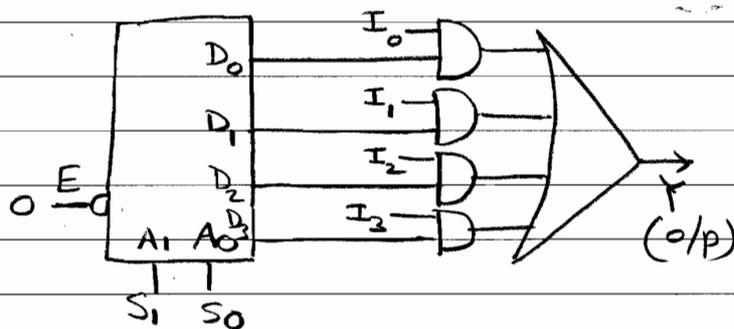

3.	I/P				o/p		
	x_3	x_2	x_1	x_0	y_2	y_1	y_0
0	0	0	0	0	0	0	0
1	0	0	0	1	0	0	1
2	0	0	1	0	0	1	0
3	0	0	1	1	0	1	1
4	0	1	0	0	1	0	0
5	0	1	0	1	1	0	1
6	0	1	1	0	1	1	0
7	0	1	1	1	1	1	1
8	1	0	0	0	1	1	1
9	1	0	0	1	1	1	0
10	1	0	1	0	1	0	1
11	1	0	1	1	1	0	0
12	1	1	0	0	0	1	1
13	1	1	0	1	0	1	0
14	1	1	1	0	0	0	1
15	1	1	1	1	0	0	0

4-to-16 Decoder

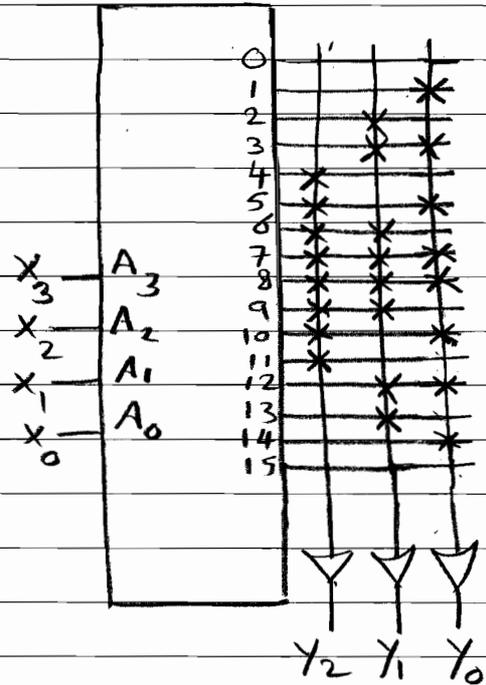


4.a.

x	y	z	F_1	F_2	F_3
0	0	0	0	1	1
1	0	0	1	1	0
2	0	1	0	0	1
3	0	1	1	0	0
4	1	0	0	1	0
5	1	0	1	1	1
6	1	1	0	1	0
7	1	1	1	1	0

$$F_1 = (x + \bar{y})(x + z)$$


$$= x + xz + x\bar{y} + \bar{y}z$$

(3-to-8 Decoder)

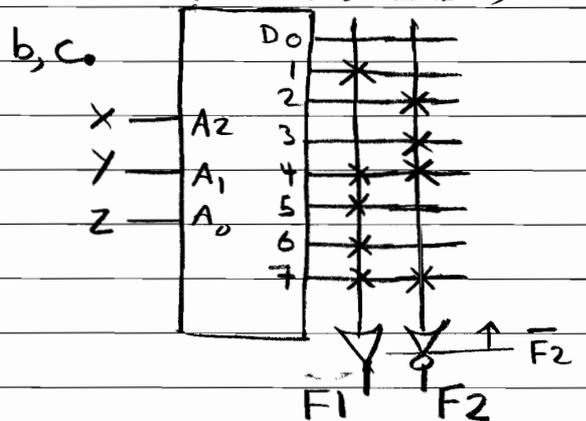


d Mux Select

i.	X	Y	Z	F ₃
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

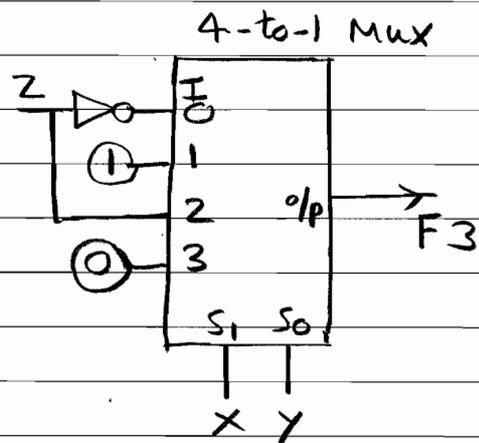


Mux select

ii.	X	Y	Z	F ₃
0	0	0	0	1
1	0	0	1	0
2	0	1	0	1
3	0	1	1	1
4	1	0	0	0
5	1	0	1	1
6	1	1	0	0
7	1	1	1	0

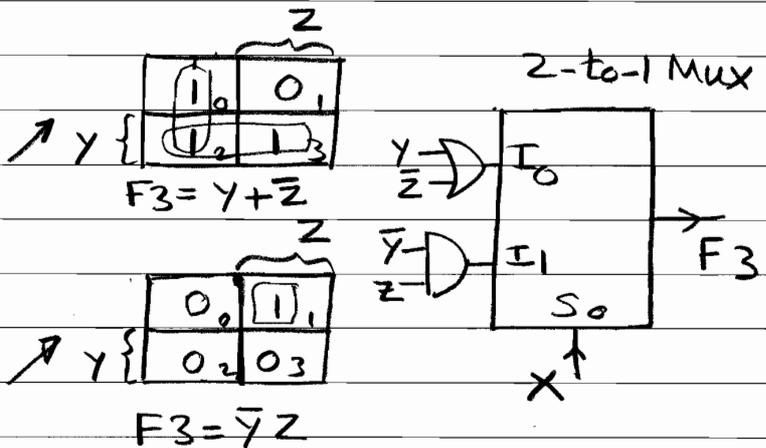

5.

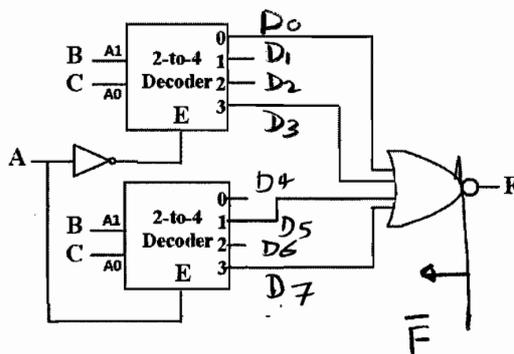

a. $\bar{F} = \sum(0, 3, 5, 7)$

$F = \sum(1, 2, 4, 6)$

b. $F = \prod(0, 3, 5, 7)$
 $= M_0 \cdot M_3 \cdot M_5 \cdot M_7$

$= M_{000} \cdot M_{011} \cdot M_{101} \cdot M_{111}$


$F(A, B, C) = (A + B + C) \cdot (A + \bar{B} + \bar{C}) \cdot (\bar{A} + B + \bar{C}) \cdot (\bar{A} + \bar{B} + \bar{C})$

sign bit H6-5

6. I/P in signed -1's complement is $x_3 x_2 x_1 x_0$

o/p $Y = |X|$ in 3-bit
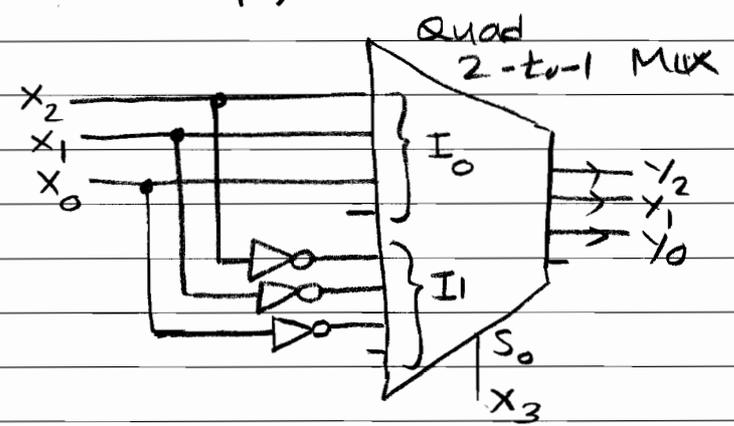
$$Y = \begin{cases} x_2 x_1 x_0 & \text{if } x_3 = 0 \\ \bar{x}_2 \bar{x}_1 \bar{x}_0 & \text{if } x_3 = 1 \\ \text{(1's comp.)} \end{cases}$$



7. 4-bit Mag. Comp.

