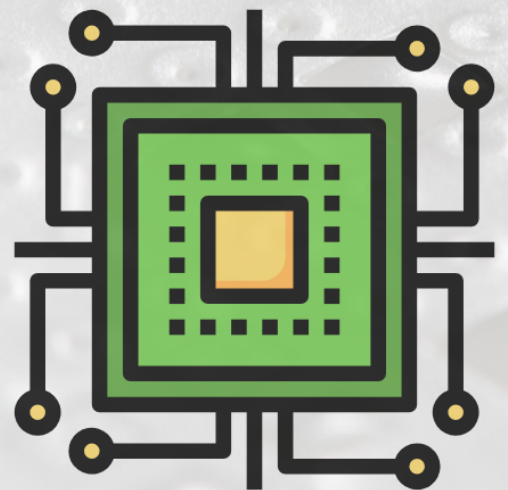



# Circuits Analysis

By Rawan Alfares



Series: two elements Connected at Single node

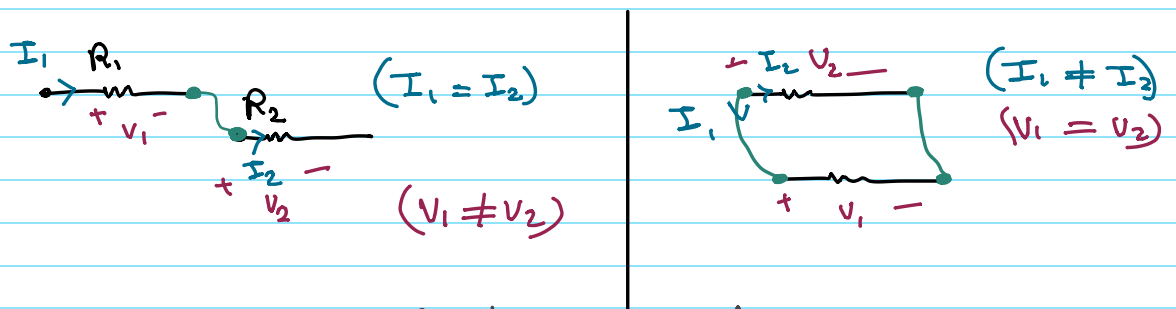Parallel: two elements Connected at a Single node pair.





\* When we have only two Resistors in parallel :

$$R_{eq} = \frac{R_1 \times R_2}{R_1 + R_2} < \min(R_1, R_2)$$

\* Connecting Resistors in Series  $R_{eq} > \max(R_1, R_2)$

Example 3

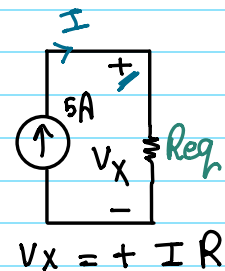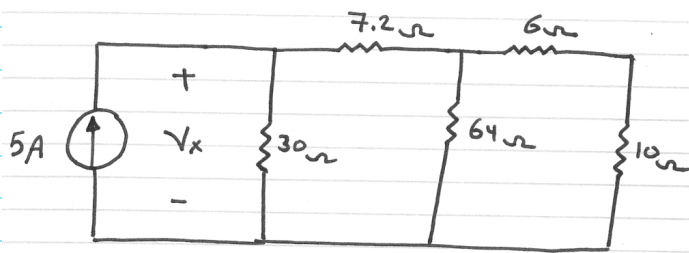

$$(6, 10) \xrightarrow{S} 6 + 10 = 16$$

$$(16, 64) \xrightarrow{P} \frac{16 \times 64}{16 + 64} = 12.8$$


$$(7.2, 12.8) \xrightarrow{S} 7.2 + 12.8 = 20$$

$$(20, 30) \xrightarrow{P} \frac{20 \times 30}{50} = 12$$

$$R_{eq} = 12\Omega$$

$$\begin{aligned} V_x &= + I R \\ &= (5)(12) \\ &= 60 \end{aligned}$$


Example 2:- Find I?

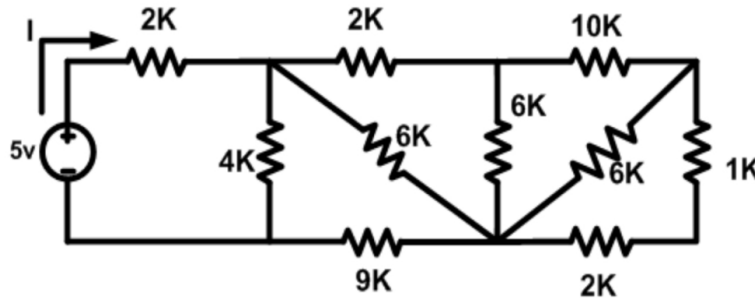

$$\begin{aligned}
 1 + 2 &= 3 \\
 3 // 6 &= 2 \\
 2 + 10 &= 12 \\
 12 // 6 &= 4 \\
 4 + 2 &= 6 \\
 6 // 6 &= 3 \\
 3 + 9 &= 12 \\
 12 // 4 &= 3 \\
 3 + 2 &= 5 \rightarrow R_{eq} = 5
 \end{aligned}$$

$$I = \frac{V}{R} = \frac{5}{5 \times 10^3} = 1 \text{ mA}$$

## Voltage Divider Rule

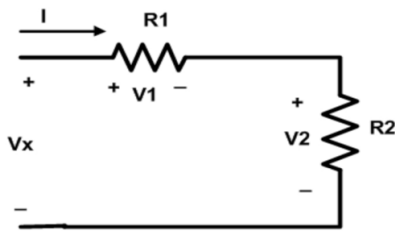

1. by using KVL

$$-V_x + V_1 + V_2 = 0$$

$$V_x = \underline{V_1 + V_2}$$

$$V_x = IR_1 + IR_2$$

$$V_x = I(R_1 + R_2) \rightarrow I = \frac{V_x}{R_1 + R_2}$$

to find  $V_1 = IR_1$

$$V_1 = \frac{R_1}{R_1 + R_2} V_x$$

$$V_2 = \frac{R_2}{R_1 + R_2} V_x$$


any V for Resistors  $V_1 = \frac{R_1}{R_1 + R_2} V_x$   $\rightarrow V_{source}$

$$V_2 = \frac{R_2}{R_1 + R_2} V_x$$

$$V_1 + V_2 = V_x$$

\* إذا كان عندك  
موزع على مقاومتين  
you can use  
Voltage divider Rule.

Example 3: Find  $V_x$ ?

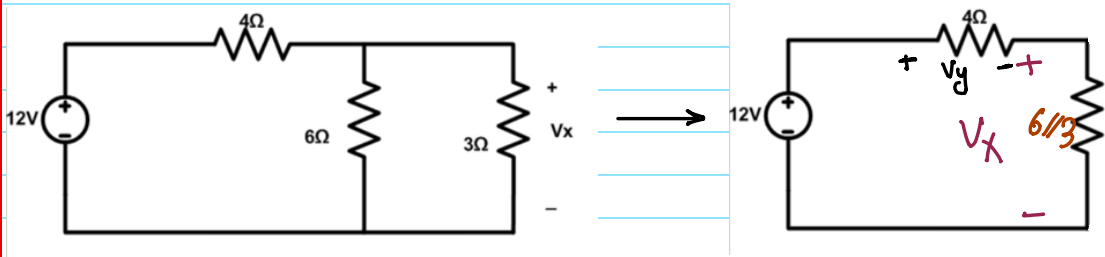


$$6//3 = 2\Omega$$

$$V_x = \frac{2}{6} * 12 = 4V$$

$$V_y = \frac{4}{8} * 12 = 8V$$

to make sure  
 $V_1 + V_2$  should equals  $V_s$   
 $8 + 4 = 12$  ✓

### Current Divider Rule

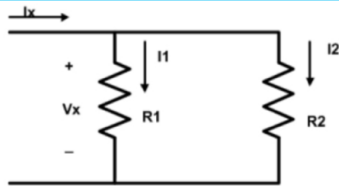


Parallel Combination  
 ... في تيار يتجزأ ...

$$I_1 = \frac{R_2}{R_1 + R_2} I_x$$

$$I_2 = \frac{R_1}{R_1 + R_2} I_x$$

$$I_x = I_1 + I_2$$

Example 4 8-

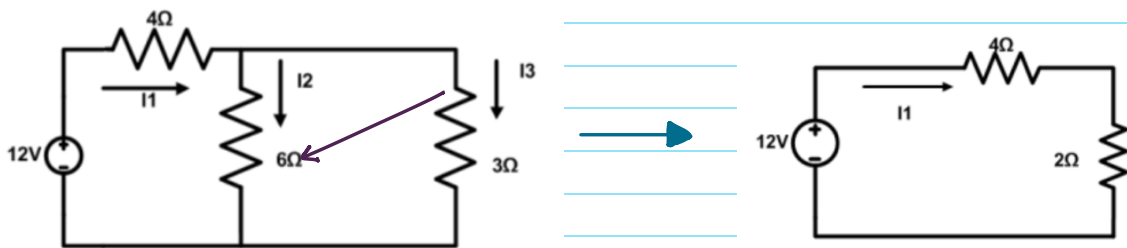



$$3//6 = 2\Omega$$

$$I_1 = \frac{V}{R} = \frac{12}{6} = 2A$$

$$I_3 = 2 * \frac{6}{9} = 1.3A$$

$$I_2 = I_3 - I_1 = 2 - 1.3 = 0.7A$$

Example 5 :- find  $V_o$

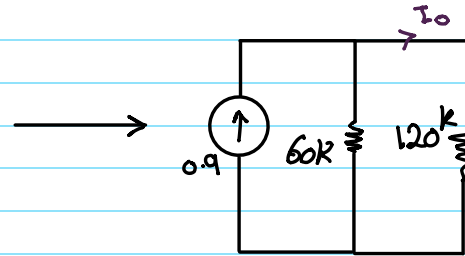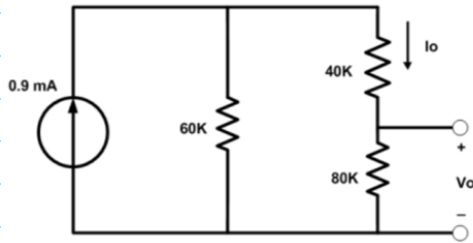

$$V_o = I_o R$$


$$= 80 \times 10^3 \times I_o \rightarrow \textcircled{1}$$

$$I_o = 0.9 \times \frac{60K}{180K} = 0.3 \text{ mA}$$


$$V_o = 80 \times 10^3 \times 0.3 \times 10^{-3}$$

$$= 24 \text{ V}$$

Example 6 :- find  $I_o$  :-

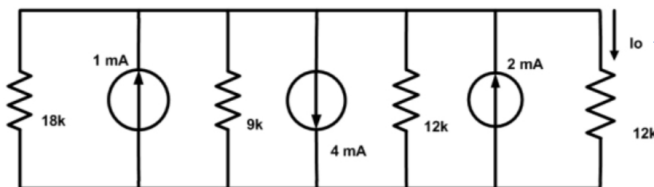

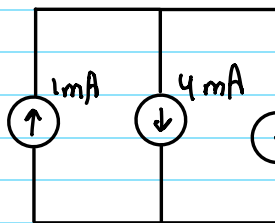الإشي المجهول دائماً ما ينقلب عليه ولا ينسك




$$I_T = -1 + 4 - 2$$

$$= 1$$

اتجاهه نفس اتجاه الأكبر

$$18 // 9 \rightarrow 6 \Omega$$

$$6 // 12 \rightarrow 4 \Omega$$

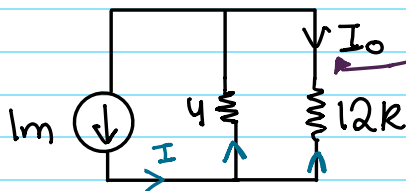


لكن هم فارضين التيار لختت على المطلوب فذلك نضع سالب في الجواب النهائي

$$I_o = 1 \times 10^{-3} \times \frac{4}{4+12}$$

$$I_o = -0.25 \text{ mA}$$

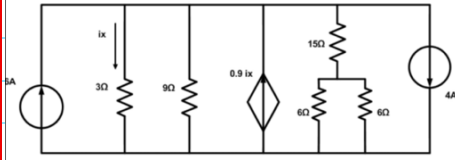**Example 7:** find the power supplied by  $0.9 i_x$  source?




$$6 \parallel 6 = 3$$

$$3 + 15 = 18$$

$$18 \parallel 9 = 6 \Omega = R_{eq.}$$
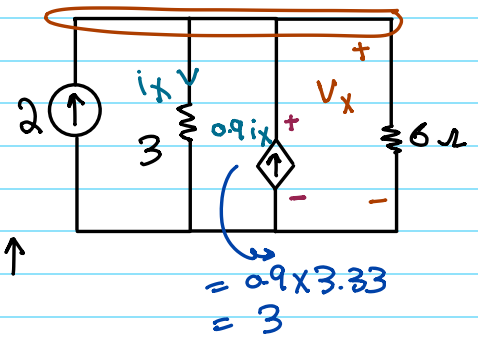
$$6 \uparrow - 4 \downarrow = 2 \uparrow$$



**By using KCL:-**

$$\sum I_{in} = \sum I_{out}$$

$$2 + 0.9 i_x = i_x + \frac{V_x}{6}$$

$$2 + 0.9 i_x = i_x + \frac{3 i_x}{2.6}$$

$$2 = 0.6 i_x$$

$$i_x = 3.33 \text{ A}$$

$$V_x = 3 i_x$$

$$= (3)(3.33)$$

$$V_x = 10 \text{ V}$$

$$\text{Power} = -V i$$



$$= -(10)(3)$$

$$\text{power} = -30 \text{ watt.}$$


supplying
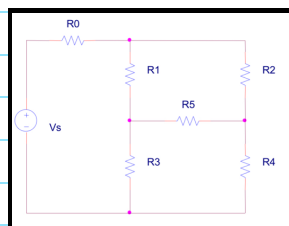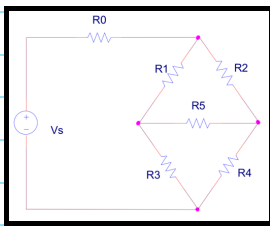
## Bridge Circuits

one type of resistive circuit that can't be simplified through series or parallel combinations.


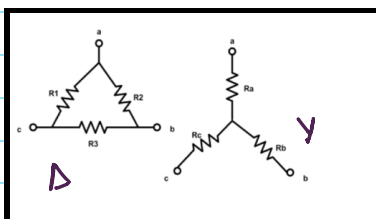
## Delta to wye and wye to delta transformation



### Y-Δ transformation

1.  $R_1 = \frac{R_{ab} + R_{ac} + R_{bc}}{R_b}$

2.  $R_2 = \frac{R_{ab} + R_{ac} + R_{bc}}{R_c}$

3.  $R_3 = \frac{R_{ab} + R_{ac} + R_{bc}}{R_a}$

### Δ-Y transformation


1.  $R_a = \frac{R_1 R_2}{R_1 + R_2 + R_3}$

2.  $R_b = \frac{R_2 R_3}{R_1 + R_2 + R_3}$

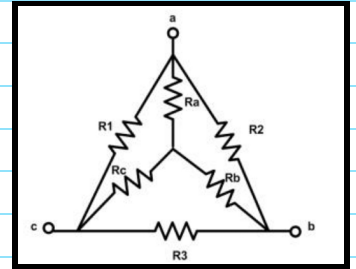3.  $R_c = \frac{R_1 R_3}{R_1 + R_2 + R_3}$

Note:

the equations above must be used along with the circuit diagrams shown. the labeling of the resistors and nodes in the diagrams is critical.




→ for Balance Case :-


1.  $R_1 = R_2 = R_3 = R_\Delta$
2.  $R_a = R_b = R_c = R_Y$

$$R_\Delta = 3 R_Y$$

Example :- find  $R_{eq}$  :-

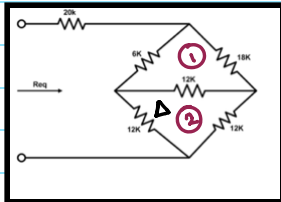
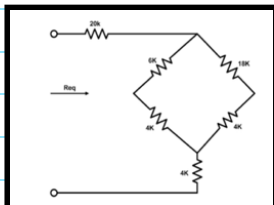
$$R_\Delta = 12, R_Y = \frac{R_\Delta}{3} = \frac{12}{3} = 4$$



substitute


$$18 + 4 = 22 \text{ K}$$

$$6 + 4 = 10 \text{ K}$$

$$22 // 10 = 6.875 \text{ K}$$

$$6.875 + 4 + 20 = 30.875 \text{ K} = R_{eq}$$

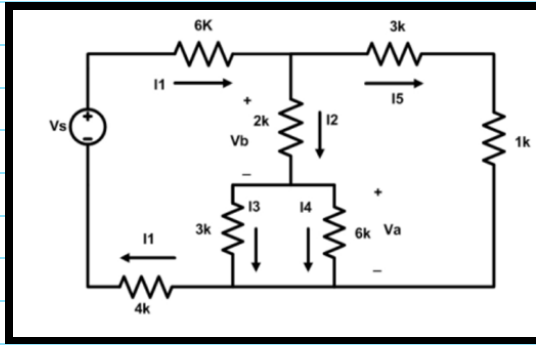Example: given  $I_4 = 0.5 \text{ mA}$ , find  $V_s$




$$V_a = +IR$$

$$= 0.5 \text{ m} \times 6 \text{ k}$$

$$= 3$$
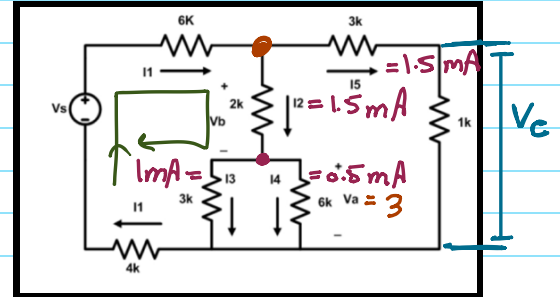
$$I_3 = \frac{V_a}{3 \text{ k}} = \frac{3}{3 \text{ k}} = 1 \text{ mA}$$



by KCL :-

$$I_2 = 1 \text{ m} + 0.5 \text{ m}$$

$$I_2 = 1.5 \text{ mA}$$

$$V_b = (2)(1.5)$$

$$= 3 \text{ V}$$

$$V_c = V_b + V_a$$

$$= 3 + 3 = 6 \text{ V}$$

$$I_5 = \frac{V_c}{4 \text{ k}} = \frac{6}{4 \text{ k}} = 1.5 \text{ mA}$$

$$I_1 = I_5 + I_2$$

$$= 1.5 + 1.5$$

$$= 3 \text{ mA}$$

$$-V_s + (10)(3) + 6$$

$$V_s = 36 \text{ V}$$

Ammeter → designed to measure Current

Voltmeter → designed to measure Voltage.

رَبَّنَا تَقَبَّلْ مِنَّا إِنَّكَ أَنْتَ السَّمِيعُ الْعَلِيمُ