

Homework Solutions Electronics II

6.34

From the circuit diagram

$$I_{C1} = I_{C2} = I_{C3} = I_{C4} = I_{C5} = I_{C6} = I_{C7} = I_{C8}$$

$$I_{C8} = I_{C9} = I_{C10} = I_{C11} = I_R$$

$$I_R = \frac{V_{B1} - V_{B2}}{10k} \quad ; \quad V_{B1} = 10 - 0.7 = 9.3 \text{ V}$$

$$V_{B2} = -10 + 0.7 = -9.3 \text{ V}$$

$$\therefore I_R = \frac{9.3 + 9.3}{10k} = 1.86 \text{ mA}$$

$$V_{B6} = V_{B5} = 0.7$$

$$V_{C5} = 0.7$$

$$V_{C6} = 5 - (1k)(1.86) = 3.14 \text{ V}$$

$$V_{C3} = (2k)(1.86) = 3.72 \text{ V}$$

$$I_{R4} = I_{C8} + I_{C7} = 3.72 \text{ mA}$$

$$V_{C7} = -(1k)(3.72) = -3.72 \text{ V}$$

$$V_{C11} = (1k)(1.86 \text{ mA}) = 1.86 \text{ V}$$


$$V_{C10} = 5 - 0.7 = 4.3 \text{ V}$$

6.61

Since $I_{D1} = I_{D2}$, and $V_{AN} = |V_{AP}|$

$$\therefore r_{D1} = r_{D2} = r_o$$

ac small signal Equivalent CKT

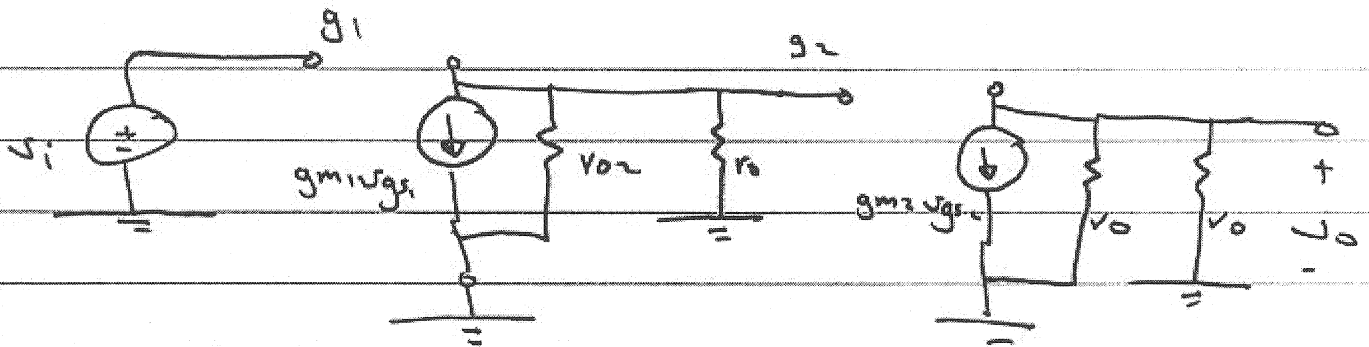

$$V_o = -g_{m2} (r_{D2} \parallel r_o) V_{gs2}$$

$$V_{gs2} = V_{g2} - V_{s2} = V_{g2}$$

$$V_{g2} = - (r_{D1} \parallel r_o) g_{m1} V_{gs1}$$

$$V_{gs1} = V_{g1} = V_i$$

$$\therefore V_o = \left(\frac{1}{2}\right) \left(\frac{1}{2}\right) (r_o^2) g_{m1} g_{m2} V_i$$

$$V_o = \frac{1}{4} r_o^2 g_{m1} g_{m2} V_i$$

6.65

Since $V_{BE2} = V_{BE3}$
and $I_{S2} = 5 I_{S3}$

$$\therefore I_{C2} = 5 I_{C3}$$

$$I_{C3} = I_R = \frac{3 - 0.7}{25k} = 0.1 \text{ mA}$$

$$I_{C2} = 0.5 \text{ mA}$$

Since $I_{C2} = 5 I_{C3}$


$$r_{o2} = \frac{V_A}{I_{C2}} = \frac{50}{0.5} = 100k$$

$$r_{o3} = \frac{V_A}{I_{C3}} = \frac{50}{0.1} = 500k$$

Since $I_{C1} = I_{C2}$

$$\therefore r_{o1} = r_{o2} = 100k$$

ac small signal Equivalent circuit

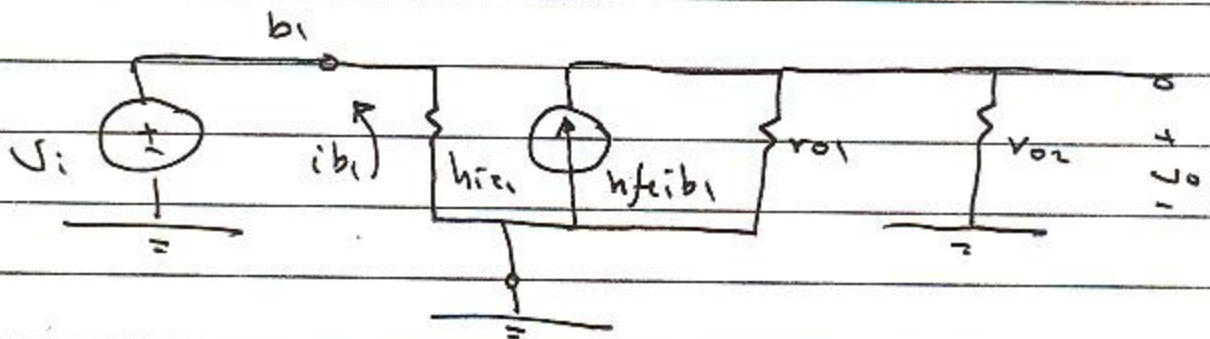

Total resistance at the collector of Q_1
is $r_{o2} \parallel r_{o1} = 50k$

$$h_{ie1} = \frac{\beta V_T}{I_{CQ1}} = \frac{(50)(25.69)}{0.5} = 2.569 \text{ k}$$

$$g_{m1} = \frac{h_f}{h_{ie1}} = 19.46 \text{ mS}$$

$$v_o = (r_{o1} \parallel r_{o2}) h_{fe} i_{b1}$$

$$i_{b1} = \frac{v_i}{h_{ie1}}$$

$$\therefore \frac{v_o}{v_i} = -9.73$$

$$Z_o = r_{o1} \parallel r_{o2} = 50 \text{ k}$$

6.140

$$V_T = 0.6 \text{ V}$$

$$K_n \frac{W}{L} = 2 \text{ mA/V}^2$$

$$V_A = 20$$

$$I_R = 100 \mu\text{A}$$

In this problem we must use the exact equation for I_{DS} .

$$I_{DS2} = \frac{1}{2} K_n \frac{W}{L} (V_{GS2} - V_T)^2 \left(1 + \frac{V_{DS}}{V_A} \right)$$

$$V_{DS2} = V_{GS3} + V_{GS1} = 2V_{GS1} = 2V_{GS2}$$

$$I_{DS2} = I_R = 100 \mu\text{A}$$

$$I_{DS2} = \left(\frac{1}{2} \right) (2 \times 10^{-3}) (V_{GS2} - 0.6)^2 \left(1 + \frac{2V_{GS2}}{20} \right) = 100 \mu\text{A}$$

$$\therefore V_{GS2} = V_{GS1} \approx 0.9028 \text{ V}$$

$$I_{DS3} = I_{DS1} = \left(\frac{1}{2} \right) (2 \times 10^{-3}) (V_{GS1} - 0.6)^2 \left(1 + \frac{V_{GS1}}{V_A} \right)$$

$$\therefore I_{DS3} = I_{DS1} = 95.8266 \mu\text{A}$$

$$\therefore I_O = 95.8266 \mu\text{A}$$

But for the Circuit of fig 6.61(c)

$$I_O = I_R = 100 \mu\text{A}$$

$$\text{Since } V_{DS1} = V_{DS2}$$

$$V_{GS1} = V_{GS2}$$