

ENEE2360

Analog Electronics

T5: Zener Diode


INSTRUCTOR: NASSER ISMAIL

Zener Diode

Simple Voltage Regulator


- *The Zener is used as a voltage regulator to maintain a constant dc output under variations in load current and ac line voltage*
- *It can also be used as protection device against overvoltage*
- *Analysis starts by defining state of diode followed by using appropriate model, then find unknown quantities*

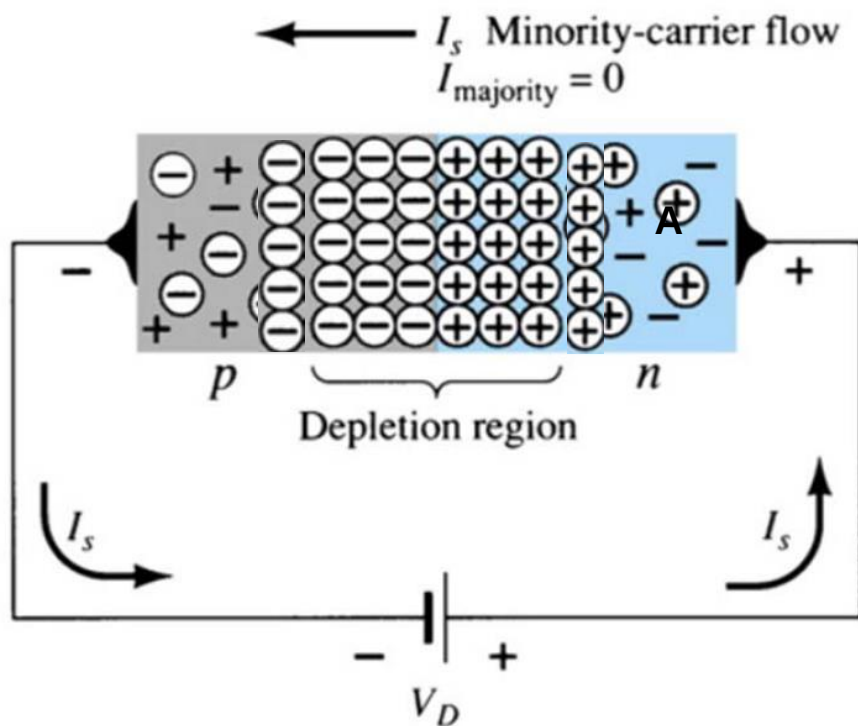Reverse bias of a pn junction Breakdown Voltage




The electric field may become large enough for the covalent bond to break, causing electron-hole pairs to be created.

Regulator :

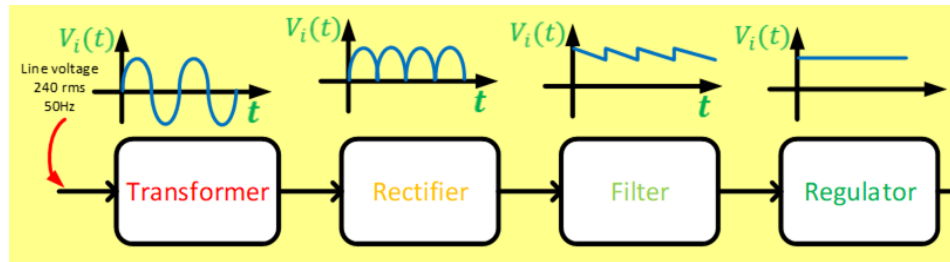


Used to maintain a constant dc output voltage under variation in the load current from the dc power supply and under variation in the ac line voltage

$$V_o = \frac{RL}{RL + RS} \cdot V_s$$

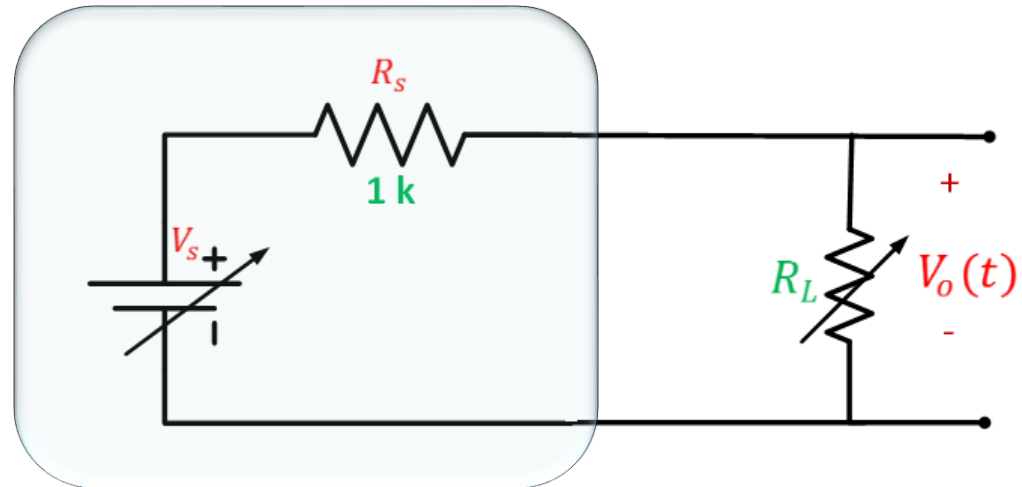


Voltage Regulator

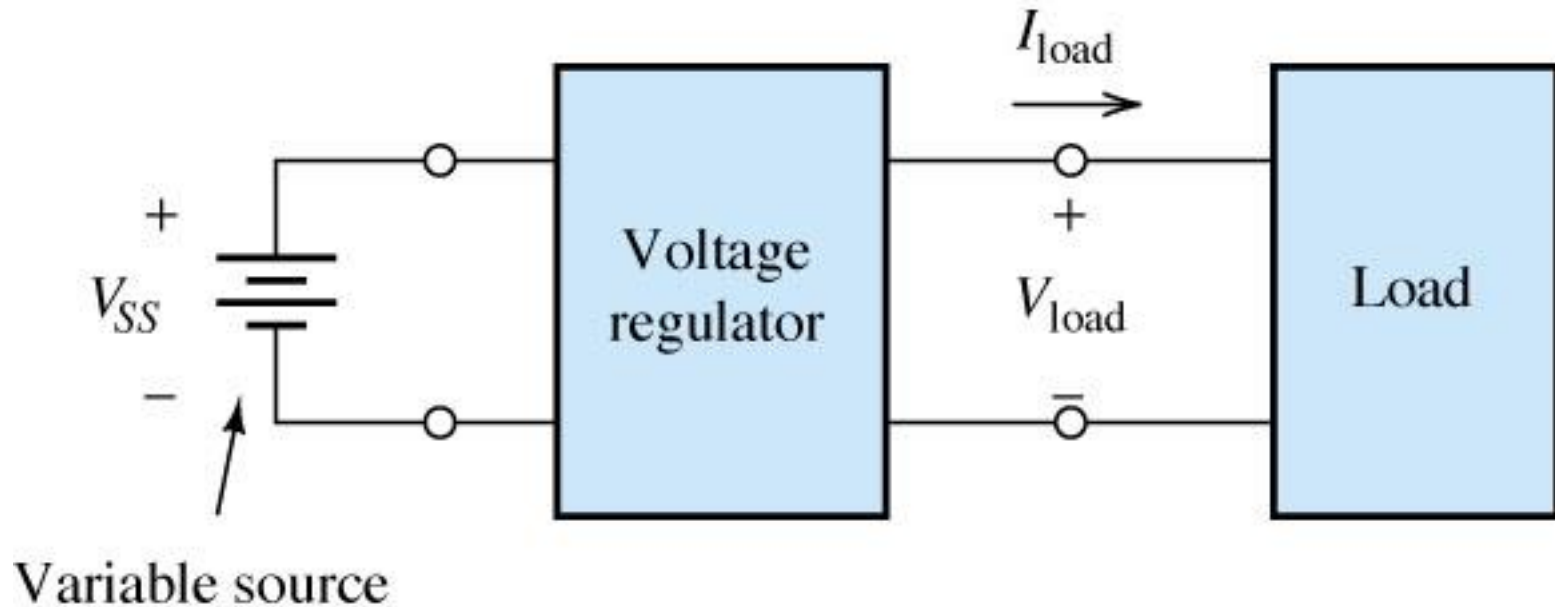


A voltage regulator supplies constant voltage to a load.

Simple voltage regulator

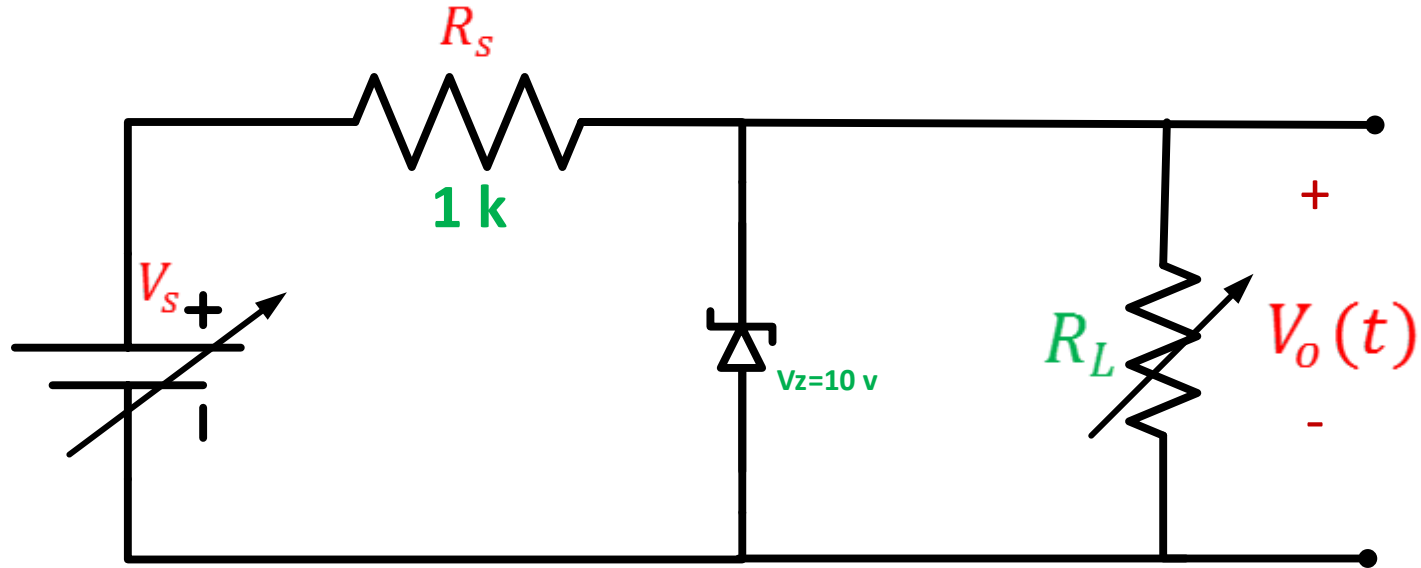


Zener Diode V-I Curve

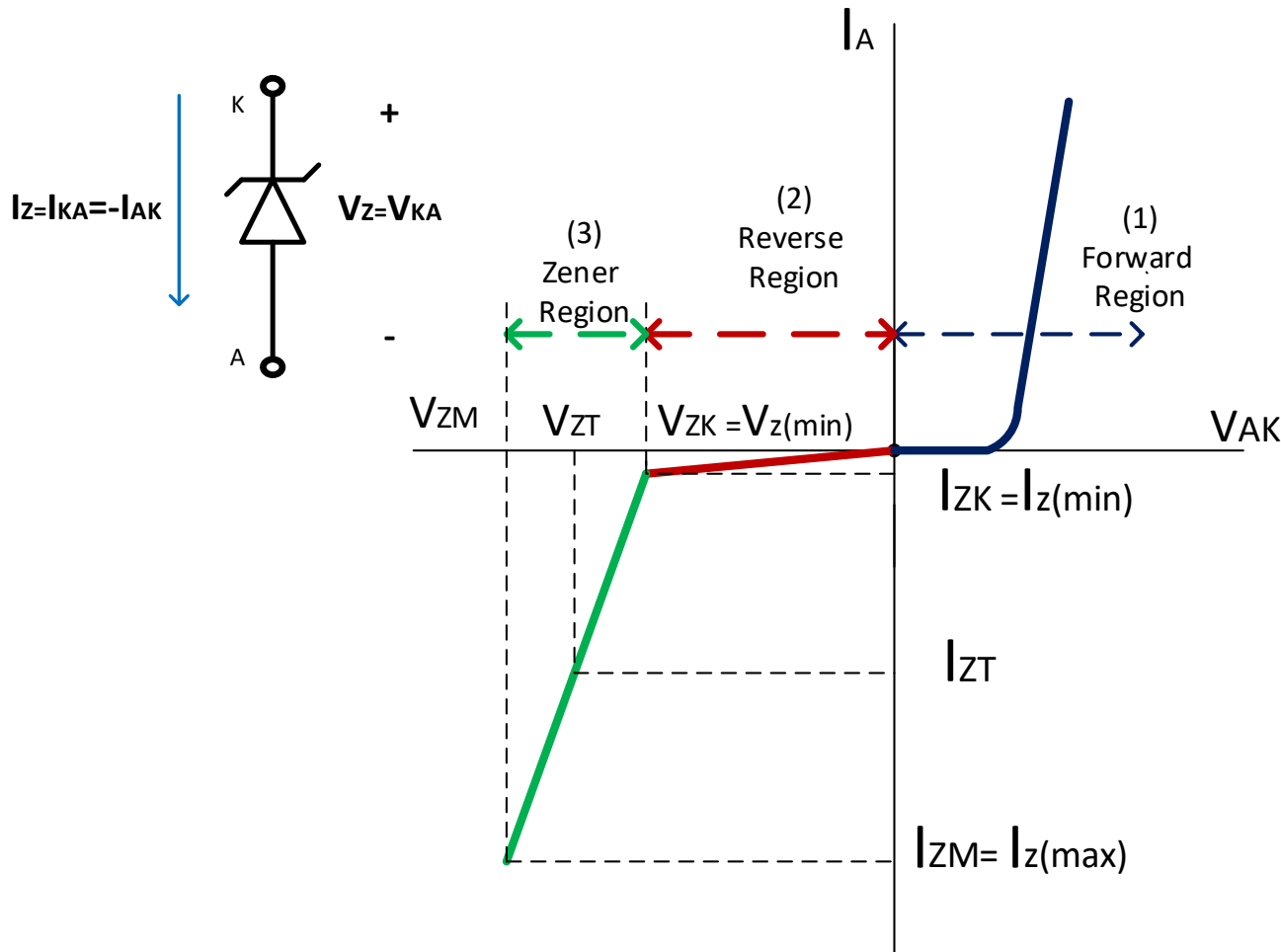

- In data sheet , we have I_{ZT} , V_{ZT}
- Zener currents will be assumed positive if passing from cathode to Anode
- If $I_Z < I_{ZK}$ zener will act as an open circuit
- If $I_Z > I_{Zmax}$ zener will be damaged

- If $I_{ZK} < I_Z < I_{Zmax}$ zener will be in voltage regulation (zener) region

Zener Diode Operation Regions

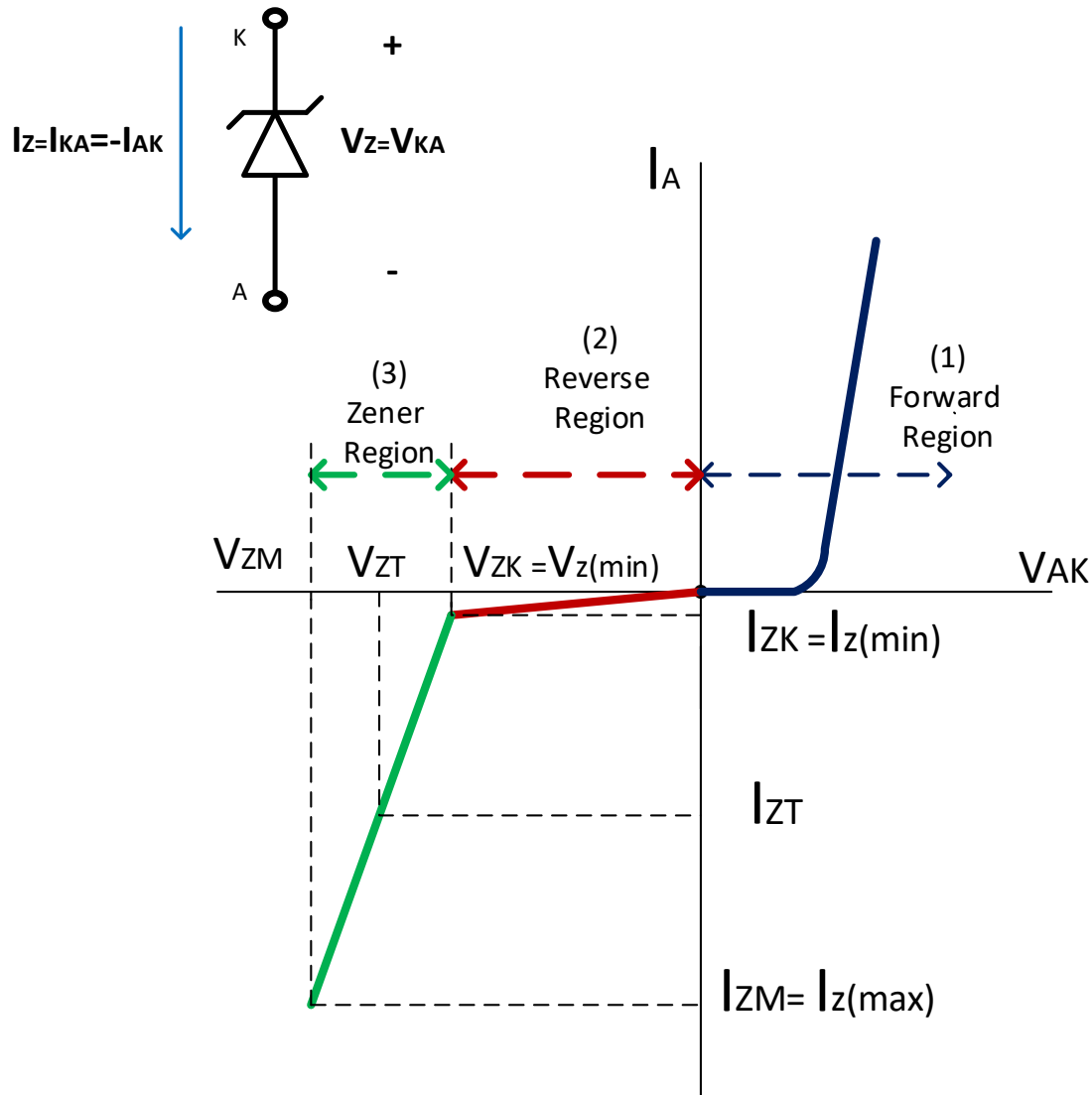

Region (1)

➤ When $V_{AK} > 0$, zener acts as regular diode ON

Region (2)

➤ When $0 < V_{KA} < V_{ZK}$, zener acts as regular diode OFF

Region (3)

➤ When $V_{KA} > V_{ZK}$, This is the intended operating region, and the zener acts as a voltage regulator

Zener Diode Operation & Models




The Zener is a diode that is operated in reverse bias at the Zener Voltage (V_Z).

Conditions for zener diode to operate in the breakdown (Zener/ON) region When

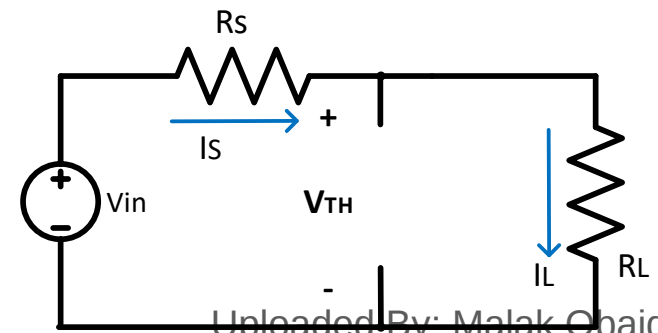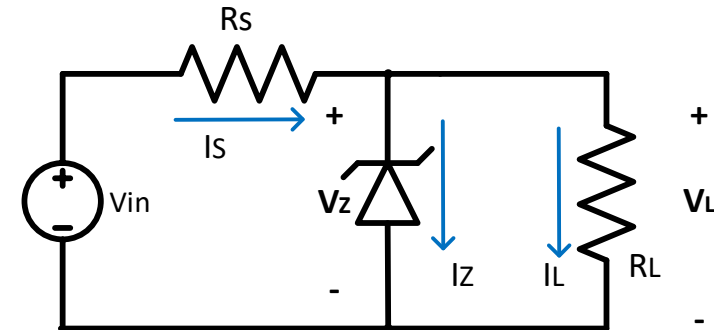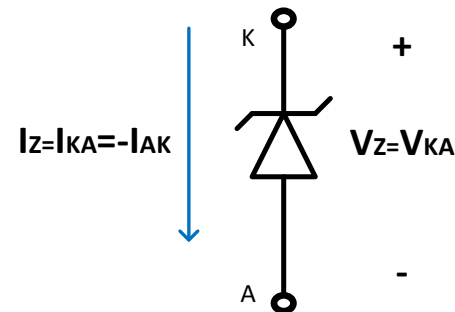1. Cathode is more positive than anode
2. $V_{th} \geq V_Z$
3. $I_Z > I_Z(\min)$
4. $I_Z < I_Z(\max)$


$\Rightarrow$ Voltage across the Zener is V_Z

- Zener current: $I_Z = I_S - I_L$
- The Zener Power: $P_Z = V_Z I_Z$




Zener Diode Models

1. Ideal Model

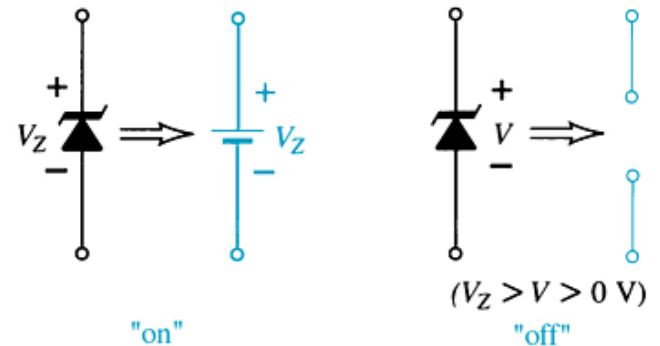


2. Simplified Model **(will not be used in this course)**

$$I_Z = I_{KA} = -I_{AK}$$

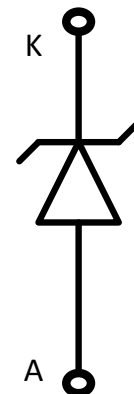

$$V_Z = V_{KA}$$

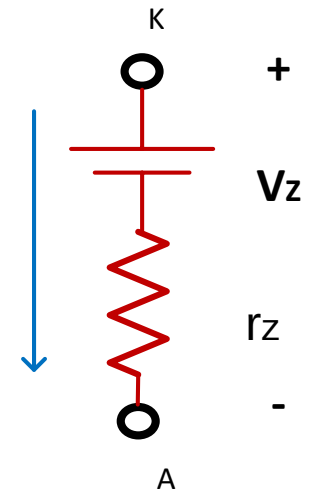

Fixed V_{in} , Variable R_L

- Due to the value of V_Z , there is specific values of R_L (I_L) that ensure the zener is in the ON (regulation) state
- Too small values of R_L can result in zener being OFF


$$V_L = V_Z = \frac{R_L}{R_L + R_S} V_{in}$$

$$V_{th} \geq V_Z$$

$$R_{L(min)} = \frac{R_S \cdot V_Z}{V_{in} - V_Z}$$

$$R_L \geq R_{L(min)} \Rightarrow I_{L(max)} = \frac{V_L}{R_L} = \frac{V_L}{R_{L(min)}}$$

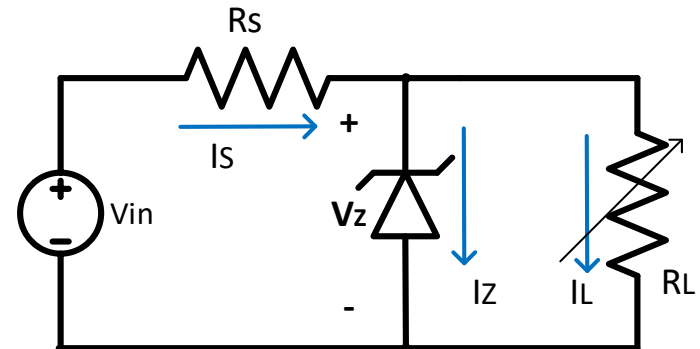Also, values of $R_L \geq R_{L(max)}$ can result in $\Rightarrow I_Z > I_{Z(max)}$



$$I_{L(min)} = I_S - I_{Z(max)}$$

⇓

$$R_{L(max)} = \frac{V_Z}{I_{L(min)}}$$

Example

Given the following values of R_L , find the mode of operation of the zener and the voltage V_L

- a) $R_L = 0.1 \text{ k}\Omega$
- b) $R_L = 0.5 \text{ k}\Omega$
- c) $R_L = 5 \text{ k}\Omega$
- d) $R_L = \infty$

SOLUTION


- a) $R_L = 0.1 \text{ k}\Omega$

using ideal model


$$V_{th} = \frac{R_L}{R_L + R_S} V_{in} = \frac{0.1}{0.1 + 1} 35 \text{ V} = 3.18 \text{ V}$$

Zener works in region 2, it acts as open circuit
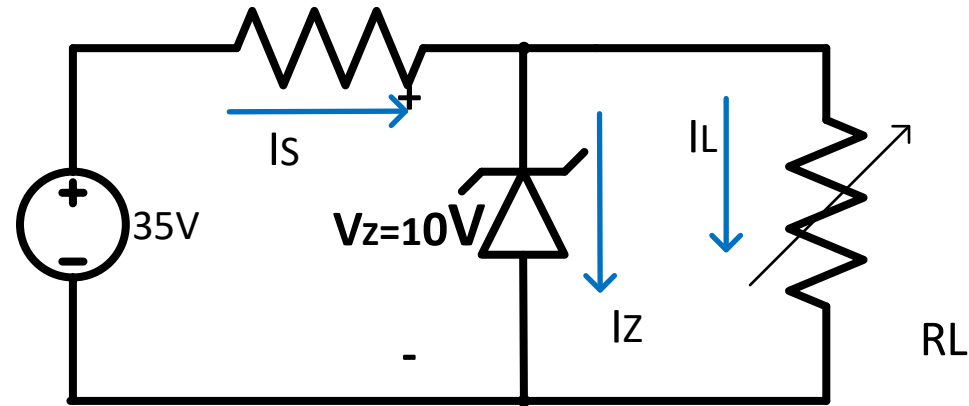
$$V_L = 3.18 \text{ V (it is not regulated)}$$



Example

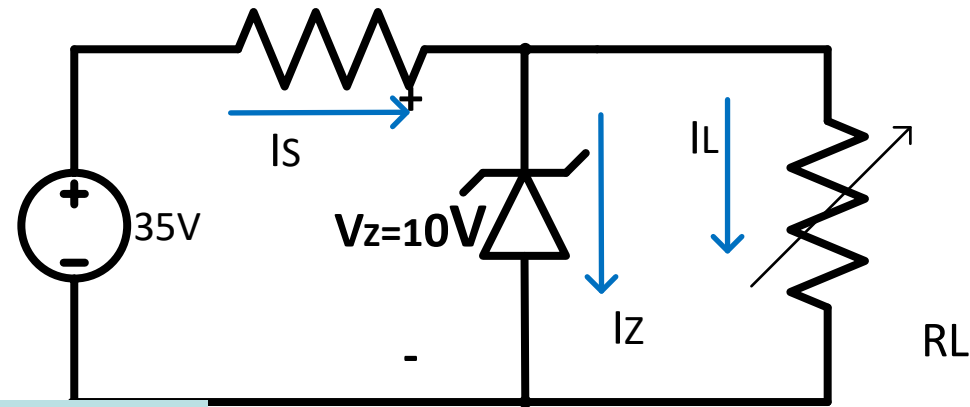

b) $R_L = 0.5 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_S} V_{in} = \frac{0.5}{0.5 + 1} 35 \text{ V} = 11.67 \text{ V}$$

$$V_{th} > V_Z$$

Zener works in region 3, it works as voltage regulator


$$V_L = V_Z = 10 \text{ V}$$

$$I_S = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{0.5 \text{ k}\Omega} = 20 \text{ mA}$$

$$I_Z = I_S - I_L = 5 \text{ mA}$$

Example

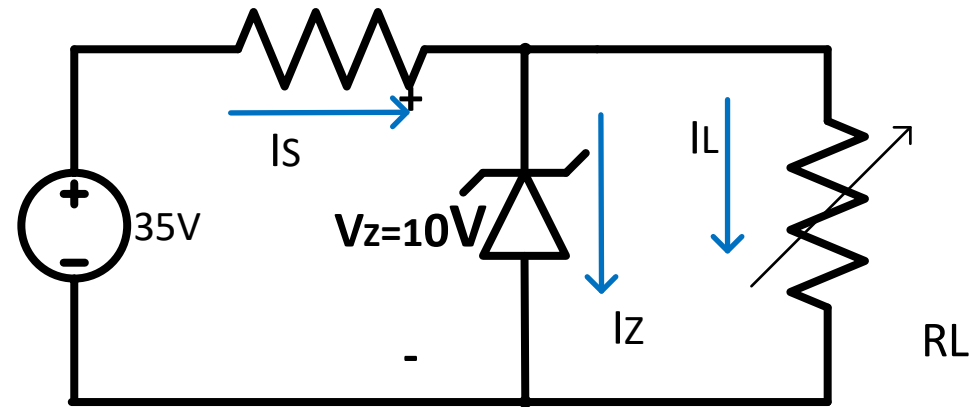

c) $R_L = 5\text{ k}\Omega$

using ideal model

$$V_{th} = \frac{R_L}{R_L + R_S} V_{in} = \frac{5}{5+1} 35\text{ V} = 29.17\text{ V}$$

$$V_{th} > V_Z$$

Zener works in region 3, it works as voltage regulator


$$V_L = V_Z = 10\text{ V}$$

$$I_S = \frac{35\text{ V} - 10\text{ V}}{1\text{ k}\Omega} = 25\text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{5\text{ k}\Omega} = 2\text{ mA}$$

$$I_Z = I_S - I_L = 23\text{ mA}$$

Example

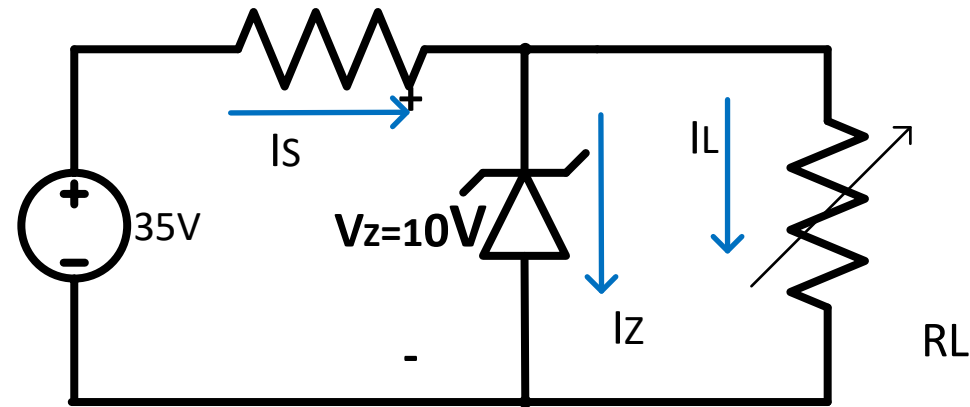

d) $R_L = 5 \text{ k}\Omega$

using ideal model

$$V_{th} = \frac{\infty}{\infty + R_S} V_{in} = 35 \text{ V}$$

$$V_{th} > V_Z$$

Zener works in region 3, it works as voltage regulator

$$V_L = V_Z = 10 \text{ V}$$


$$I_S = \frac{35 \text{ V} - 10 \text{ V}}{1 \text{ k}\Omega} = 25 \text{ mA}$$

$$I_L = \frac{V_L}{R_L} = \frac{10}{\infty} = 0$$

$$I_Z = I_S - I_L = 25 \text{ mA}$$

Example

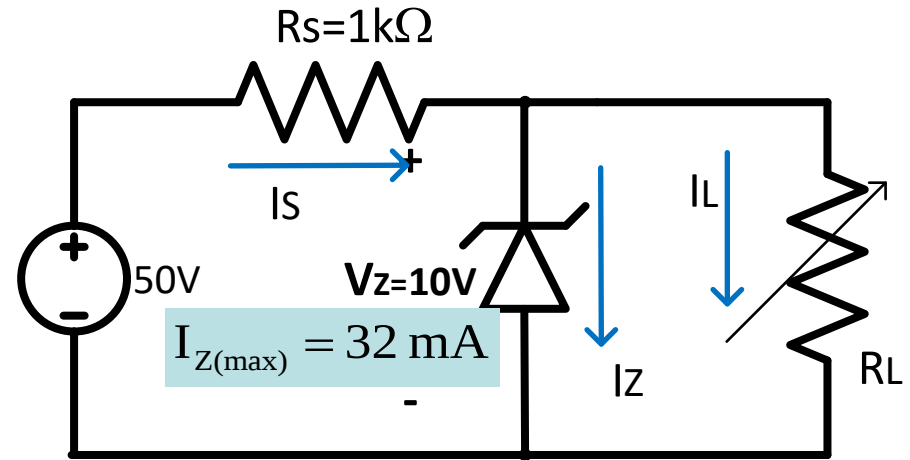- 1) Determine Range of R_L & I_L that will result in V_L being maintained at 10V
- 2) Determine the power rating of the zener diode



SOLUTION

- 1) To find $R_{L(\min)}$ that will turn the zener diode ON:

$$V_L = V_Z = \frac{R_L}{R_L + R_S} V_i \Rightarrow$$

$$R_L = \frac{R_S}{V_i - V_Z} V_Z$$

$$R_{L(\min)} = \frac{1 \text{ k}\Omega}{50 - 10} 10 = 250 \Omega$$

- 2) To find $R_{L(\max)} \Rightarrow$ we need $I_{L(\min)}$

$$I_{L(\min)} = I_S - I_{Z(\max)}$$

$$I_S = \frac{V_i - V_Z}{R_S} = \frac{50 - 10}{1 \text{ k}\Omega} = 40 \text{ mA}$$

$$I_{L(\min)} = 40 - 32 = 8 \text{ mA}$$

$\Downarrow$

$$R_{L(\max)} = \frac{V_L}{I_{L(\min)}} = \frac{10 \text{ V}}{8 \text{ mA}} = 1.25 \text{ k}\Omega$$

$$3) P_{Z(\max)} = V_Z \cdot I_{Z(\max)} = 10 \text{ V} \cdot 32 \text{ mA} = 320 \text{ mW}$$

The zener diode is chosen with power rating $\geq P_{Z(\max)}$

Fixed R_L , Variable V_{in}

For Fixed R_L , the voltage V_{in} must be large enough to turn the zener diode on (regulation region (3))


If $I_Z(\min) = 0$

$$V_{in} = V_{in(\min)} = \frac{R_L + R_S}{R_L} V_Z$$

If $I_Z(\min) > 0$

$$V_{in(\min)} = I_{S(\min)} \cdot R_S + V_Z$$

$$I_{S(\min)} = I_{Z(\min)} + I_L$$

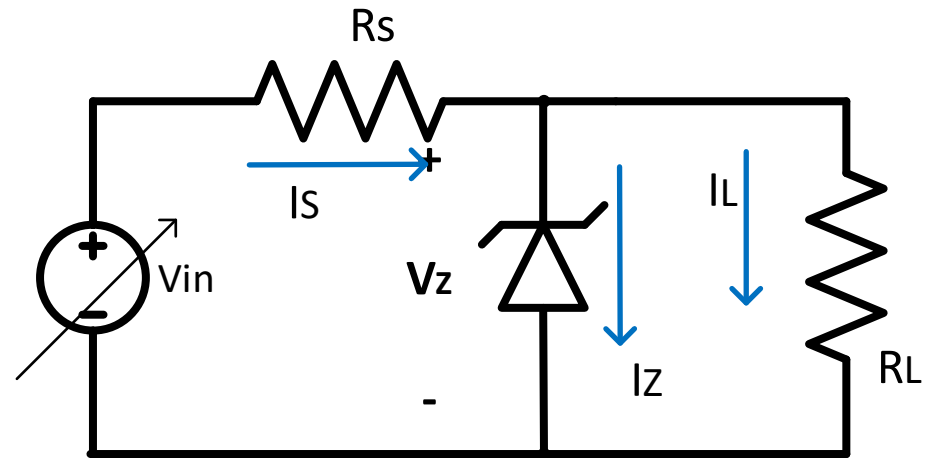

$V_{in(\max)}$ is limited by maximum zener current $I_{Z(\max)}$

$$I_S = I_Z + I_L$$

$$I_{S(\max)} = I_{Z(\max)} + I_L$$

$$V_{in(\max)} = I_{S(\max)} \cdot R_S + V_Z$$

$$\Downarrow$$

$$V_{in(\min)} \leq V_{in} \leq V_{in(\max)}$$

Example

Find the range of values of V_i that will maintain the zener in the ON (regulation) State

$$V_{in(min)} = \frac{R_L + R_S}{R_L} V_Z$$

$$= \frac{1200 + 220}{1200} 20 = 23.07 \text{ V}$$


$$I_S = I_Z + I_L$$

$$I_{S(max)} = I_{Z(max)} + I_L$$

$$I_L = \frac{V_L}{R_L} = \frac{20 \text{ V}}{1200 \Omega} = 16.67 \text{ mA}$$

$$I_{S(max)} = 60 \text{ mA} + 16.67 \text{ mA} = 76.67 \text{ mA}$$
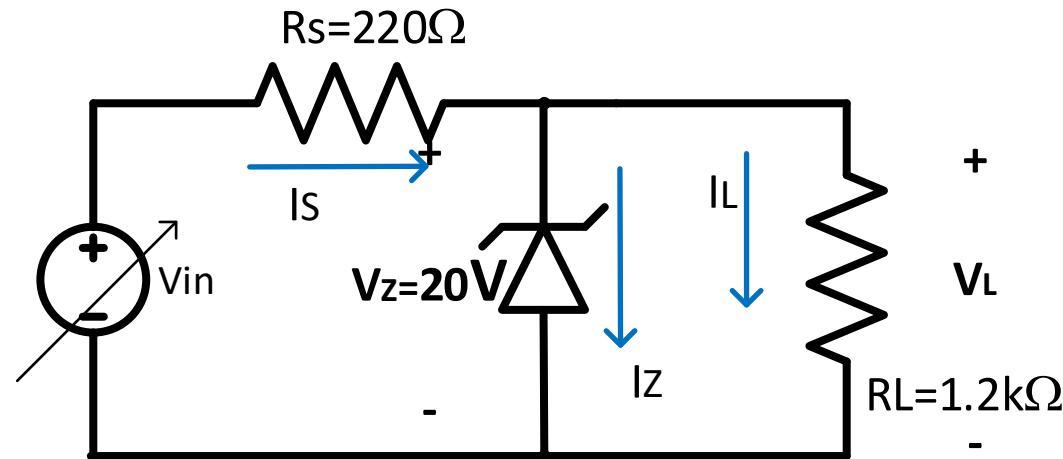
$$V_{i(max)} = (76.67 \text{ mA}) \cdot (220 \Omega) + 20 \text{ V} = 36.87 \text{ V}$$



$$I_{Z(max)} = 60 \text{ mA}$$

$$\therefore 23.07 \text{ V} \leq V_{in} \leq 36.87 \text{ V}$$

Design of R_s (Current limiting Resistor)

Given : $V_Z, I_{Z(\min)}, I_{Z(\max)}, V_{in(\min)}, V_{in(\max)}, R_{L(\min)}, R_{L(\max)}$


Find range of acceptable R_s in the voltage regulator

$$1) I_Z = I_S - I_L \geq I_{Z(\min)}$$

Worst Case : the smallest value of $(I_S - I_L)$

must be always higher than $> I_{Z(\min)}$
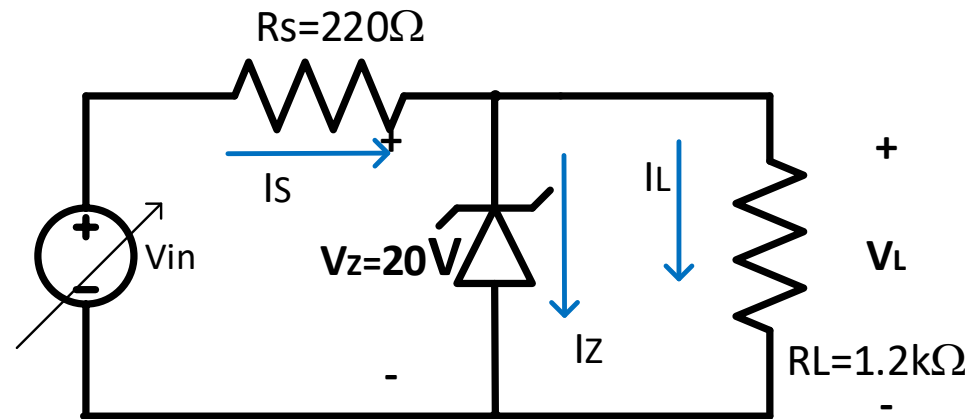
$$I_{S(\min)} - I_{L(\max)} \geq I_{Z(\min)}$$



$$\frac{V_{S(\min)} - V_Z}{R_S} - I_{L(\max)} \geq I_{Z(\min)}$$

$$I_{Z(\min)} + I_{L(\max)} \leq \frac{V_{S(\min)} - V_Z}{R_S}$$

$$R_S \leq \frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}}$$

Design of Rs (Current limiting Resistor)

Given : $V_Z, I_{Z(\min)}, I_{Z(\max)}, V_{in(\min)}, V_{in(\max)}, R_{L(\min)}, R_{L(\max)}$

Find range of acceptable Rs in the voltage regulator

$$2) I_Z \leq I_{Z(\max)}$$

Worst Case : the largest value of $(I_S - I_L)$ must be always smaller than $I_{Z(\max)}$

$$I_{S(\max)} - I_{L(\min)} \leq I_{Z(\max)}$$

Note That

$$I_{L(\min)} = \frac{V_Z}{R_{L(\max)}}$$

$$I_{L(\max)} = \frac{V_Z}{R_{L(\min)}}$$

$$\frac{V_{S(\max)} - V_Z}{R_S} - I_{L(\min)} \leq I_{Z(\max)}$$

$$I_{Z(\max)} + I_{L(\min)} \geq \frac{V_{S(\max)} - V_Z}{R_S}$$

$$R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_S \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

Design of R_s (Current limiting Resistor)

Given :

$$V_Z = 10 \text{ V},$$

$$I_{Z(\min)} = 5 \text{ mA}, I_{Z(\max)} = 200 \text{ mA},$$

$$V_{in(\min)} = 15 \text{ V}, V_{in(\max)} = 20 \text{ V},$$

$$R_{L(\min)} = 500, R_{L(\max)} = \infty$$

Find R_s ?

$$\frac{V_{S(\min)} - V_Z}{I_{Z(\min)} + I_{L(\max)}} \geq R_s \geq \frac{V_{S(\max)} - V_Z}{I_{Z(\max)} + I_{L(\min)}}$$

$$I_L(\max) = \frac{V_Z}{R_L(\min)} = 10/500 = 20 \text{ mA}$$

and

$$I_L(\min) = \frac{V_Z}{R_L(\max)} = 10/\text{infinity} = 0$$

$$200 \Omega \geq R_s \geq 50 \Omega$$

$$\text{let } R_s = 100 \Omega$$

Clipper circuits using Zeners

- a) When $V_i(t) < -0.7$ V, Zener works in region (1) as regular diode ON

$$0.7 + i_D(t) \cdot R + V_i(t) = 0$$

$$i_D(t) = \frac{-V_i(t) - 0.7}{R} > 0$$

$$V_i(t) < -0.7$$




$$\therefore V_O(t) = -0.7$$

- b) When $V_z > V_i(t) > -0.7$ V, Zener works in region (2) as regular diode OFF

$$\therefore V_O(t) = V_i(t)$$

- c) When $V_i(t) > V_z$, Zener works in region (3) as voltage regulator



$$\therefore V_O(t) = V_z$$

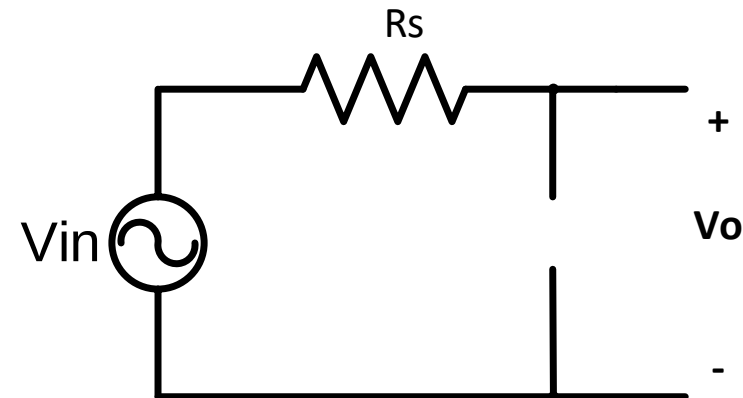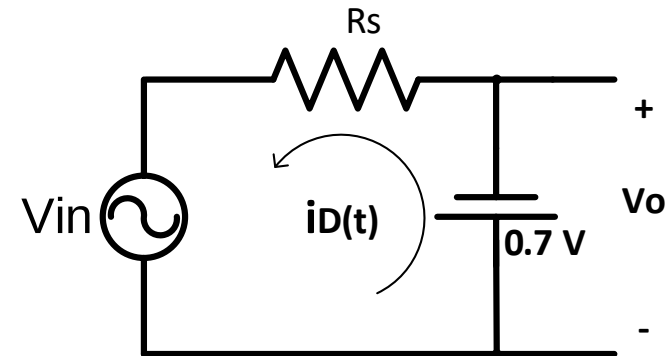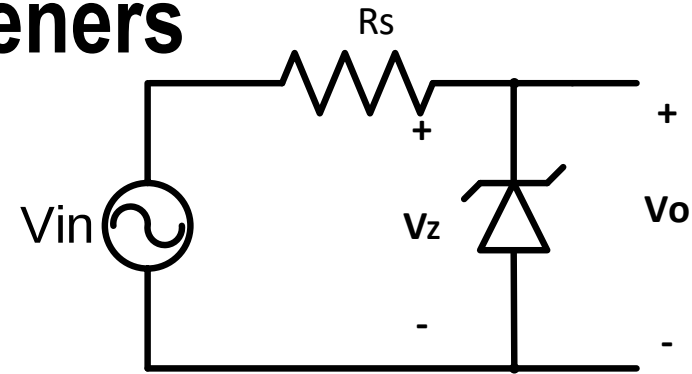

Clipper circuits using Zeners

c) When $V_i(t) > V_z$, Zener works in region (3) as voltage regulator

$$\therefore V_o(t) = V_z$$

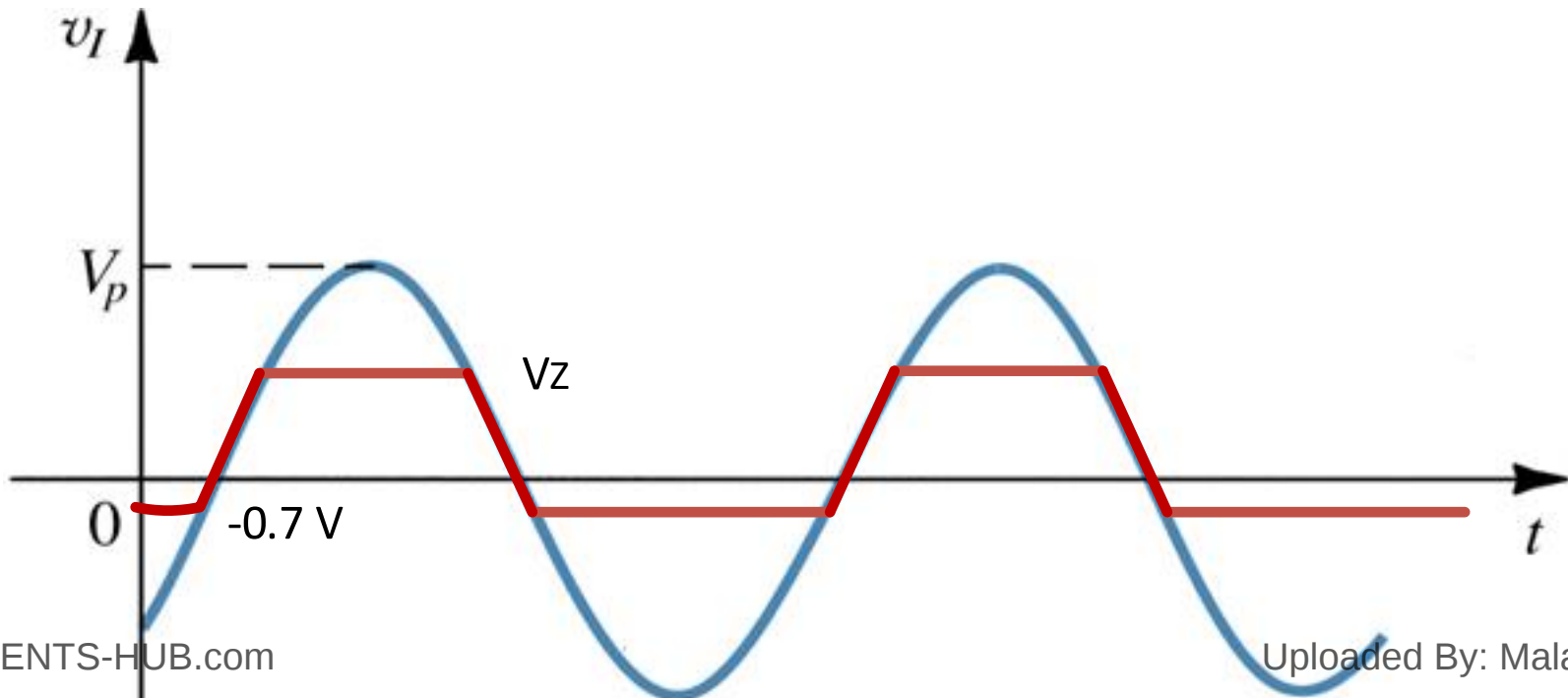
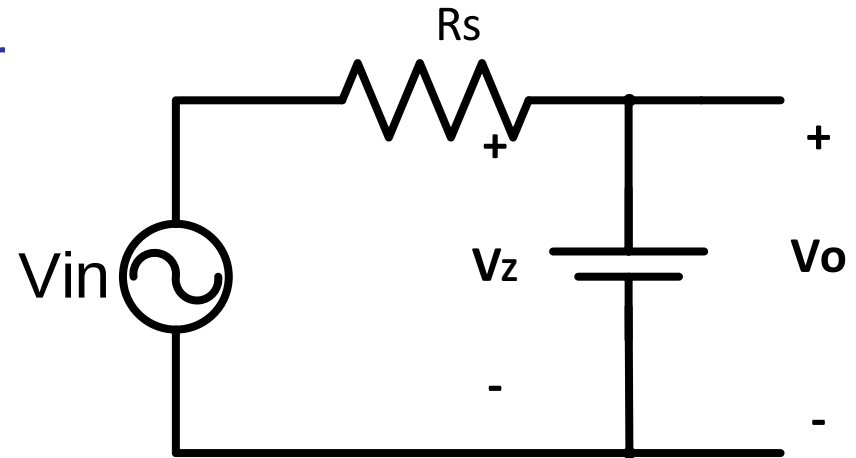


Clipper circuits using Zeners

Find and sketch $V_o(t)$


- a) When $0.7V < V_i(t) < V_{z2}$,
 D1- regular diode ON
 D2- regular diode OFF

$$\therefore V_o(t) = V_i(t)$$

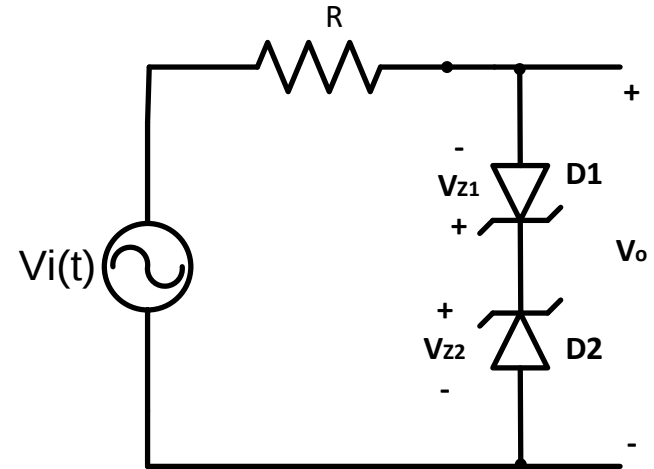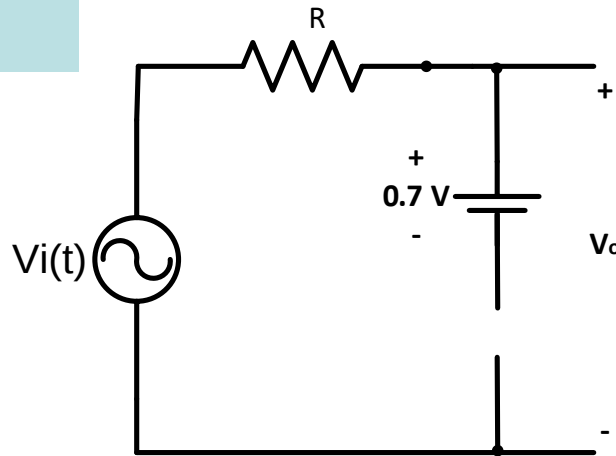

- b) When $V_i(t) > V_{z2}$
 D1 – ON (region 1)
 D2- Zener ON (region 3)

$$\therefore V_o(t) = V_{z2} + 0.7$$

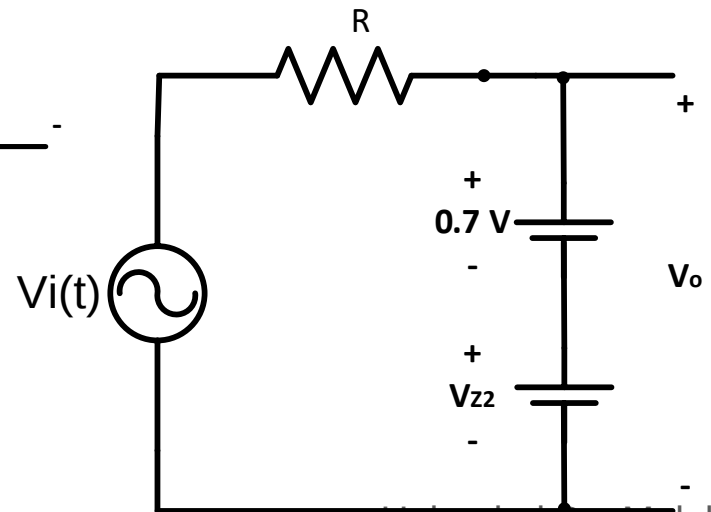


Clipper circuits using Zeners

c) When $-0.7V > V_i(t) > -V_{Z1}$,

D1- regular diode OFF

D2- regular diode ON

$$\therefore V_O(t) = V_i(t)$$

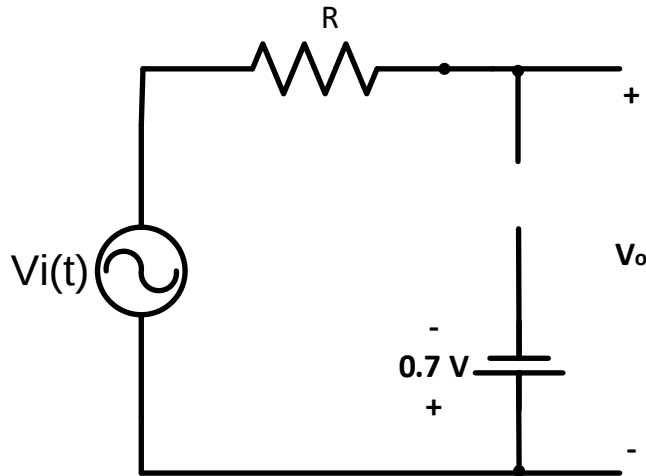

d) When $V_i(t) < -V_{Z1}$

D2 – ON (region 1)

D1- Zener ON (region 3)

$$\therefore V_O(t) = -V_{Z1} - 0.7$$

