



FACULTY OF ENGINEERING AND TECHNOLOGY
DEPARTMENT OF ELECTRICAL AND COMPUTER
ENGINEERING

ENEE 2101

Circuits Laboratory

Experiment.4 Prelab

Network Theorems

Prepared by:

Malak Qasem 1210484

Supervised by:



Dr. Jaser Sa'Ed

Teacher assistance:

Eng. Mohammed Deek

October 10, 2024

Part A: Proportionality

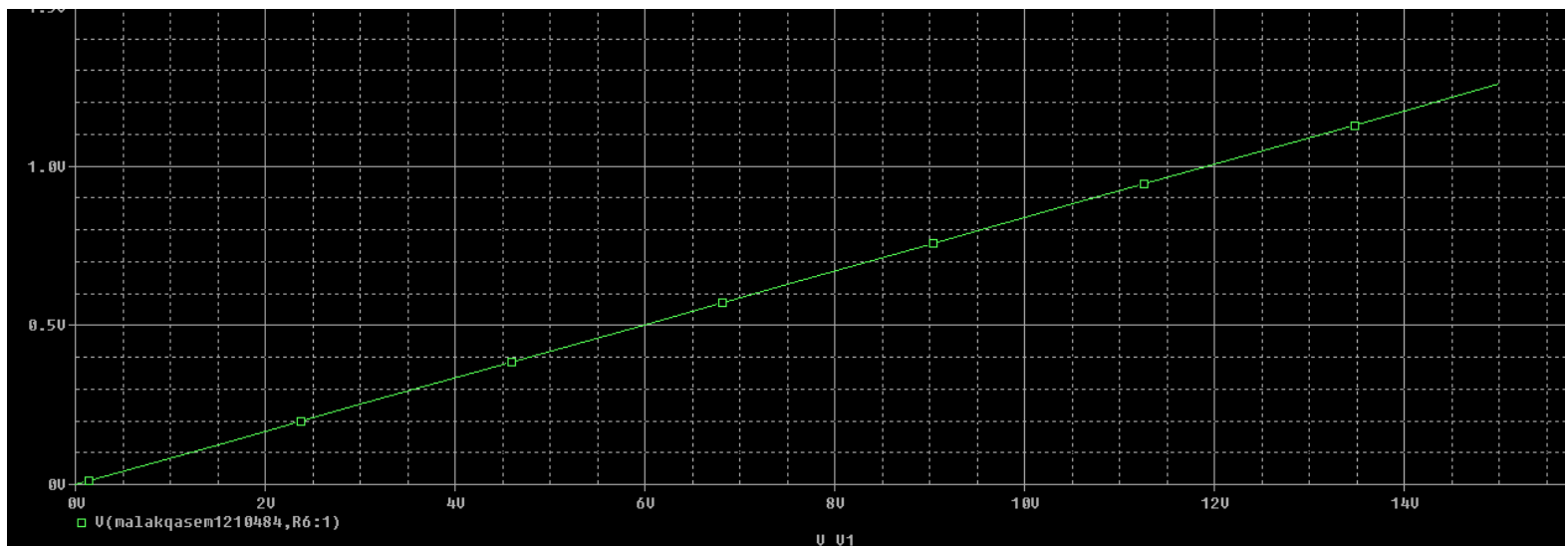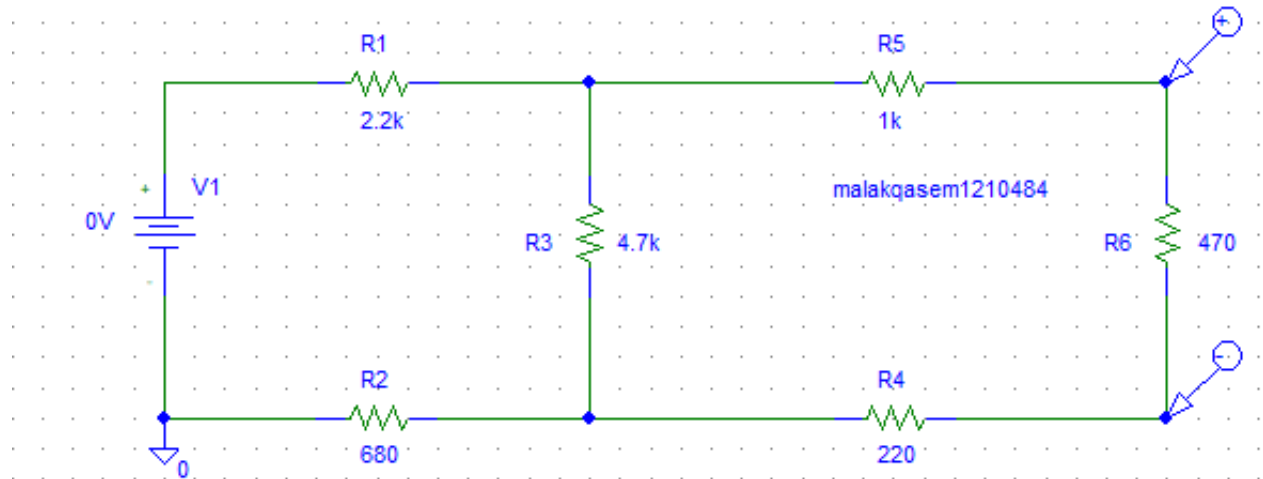

Part B: Superposition

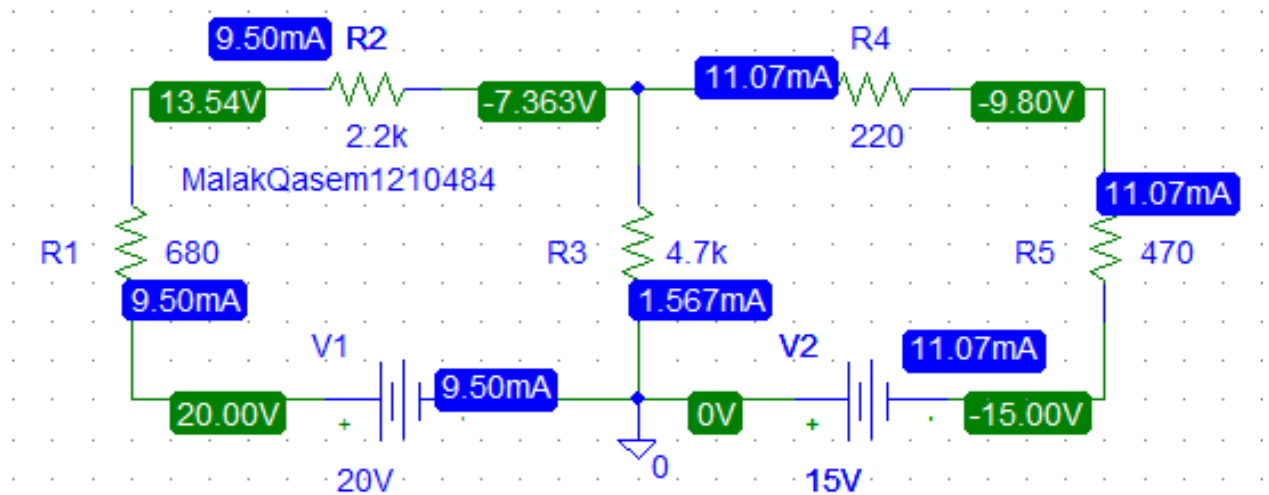


Figure 4.2

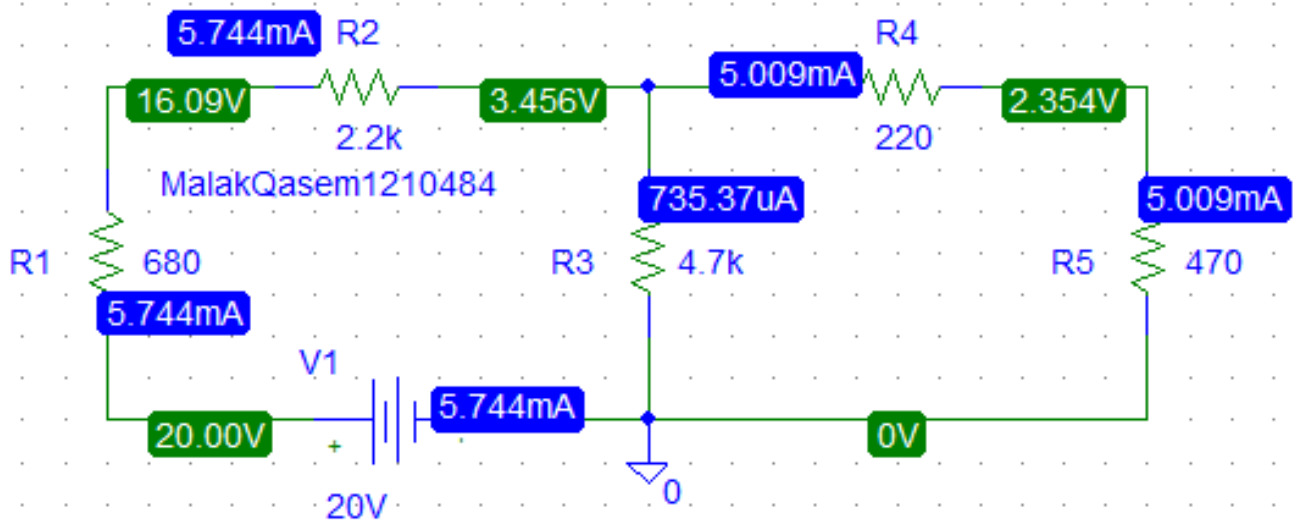


Figure 4.3


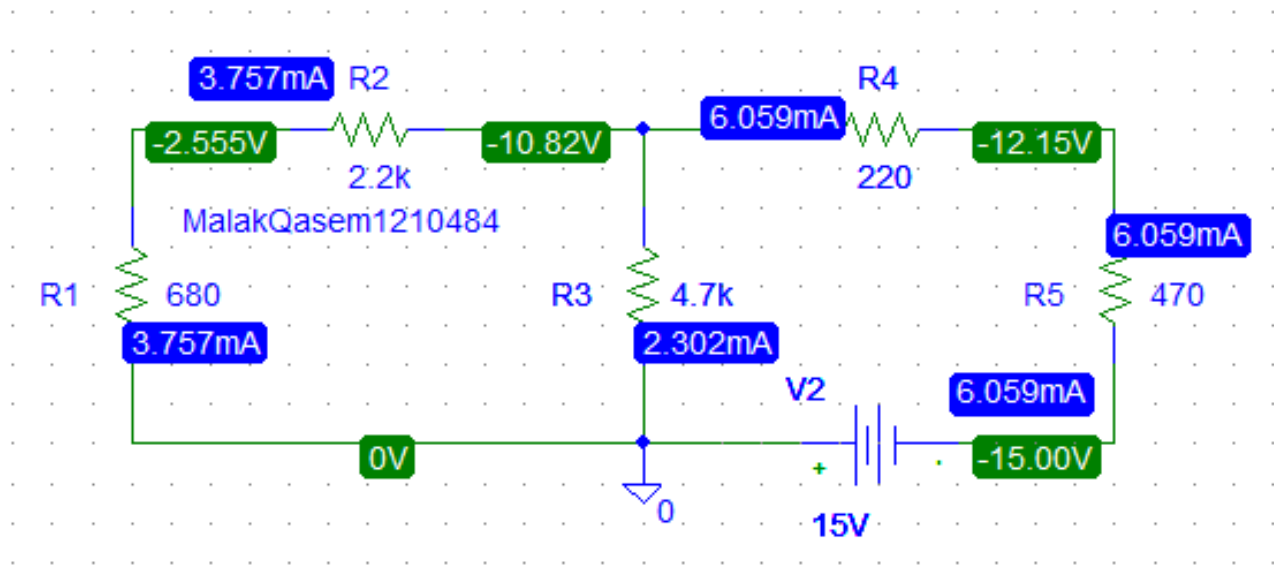


Figure 4.4

Part C: Thevenin's Theorem

1)

Malak Qasem
1210484

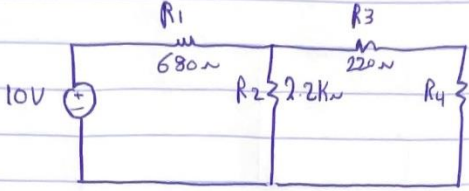


$10V$ $R_1 = 680\Omega$ $R_2 = 2.2k\Omega$ $R_3 = 220\Omega$ $R_4 = 330\Omega$ $R_L = 330\Omega$
Find V_{th} & R_{th}

• Find V_{th} using Voltage divider at " $2.2k\Omega$ "

$$V_{th} = V_{in} \times \frac{R_2}{R_2 + R_1} \Rightarrow V_{th} = 10V \times \frac{2200}{2200 + 680}$$

$\therefore V_{th} = 7.639 \text{ Volt}$

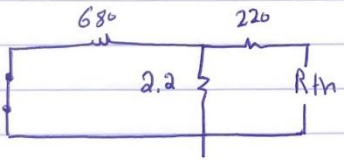• Find R_{th} using "short circuit" & but the Voltage ($10V$) at SC




680Ω 220Ω 2.2 R_{th} $680 // 2.2 + 220$

$$\therefore R_{th} = 220 + \frac{680 \times 2200}{680 + 2200} \Rightarrow \therefore R_{th} = 739.44\Omega$$

$\therefore R_{th} = 739.44\Omega$

\therefore Thevenin equivalent Circuit:

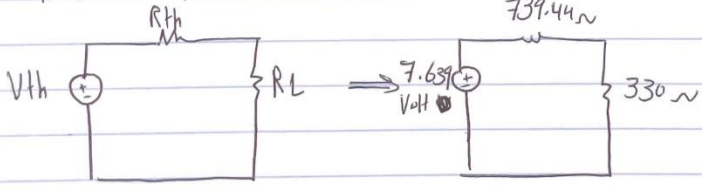

V_{th} R_{th} R_L $7.639V_{th}$ 739.44Ω 330Ω

2)

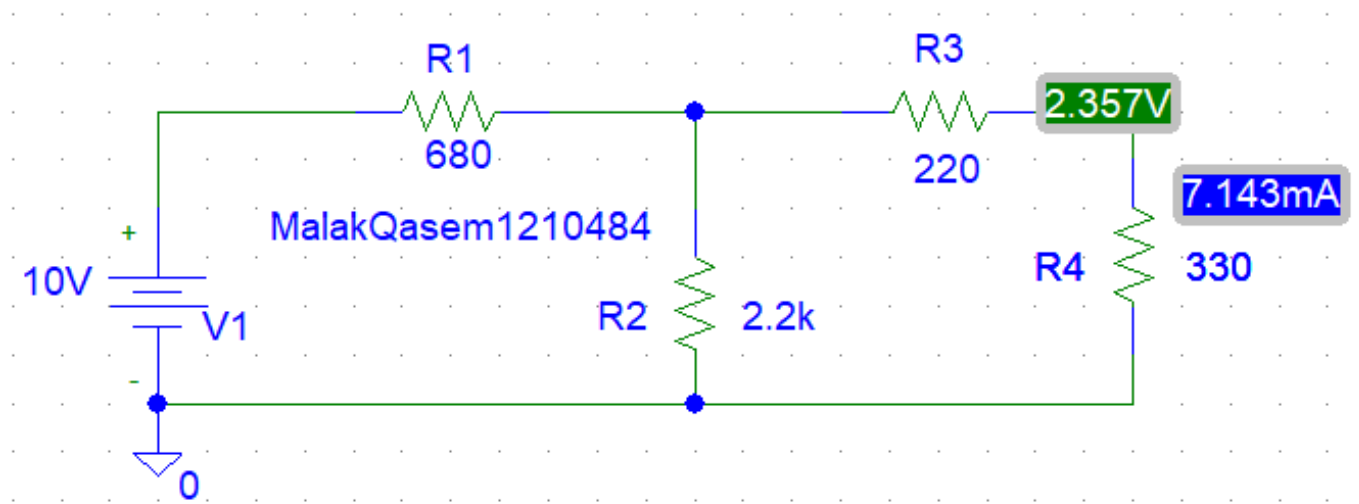


Figure 4.5

3)

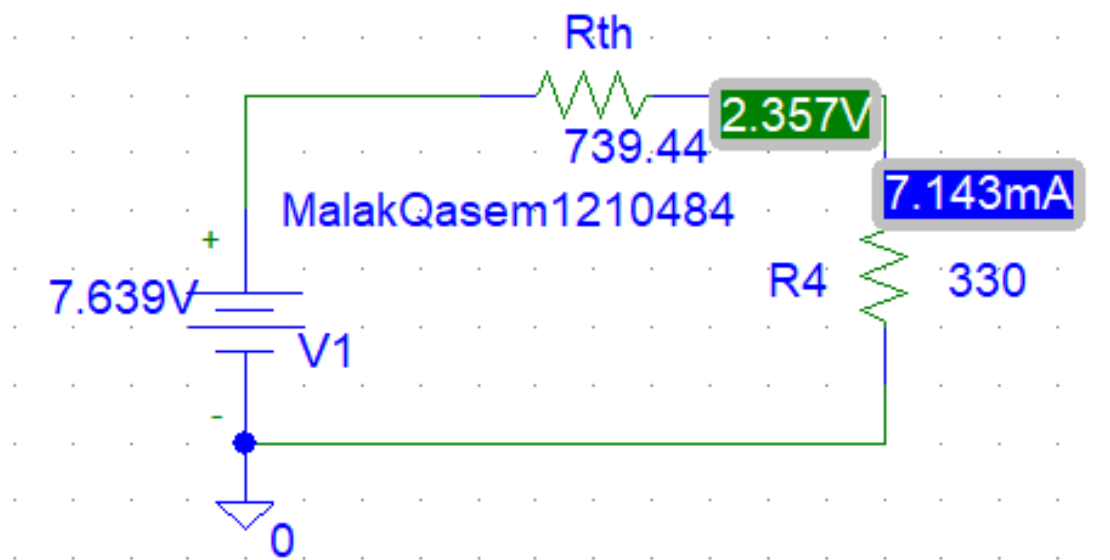



Figure 4.7

Part D: Δ -Y Transformation

1)

Malak Qasem

1210484

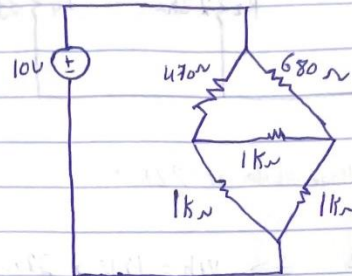


transform Δ to Y use This equation "for $1k\Omega$ Resistors":

$$R_1 = \frac{R_A \cdot R_B}{R_A + R_B + R_C}, \quad R_2 = \frac{R_B \cdot R_C}{R_A + R_B + R_C}, \quad R_3 = \frac{R_C \cdot R_A}{R_A + R_B + R_C}$$


Knowing That ~~1k~~ $R_A = R_B = R_C = 1k\Omega$

$$\Rightarrow R_1 = R_2 = R_3 = \frac{1k\Omega \cdot 1k\Omega}{1k\Omega + 1k\Omega + 1k\Omega} = \frac{1k\Omega^2}{3k\Omega} = 333.33\Omega$$


\Rightarrow The resulting circuit:

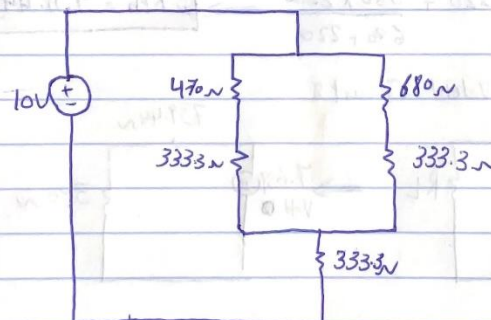

2)

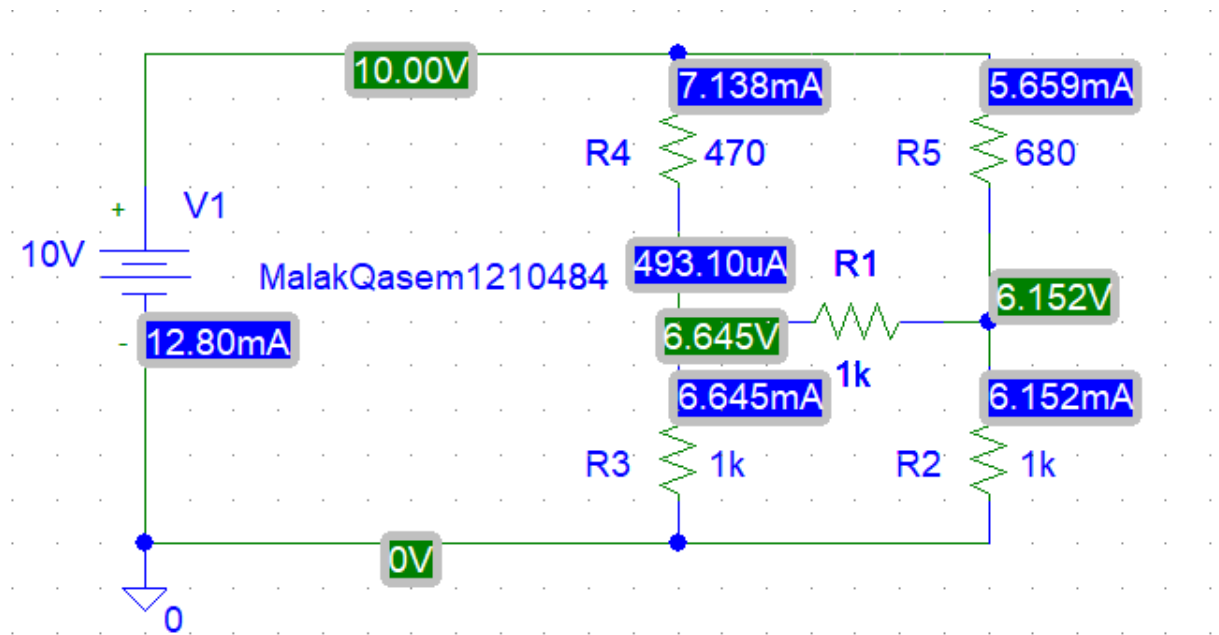

3)

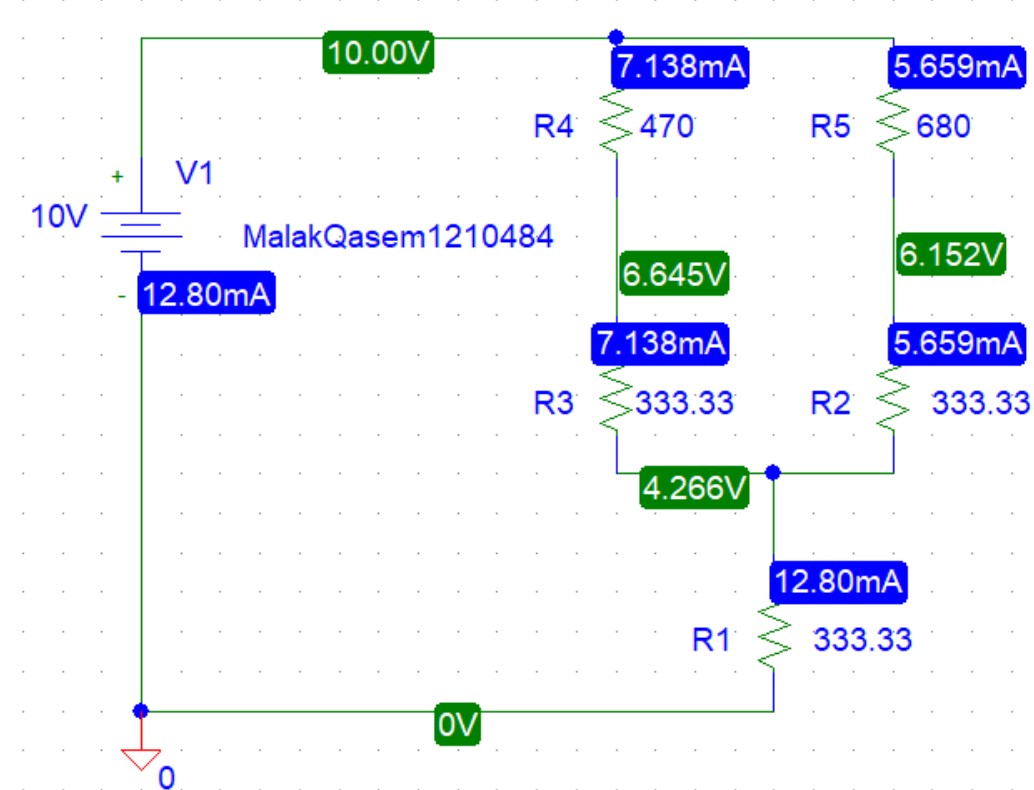

Part E: Reciprocity Theorem

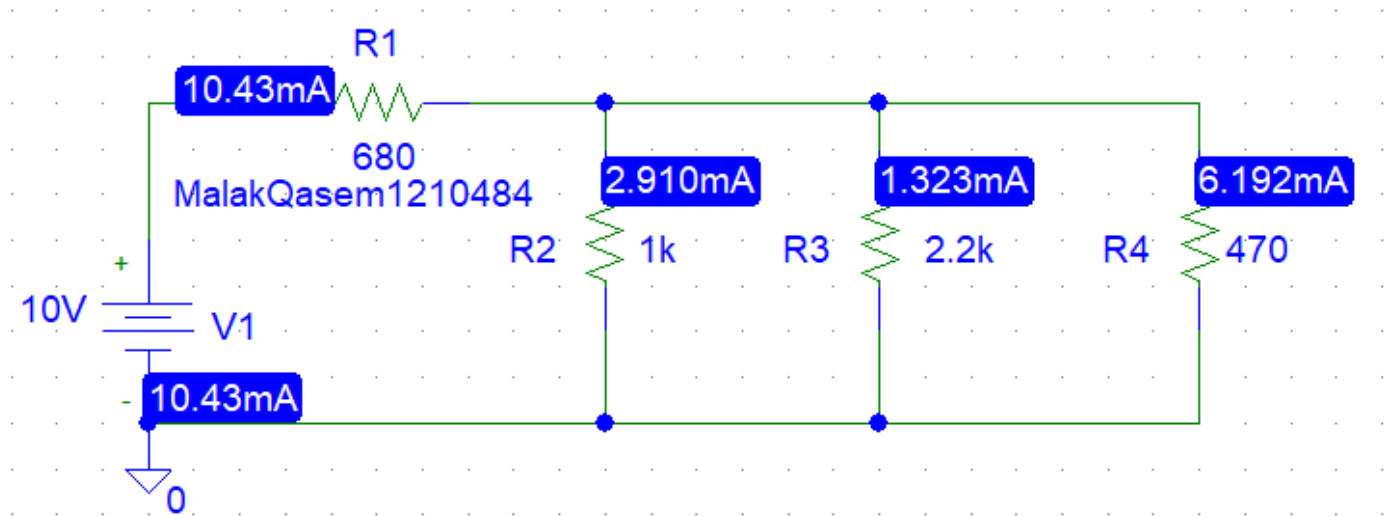


Figure 4.8

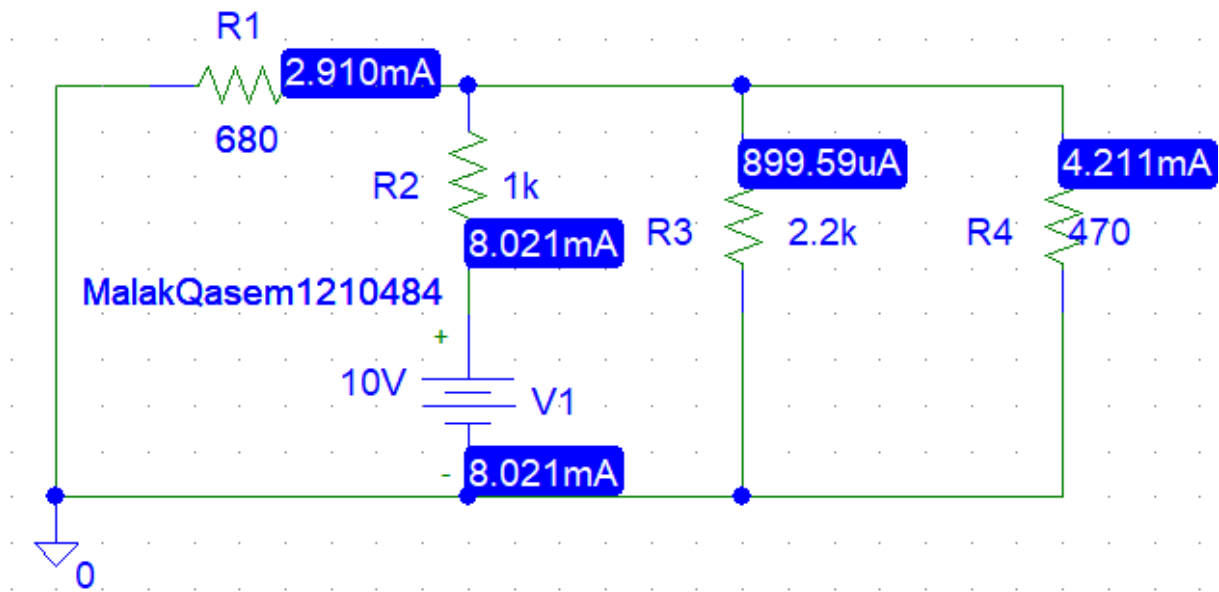


Figure 4.9