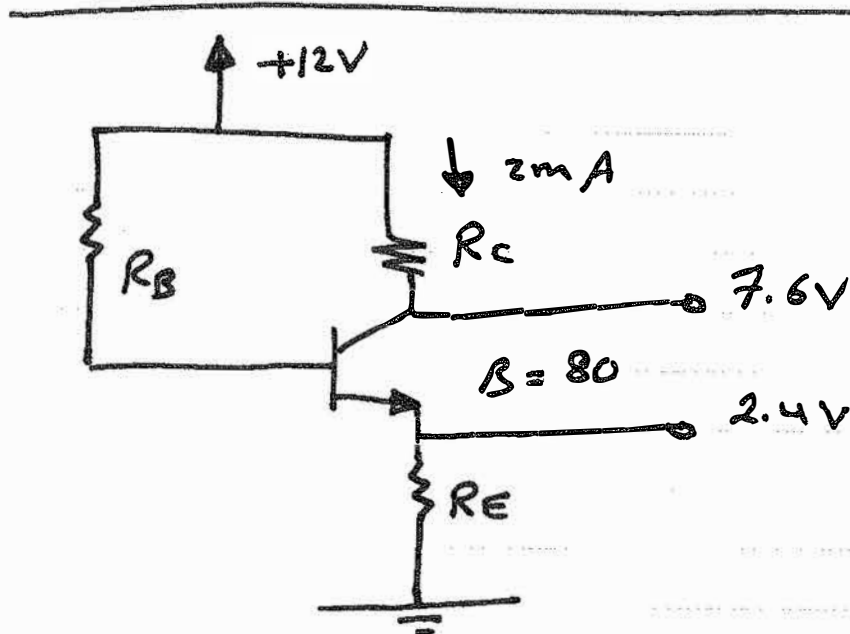


# ENEE236 CH4 SOLUTIONS

10



$$I_C = 2mA$$

$$I_E = I_C + I_B = 2mA + \frac{2mA}{80} = 2.025mA$$

$$V_E = 2.4 = R_E I_E$$

$$\therefore R_E = \frac{2.4}{2.025} = 1.185K$$

$$R_C = \frac{12 - 7.6}{2mA} = 2.2K$$

$$12 = R_B I_B + V_{BE} + V_E$$


$$\therefore R_B = \frac{12 - 2.4 - 0.7}{\frac{2mA}{80}} = 356K$$

$$V_{CE} = V_C - V_E = 5.2V$$

$$V_B = V_{BE} + V_E = 3.1V$$

-1-

11

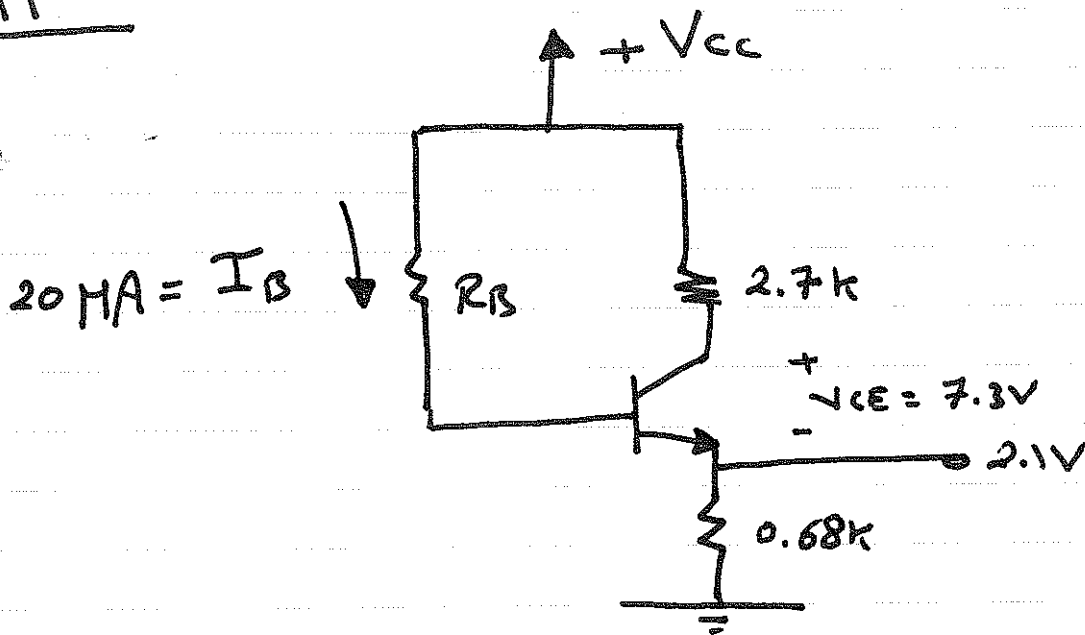

$$\beta = \frac{I_E}{I_B} - 1$$

$$I_E = \frac{V_E}{0.68k} = \frac{2.1}{0.68} = 3.088mA$$


$$\therefore \beta = \frac{3.088mA}{20mA} - 1 = 153.4$$

$$I_C = \beta I_B = 3.068mA$$

$$V_{CC} = (2.7k)I_C + V_{CE} + V_E = 17.68V$$

$$V_{CC} = R_B I_B + V_{BE} + V_E$$
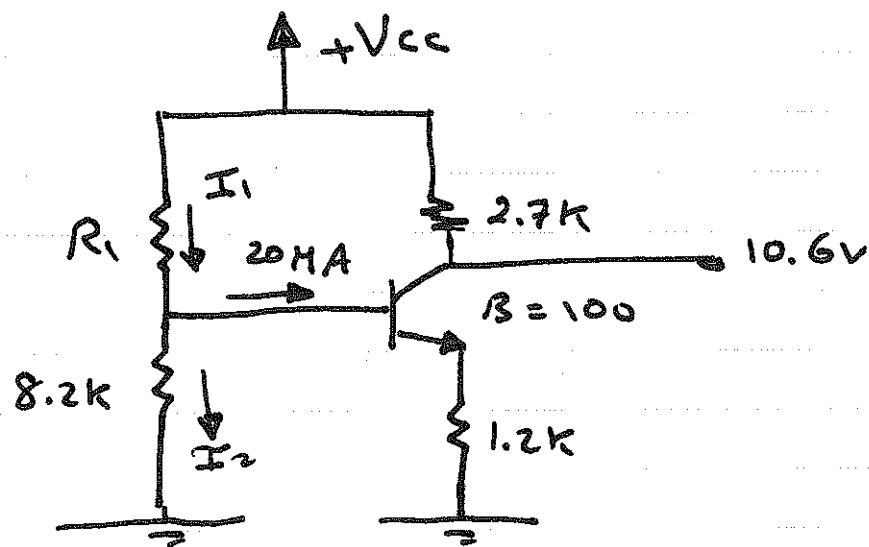
$$\therefore R_B = \frac{V_{CC} - V_E - V_{BE}}{I_B} = 744.18k$$



$$I_C = \beta I_B = 2mA$$

$$I_E = I_C + I_B = 2.02mA$$

$$V_E = (1.2k)(2.02mA) = 2.424V$$

$$V_{CE} = V_C - V_E = 10.6 - 2.424 = 8.176V$$

$$V_{CC} = 2.7k I_C + 10.6 = 16V$$


$$V_B = V_{BE} + (1.2k)(I_E) = 3.124V$$

$$I_2 = \frac{V_B}{8.2k} = 0.381mA$$

$$I_1 = I_2 + I_B = 0.4mA$$

$$R_1 = \frac{V_{CC} - V_B}{I_1} = 32.11k$$

33

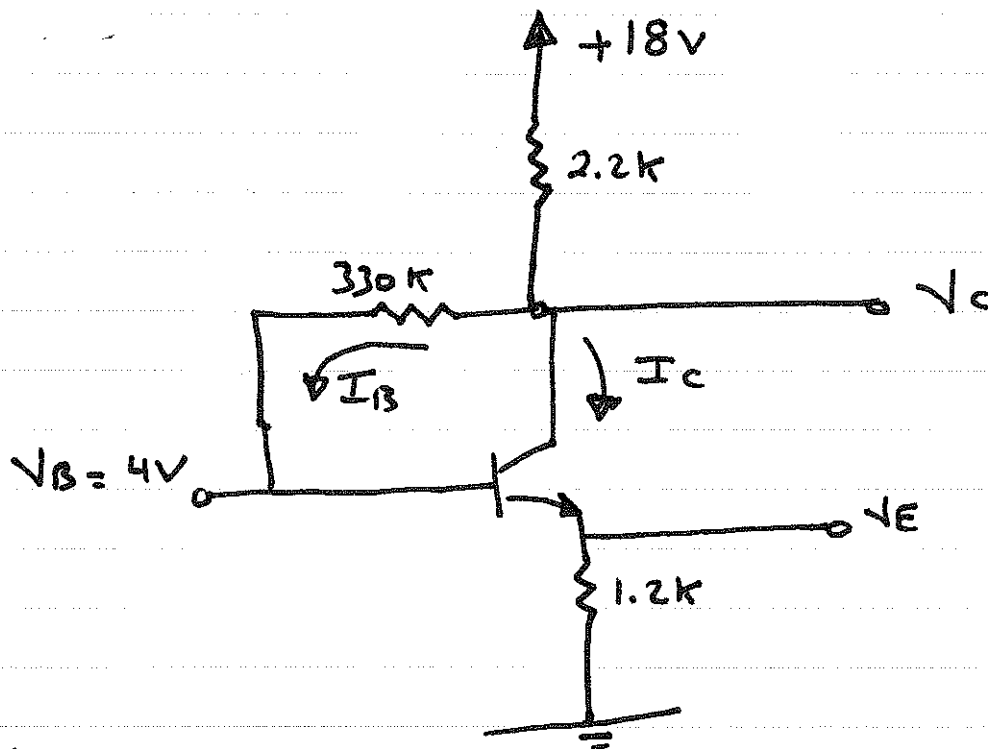

$$V_B = 4V = 0.7 + V_E$$

$$\therefore V_E = 3.3V$$

$$I_E = \frac{V_E}{1.2k} = 2.75mA$$

$$V_{CC} = (2.2k)(I_E) + 330k I_B + V_B$$

$$\therefore I_B = 0.0241mA$$

$$\frac{I_E}{I_B} = \beta + 1$$


$$\therefore \beta = 113.15$$

$$I_C = \beta I_B = 2.726mA$$

$$V_C = 18 - (2.2k)(2.75) = 11.95$$

$$V_{CE} = V_C - V_E = 8.65V$$

34

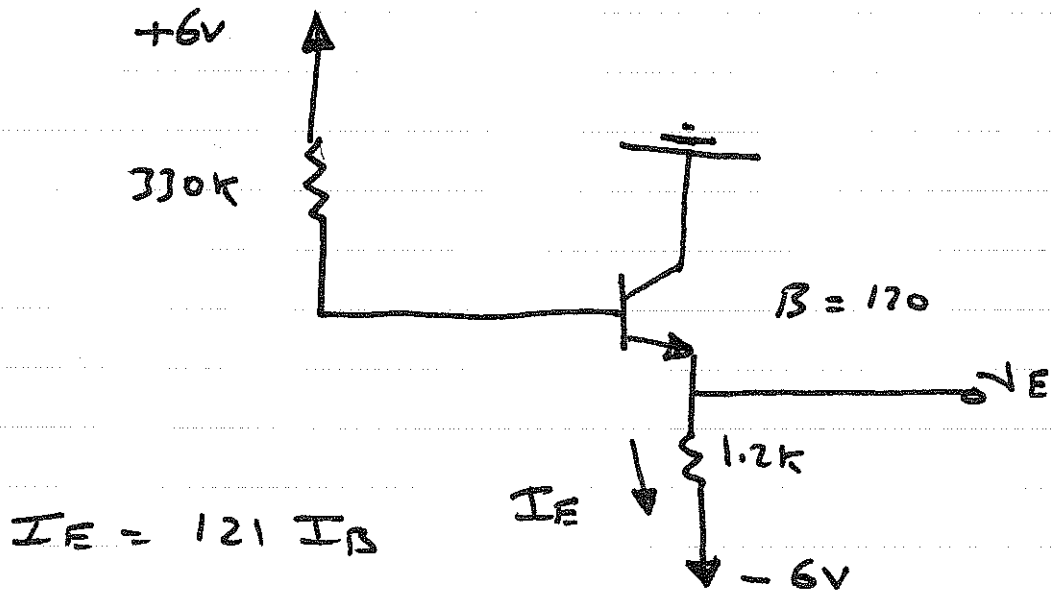

$$I_E = 121 I_B$$

$$6 = 330k I_B + V_{BE} + 1.2k I_E - 6$$

$$\therefore I_E = \frac{12 - 0.7}{1.2k + \frac{330k}{121}} = 2.88 \text{ mA}$$

$$V_E = (1.2k) I_E - 6 = -2.55 \text{ V}$$

43

$$V_E = \frac{1}{8} V_{CC} = 3V$$

$$R_E = \frac{V_E}{I_E}$$

$$I_E = I_C + I_B$$

$$\therefore R_E = \frac{3V}{4mA + \frac{4mA}{110}} = 0.743k$$

$$R_{TH} = \frac{(\beta+1)R_E}{10} = 8.25k$$

$$I_E = \frac{V_{TH} - 0.7}{R_E + \frac{R_{TH}}{\beta+1}}$$

$$\therefore V_{TH} = 3.97V$$

$$R_{TH} = \frac{R_1 R_2}{R_1 + R_2} = 8.25k$$


$$V_{TH} = \frac{R_2}{R_1 + R_2} = 3.97V$$

$$\therefore R_1 = 49.87k$$

$$R_2 = 9.88k$$

$$V_{CC} = R_C I_C + V_{CE} + R_E I_E$$
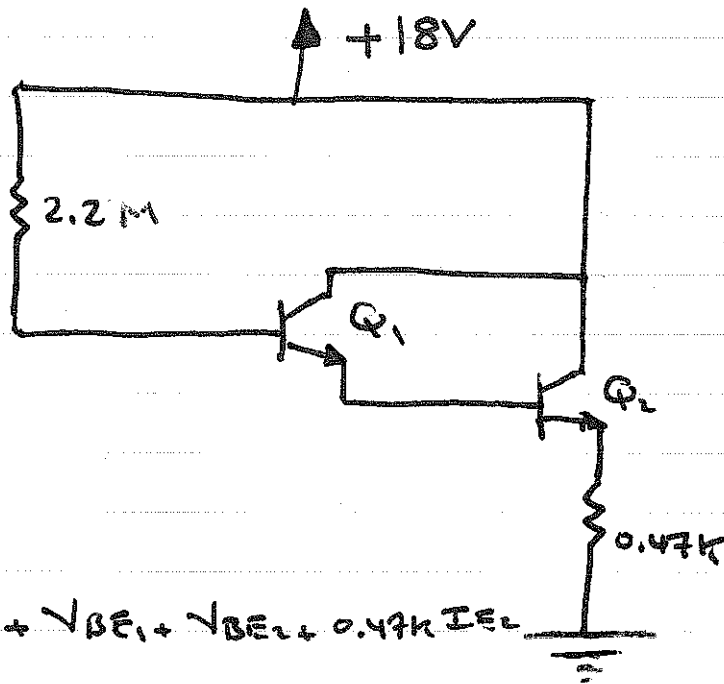
$$\therefore R_C = \frac{24 - 8 - 3}{4mA} = 3.25k$$



$$\beta_1 = 50$$

$$\beta_2 = 75$$

$$18 = 2.2M I_{B1} + V_{BE1} + V_{BE2} + 0.47K I_{E2}$$

$$I_{E2} = (\beta_2 + 1) I_{B2}$$

$$I_{B2} = I_{E1}$$

$$I_{E1} = (\beta_1 + 1) I_{B1}$$

$$I_{E2} = (\beta_2 + 1) (\beta_1 + 1) I_{B1}$$

$$\therefore I_{B1} = \frac{18 - 1.4}{2.2M + 0.47K (51)(76)}$$

$$I_{B1} = 4.128 \mu A$$

$$I_{C1} = \beta_1 I_{B1} = 206.38 \mu A$$


$$I_{C2} = 15.788 \mu A$$

$$V_{C1} = V_{C2} = 18V$$

$$V_{E1} = V_{BE2} + (0.47K)(I_{E2}) = 8.22V$$

$$V_{E2} = (0.47K)(I_{E2}) = 7.52V$$

56

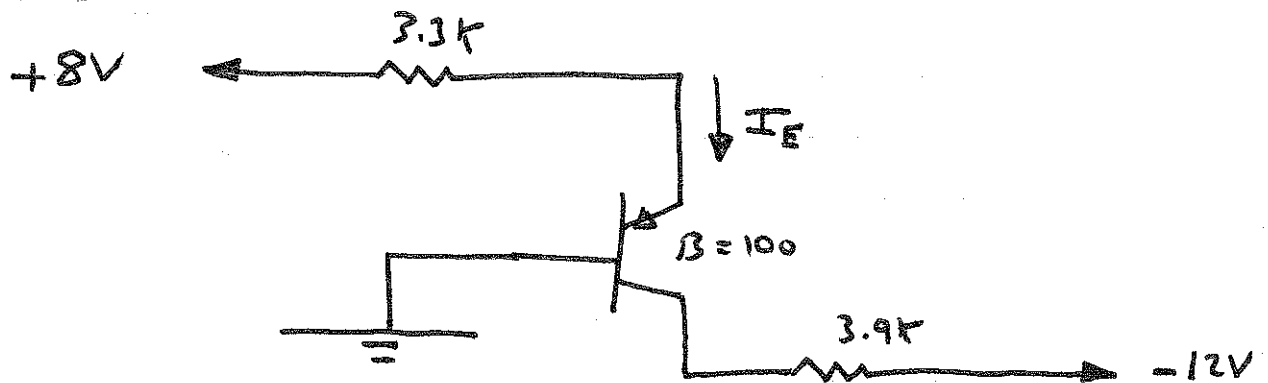

$$8 = 3.3k I_E + V_{EB}$$

$$\therefore I_E = 2.712 \text{ mA} ; I_C = 2.19 \text{ mA}$$

$$V_C = (3.9k)(I_C) - 12$$

$$V_C = 3.458 \text{ V}$$