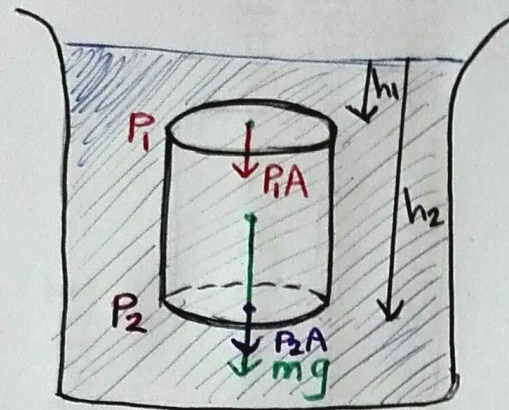


Experiment 3: Density of Liquids →

$$\text{pressure} = \frac{\text{Force}}{\text{Area}} \Rightarrow P = \frac{F}{A}$$



$$|P_2 > P_1|$$

$$\text{Static Equilibrium} \Rightarrow \sum \vec{F} = 0$$

$$P_2 A - P_1 A - mg = 0$$

$$(P_2 - P_1) A = mg$$


$$\text{use } \rho = m/V \Rightarrow \left\{ \text{Density} = \frac{\text{mass}}{\text{Volume}} \right\}$$

$$(P_2 - P_1) A = \rho V g$$

$$(P_2 - P_1) A = \rho A (h_2 - h_1) g$$

$$P_2 - P_1 = \rho (h_2 - h_1) g$$

Experiment 80

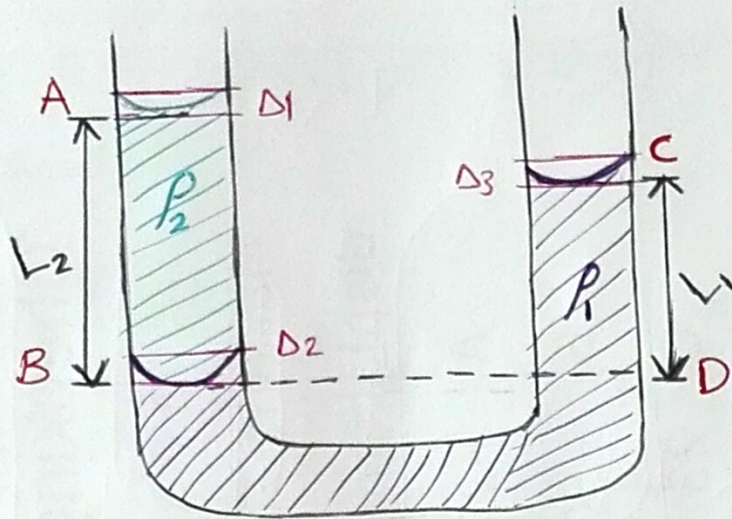

$$\boxed{\rho_1 > \rho_2}$$

$$\left[\begin{array}{l} \rho_1 \equiv \text{water} \\ \rho_{H_2O} = 1 \text{ g/cm}^3 \\ \rho_2 \equiv \text{oil} \end{array} \right.$$

$$P_B - P_A = \rho_2 L_2 g$$

$$P_D - P_C = \rho_1 L_1 g$$

$$P_B = P_D \quad \text{"Same vertical height"}$$

$$P_A = P_C = P_a \quad \text{"} P_a = \text{Atmospheric pressure"}$$

$$\rho_2 g L_2 = \rho_1 g L_1$$

$$\rho_2 L_2 = \rho_1 L_1$$

$$\Rightarrow \rho_{oil} L_2 = \rho_{H_2O} L_1$$

$$\rho_{oil} L_2 = (1 \text{ g/cm}^3) L_1$$

$$\rho_{oil} L_2 = L_1 \quad \text{"} \rho_{oil} \text{ in g/cm}^3 \text{"}$$

Data,

L_1 (cm)	1.6	3.3					L_1
L_2 (cm)	2.0	4.1					L_2


$$\Rightarrow L_1 = \rho L_2 \quad \text{"renamed } \rho_{oil} \text{ as } \rho"$$

- A graph of L_1 versus L_2 is a straight line with a slope equal to ρ .

$$\textcircled{L_1} = \textcircled{\rho} \textcircled{L_2}$$

Y-axis \swarrow slope \searrow X-axis
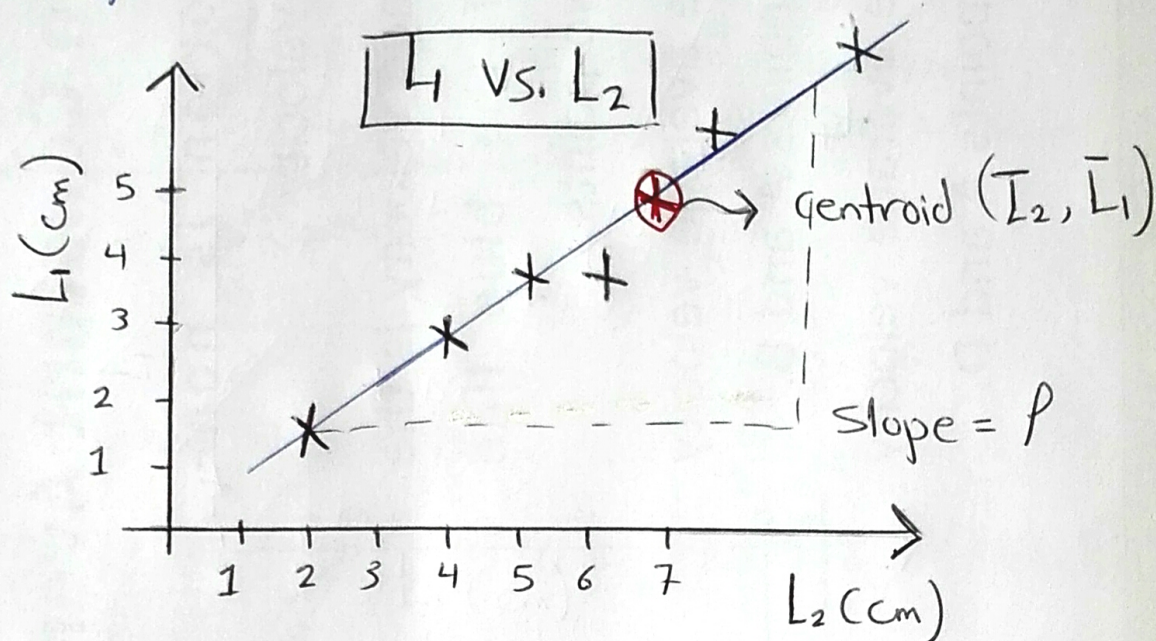
$$\begin{cases} y = mx + b \\ m = \text{slope} \\ b = \text{intercept} \end{cases}$$



- $\rho_{exp} = \text{slope}$, $\rho_{exp} \pm \Delta \rho$

Note $\rho_{theoretical} = 0.82 \text{ g/cm}^3$ "Paraffin oil"

STUDENTS HUB.com $\rho = \frac{L_1}{L_2}$

Uploaded By: Malak Obaid

$$\Delta \rho = \rho_{exp} \left[\frac{\Delta L_1}{\bar{L}_1} + \frac{\Delta L_2}{\bar{L}_2} \right]$$

$$\Delta L_1 = \Delta_2 + \Delta_3$$

$$\Delta L_2 = \Delta_1 + \Delta_2$$

Note


$\Delta_1, \Delta_2, \Delta_3 \Rightarrow$ in Cm

By estimation

Experiment 4: DC Circuits

* Voltage = Current \times Resistance


$$V = IR \text{ "Ohm's Law"}$$

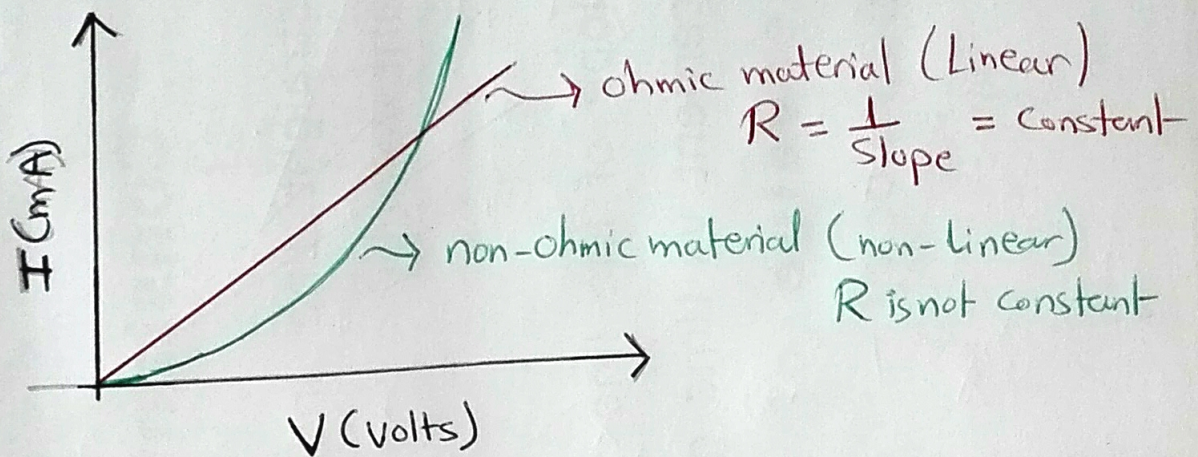

Experiment


part II

Carbon Resistance

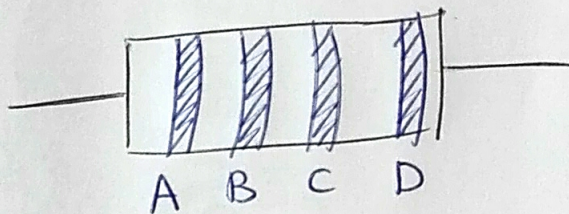

$$R = (AB \times 10^C \pm D(AB \times 10^C)) \Omega$$

STUDENTS-HUB.COM

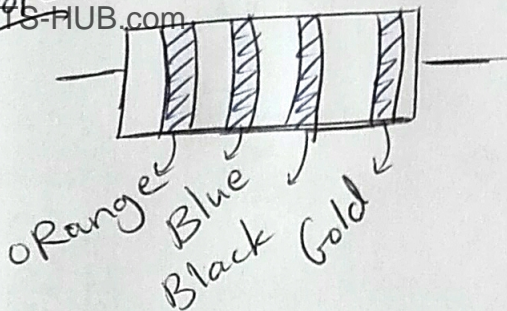


$$R = 36 \times 10^0 \pm (0.05 \times 36)$$


$$(36.0 \pm 1.8) \Omega$$

Uploaded By: Malak Obaid

• Circuit →

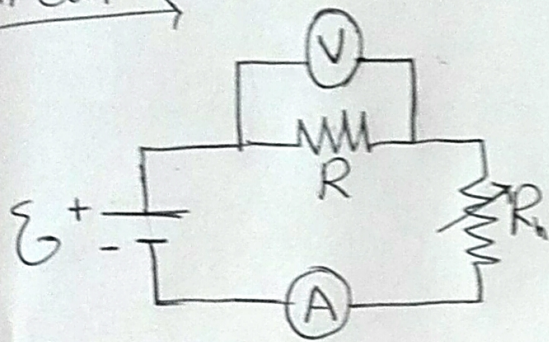

I (mA)							\bar{I}
V (volts)	0.5	1.0	1.5	2.0	2.5	3.0	\bar{V}

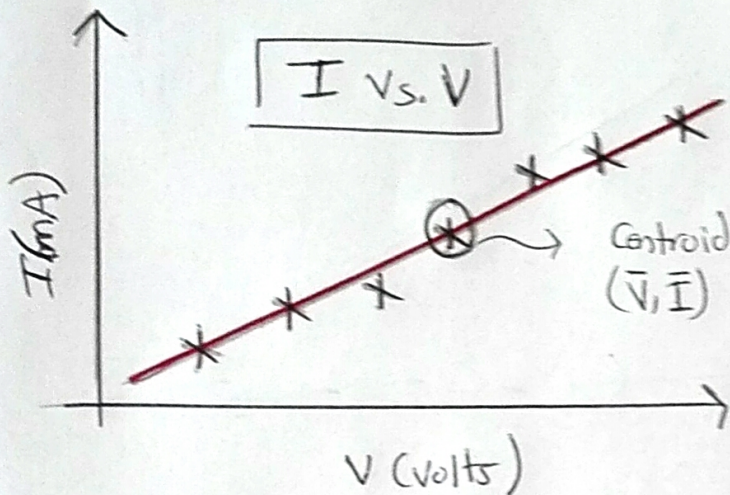

$$R_{exp} = \frac{1}{\text{slope}}$$

$$R = \frac{V}{I}$$

$$\Delta R = R_{exp} \left[\frac{\Delta V}{V} + \frac{\Delta I}{I} \right]$$

ΔV
 ΔI } By estimation
smallest division
in device.


• Range Test →

Note $R_{th} = (36.0 \pm 1.8) \Omega \Rightarrow R_{th} = (34.2, 37.8) \Omega$

$R_{exp} = (32 \pm 2) \Omega \Rightarrow R_{exp} = (30, 34) \Omega$

→ Not accepted "No intersection between the
True and experimental intervals"


Two Resistors in Series

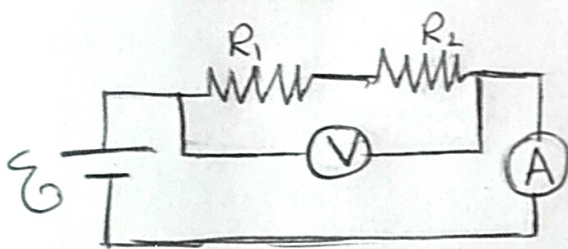

$$R_s = R_1 + R_2$$

$$R_{s,exp} = \frac{V}{I}$$

Two Resistors in Parallel

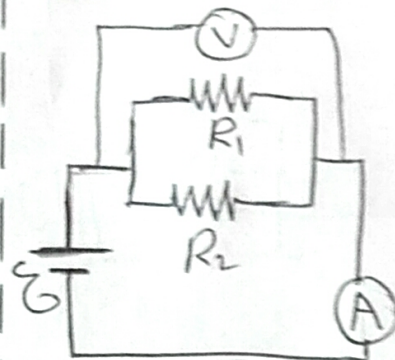

$$R_p = \frac{R_1 R_2}{R_1 + R_2}$$

$$R_{p,exp} = \frac{V}{I}$$