

Q59 $\mathcal{E} = 20 \text{ V}$ $q_e = 1.6 \times 10^{-19}$

a) The work done by the battery relates to the potential energy

$$W = q_e \mathcal{E} \Rightarrow W = q_e \mathcal{E} = 20 \text{ eV}$$

$$P_e = n_e \mathcal{E}$$

b) $P_e = \mathcal{E} I$, , , $I = \frac{q_e}{t}$ and $q_e = \frac{Ne}{t} \Rightarrow I = \frac{Ne}{t} \Rightarrow P = \frac{Ne}{t} \mathcal{E} = \frac{n_e}{t} \mathcal{E} = (5.17 \times 10^{18} / \text{s}) (1.6 \times 10^{-19}) (20)$

Q62 $C = 1 \times 10^{-6} \text{ F}$, $U = 0.6 \text{ J}$, $R = 1 \text{ M}\Omega = 1 \times 10^6 \Omega$

a) The initial energy stored in a capacitor is given by $U_e = \frac{q_0^2}{2C} \Rightarrow q_0 = \sqrt{2UC} = \sqrt{2(0.6)(1 \times 10^{-6})} = 1.095 \times 10^{-3}$

b) I discharge $\Rightarrow I = \frac{q_0}{RC} e^{-t/\tau}$, before that we want to find $\tau \Rightarrow \tau = RC = 1 \times 10^{-6} \times 10^6 = 1 \text{ s}$

and because we want to find I when the discharge starts $\therefore t = 0$ $\therefore$ the equation became $\Rightarrow I_0 = \frac{q_0}{RC} = \frac{q_0}{\tau} = \frac{1.095 \times 10^{-3}}{1} = 1.095 \times 10^{-3} \text{ A}$

c) $V_c = \frac{q}{C} \Rightarrow$ Now $q = q_0 e^{-t/\tau} \therefore V_c = \frac{q_0 e^{-t/\tau}}{C} = \frac{1.095 \times 10^{-3} e^{-t/1}}{1 \times 10^{-6}} = 1095 e^{-t} \text{ V}$

d) $V_R = I R = (1.095 \times 10^{-3}) (1 \times 10^6) e^{-t/1} = 1095 e^{-t}$

e) $P = I^2 R = (1.095 \times 10^{-3})^2 (1 \times 10^6) e^{-2t/1}$