



BIRZEIT UNIVERSITY

ANSWER BOOKLET

Student: <u>Digital</u> Number <u>8</u>
Course: Department: Number:
Division: Instructor:
Date: Day Month Year

For Instructor's Use





Question	Grade
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	
Total	

⊛ Binary adder

⇒ gate level HDL Ex 4.2


⇒ data flow HDL Ex 4.4

⊛ 3 state Gates

    

e.g. `bufif1 (out, A, control);` ⇒ $out = A$ if $c = 1$
`notif1 (Y, B, enable);` $y = B'$ if $enable = 0$

Ex

 

if $select = 1$

$out = A$

if $select = 0$

$out = B$

* mux (tri) in gate level page 152

* mux with data flow HDL example 4-6

⊗ comparator with data flow
HDL Example 4-5

Example: Design a logic circuit with 3 inputs A, B, and C and one output that indicates whether the input number is prime or not.

Write a gate level HDL to describe this circuit.


Write a test bench that tests the circuit for all possible input combinations and generates a log file of the results.

Solution

A	B	C	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

A \ B	00	01	11	10
0		1	1	1
1		1	1	

$$P = C + A'B$$

 


```

module prime(A,B,C,y);
  input A,B,C;
  output y;
  wire e1,e2;
  not g1(e1,A);
  and g2(e2,e1,B);
  or g3(y,e2,C);
endmodule

```

```

module test
  reg [2:0] D;
  wire out;
  prime pr1(D[2],D[1],D[0],out);
  initial
    begin
      D = 3'b000;
      repeat(8)
        #10 D = D + 1'b1;
      end
  initial
    $monitor("ABC = %b y = %b", D, out);
endmodule

```

④ $S = A + B$

\Rightarrow assign $S = A + B$; continuous assignment
data flow

always @ (A or B)

$S = A + B$;

procedural assignment
behavioural description

⑥ Verilog HDL operators

1) Arithmetic $+$, $-$, $*$, $/$, $\%$

2) Logic (bitwise or reduction operator)
 \sim , $\&$, $|$, $^$

③ Logical : $!$, $\&\&$, $||$

eg $A = 101$ $B = 011$ $C = 000$

$A \& B = 001$

$A \&\& B = (1) \&\& (1) = 1$

$A \&\& C = (1) \&\& (0) = 0$

④ Shift \gg shift right

\ll " left

$\{ , \}$ concatenation

eg $\{ C, S \} = X + Y + Z$

⑤ Relational $>$, $<$, $==$, $!=$, $>=$, $<=$

eg $R = 11010$

⑧ Loop Statements

- Verilog HDL has four types of loops that allow procedural statements to be executed repeatedly: repeat, forever, while, for.
- All looping statements must appear inside an initial or always block.

Ex:

integer count;

initial

begin

count = 0;

while (count < 100) // forever // repeat(20)

#5 count = count + 2

end

Ex: for (i=0; i<8; i=i+1)

procedural statement

HDL Example 8-1

④ Logic Synthesis

- ASIC, PLD and FPGA

assign for combinational circuits

assign $y = A \mid B$ (gate circuit)

// $y = A + B$ (full adder)

// $y = A - B$ (// // with xor gates)

// $y = s ? I_1 : I_0$ (2x1 mux)

- always : for sequential or combinational circuits

e.g. always @ (I₁ or I₀ or s)

if (s) $y = I_1$;
else $y = I_0$;
(2x1 mux)

- case statement (large mux).