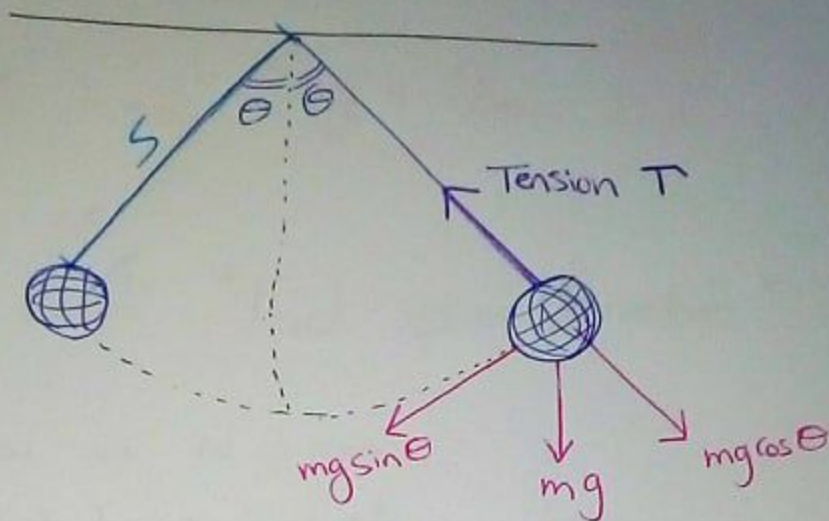


Experiment 7: Measuring g at BZU

• Simple pendulum

$$\theta \leq 15^\circ$$



$$L = S + \frac{d}{2}$$

$$F_c = T - mg \cos \theta = \frac{mv^2}{L}$$

$$\text{Period} \equiv T = \frac{2\pi}{\omega} = 2\pi \sqrt{\frac{L}{g}}$$

$$T = 2\pi \sqrt{\frac{L}{g}}$$

$$T^2 = \frac{4\pi^2}{g} L$$

Experiment

		10 periods		$T = t_{\text{avg}}/2$		
S (cm)	L (cm)	t_1 (sec)	t_2 (sec)	t_{avg} (sec)	T (sec)	T^2 (sec ²)
39.0	40.0	—	—			
50.5	51.5	—	—			

T^2 vs. $L \Rightarrow$ A straight line with slope = $\frac{4\pi^2}{g}$

$$g_{\text{exp}} = \frac{4\pi^2}{\text{Slope}}$$

$$\frac{\Delta g}{g_{\text{exp}}} = \frac{\Delta \text{slope}}{\text{slope}} \Rightarrow \Delta g = g_{\text{exp}} \frac{\Delta \text{slope}}{\text{slope}}$$

By using Excel "Least square fit method"

$$\text{slope } m \Rightarrow m \pm \Delta m$$

$$Y\text{-intercept } b \Rightarrow b \pm \Delta b$$

Experiment 9: RC circuit

Capacitor $Q = CV$; $[C] = F$

Charging the capacitor


at $t = 0$, $Q = 0$, $V_c = 0$

at $t \rightarrow \infty$, $Q = Q_0 = C\varepsilon \equiv \text{max. charge}$
 $V_c = \varepsilon$


$$V_c(t) = \varepsilon (1 - e^{-t/\tau})$$

$$Q(t) = C\varepsilon (1 - e^{-t/\tau})$$

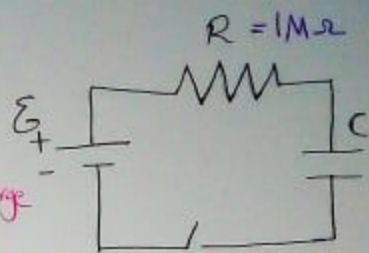$\tau \equiv \text{time constant}$ $\tau = RC$



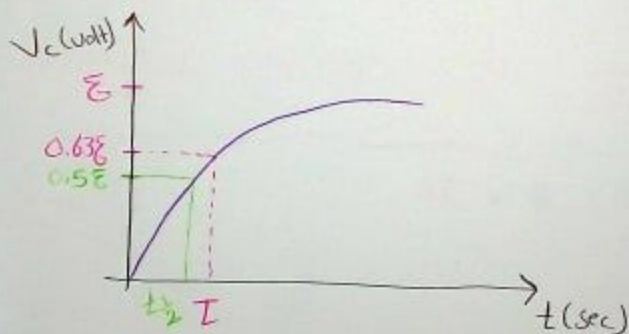at $t = \tau \Rightarrow V_c = 0.63\varepsilon$, $Q = 0.63 C\varepsilon = 0.63 Q_0$




Discharging the capacitor

at $t = 0$, $Q = Q_0 = \varepsilon C$, $V = \varepsilon$

$t \rightarrow \infty$, $Q = V = 0$

$$V_c(t) = \varepsilon e^{-t/\tau}$$

$$Q = C\varepsilon e^{-t/\tau}$$

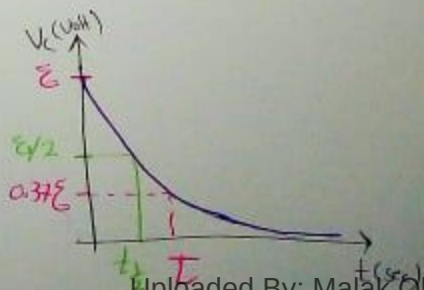


at $t = \tau \Rightarrow V_c = 0.37\varepsilon$, $Q = 0.37 Q_0$

• $t_{\frac{1}{2}} \equiv$ Half time

$$t_{\frac{1}{2}} = \tau \ln 2$$

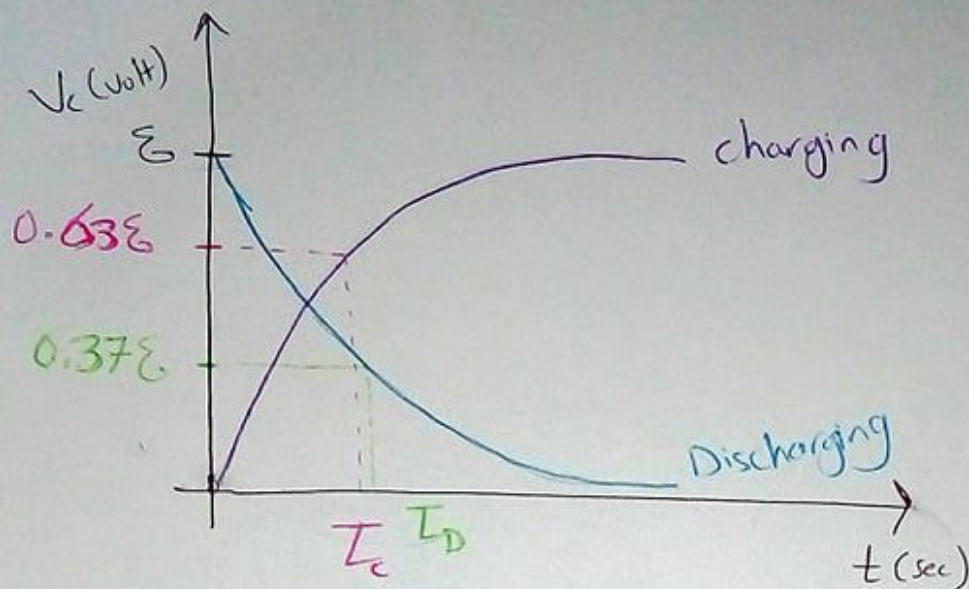at $t = t_{\frac{1}{2}} \Rightarrow V_c = \frac{\mathcal{E}}{2}$



$\Rightarrow$ Discharging $V_c = \mathcal{E} e^{-t/\tau}$

$$\ln V_c = \ln \mathcal{E} - \frac{t}{\tau} \sim \text{X-axis}$$

Y-axis

$\ln V_c$ Vs. t

Straight line with slope $= -\frac{1}{\tau} = -\frac{1}{RC}$ and Y-intercept $= \ln \mathcal{E}$

$$C_{exp} = \frac{\tau}{R}$$

$$\Delta \tau \equiv \sigma_m(\tau)$$

$$\frac{\Delta C}{C_{exp}} = \frac{\Delta \tau}{\tau} + \frac{\Delta R}{R}$$