STUDENTS-HUB.com

STUDENTS-HUB.com



Transformer: Used to increase or decrease the amplitude of the ac line voltage Rectifier: used to convert the ac voltage (zero- average value) into either positive and negative pulsating dc.

Filter : used to smooth out the pulsating dc produced by the rectifier by removing its ac ripple contents and passing its dc component (average value) Regulator: used to maintain a constant DC output voltage under variations in the load Current drawn from the supply and under variation in AC line voltage anonymous

- An ideal power supply maintains a constant voltage at its output terminal , no matter what current it drawn from it .
- The output voltage of a practical power supply changes with load current.
- One measure of power supply performance is called percent voltage regulation.

 $Vr = \frac{VNL - VFL}{VFL} \times 100\%$

STUDENTS-HUB.com

Simple Voltage Regulator





$Pd, max = 12.5 \times 250 = 3.125 watt$

When $RL = \omega$ (OPEN CIRCUIT)

STUDENTS-HUB.com

Uploaded By: anonymous

mΑ

Simple Voltage Regulator



STUDENTS-HUB.cVm = 7.6%

Uploaded By: anonymous

 $Vr = rac{VNL - VFL}{VFL} \times 100\%$



1. Variation in IL will cause Iz to vary. This in turns will cause variation in Vz=Vo

2. The Zener power dissipation will increase as IL decreases.

STUDENTS-HUB.com

Types of Regulators





Blog Diagram of the series regulator

Control element: is a device whose operating state adjusts as necessary to maintain a constant Vo.

It is in series path between Vi and Vo

STUDENTS-HUB.com

Series Regulators



STUDENTS-HUB.com

Series Regulators

An Op-amp used in series voltage regulators



Assume Vo \downarrow Vo' \uparrow VBE \uparrow IE \uparrow Vo \uparrow STUDENTS-HUB.com



Determine the output voltage for the regulator below.



Practical DC Power supply

Determine the output voltage for the regulator below if R3 = R2 = 10K and Vz = 5.1V



An Op-amp used in series voltage regulators <u>Current Limiting:</u>

 $\frac{0.7}{IL(\max)}$ Rsc =- In normal operation Q2 is off (VBE2< 0.7V) IB1=Io; IL \approx IE=(β +1).Io -when IL=IL(max) VBE2 = 0.7VQ2 turns on; Io=IB1+IC2 Q1 will conduct less current



PASS TRANSISTOR

Voltage Regulators example

- Given the following series voltage regulator
- 1) Complete the design of the following voltage regulator (Find the values of R1, R2 and R3) assuming that the voltage across the load resistor R_L is equal to 12V. Assume Iz(min) = 2mA.
- 2)Show how to modify the circuit to limit the load current to 1A.
- 3)Find the output voltage for the modified circuit of part 2) when the load resistor $R_L = 100\Omega$ and when $R_L = 8\Omega$



1) Complete the design of the following voltage regulator (Find of R1, R2 and R3) assuming that the voltage across the load resistor R_L is equal to 12V. Assume Iz(min) = 2mA.

$$V_o = \left(1 + \frac{R_1}{R_2}\right) V_Z = 12 \text{ V}$$

$$\therefore \frac{R1}{R2} = \frac{V_0}{V_Z} - 1 = \frac{12}{4} - 1 = 2$$

$$\text{choose } R_1 = 20 \text{ k}\Omega$$

$$\therefore R_2 = 10 \text{ k}\Omega$$

$$I_Z > I_{Z(Min)} = \frac{V_{IN(Min)} - V_Z}{R_3}$$



$$R_{3} \leq \frac{V_{IN(Min)} - V_{Z}}{I_{Z(Min)}}$$
$$R_{3} \leq \frac{20 - 4}{2 \text{ mA}} = 8 \text{ k}\Omega$$

Uploaded By: anonymous

STUDENTS-HUB.com



The change for current limit is done by adding Q2 and Rsc as shown

&
$$R_{SC} = \frac{V_{BE}}{I_{L(Max)}} = \frac{0.7 \text{ V}}{1 \text{ A}} = 0.7 \Omega$$

STUDENTS-HUB.com

3)Find the output voltage for the modified circuit of part 2) when the load resistor $R_L = 100\Omega$ and when $R_L = 8\Omega$.



For
$$R_L = 100$$
 ohm, Assume Vo = 12V, then $I_L = \frac{12V}{100\Omega} = 0.12A$ $I_{L(Max)} = 1A$

which is smaller than $I_{L(max)}$,

 \therefore V_o = 12 V and is not affected by the current limit circuit

For
$$R_L = 8$$
 ohm, Assume Vo = 12V, then $I_L = \frac{12V}{8\Omega} = 1.5A$

which is bigger than $I_{L(max)}$, and the current limit circuit limits the current to the maximum allowable value which is 1 A

$$\therefore V_{O} = I_{L(Max)} * R_{L} = 1A * 8\Omega = 8 V$$

STUDENTS-HUB.com



- The Control element is in parallel with the load



- The control element maintains a constant load voltage by shunting more or less current from the load
- When the load voltage decrease, the control element shunt less STOPENTS-HUB.com Uploaded By: anonymous



STUDENTS-HUB.com

An Op-amp used in Shunt voltage regulators

$$Vo = Vz \left(1 + \frac{R1}{R2}\right)$$

$$Operation:$$

$$Vop = AdVd$$

$$Vop = Ad\left(\frac{R2}{R1 + R2}Vo - Vz\right)$$

$$Vop = Vz \left(\frac{R2}{R1 + R2}Vo - Vz\right)$$

∴ The transistor conduct Less, Ic ↓, IL ↑ Vo ↑ STUDENTS-HUB.com



STUDENTS-HUB.com



STUDENTS-HUB.com

in

GND





Fixed Voltage Regulator

Positive-Voltage Regulators in the 78XX Series

IC Part	Output Voltage (V)	Minimum V _i (V)
7805	+5	+7.3
7806	+6	+8.3
7808	+8	+10.5
7810	+10	+12.5
7812	+12	+14.5
7815	+15	+17.7
7818	+18	+21.0
7824	+24	+27.1

STUDENTS with Must be higher than Vo by at least 2V for proper operation of the voltage regulator Uploaded By: anonymous

Fixed Voltage Regulator

Negative-Voltage Regulators in the 79XX Series

IC Part	Output Voltage (V)	Minimum V _i (V)
7905	-5	-7.3
7906	-6	-8.4
7908	-8	-10.5
7909	-9	-11.5
7912	-12	-14.6
7915	-15	-17.7
7918	-18	-20.8
7924	-24	-27.1

STUDENTS-HUB.com



STUDENTS-HUB.com

Three Terminal Circuit Regulators

Dc Power Supply



STUDENTS-HUB.com

Three Terminal Circuit Regulators Dual Polarity Dc Power Supply



Changing the fixed Voltage Regulator to adjustable



 I_Q is in milliampere and change with temperature STUDENTS-HUB.com

Example

- Find the minimum and maximum output voltage (Vo) for the following IC voltage regulator. Note that R2 is a variable resistor that can be varied from 0 to $3k\Omega$
- What is the range of values of VIN required for proper operation of the circuit



STUDENTS-HUB.com

Find the minimum and maximum output voltage (Vo) for the following IC voltage regulator. Note that R2 is a variable resistor that can be varied from 0 to $3k\Omega$

$$\therefore Vo = V_{REG} \left(1 + \frac{R_2}{R_1}\right) + R_2 I_Q$$

$$V_{O(MIN)} = V_{REG} = 8 V \text{ (when } R_2 = 0 \Omega\text{)}$$

$$V_{O(MAX)} = \frac{V_{REG}}{R_1} (R_1 + R_2) + I_Q (R_2)$$

$$= \frac{8V}{2k\Omega} (2k\Omega + 3k\Omega) + 3mA.(3k\Omega)$$

$$= (4mA).(5k\Omega) + 9V = 29V \text{ (when } R_2 = 3k\Omega k\text{)}$$



STUDENTS-HUB.com

What is the range of values of VIN required for proper operation of the circuit ?

Vin must be higher than Vo by at least 2V

Vo = 8V when R2 = 0Ω Vo = 29V when R2 = $3K\Omega$



```
When Vo = 8V , Vin = 8+2= 10V
When Vo = 29V , Vin = 29+2= 31V
```

STUDENTS-HUB.com

Adjustable-Voltage Regulator

Adjustable-Voltage Regulator

STUDENTS-HUB.com

- Voltage regulators are also available in circuit configurations that allow to set the output voltage to a desired regulated value.
- The LM317 is an example of an adjustable-voltage regulator, can be operated over the range of voltage from 1.25 to 37 V.





STUDENTS-HUB.com

What is the value of the output Vou? Assume Iadj = 50 μA



STUDENTS-HUB.com

Adjustable Negative Linear Voltage Regulators



STUDENTS-HUB.com