



Faculty of Engineering and Technology

Electrical and Computer Engineering Department

ENEE2110

ELECTRIC CIRCUITS LAB

Experiment.10 Prelab

Frequency selective circuits

Prepared by:

Nermin Aqra 1212126

Supervised by:

Dr. Jaser Sa'ed

Teacher assistance:

Eng.Mohammad AL-Battat

April2025

1. Calculate the cut-off frequency (f_c) for the high pass and low pass filters shown in Figures 10.13 and 10.14.

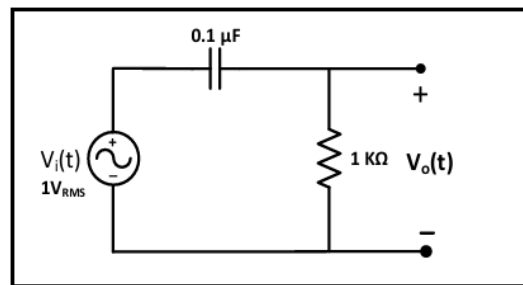


Figure 10.13

Figure 1: First-order RC High Pass Filter

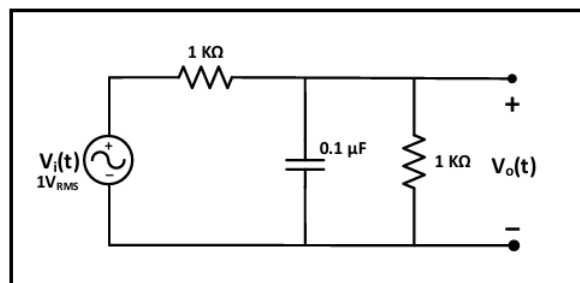


Figure 10.14

Figure 2: First-order RC Loaded Low Pass Filter

❖ **First-order RC High Pass Filter**

$$\omega_c = \frac{1}{R \times C} = \frac{1}{1 \times 10^3 \times 0.1 \times 10^{-6}} = 10000 \text{ rad/s}$$

$$\text{❖ } f_c = \frac{\omega_c}{2 \times \pi} = \frac{10000}{2 \times \pi} = 1592.356 \text{ Hz}$$

❖ **First-order RC Loaded Low Pass Filter**

$$\omega_c = \frac{1}{\left(\frac{R_s \times R_l}{R_s + R_l}\right) \times C} = \frac{1}{\left(\frac{1 \times 10^3 \times 1 \times 10^3}{1 \times 10^3 + 1 \times 10^3}\right) \times 0.1 \times 10^{-6}} = 20000 \text{ rad/s}$$

$$\text{❖ } f_c = \frac{\omega_c}{2 \times \pi} = \frac{20000}{2 \times \pi} = 3184.71337 \text{ Hz}$$

2. Simulate the circuits mentioned in step 1 using ac sweep with a Vac source at 1 V amplitude, for each of the circuits plot the magnitude in decibel scale (dB (Vo)) and phase p(Vo).

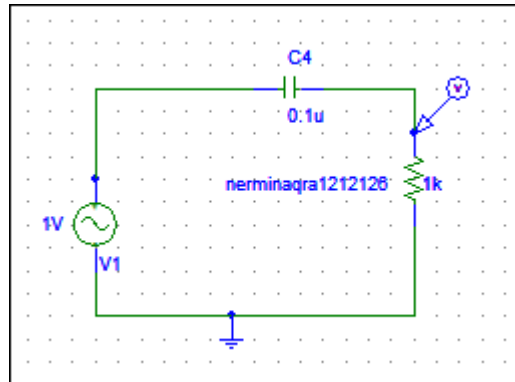


Figure 3: First-order RC High Pass Filter

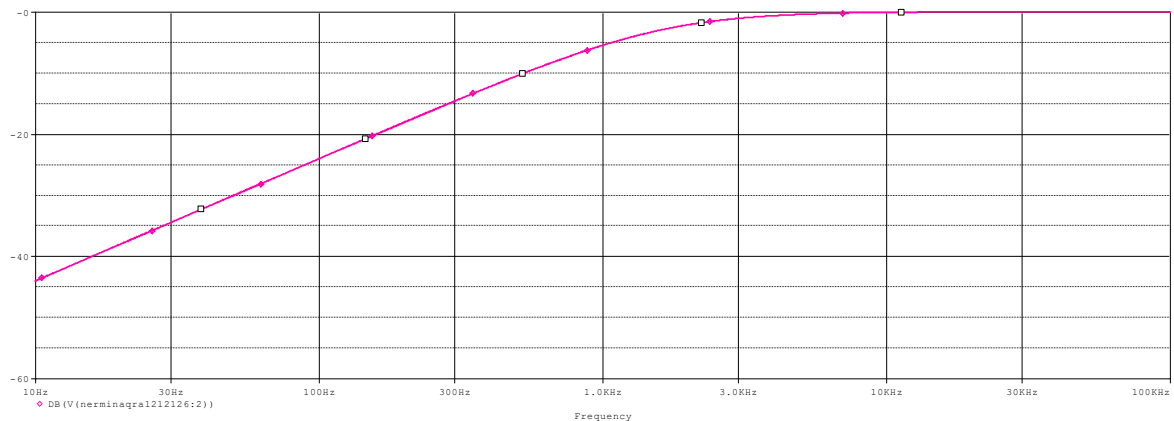


Figure 4: the magnitude in decibel scale (dB (Vo))

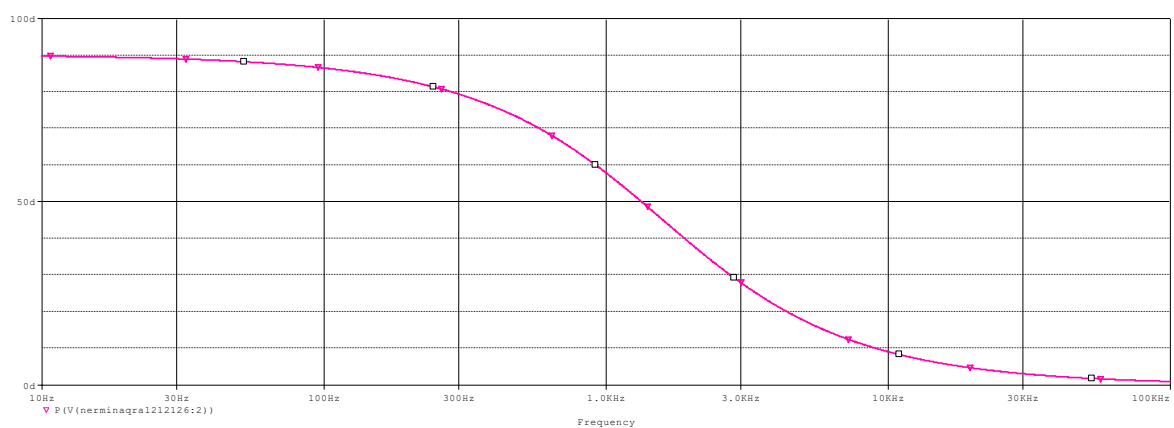


Figure 5: the magnitude phase p(Vo)

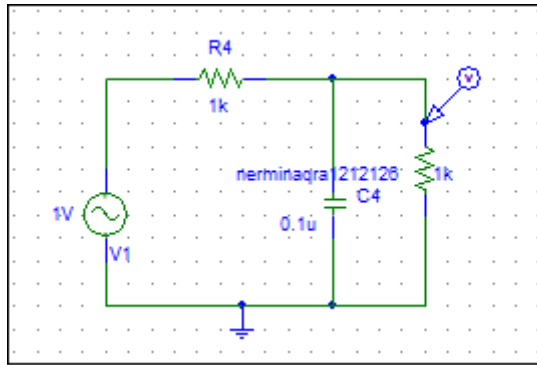


Figure 6: First-order RC Loaded Low Pass Filter

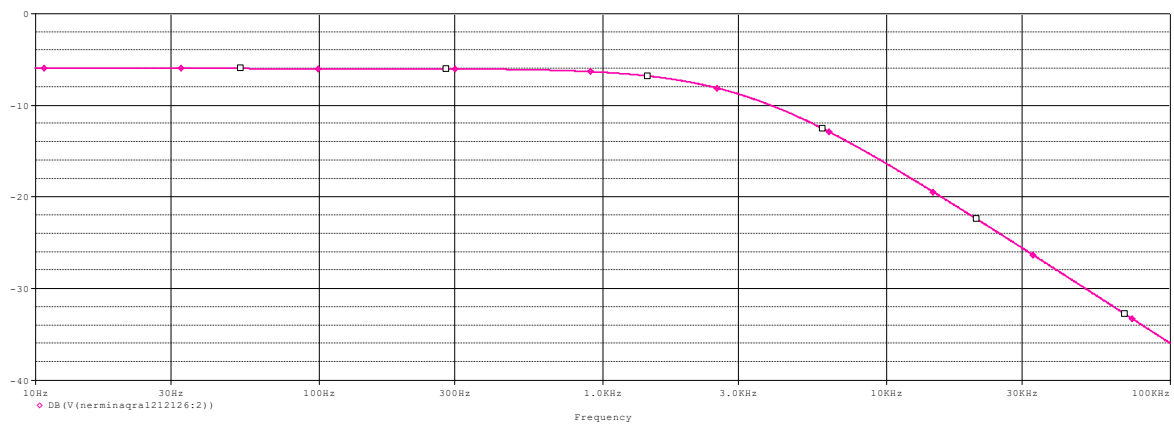


Figure 7:the magnitude in decibel scale (dB (Vo))

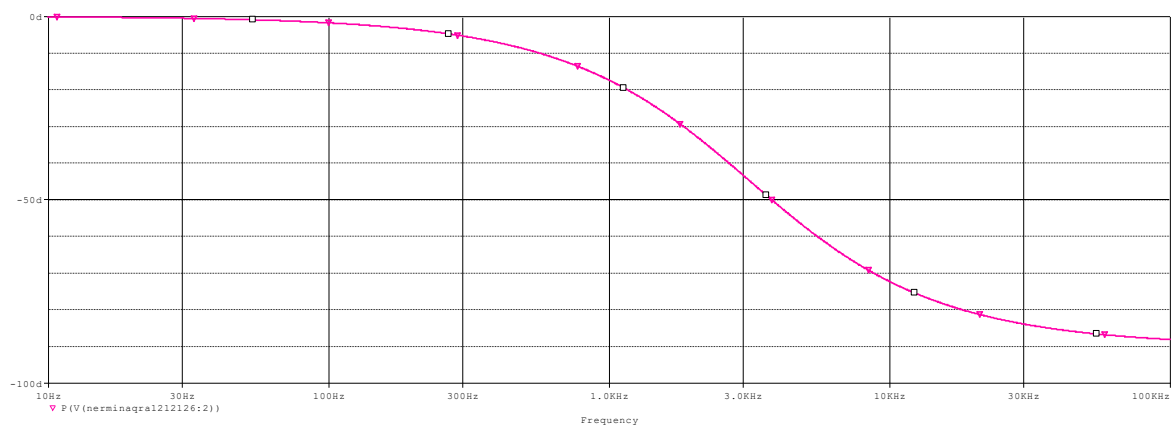


Figure 8:the magnitude phase p(Vo)

3. Calculate the center frequency (f_0), two cut-off frequencies (f_{c1} and f_{c2}), and bandwidth (β) in Hertz for the circuit in Figure 10.15 with two values of R (3.2 k Ω and 1.6 k Ω).

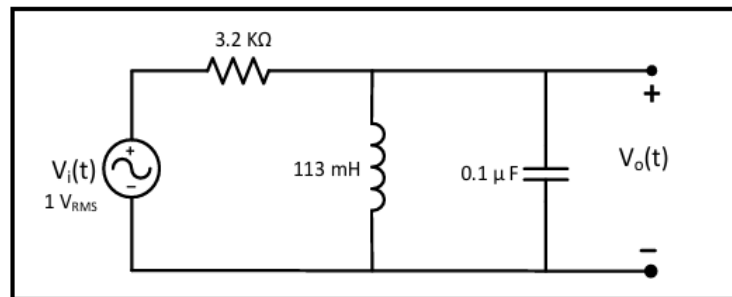


Figure 10.15

Figure 9: Parallel RLC Band Pass Filter

$$\omega_0 = \frac{1}{\sqrt{L \times C}} = \frac{1}{\sqrt{113 \times 10^{-3} \times 0.1 \times 10^{-6}}} = 9407.2086 \text{ rad/s}$$

$$\diamond f_0 = \frac{\omega_0}{2\pi} = \frac{9407.2086}{2\pi} = 1497.963 \text{ Hz}$$

When R=3.2K Ω

$$\omega_{c1,c2} = \pm \frac{1}{2 \times R \times C} + \sqrt{\left(\frac{1}{2 \times R \times C}\right)^2 + \left(\frac{1}{L \times C}\right)}$$

$$\omega_{c1,c2} = \pm \frac{1}{2 \times 3.2 \times 10^3 \times 0.1 \times 10^{-6}} + \sqrt{\left(\frac{1}{2 \times 3.2 \times 10^3 \times 0.1 \times 10^{-6}}\right)^2 + \left(\frac{1}{113 \times 10^{-3} \times 0.1 \times 10^{-6}}\right)}$$

$$\omega_{c1} = 7973.58837 \text{ rad/s} \quad \&\& \quad \omega_{c2} = 11098.58837 \text{ rad/s}$$

$$\diamond f_1 = \frac{\omega_{c1}}{2\pi} = \frac{7973.58837}{2\pi} = 1269.6796 \text{ Hz}$$

$$\diamond f_2 = \frac{\omega_{c2}}{2\pi} = \frac{11098.58837}{2\pi} = 1767.2911 \text{ Hz}$$

$$\diamond \text{Bandwidth} \rightarrow \beta = \omega_{c2} - \omega_{c1} = 11098.58837 - 7973.58837$$

$$\beta = 3125 \text{ rad/s} \rightarrow \beta = 497.611 \text{ Hz}$$

$$\diamond f_0 = \frac{\omega_0}{2\pi} = \frac{9407.2086}{2\pi} = 1497.963 \text{ Hz}$$

When $R=1.6K\Omega$

$$w_{c1,c2} = \pm \frac{1}{2 \times R \times C} + \sqrt{\left(\frac{1}{2 \times R \times C}\right)^2 + \left(\frac{1}{L \times C}\right)}$$

$$w_{c1} = \pm \frac{1}{2 \times 1.6 \times 10^3 \times 0.1 \times 10^{-6}} \sqrt{\left(\frac{1}{2 \times 1.6 \times 10^3 \times 0.1 \times 10^{-6}}\right)^2 + \left(\frac{1}{113 \times 10^{-3} \times 0.1 \times 10^{-6}}\right)}$$

$$w_{c1} = 6787.67876 \text{ rad/s} \quad \&\& \quad w_{c2} = 13037.67876 \text{ rad/s}$$

$$\diamond f_1 = \frac{w_{c1}}{2 \times \pi} = \frac{6787.67876}{2 \times \pi} = 1080.8405 \text{ Hz}$$

$$\diamond f_2 = \frac{w_{c2}}{2 \times \pi} = \frac{13037.67876}{2 \times \pi} = 2076.0634 \text{ Hz}$$

$$\diamond \text{Bandwidth} \rightarrow \beta = w_{c2} - w_{c1} = 13037.67876 - 6787.67876$$

$$\beta = 6250 \text{ rad/s} \rightarrow \beta = 995.2229 \text{ Hz}$$

$$\diamond f_0 = \frac{w_0}{2 \times \pi} = \frac{9407.2086}{2 \times \pi} = 1497.963 \text{ Hz}$$

4. Calculate the center frequency (f_0), two cut-off frequencies (f_{c1} and f_{c2}), and bandwidth (β) in Hertz for the circuit in Figure 10.15 with $R = 3.2 \text{ k}\Omega$ and with another value of $L = 60\text{mH}$.

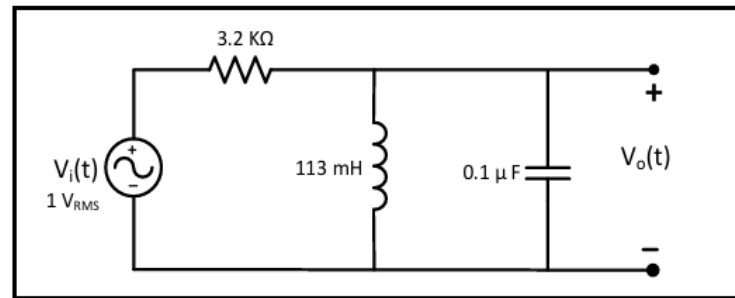


Figure 10.15

Figure 10:Figure 9: Parallel RLC Band Pass Filter

$$\omega_0 = \frac{1}{\sqrt{L \times C}} = \frac{1}{\sqrt{60 \times 10^{-3} \times 0.1 \times 10^{-6}}} = 12909.9444 \text{ rad/s}$$

$$\diamond f_0 = \frac{\omega_0}{2 \times \pi} = \frac{12909.9444}{2 \times \pi} = 2055.7236 \text{ Hz}$$

$$\omega_{c1,c2} = \pm \frac{1}{2 \times R \times C} + \sqrt{\left(\frac{1}{2 \times R \times C}\right)^2 + \left(\frac{1}{L \times C}\right)}$$

$$\omega_{c1,c2} = \pm \frac{1}{2 \times 3.2 \times 10^3 \times 0.1 \times 10^{-6}} + \sqrt{\left(\frac{1}{2 \times 3.2 \times 10^3 \times 0.1 \times 10^{-6}}\right)^2 + \left(\frac{1}{60 \times 10^{-3} \times 0.1 \times 10^{-6}}\right)}$$

$$\omega_{c1} = 11441.65599 \text{ rad/s} \quad \&\& \quad \omega_{c2} = 14566.65599 \text{ rad/s}$$

$$\diamond f_1 = \frac{\omega_{c1}}{2 \times \pi} = \frac{11441.65599}{2 \times \pi} = 1821.91974 \text{ Hz}$$

$$\diamond f_2 = \frac{\omega_{c2}}{2 \times \pi} = \frac{14566.65599}{2 \times \pi} = 2319.531209 \text{ Hz}$$

$$\diamond \text{Bandwidth} \rightarrow \beta = \omega_{c2} - \omega_{c1} = 14566.65599 - 11441.65599$$

$$\beta = 3125 \text{ rad/s} \rightarrow \beta = 497.611 \text{ Hz}$$

5. Repeat step 2 for the circuits mentioned in step 3.

➤ When $R = 3.2 \text{ k}\Omega$

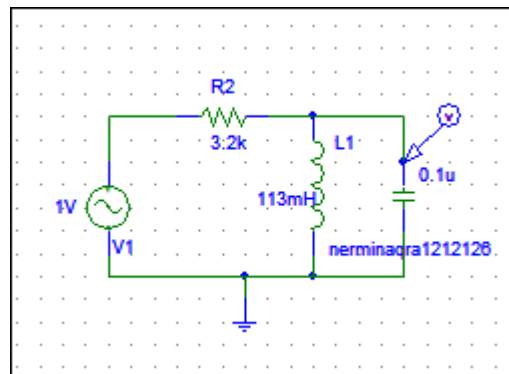


Figure 11: Parallel RLC Band Pass Filter

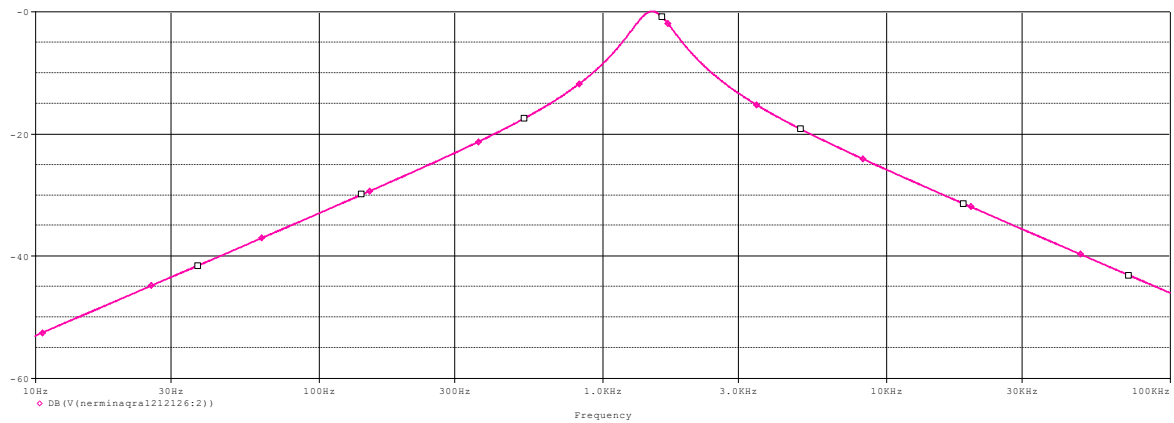


Figure 12:the magnitude in decibel scale (dB (Vo))

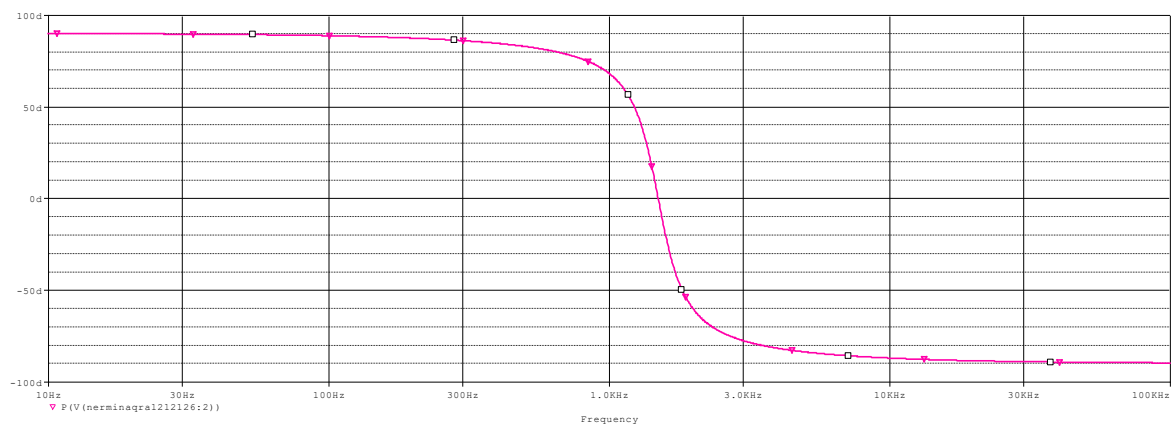


Figure 13:the magnitude phase p(Vo)

➤ When $R = 1.6 \text{ k}\Omega$

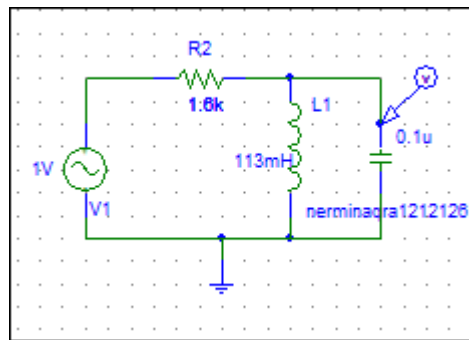


Figure 14: Parallel RLC Band Pass Filter

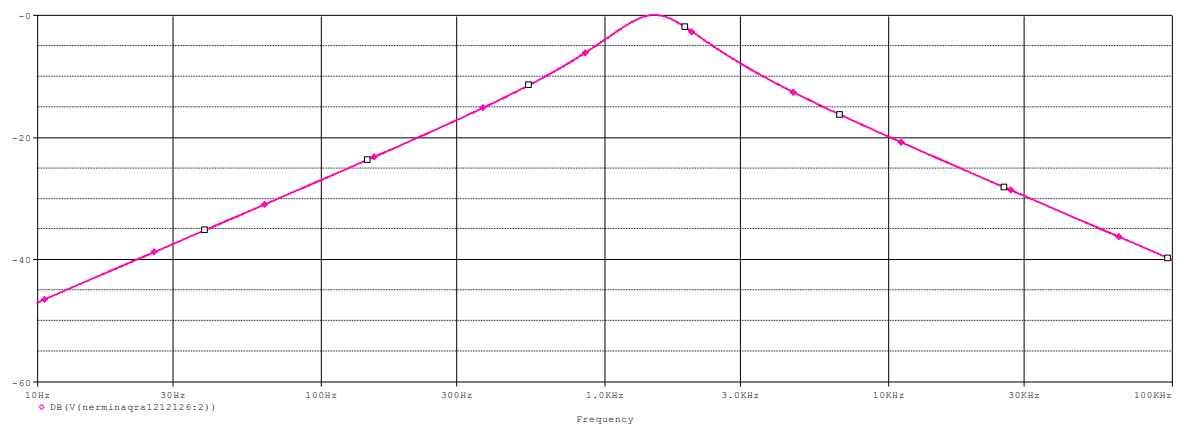


Figure 15: the magnitude in decibel scale (dB (Vo))

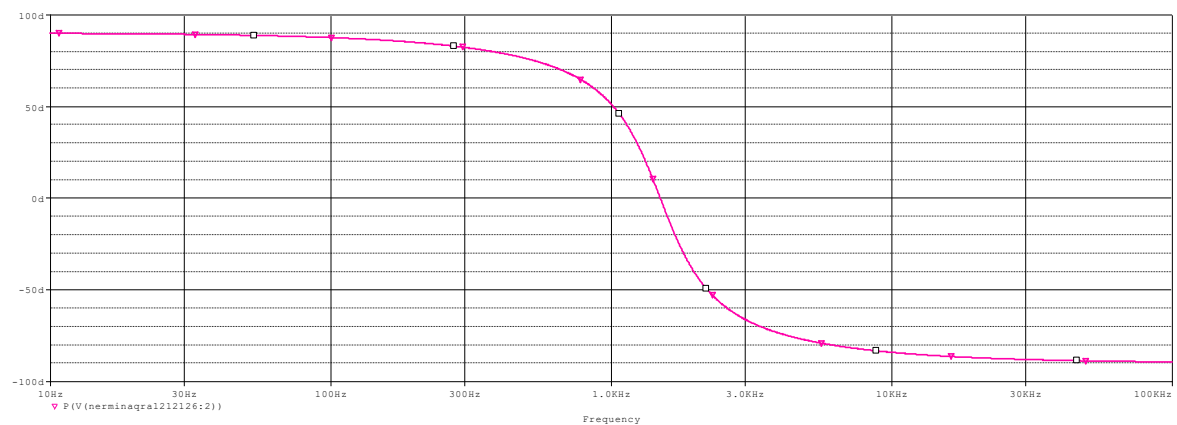


Figure 16: the magnitude phase p(Vo)

6. Calculate the center frequency (f_0), two cut-off frequencies (f_{c1} and f_{c2}), and bandwidth (β) in Hertz for the circuit in Figure 10.16 with two values of R ($3.5 \text{ k}\Omega$ and $7.1 \text{ k}\Omega$).

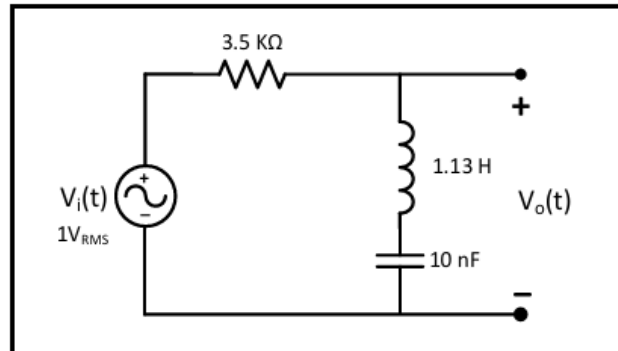


Figure 10.16

Figure 17: Series RLC Band Reject Filter

$$\omega_0 = \sqrt{\frac{1}{L \times C}} = 9407.208684 \text{ rad/s}$$

$$\diamond f_0 = \frac{\omega_0}{2 \times \pi} = \frac{9407.2086}{2 \times \pi} = 1497.963 \text{ Hz}$$

When $R = 3.5 \text{ k}\Omega$

$$\omega_{c1, c2} = \pm \frac{R}{2 \times L} + \sqrt{\left(\frac{R}{2 \times L}\right)^2 + \left(\frac{1}{L \times C}\right)}$$

$$\omega_{c1, c2} = \pm \frac{3.5 \times 10^3}{2 \times 1.13} + \sqrt{\left(\frac{3.5 \times 10^3}{2 \times 1.13}\right)^2 + \left(\frac{1}{1.13 \times 10 \times 10^{-9}}\right)}$$

$$\omega_{c1} = 7985.15992 \text{ rad/s} \quad \&\& \quad \omega_{c2} = 11082.50506 \text{ rad/s}$$

$$\diamond f_1 = \frac{\omega_{c1}}{2 \times \pi} = \frac{7985.15992}{2 \times \pi} = 1271.52228 \text{ Hz}$$

$$\diamond f_2 = \frac{\omega_{c2}}{2 \times \pi} = \frac{11082.5056}{2 \times \pi} = 1764.730191 \text{ Hz}$$

$$\diamond \text{Bandwidth} \rightarrow \beta = \omega_{c2} - \omega_{c1} = 11082.50506 - 7985.15992$$

$$\beta = 3097.34 \text{ rad/s} \rightarrow \beta = 493.20782 \text{ Hz}$$

$$\diamond f_0 = \frac{\omega_0}{2 \times \pi} = \frac{9407.2086}{2 \times \pi} = 1497.963 \text{ Hz}$$

When $R=7.1K\Omega$

$$w_{c1,c2} = \pm \frac{R}{2 \times L} + \sqrt{\left(\frac{R}{2 \times L}\right)^2 + \left(\frac{1}{L \times C}\right)}$$

$$w_{c1,c2} = \pm \frac{7.1 \times 10^3}{2 \times 1.13} + \sqrt{\left(\frac{7.1 \times 10^3}{2 \times 1.13}\right)^2 + \left(\frac{1}{1.13 \times 10 \times 10^{-9}}\right)}$$

$$w_{c1} = 6776.329307 \text{ rad/s} \quad \&\& \quad w_{c2} = 13059.51515 \text{ rad/s}$$

$$\diamond f_1 = \frac{w_{c1}}{2 \times \pi} = \frac{6776.329307}{2 \times \pi} = 1079.033329 \text{ Hz}$$

$$\diamond f_2 = \frac{w_{c2}}{2 \times \pi} = \frac{13059.51515}{2 \times \pi} = 2079.540629 \text{ Hz}$$

$$\diamond \text{Bandwidth} \rightarrow \beta = w_{c2} - w_{c1} = 13059.51515 - 6776.329307$$

$$\beta = 6283.185843 \text{ rad/s} \rightarrow \beta = \text{Hz}$$

$$\diamond f_0 = \frac{w_0}{2 \times \pi} = \frac{9407.2086}{2 \times \pi} = 1497.963 \text{ Hz}$$

7. Repeat step 2 for the circuits mentioned in step 6.

➤ **When $R=3.5K\Omega$**

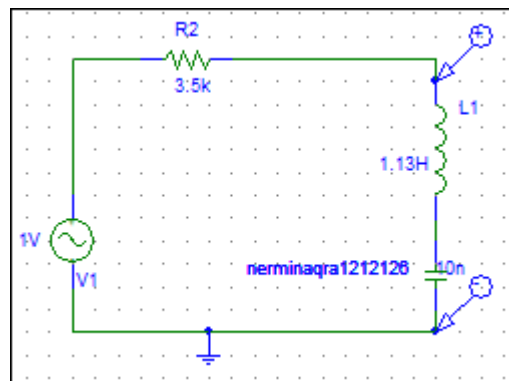


Figure 18:Series RLC Band Reject Filter

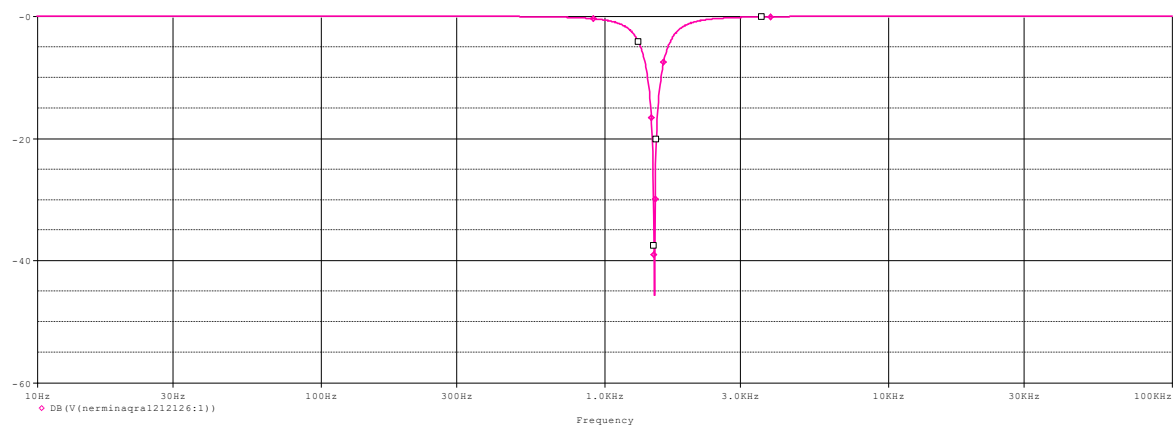


Figure 19:the magnitude in decibel scale (dB (Vo))

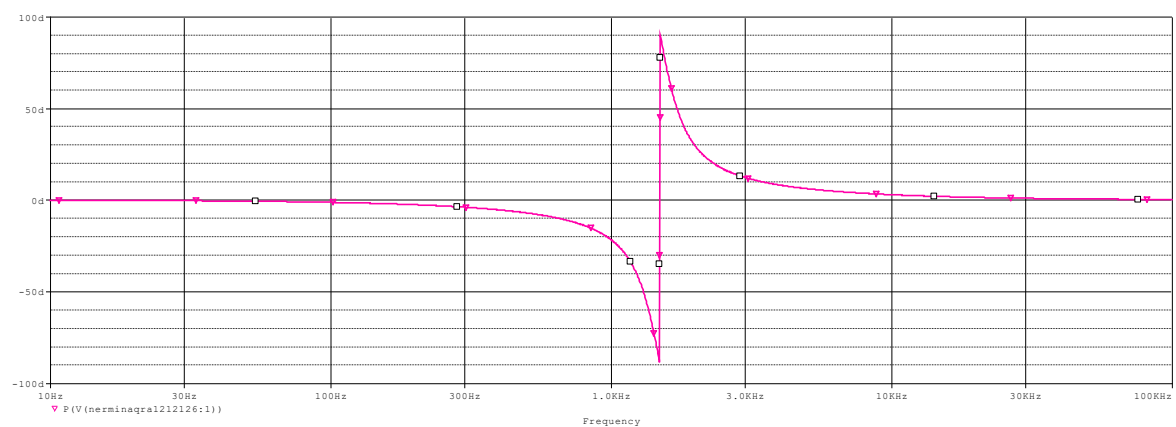


Figure 20:the magnitude phase p(Vo)

➤ When $R=7.1K\Omega$

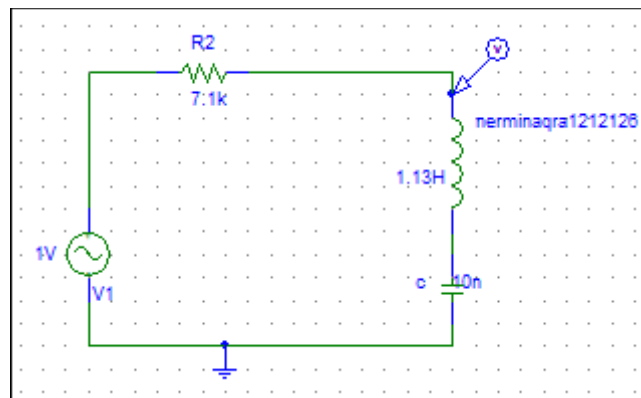


Figure 21:Series RLC Band Reject Filter

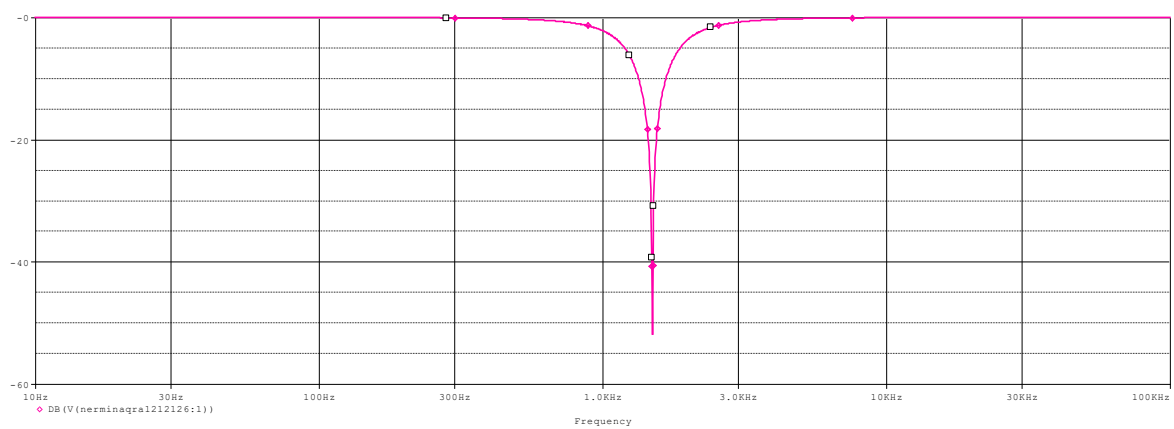


Figure 22:the magnitude in decibel scale (dB (Vo))

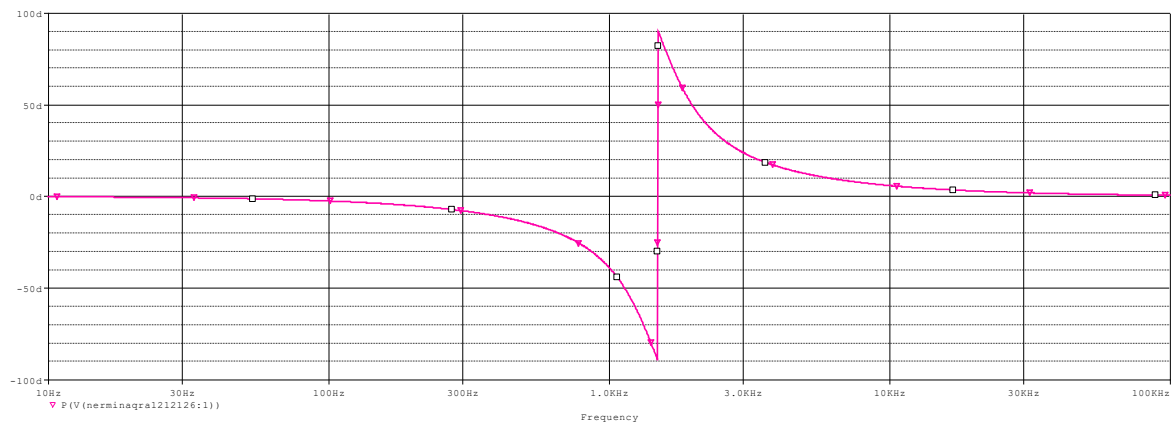


Figure 23:the magnitude phase p(Vo)