

Boolean Algebra and Logic Gates

ENCS2340 - Digital Systems

Dr. Ahmed I. A. Shawahna

Electrical and Computer Engineering Department

Birzeit University

Presentation Outline

- ❖ **Boolean Algebra**
- ❖ **Boolean Functions and Truth Tables**
- ❖ **DeMorgan's Theorem**
- ❖ **Algebraic manipulation and expression simplification**
- ❖ Logic gates and logic diagrams
- ❖ Minterms and Maxterms
- ❖ Sum-Of-Products and Product-Of-Sums
- ❖ Additional Gates and Symbols

Boolean Algebra

- ❖ Introduced by George Boole in 1854
- ❖ Two-valued Boolean algebra is also called switching algebra
- ❖ A set of two values: $B = \{0, 1\}$
- ❖ Three basic operations: **AND**, **OR**, and **NOT**
- ❖ The **AND** operator is denoted by a dot ($\cdot$)
 - ✧ $x \cdot y$ or xy is read: x **AND** y
- ❖ The **OR** operator is denoted by a plus ($+$)
 - ✧ $x + y$ is read: x **OR** y
- ❖ The **NOT** operator is denoted by ($'$) or an overbar ($\bar{}$).
 - ✧ x' or $\bar{x}$ is the complement of x

AND, OR, and NOT Operators

- ❖ The following tables define $x \cdot y$, $x + y$, and x'
- ❖ $x \cdot y$ is the **AND** operator
- ❖ $x + y$ is the **OR** operator
- ❖ x' is the **NOT** operator

x	y	$x \cdot y$
0	0	0
0	1	0
1	0	0
1	1	1

x	y	$x + y$
0	0	0
0	1	1
1	0	1
1	1	1

x	x'
0	1
1	0

Postulates of Boolean Algebra

1. Closure: the result of any Boolean operation is in $B = \{0, 1\}$

2. Identity element with respect to $+$ is 0: $x + 0 = 0 + x = x$

Identity element with respect to $\cdot$ is 1: $x \cdot 1 = 1 \cdot x = x$

3. Commutative with respect to $+$: $x + y = y + x$

Commutative with respect to $\cdot$: $x \cdot y = y \cdot x$

4. $\cdot$ is distributive over $+$: $x \cdot (y + z) = (x \cdot y) + (x \cdot z)$

$+$ is distributive over $\cdot$: $x + (y \cdot z) = (x + y) \cdot (x + z)$

5. For every x in B , there exists x' in B (called complement of x) such that: $x + x' = 1$ and $x \cdot x' = 0$

Boolean Functions

- ❖ Boolean functions are described by expressions that consist of:
 - ✧ Boolean variables, such as: x , y , etc.
 - ✧ Boolean constants: 0 and 1
 - ✧ Boolean operators: AND ($\cdot$), OR ($+$), NOT ($'$)
 - ✧ Parentheses, which can be nested
- ❖ Example: $f = x(y + w'z)$
 - ✧ The dot operator is implicit and need not be written
- ❖ Operator precedence: to avoid ambiguity in expressions
 - ✧ Expressions within parentheses should be evaluated first
 - ✧ The NOT ($'$) operator should be evaluated second
 - ✧ The AND ($\cdot$) operator should be evaluated third
 - ✧ The OR ($+$) operator should be evaluated last

Truth Table

- ❖ A truth table can represent a Boolean function
- ❖ List all possible combinations of 0's and 1's assigned to variables
- ❖ If n variables then 2^n rows
- ❖ Example: Truth table for $f = xy' + x'z$

x	y	z	y'	xy'	x'	x'z	f = xy' + x'z
0	0	0	1	0	1	0	0
0	0	1	1	0	1	1	1
0	1	0	0	0	1	0	0
0	1	1	0	0	1	1	1
1	0	0	1	1	0	0	1
1	0	1	1	1	0	0	1
1	1	0	0	0	0	0	0
1	1	1	0	0	0	0	0

DeMorgan's Theorem

$$\diamond (x + y)' = x' y'$$

$$\diamond (x y)' = x' + y'$$

Can be verified
Using a Truth Table

x	y	x'	y'	x+y	(x+y)'	x'y'	x y	(x y)'	x' + y'
0	0	1	1	0	1	1	0	1	1
0	1	1	0	1	0	0	0	1	1
1	0	0	1	1	0	0	0	1	1
1	1	0	0	1	0	0	1	0	0

Identical

Identical

❖ Generalized DeMorgan's Theorem:

$$\diamond (x_1 + x_2 + \cdots + x_n)' = x_1' \cdot x_2' \cdot \cdots \cdot x_n'$$

$$\diamond (x_1 \cdot x_2 \cdot \cdots \cdot x_n)' = x_1' + x_2' + \cdots + x_n'$$

Complementing Boolean Functions

- ❖ What is the complement of $f = x'yz' + xy'z'$?
- ❖ Use DeMorgan's Theorem:
 - ✧ Complement each variable and constant
 - ✧ Interchange AND and OR operators
- ❖ So, what is the complement of $f = x'yz' + xy'z'$?

Answer: $f' = (x + y' + z)(x' + y + z)$

- ❖ **Example 2:** Complement $g = (a' + bc)d' + e$

❖ **Answer:** $g' = (a(b' + c') + d)e'$

Algebraic Manipulation of Expressions

❖ The objective is to acquire skills in manipulating Boolean expressions, to transform them into simpler form.

❖ **Example 1:** prove $x + xy = x$ (absorption theorem)

❖ **Proof:** $x + xy = x \cdot 1 + xy$

$$= x \cdot (1 + y)$$

$$= x \cdot 1 = x$$

$$x \cdot 1 = x$$

Distributive $\cdot$ over $+$

$$(1 + y) = 1$$

❖ **Example 2:** prove $x + x'y = x + y$ (simplification theorem)

❖ **Proof:** $x + x'y = (x + x')(x + y)$ Distributive $+$ over $\cdot$

$$= 1 \cdot (x + y)$$

$$= x + y$$

$$(x + x') = 1$$

Consensus Theorem

❖ **Prove that:** $xy + x'z + yz = xy + x'z$ (consensus theorem)

❖ **Proof:** $xy + x'z + yz$

$$= xy + x'z + 1 \cdot yz$$

$$= xy + x'z + (x + x')yz$$

$$= xy + x'z + \cancel{xyz} + \cancel{x'yz}$$

$$= xy + xyz + x'z + x'yz$$

$$= xy \cdot 1 + xyz + x'z \cdot 1 + x'zy$$

$$= xy(1 + z) + x'z(1 + y)$$

$$= xy \cdot 1 + x'z \cdot 1$$

$$= xy + x'z$$

$$yz = 1 \cdot yz$$

$$1 = (x + x')$$

Distributive $\cdot$ over $+$

Associative commutative $+$

$$xy = xy \cdot 1, \quad x'yz = x'zy$$

Distributive $\cdot$ over $+$

$$1 + z = 1, \quad 1 + y = 1$$

$$xy \cdot 1 = xy, \quad x'z \cdot 1 = x'z$$

Summary of Boolean Algebra

	Property	Dual Property
Identity	$x + 0 = x$	$x \cdot 1 = x$
Complement	$x + x' = 1$	$x \cdot x' = 0$
Null	$x + 1 = 1$	$x \cdot 0 = 0$
Idempotence	$x + x = x$	$x \cdot x = x$
Involution	$(x')' = x$	
Commutative	$x + y = y + x$	$x y = y x$
Associative	$(x + y) + z = x + (y + z)$	$(x y) z = x (y z)$
Distributive	$x (y + z) = xy + xz$	$x + yz = (x + y)(x + z)$
Absorption	$x + xy = x$	$x(x + y) = x$
Simplification	$x + x'y = x + y$	$x(x' + y) = xy$
DeMorgan	$(x + y)' = x' y'$	$(x y)' = x' + y'$

Duality Principle

- ❖ The **dual** of a Boolean expression can be obtained by:
 - ✧ Interchanging AND ($\cdot$) and OR ($+$) operators
 - ✧ Interchanging 0's and 1's
- ❖ Example: the dual of $x(y + z')$ is $x + yz'$
 - ✧ The complement operator does not change
- ❖ The properties of Boolean algebra appear in **dual pairs**
 - ✧ If a property is proven to be true then its dual is also true

	Property	Dual Property
Identity	$x + 0 = x$	$x \cdot 1 = x$
Complement	$x + x' = 1$	$x \cdot x' = 0$
Distributive	$x(y + z) = xy + xz$	$x + yz = (x + y)(x + z)$

Expression Simplification

- ❖ Using Boolean algebra to simplify expressions
- ❖ Expression should contain the smallest number of **literals**
- ❖ A **literal** is a variable that may or may not be complemented
- ❖ **Example:** Simplify the following Boolean function to a minimum number of literals.

$$F(A, C) = (A + C)' + (A + C)(A' + C')$$

- ❖ **Solution:** $(A + C)' + (A + C)(A' + C')$ (6 literals)
- $= (A + C)' + (A' + C')$ by simplification (4 literals)
- $= A'C' + A' + C'$ by DeMorgan (4 literals)
- $= A' + C'$ by absorption (2 literals)

Expression Simplification

❖ **Example:** Simplify $A'B' + B'C + AB'C' + AB$ to a minimum number of literals

❖ **Solution:** $A'B' + B'C + AB'C' + AB$ (9 literals)

$= B'(A' + C + AC') + AB$ by distributive (7 literals)

$= B'(A' + C + A) + AB$ by simplification (6 literals)

$= B'(C + 1) + AB$ by complement (4 literals)

$= B' + AB$ by null and identity (3 literals)

$= B' + A$ by simplification (2 literals)

Expression Simplification

❖ **Example:** Simplify $ab + a'cd + a'bd + a'cd' + abcd$ to a minimum number of literals

❖ **Solution:** $ab + a'cd + a'bd + a'cd' + abcd$ (15 literals)

$= ab + abcd + a'cd + a'cd' + a'bd$ by commutative (15 literals)

$= ab(1 + cd) + a'c(d + d') + a'bd$ by distributive (11 literals)

$= ab + a'c + a'bd$ by complement, null, and identity (7 literals)

$= ba + ba'd + a'c$ by commutative (7 literals)

$= b(a + a'd) + a'c$ by distributive (6 literals)

$= b(a + d) + a'c$ by simplification (5 literals)

Expression Simplification

❖ **Example:** Simplify $(A' + B' + C')(A + C')(B + C')(B' + C)$ to a minimum number of literals

❖ **Solution:**

$$\begin{aligned} & (A' + B' + C')(A + C')(B + C')(B' + C) && (9 \text{ literals}) \\ &= A'B'C' + AC' + BC' + B'C && \text{by dual} \quad (9 \text{ literals}) \\ &= C'(A'B' + A + B) + B'C && \text{by distributive} \quad (7 \text{ literals}) \\ &= C'(A + B' + B) + B'C && \text{by simplification} \quad (6 \text{ literals}) \\ &= C'(A + 1) + B'C && \text{by complement} \quad (4 \text{ literals}) \\ &= C' + B'C && \text{by null and identity} \quad (3 \text{ literals}) \\ &= C' + B' && \text{by simplification} \quad (2 \text{ literals}) \end{aligned}$$

Then, we take the **dual** again, this leads to

$$= C'B'$$

Dual and Complementing Boolean Functions

❖ The complement of a function can be achieved by taking its **dual** and **complementing each literal**

❖ **Example:** what is the complement of $f = x'yz' + xy'z'$?

The dual

$$(x' + y + z')(x + y' + z')$$

Complement each literal

$$(x + y' + z)(x' + y + z) = f'$$

❖ **Example:** what is the complement of $g = (a' + bc)d' + e$?

The dual

$$((a' \cdot (b + c)) + d') \cdot e$$

Complement each literal

$$((a \cdot (b' + c')) + d) \cdot e'$$

$$(a(b' + c') + d)e' = g'$$


Importance of Boolean Algebra

- ❖ Our objective is to learn how to design digital circuits
- ❖ These circuits use signals with two possible values
- ❖ Logic **0** is a **low** voltage signal (around 0 volts)
- ❖ Logic **1** is a **high** voltage signal (e.g. 5 or 3.3 volts)
- ❖ The physical value of a signal is the actual voltage it carries, while its logic value is either 0 (low) or 1 (high)
- ❖ Having only two logic values (0 and 1) simplifies the implementation of the digital circuit


Next . . .

- ❖ Boolean Algebra
- ❖ Boolean Functions and Truth Tables
- ❖ DeMorgan's Theorem
- ❖ Algebraic manipulation and expression simplification
- ❖ **Logic gates and logic diagrams**
- ❖ **Minterms and Maxterms**
- ❖ **Sum-Of-Products and Product-Of-Sums**
- ❖ Additional Gates and Symbols


Logic Gates and Symbols

 


AND gate

 


OR gate

 


NOT gate (inverter)

 

 AND: Switches in series
logic 0 is open switch



 OR: Switches in parallel
logic 0 is open switch



NOT: Switch is normally
closed when x is 0

- ❖ In the earliest computers, relays were used as mechanical switches controlled by electricity (coils)
- ❖ Today, tiny transistors are used as electronic switches that implement the logic gates (CMOS technology)


Truth Table and Logic Diagram

- ❖ Given the following logic function: $f = x(y' + z)$
- ❖ Draw the corresponding truth table and logic diagram

Truth Table

x	y	z	$y' + z$	$f = x(y' + z)$
0	0	0	1	0
0	0	1	1	0
0	1	0	0	0
0	1	1	1	0
1	0	0	1	1
1	0	1	1	1
1	1	0	0	0
1	1	1	1	1

Logic Diagram

 

Truth Table and Logic Diagram describe the same function f . Truth table is unique, but logic expression and logic diagram are not. This gives flexibility in implementing logic functions.

Combinational Circuit

❖ A combinational circuit is a block of logic gates having:


n inputs: $x_1, x_2, \dots, x_n$

m outputs: $f_1, f_2, \dots, f_m$


❖ Each output is a function of the input variables

❖ Each output is determined from present combination of inputs

 ❖ Combination circuit performs operation specified by logic gates



 Example of a Simple Combinational Circuit



❖ The above circuit has:

✧ Three inputs: x , y , and z

✧ Two outputs: f and g

❖ What are the logic expressions of f and g ?

❖ **Answer:** $f = xy + z'$

$g = xy + yz$

From Truth Tables to Gate Implementation

- ❖ Given the truth table of a Boolean function f , how do we implement the truth table using logic gates?

Truth Table

x	y	z	f
0	0	0	0
0	0	1	0
0	1	0	1
0	1	1	1
1	0	0	0
1	0	1	1
1	1	0	0
1	1	1	1

What is the logic expression of f ?

What is the gate implementation of f ?

To answer these questions, we need to define Minterms and Maxterms

Minterms and Maxterms

- ❖ **Minterms** are AND terms with every variable present in either true or complement form
- ❖ **Maxterms** are OR terms with every variable present in either true or complement form

Minterms and Maxterms for 2 variables x and y

x	y	index	Minterm	Maxterm
0	0	0	$m_0 = x'y'$	$M_0 = x + y$
0	1	1	$m_1 = x'y$	$M_1 = x + y'$
1	0	2	$m_2 = xy'$	$M_2 = x' + y$
1	1	3	$m_3 = xy$	$M_3 = x' + y'$

- ❖ For n variables, there are 2^n Minterms and Maxterms

Minterms and Maxterms for 3 Variables

x	y	z	index	Minterm	Maxterm
0	0	0	0	$m_0 = x'y'z'$	$M_0 = x + y + z$
0	0	1	1	$m_1 = x'y'z$	$M_1 = x + y + z'$
0	1	0	2	$m_2 = x'yz'$	$M_2 = x + y' + z$
0	1	1	3	$m_3 = x'yz$	$M_3 = x + y' + z'$
1	0	0	4	$m_4 = xy'z'$	$M_4 = x' + y + z$
1	0	1	5	$m_5 = xy'z$	$M_5 = x' + y + z'$
1	1	0	6	$m_6 = xyz'$	$M_6 = x' + y' + z$
1	1	1	7	$m_7 = xyz$	$M_7 = x' + y' + z'$

Maxterm M_i is the **complement** of Minterm m_i

$$M_i = m_i' \text{ and } m_i = M_i'$$

Purpose of the Index

- ❖ Minterms and Maxterms are designated with an index
- ❖ The **index** for the Minterm or Maxterm, expressed as a **binary number**, is used to determine whether the variable is shown in the true or complemented form
- ❖ For Minterms:
 - ✧ '1' means the variable is **Not Complemented**
 - ✧ '0' means the variable is **Complemented**
- ❖ For Maxterms:
 - ✧ '0' means the variable is **Not Complemented**
 - ✧ '1' means the variable is **Complemented**

Sum-Of-Minterms (SOM) Canonical Form

Truth Table

x y z	f	Minterm
0 0 0	0	
0 0 1	0	
0 1 0	1	$m_2 = x'yz'$
0 1 1	1	$m_3 = x'yz$
1 0 0	0	
1 0 1	1	$m_5 = xy'z$
1 1 0	0	
1 1 1	1	$m_7 = xyz$

Sum of Minterm entries
that evaluate to '**1**'

Focus on the '**1**' entries

$$f = m_2 + m_3 + m_5 + m_7$$

$$f = \sum (2, 3, 5, 7)$$

$$f = x'yz' + x'yz + xy'z + xyz$$

Example - Sum-Of-Minterms

❖ Express the Boolean function $F(A, B, C) = A + B'C$ as a sum of minterms.

✧ The first term A is missing two variables; therefore,

$$\begin{aligned} A &= A(B + B') = AB + AB' \\ &= AB(C + C') + AB'(C + C') = ABC + ABC' + AB'C + AB'C' \end{aligned}$$

✧ The second term $B'C$ is missing one variable; therefore,

$$B'C = (A + A')B'C = AB'C + A'B'C$$

✧ Combining all terms (and remove duplicate terms), we have

$$\begin{aligned} F &= A + B'C = ABC + ABC' + AB'C + AB'C' + A'B'C \\ &= m_7 + m_6 + m_5 + m_4 + m_1 \end{aligned}$$

$$F(A, B, C) = \sum (1, 4, 5, 6, 7)$$

Example - Sum-Of-Minterms

❖ Express the Boolean function $F(A, B, C) = A + B'C$ as a sum of minterms.

✧ An alternative procedure is to obtain the truth table of the function directly from the algebraic expression and then read the minterms from the truth table.

$$F(A, B, C) = \sum (1, 4, 5, 6, 7)$$

A B C	F	Minterm
0 0 0	0	
0 0 1	1	$m_1 = A'B'C$
0 1 0	0	
0 1 1	0	
1 0 0	1	$m_4 = AB'C'$
1 0 1	1	$m_5 = AB'C$
1 1 0	1	$m_6 = ABC'$
1 1 1	1	$m_7 = ABC$

Example - Sum-Of-Minterms

❖ Express $f(a, b, c, d) = \Sigma(2, 3, 6, 10, 11)$ in the sum-of-minterms form

$$\diamond f(a, b, c, d) = m_2 + m_3 + m_6 + m_{10} + m_{11}$$

$$\diamond f(a, b, c, d) = a'b'cd' + a'b'cd + a'bcd' + ab'cd' + ab'cd$$

❖ Express $g(a, b, c, d) = \Sigma(0, 1, 12, 15)$ in the sum-of-minterms form

$$\diamond g(a, b, c, d) = m_0 + m_1 + m_{12} + m_{15}$$

$$\diamond g(a, b, c, d) = a'b'c'd' + a'b'c'd + abc'd' + abcd$$

Product-Of-Maxterms (POM) Canonical Form

Truth Table

x y z	f	Maxterm
0 0 0	0	$M_0 = x + y + z$
0 0 1	0	$M_1 = x + y + z'$
0 1 0	1	
0 1 1	1	
1 0 0	0	$M_4 = x' + y + z$
1 0 1	1	
1 1 0	0	$M_6 = x' + y' + z$
1 1 1	1	

Product of Maxterm entries
that evaluate to '0'

Focus on the '0' entries

$$f = M_0 \cdot M_1 \cdot M_4 \cdot M_6$$

$$f = \prod (0, 1, 4, 6)$$

$$f = (x + y + z)(x + y + z')(x' + y + z)(x' + y' + z)$$

Example - Product-Of-Maxterms

❖ Express the Boolean function $f(x, y, z) = xy + x'z$ as a product of maxterms.

✧ Convert the function into OR terms by using the distributive law,

$$\begin{aligned} f &= xy + x'z = (xy + x')(xy + z) = (x' + x)(x' + y)(x + z)(y + z) \\ &= (x' + y)(x + z)(y + z) \end{aligned}$$

✧ Each term is missing one variables; therefore,

$$\begin{aligned} f &= (x' + y)(x + z)(y + z) = (x' + y + zz')(x + yy' + z)(xx' + y + z) \\ &= (x' + y + z)(x' + y + z')(x + y + z)(x + y' + z)(x + y + z)(x' + y + z) \end{aligned}$$

✧ Removing duplicate terms, we have

$$\begin{aligned} f &= (x' + y + z)(x' + y + z')(x + y + z)(x + y' + z) \\ &= M_4 \cdot M_5 \cdot M_0 \cdot M_2 \end{aligned}$$

$$f(x, y, z) = \prod(0, 2, 4, 5)$$

Example - Product-Of-Maxterms

- ❖ Express the Boolean function $f(x, y, z) = xy + x'z$ as a product of maxterms.
- ✧ An alternative procedure is to obtain the truth table of the function directly from the algebraic expression and then read the maxterms from the truth table

$$F(x, y, z) = \prod(0, 2, 4, 5)$$

x y z	f	Maxterm
0 0 0	0	$M_0 = A + B + C$
0 0 1	1	
0 1 0	0	$M_2 = A + B' + C$
0 1 1	1	
1 0 0	0	$M_4 = A' + B + C$
1 0 1	0	$M_5 = A + B' + C$
1 1 0	1	
1 1 1	1	

Examples - Product-Of-Maxterms

❖ Express $f(a, b, c, d) = \prod(1, 3, 11)$ in the product-of-maxterms form

$$\diamond f(a, b, c, d) = M_1 \cdot M_3 \cdot M_{11}$$

$$\diamond f(a, b, c, d) = (a + b + c + d')(a + b + c' + d')(a' + b + c' + d')$$

❖ Express $g(a, b, c, d) = \prod(0, 5, 13)$ in the product-of-maxterms form

$$\diamond g(a, b, c, d) = M_0 \cdot M_5 \cdot M_{13}$$

$$\diamond g(a, b, c, d) = (a + b + c + d)(a + b' + c + d')(a' + b' + c + d')$$

Conversions between Canonical Forms

❖ The same Boolean function f can be expressed in two ways:

✧ Sum-of-Minterms $f = m_0 + m_2 + m_3 + m_5 + m_7 = \sum(0, 2, 3, 5, 7)$

✧ Product-of-Maxterms $f = M_1 \cdot M_4 \cdot M_6 = \prod(1, 4, 6)$

Truth Table

x	y	z	f	Minterms	Maxterms
0	0	0	1	$m_0 = x'y'z'$	
0	0	1	0		$M_1 = x + y + z'$
0	1	0	1	$m_2 = x'yz'$	
0	1	1	1	$m_3 = x'yz$	
1	0	0	0		$M_4 = x' + y + z$
1	0	1	1	$m_5 = xy'z$	
1	1	0	0		$M_6 = x' + y' + z$
1	1	1	1	$m_7 = xyz$	

To convert from one canonical form to another, interchange the symbols $\sum$ and $\prod$ and list those numbers missing from the original form.

Function Complement

Truth Table

x	y	z	f	f'
0	0	0	1	0
0	0	1	0	1
0	1	0	1	0
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	0	1
1	1	1	1	0

Given a Boolean function f

$$f(x, y, z) = \sum (0, 2, 3, 5, 7) = \prod (1, 4, 6)$$

Then, the complement f' of function f

$$f'(x, y, z) = \prod (0, 2, 3, 5, 7) = \sum (1, 4, 6)$$

The complement of a function expressed by a Sum of Minterms is the Product of Maxterms with the same indices. Interchange the symbols Σ and Π , but keep the same list of indices.

Example

- ❖ Write the complement of the following function using sum of minterms

$$f(z, y, x) = \sum(0, 2, 3, 4, 6)$$

- ✧ Since the system has 3 input variables (z, y, x), the number of minterms and maxterms $= 2^3 = 8$

$$f(z, y, x) = \sum(0, 2, 3, 4, 6)$$

$$f'(z, y, x) = \prod(0, 2, 3, 4, 6) = \sum(1, 5, 7)$$

$$= z'y'x + zy'x + zyx$$

Example

❖ Given that $f(x, y, z, w) = \sum(0, 1, 2, 4, 5, 7)$, derive the product of maxterms expression of f and the two canonical form expressions of f'

✧ Since the system has 4 input variables (x, y, z, w), the number of minterms and maxterms $= 2^4 = 16$

$$f(x, y, z, w) = \sum(0, 1, 2, 4, 5, 7)$$

$$f(x, y, z, w) = \prod(3, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$f'(x, y, z, w) = \sum(3, 6, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$f'(x, y, z, w) = \prod(0, 1, 2, 4, 5, 7)$$

Summary of Minterms and Maxterms

- ❖ There are 2^n Minterms and Maxterms for Boolean functions with n variables, indexed from 0 to $2^n - 1$
- ❖ Minterms correspond to the **1-entries** of the function
- ❖ Maxterms correspond to the **0-entries** of the function
- ❖ Any Boolean function can be expressed as a Sum-of-Minterms and as a Product-of-Maxterms
- ❖ For a Boolean function, given the list of Minterm indices one can determine the list of Maxterms indices (and vice versa)
- ❖ The complement of a Sum-of-Minterms is a Product-of-Maxterms with the same indices (and vice versa)

Operations on Functions

- ❖ The **AND** operation on two functions corresponds to the **intersection** of the two sets of minterms of the functions
- ❖ The **OR** operation on two functions corresponds to the **union** of the two sets of minterms of the functions

❖ **Example:** Let $F(A, B, C) = \Sigma m(1, 3, 6, 7)$ and
 $G(A, B, C) = \Sigma m(0, 1, 2, 4, 6, 7)$

✧ $F \cdot G = \Sigma m(1, 6, 7)$

✧ $F + G = \Sigma m(0, 1, 2, 3, 4, 6, 7)$

✧ $F' \cdot G = ??$

▪ $F' = \Sigma m(0, 2, 4, 5)$

▪ $F' \cdot G = \Sigma m(0, 2, 4)$

Equal Functions


- ❖ Two functions are **equal if and only if** they have the same sum of minterms and the same product of maxterms.
- ❖ **Example:** Are the function $F_1 = a'b' + ac + bc'$ and the function $F_2 = a'c' + ab + b'c$ equal?
 - ✧ $F_1 = \Sigma m(0, 1, 2, 5, 6, 7) = \Pi(3, 4)$
 - ✧ $F_2 = \Sigma m(0, 1, 2, 5, 6, 7) = \Pi(3, 4)$
 - ✧ Thus, they are equal.
- ❖ **Example:** Are the function $F_1(x, y, z) = \Sigma m(1, 2, 4, 5, 6, 7)$ and the function $F_2(a, b) = \Pi(0, 3)$ equal?
 - ✧ $F_1 = \Sigma m(1, 2, 4, 5, 6, 7) = \Pi(0, 3)$
 - ✧ $F_2 = \Pi(0, 3) = \Sigma m(1, 2)$
 - ✧ Thus, they are not equal.

Sum-of-Products and Products-of-Sums

- ❖ Canonical forms contain a larger number of literals
 - ✧ Because the Minterms (and Maxterms) must contain, by definition, all the variables either complemented or not
- ❖ Another way to express Boolean functions is in **standard** form
- ❖ Two standard forms: **Sum-of-Products** and **Product-of -Sums**
- ❖ Sum of Products (**SOP**)
 - ✧ Boolean expression is the **ORing** (sum) of **AND terms** (products)
 - ✧ Examples: $f_1 = xy' + xz$ $f_2 = y + xy'z$
- ❖ Products of Sums (**POS**)
 - ✧ Boolean expression is the **ANDing** (product) of **OR terms** (sums)
 - ✧ Examples: $f_3 = (x + z)(x' + y')$ $f_4 = x(x' + y' + z)$


Two-Level Gate Implementation

$$f_1 = xy' + xz$$

 


**AND-OR
implementations**

$$f_2 = y + xy'z$$

 


3-input AND gate

$$f_3 = (x + z)(x' + y')$$

 

**OR-AND
implementations**

$$f_4 = x(x' + y' + z)$$

 


3-input OR gate

Two-Level vs. Three-Level Implementation

- ❖ $h = ab + cd + ce$ (6 literals) is a sum-of-products
- ❖ h may also be written as: $h = ab + c(d + e)$ (5 literals)
- ❖ However, $h = ab + c(d + e)$ is a **non-standard form**
 - ✧ $h = ab + c(d + e)$ is not a sum-of-products nor a product-of-sums


2-level implementation

$$h = ab + cd + ce$$

 

3-level implementation

$$h = ab + c(d + e)$$

 


Next . . .

- ❖ Boolean Algebra
- ❖ Boolean Functions and Truth Tables
- ❖ DeMorgan's Theorem
- ❖ Algebraic manipulation and expression simplification
- ❖ Logic gates and logic diagrams
- ❖ Minterms and Maxterms
- ❖ Sum-Of-Products and Product-Of-Sums
- ❖ **Additional Gates and Symbols**


Additional Logic Gates and Symbols

❖ Why?

 
- ❖ Low-cost implementation
- ❖ Useful in implementing Boolean functions




AND gate

 


OR gate

 


NOT gate (inverter)

 


NAND gate

 


NOR gate

 


Buffer

 

XOR gate

 


XNOR gate

 


3-state gate

NAND Gate

 - ❖ The NAND gate has the following symbol and truth table
- ❖ NAND represents **NOT AND**
- ❖ The small bubble circle represents the invert function



NAND gate

 


Another symbol for NAND

x	y	NAND
0	0	1
0	1	1
1	0	1
1	1	0


- ❖ NAND gate is implemented efficiently in CMOS technology
 - ✧ In terms of chip area and speed

NOR Gate

 - ❖ The NOR gate has the following symbol and truth table
- ❖ NOR represents **NOT OR**
- ❖ The small bubble circle represents the invert function



NOR gate

 

Another symbol for NOR

x	y	NOR
0	0	1
0	1	0
1	0	0
1	1	0

- ❖ NOR gate is implemented efficiently in CMOS technology
 - ✧ In terms of chip area and speed

Non-Associative NAND / NOR Operations

- ❖ Unlike AND, NAND operation is NOT associative

$$(x \text{ NAND } y) \text{ NAND } z \neq x \text{ NAND } (y \text{ NAND } z)$$

$$(x \text{ NAND } y) \text{ NAND } z = ((xy)'z)' = ((x' + y')z)' = xy + z'$$

$$x \text{ NAND } (y \text{ NAND } z) = (x(yz)')' = (x(y' + z'))' = x' + yz$$

- ❖ Unlike OR, NOR operation is NOT associative


$$(x \text{ NOR } y) \text{ NOR } z \neq x \text{ NOR } (y \text{ NOR } z)$$

$$(x \text{ NOR } y) \text{ NOR } z = ((x + y)' + z)' = ((x'y') + z)' = (x + y)z'$$


$$x \text{ NOR } (y \text{ NOR } z) = (x + (y + z)')' = (x + (y'z'))' = x'(y + z)$$

Multiple-Input NAND / NOR Gates

 
NAND/NOR gates can have multiple inputs, similar to AND/OR gates




2-input NAND gate

 


3-input NAND gate

 


4-input NAND gate

 

2-input NOR gate

 

3-input NOR gate

 

4-input NOR gate

Note: a 3-input NAND is a single gate, NOT a combination of two 2-input gates. The same can be said about other multiple-input NAND/NOR gates.


Exclusive OR / Exclusive NOR

- ❖ Exclusive OR (XOR) is an important Boolean operation used extensively in logic circuits
- ❖ Exclusive NOR (XNOR) is the complement of XOR


x	y	XOR
0	0	0
0	1	1
1	0	1
1	1	0

x	y	XNOR
0	0	1
0	1	0
1	0	0
1	1	1

XNOR is also known
as **equivalence**

 

XOR gate

 

XNOR gate

XOR / XNOR Functions

- ❖ The XOR function is: $x \oplus y = xy' + x'y$
- ❖ The XNOR function is: $(x \oplus y)' = xy + x'y'$
- ❖ XOR and XNOR gates are complex
 - ✧ Can be implemented as a true gate, or by
 - ✧ Interconnecting other gate types
- ❖ XOR and XNOR gates do not exist for more than two inputs
 - ✧ For 3 inputs, use two XOR gates
 - ✧ The cost of a 3-input XOR gate is greater than the cost of two XOR gates
- ❖ Uses for XOR and XNOR gates include:
 - ✧ Adders, subtractors, multipliers, counters, incrementers, decrementers
 - ✧ Parity generators and checkers

XOR and XNOR Properties

$$\diamond x \oplus 0 = x$$

$$x \oplus 1 = x'$$

$$\diamond x \oplus x = 0$$

$$x \oplus x' = 1$$

$$\diamond x \oplus y = y \oplus x$$

$$\diamond x' \oplus y' = x \oplus y$$

$$\diamond (x \oplus y)' = x' \oplus y = x \oplus y'$$



XOR and XNOR are **associative** operations

$$\diamond (x \oplus y) \oplus z = x \oplus (y \oplus z) = x \oplus y \oplus z$$

$$\diamond ((x \oplus y)' \oplus z)' = (x \oplus (y \oplus z)')' = x \oplus y \oplus z$$

Positive and Negative Logic

  - ❖ Choosing the high-level **H** to represent logic **1** defines a **positive logic system**
- ❖ Choosing the low-level **L** to represent logic **1** defines a **negative logic system**
- ❖ It is up to the user to decide on a positive or negative logic polarity



Positive and Negative Logic

- ❖ The *conversion* from positive logic to negative logic and vice versa is essentially an operation that changes 1's to 0's and 0's to 1's in both the inputs and the output of a gate
- ❖ Since this operation produces the *dual* of a function, the change of all terminals from one polarity to the other results in taking the dual of the function

x	y	z
L	L	L
L	H	L
H	L	L
H	H	H


(a) Truth table with H and L

x	y	z
0	0	0
0	1	0
1	0	0
1	1	1

(c) Truth table for positive logic

x	y	z
1	1	1
1	0	1
0	1	1
0	0	0


(e) Truth table for negative logic

 

(b) Gate block diagram



(d) Positive logic AND gate

 

(f) Negative logic OR gate