
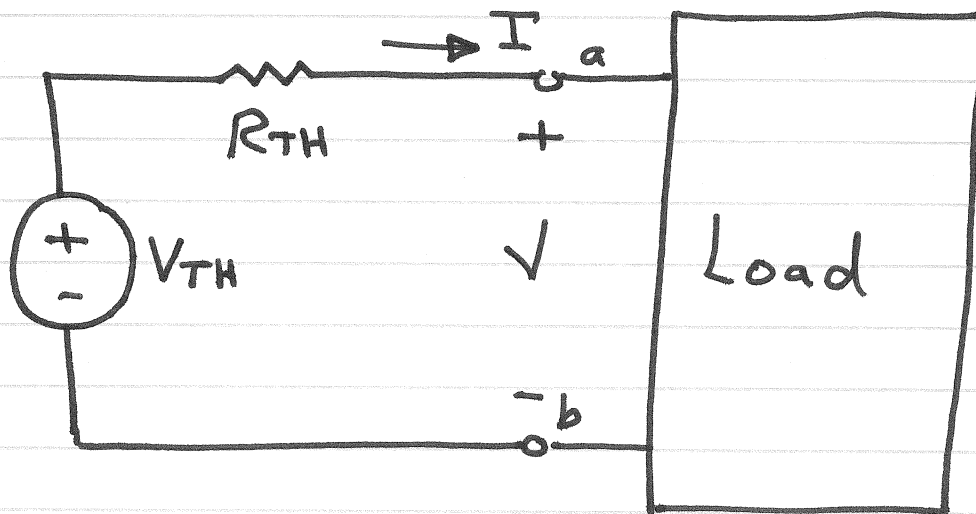


# Thevenin's Theorem

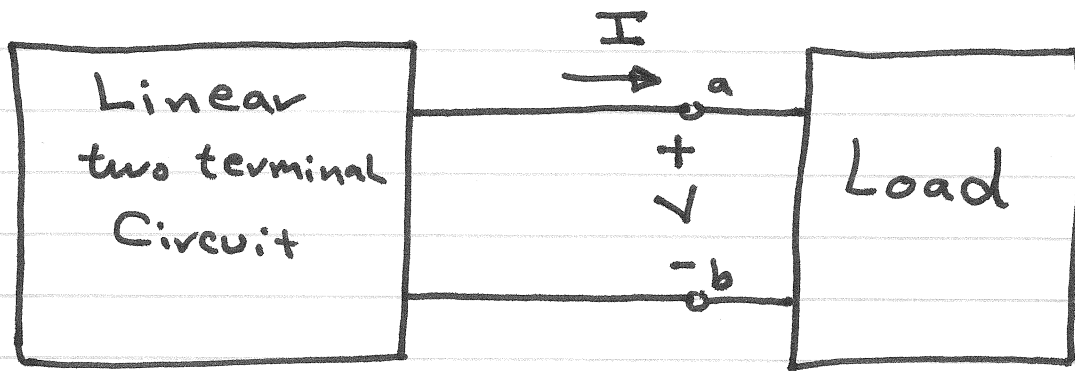


It states that a Linear two terminal Circuit Can be replaced by an equivalent Circuit Consisting of a voltage Source  $V_{TH}$  in series with a resistor  $R_{TH}$ , where  $V_{TH}$  is the open circuit voltage at the terminals and  $R_{TH}$  is the input or equivalent resistance at the terminals when the independent sources


are turn off.

How to find Thevenin's Voltage?

$$V_{TH} = V_{oc}$$

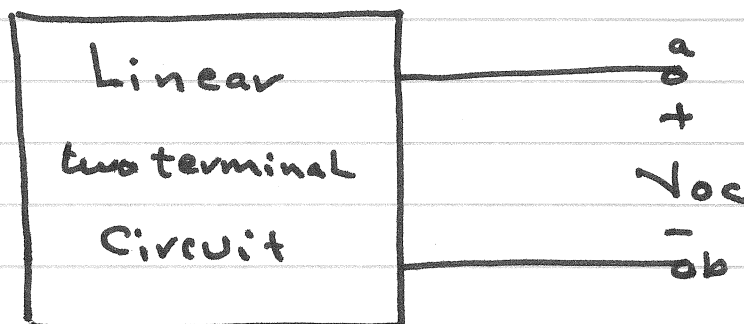

How to find Thevenin's Resistance?

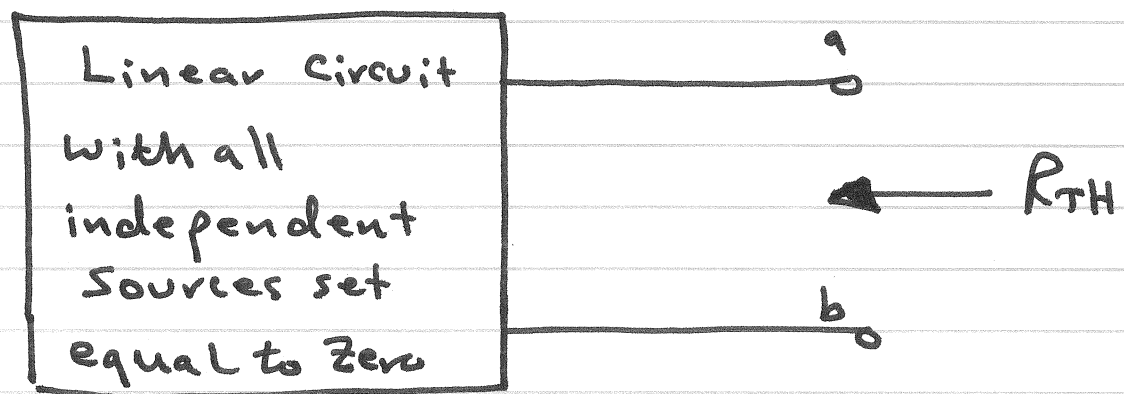

- a-b open circuited
- Turn off all independent sources

# How to find $R_{TH}$ ?

## Care I

If the circuit has no dependent sources

- Turn off all independent sources
- $R_{TH}$  can be obtained via simplification of either parallel or series connection seen from a-b.

## Care II

If the circuit has dependent sources



- Turn off all independent sources
- Apply a voltage source  $V_T$  at a-b

$$R_{TH} = \frac{V_T}{I_T}$$

- Alternatively, Apply a current source  $I_T$  at a-b

$$R_{TH} = \frac{V_T}{I_T}$$

# Norton's Theorem

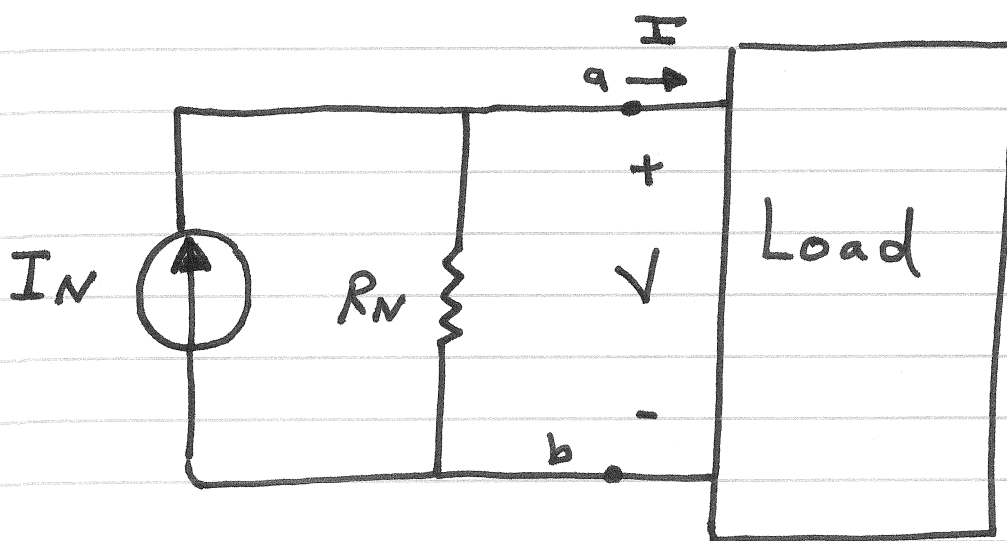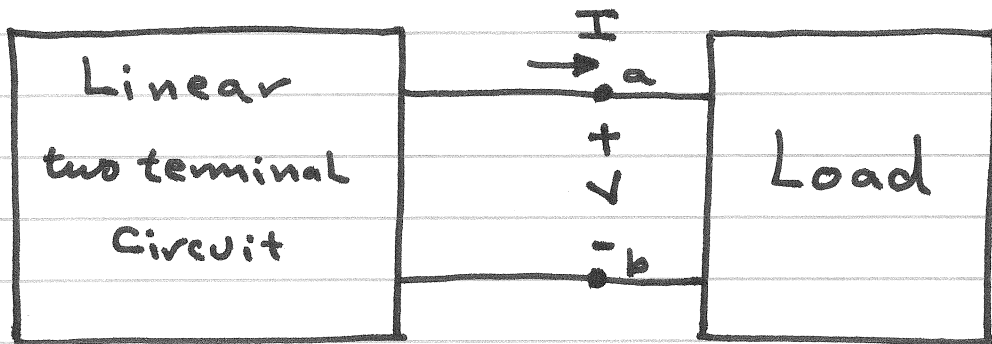

It states that a Linear two terminal Circuit can be replaced by an equivalent circuit of a current source  $I_N$  in parallel with a resistor  $R_N$ .

where


- $I_N$  is the short circuit current through the terminals.

.  $R_N$  is the input or equivalent resistance at the terminals when the independent sources are turned off.


.  $R_N = R_{TH}$

# Norton's Theorem



- How to find  $I_N$

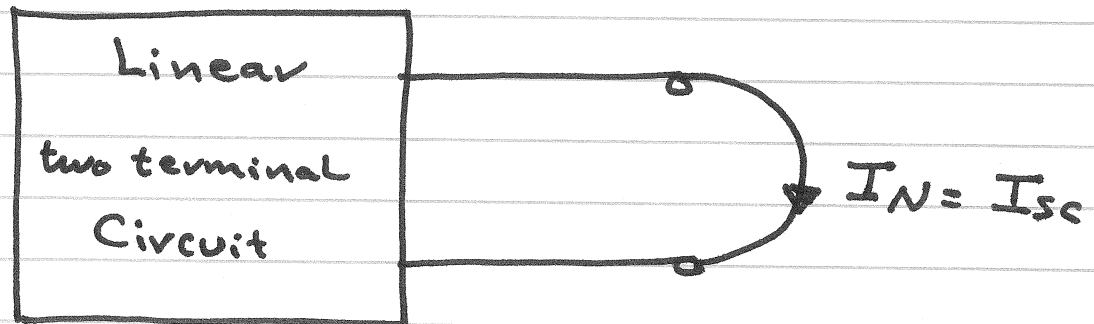


- How to find  $R_N = R_{TH}$

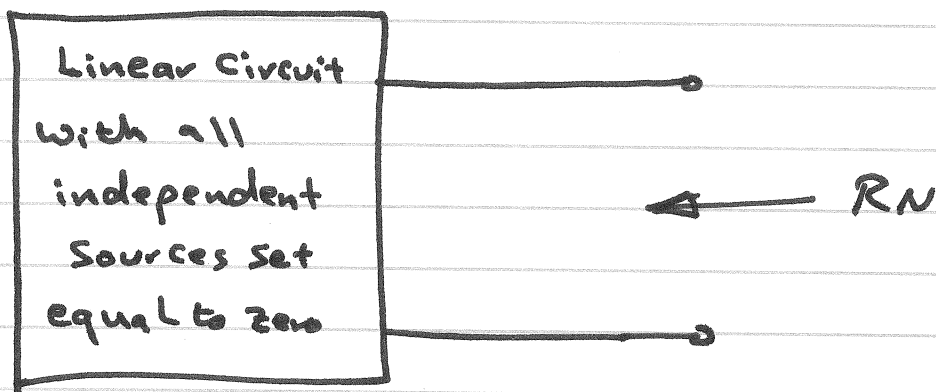

Find  $V_o$  using thevenin's theorem

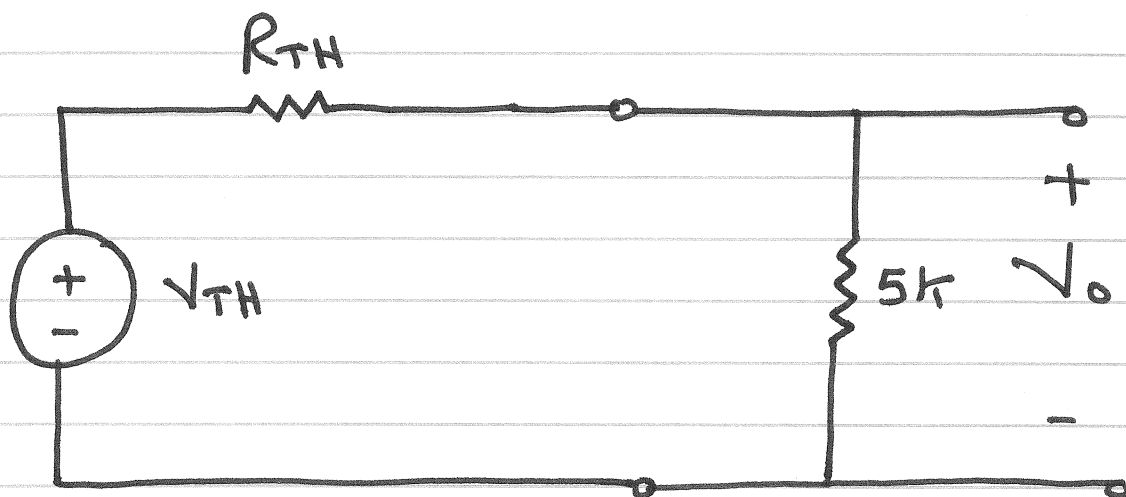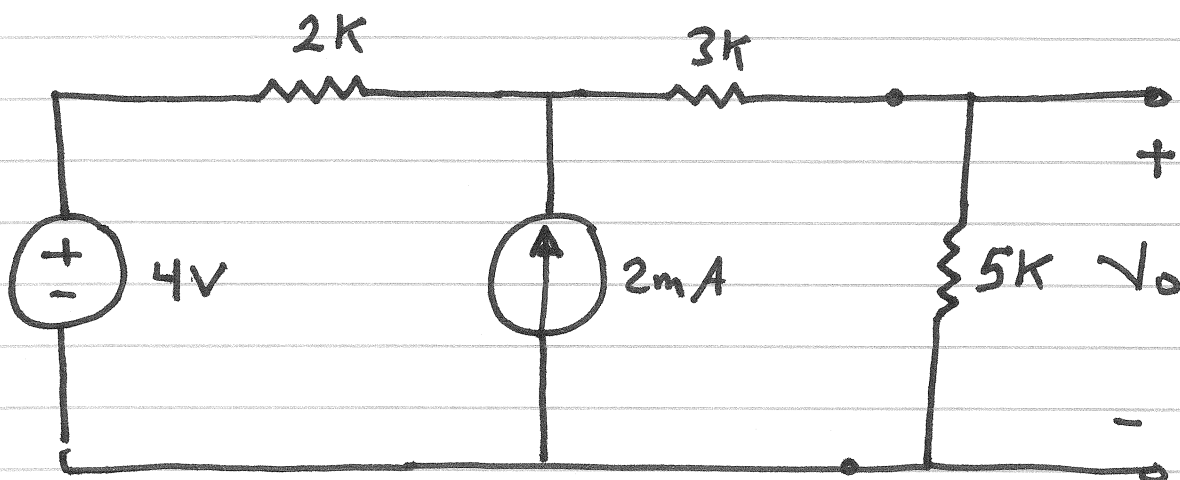


1) To find  $V_{TH}$

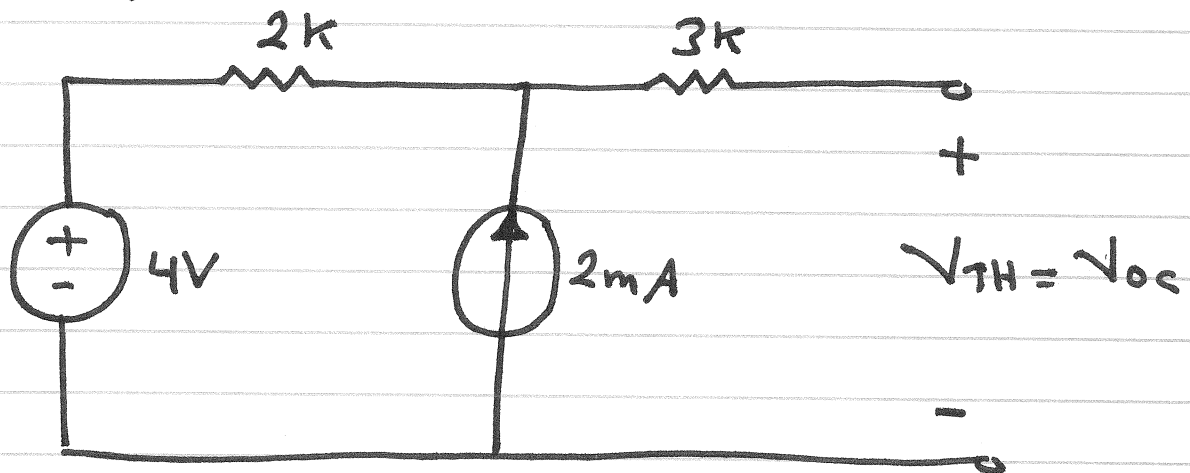


$$V_{TH} = (2k)(2mA) + 4 = 8V$$

2) To find  $R_{TH}$

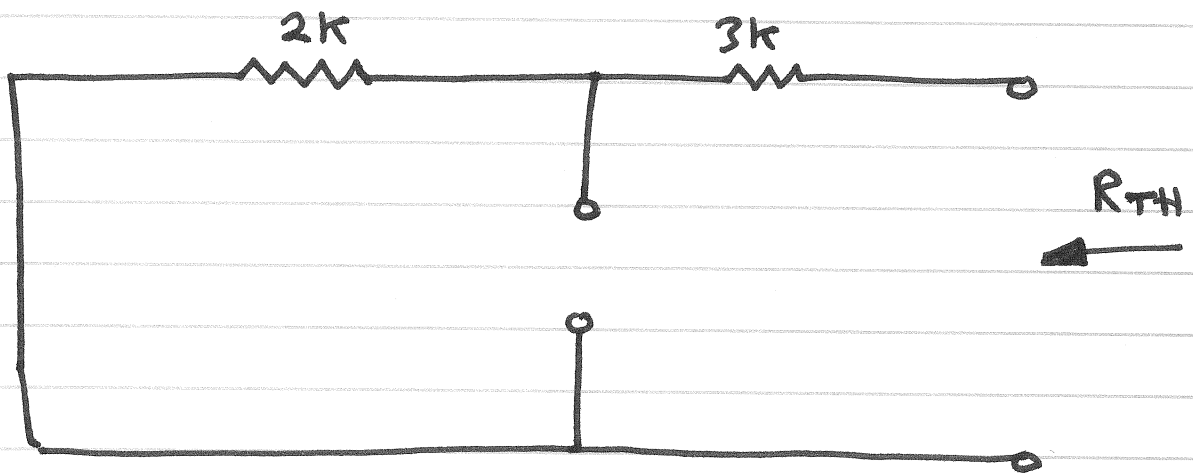

$$R_{TH} = 3k + 2k = 5k\Omega$$



3) To find  $V_o$

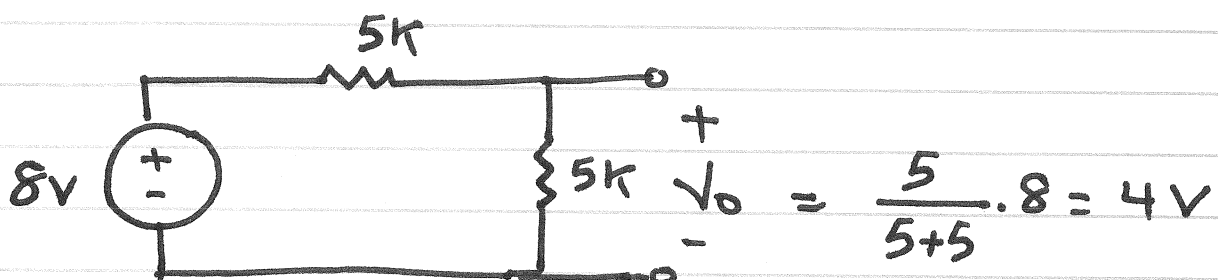

$$V_o = \frac{5}{5+5} \cdot 8 = 4V$$





Find  $V_o$  using Norton's theorem

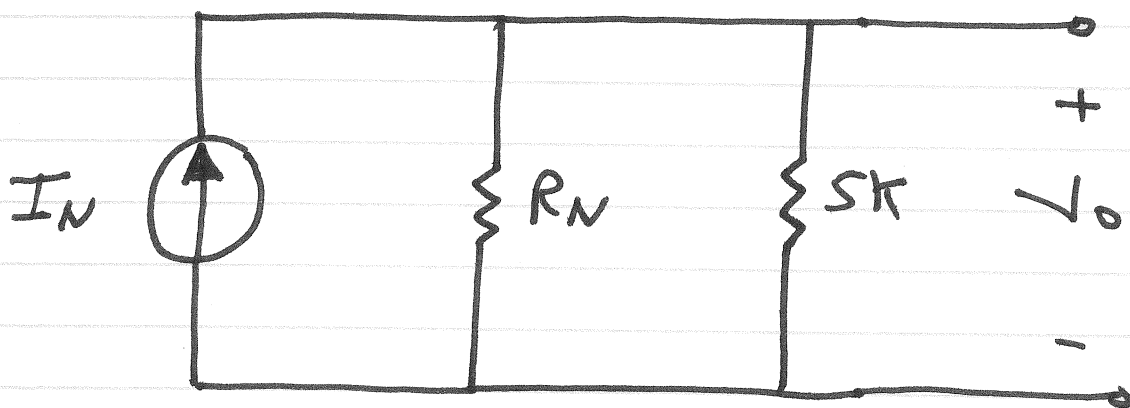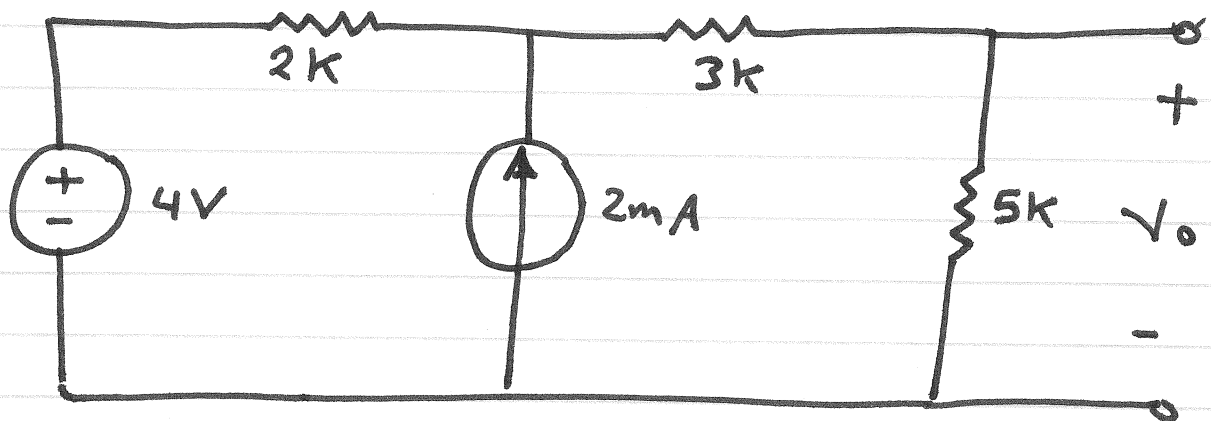

$$V_o = (R_N \parallel 5k) I_N$$

1) To find  $I_N$

$$I_N = I_{sc}$$

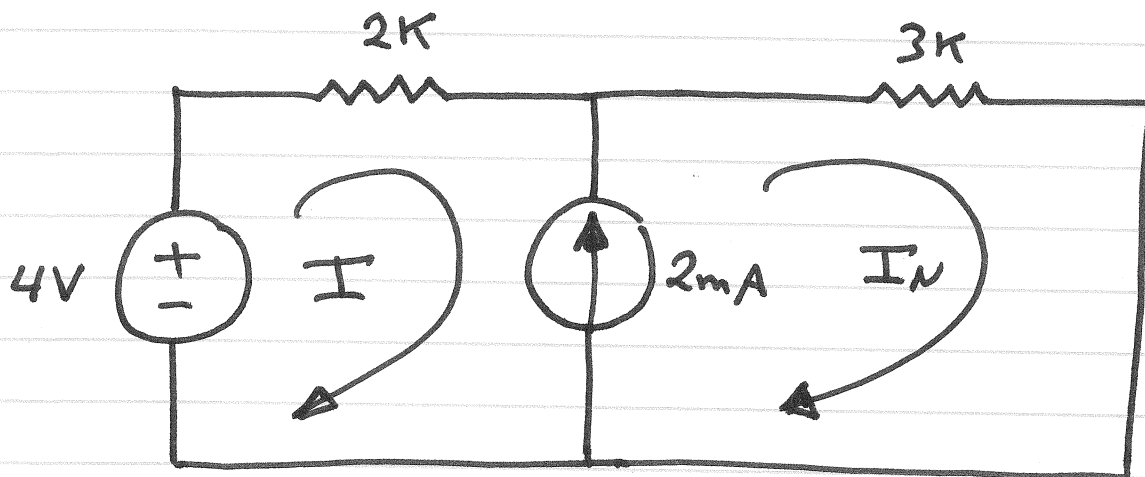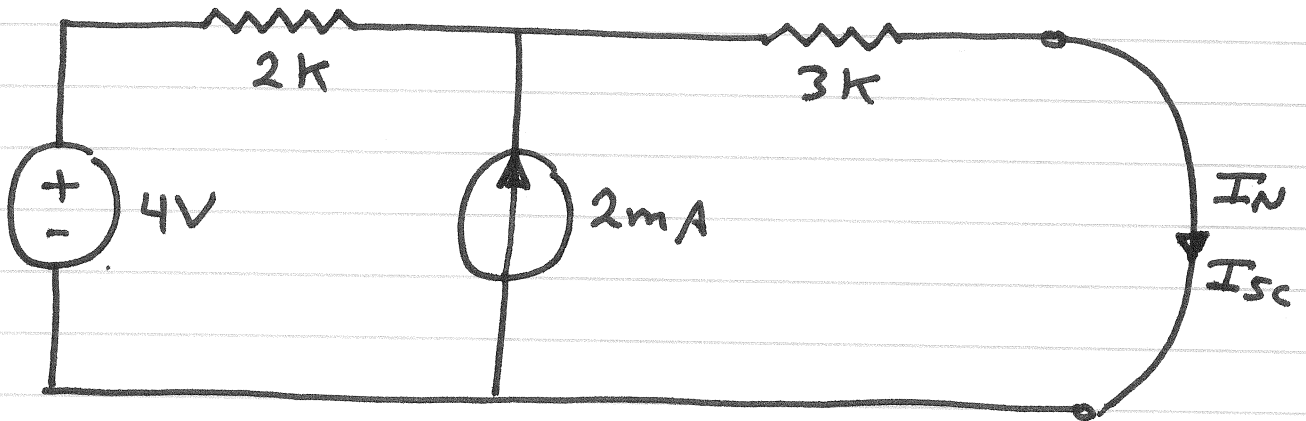


$$2\text{mA} = I_N - I \quad \text{Constraint equation}$$

$$4 = (2\text{k})I + (3\text{k})I_N \quad \text{Supermesh equation}$$

$$\therefore I_N = 1.6\text{mA}$$


2) To find  $R_N = R_{TH}$

turn off all the independent sources

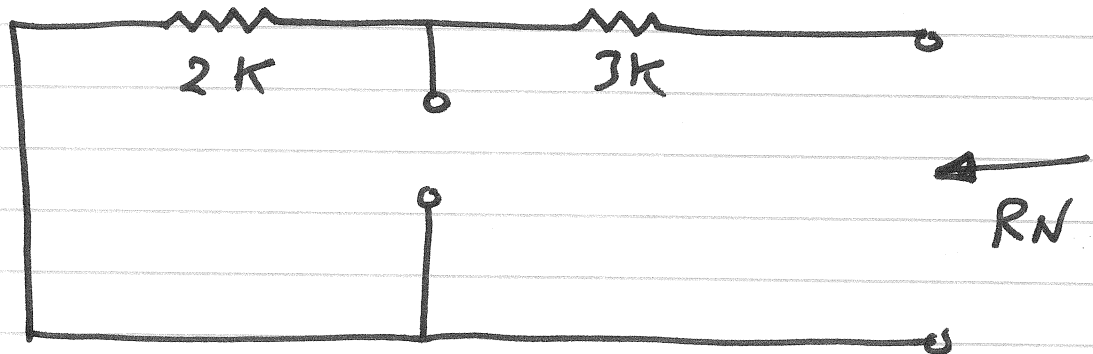

$$R_N = 3k + 2k = 5k$$



3) To find  $V_o$

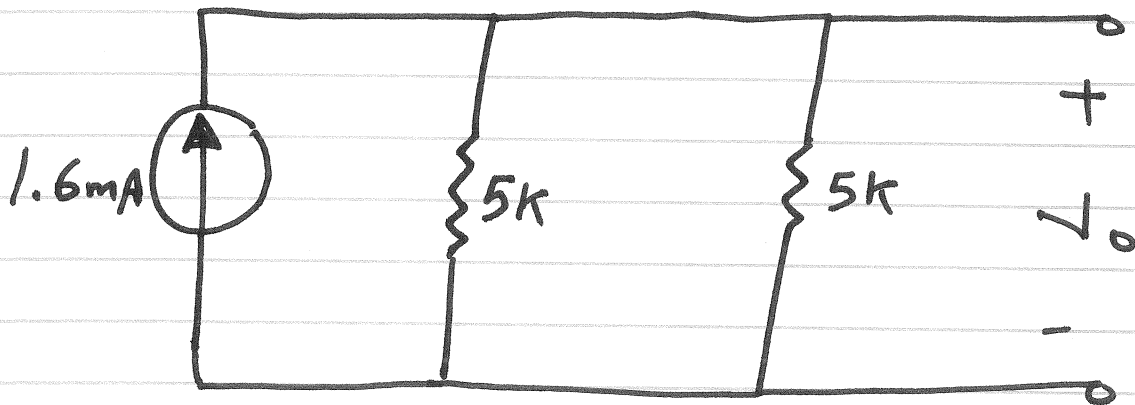


$$V_o = (5k || 5k) (1.6mA)$$

$$V_o = 4V$$

Find  $V_o$  using thevenin's theorem

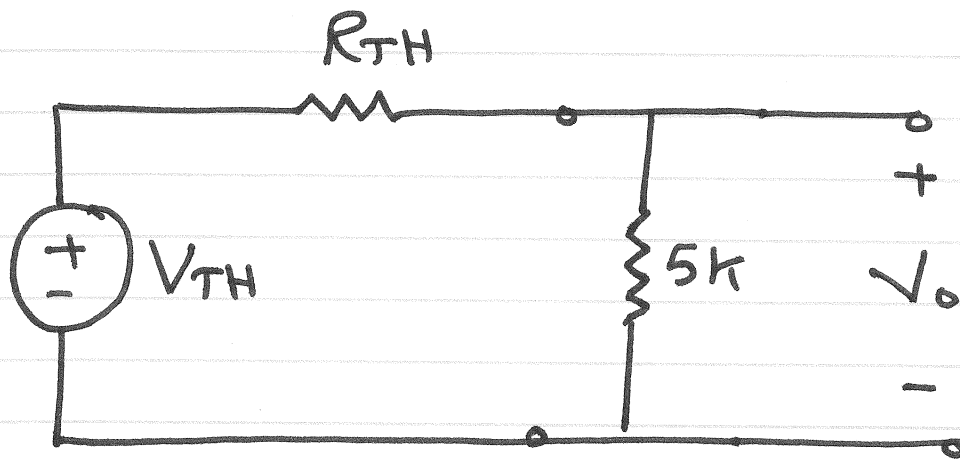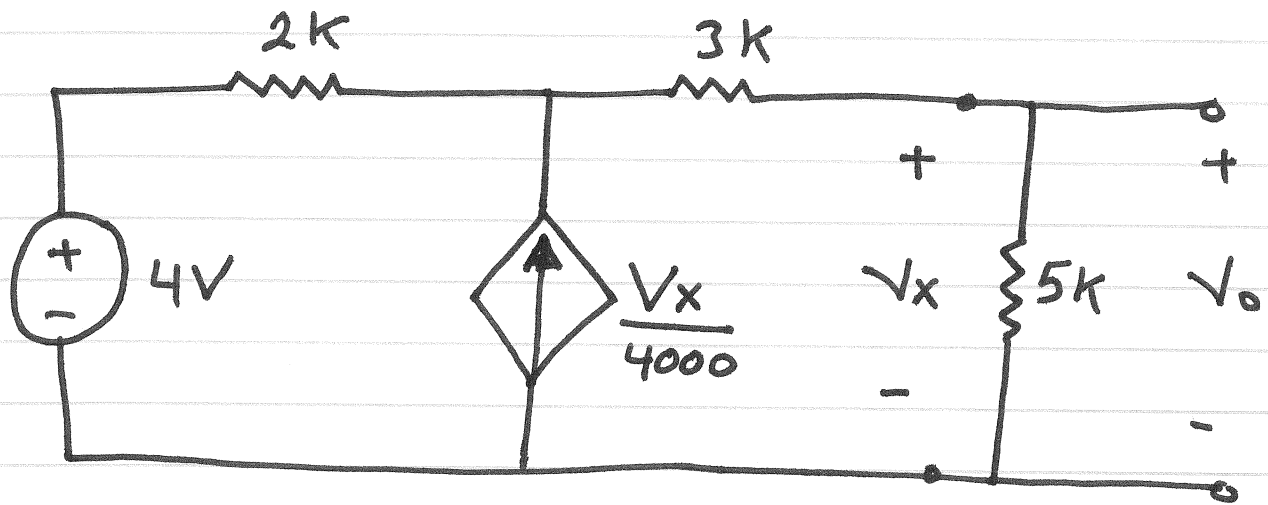

1) To find  $V_{TH}$

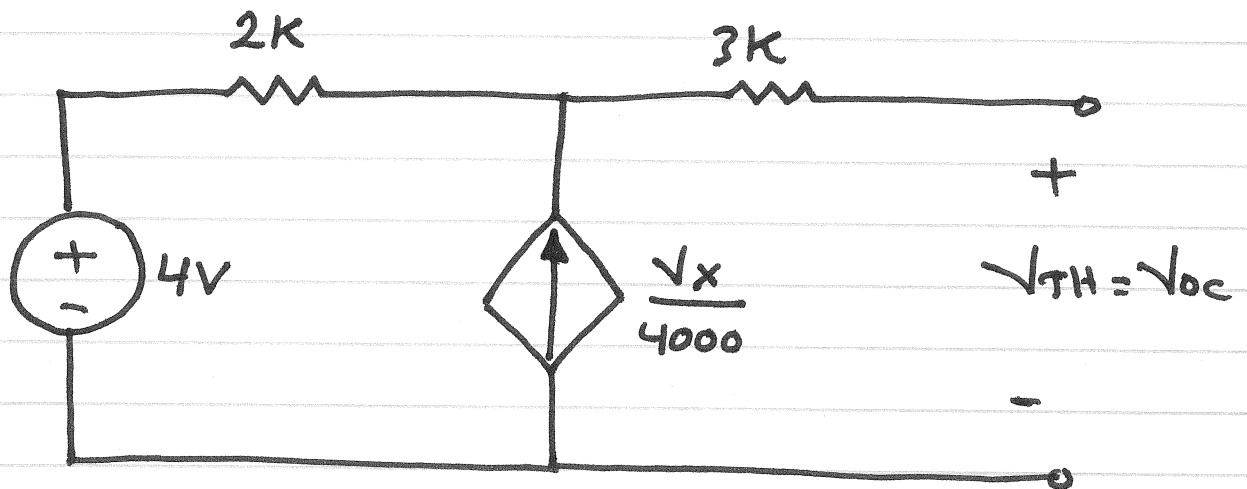


$$V_{TH} = (2K) \left( \frac{V_x}{4000} \right) + 4$$

$$V_x = V_{TH}$$


$$\therefore V_{TH} = 8V$$

2) To find  $R_{TH}$

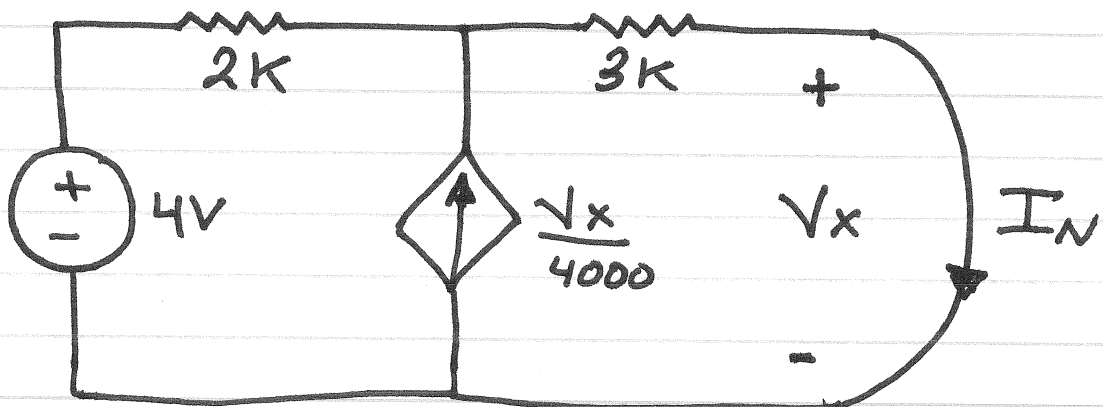a) method 1 :  $R_{TH} = \frac{V_{TH}}{I_N}$


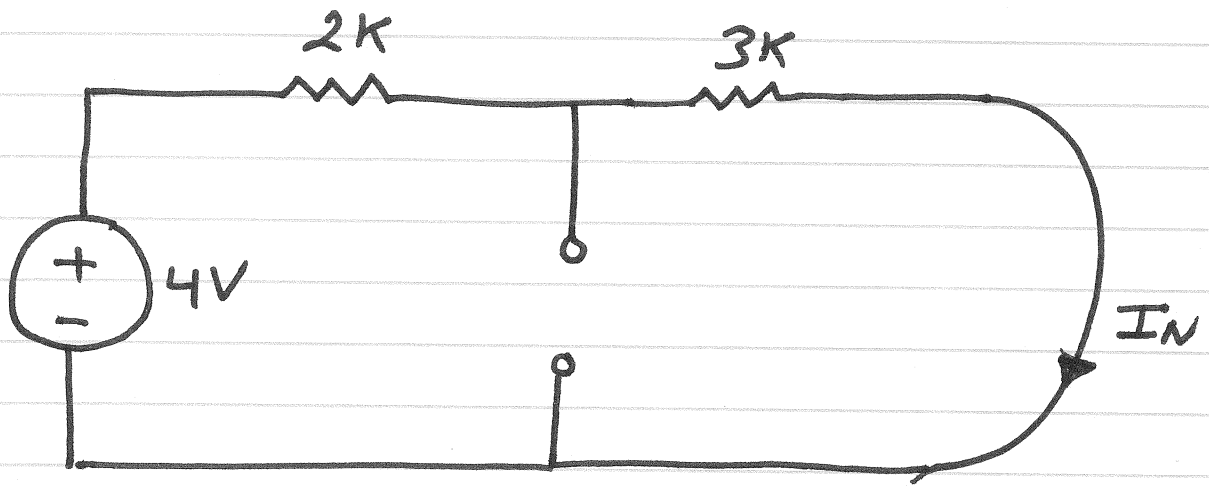
$$V_x = 0 \rightarrow \frac{V_x}{4000} = 0 \rightarrow \text{open circuit}$$





$$I_N = \frac{4V}{5k} = 0.8 \text{ mA}$$

$$\therefore R_{TH} = \frac{8V}{0.8 \text{ mA}} = 10k$$

b) method 2 :  $R_{TH} = \frac{V_T}{I_T}$

all independent  
sources set to  
Zero

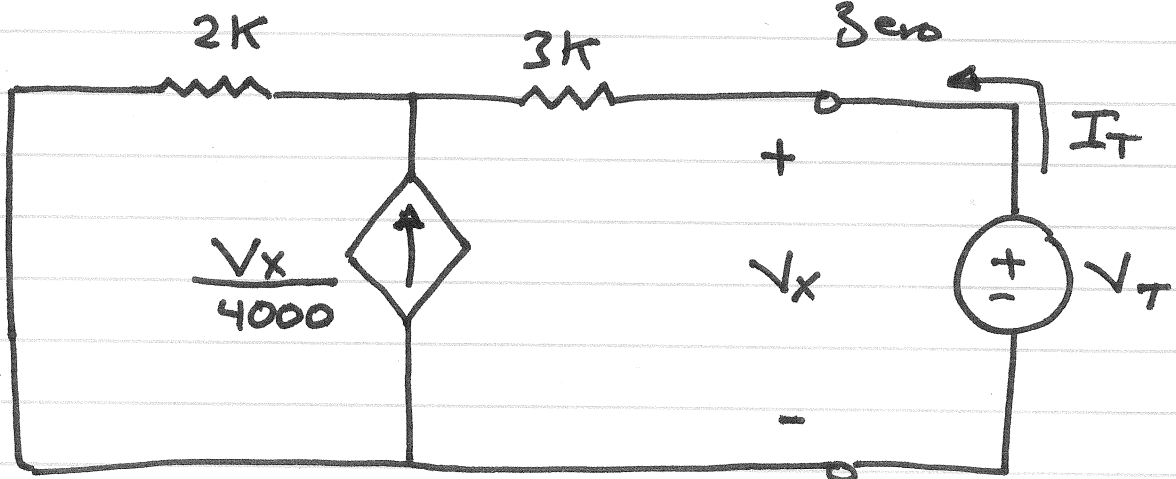

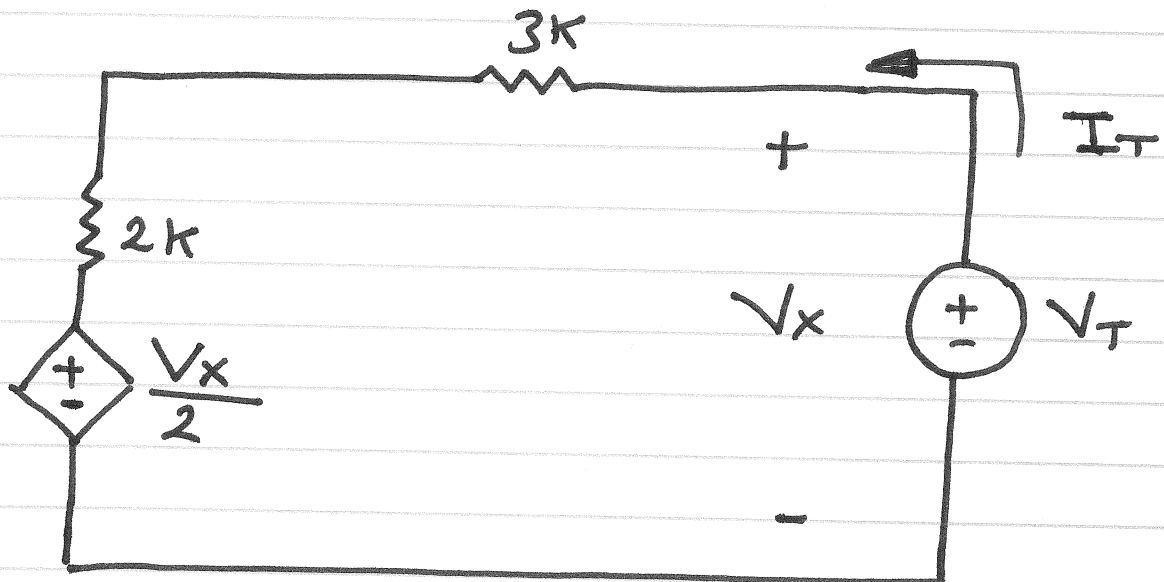


KVL :

$$-V_T + 3k I_T + 2k I_T + \frac{V_x}{2} = 0$$

$$V_x = V_T$$
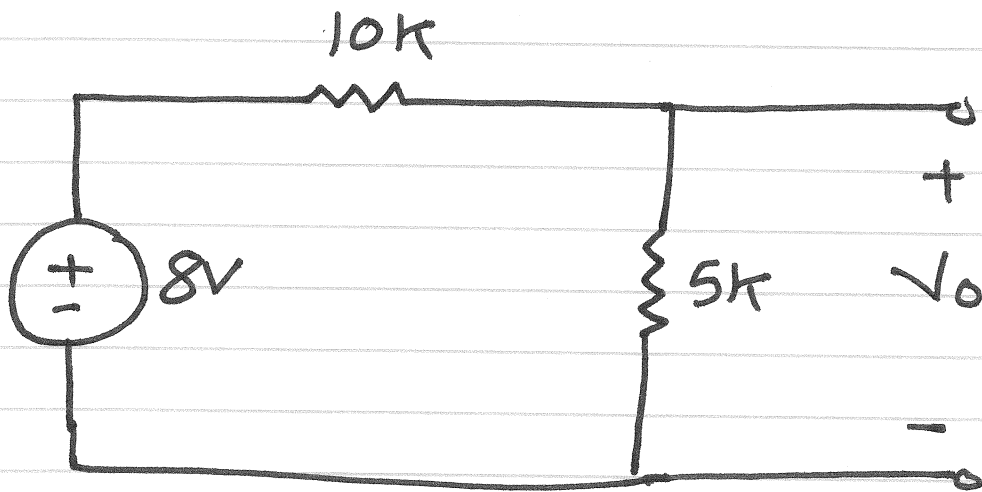
$$\therefore R_{TH} = \frac{V_T}{I_T} = 10k$$





$$V_o = \frac{5k}{5k + 10k} (8V)$$


$$V_o = \frac{8}{3} V$$



Find  $I_x$  using thevenin's theorem

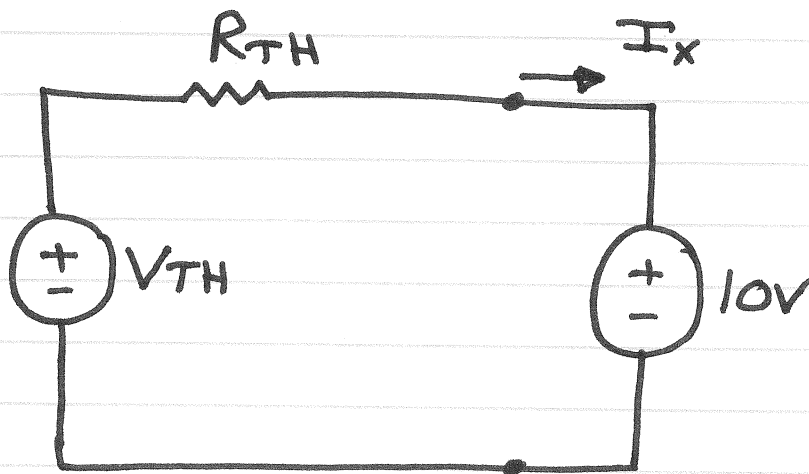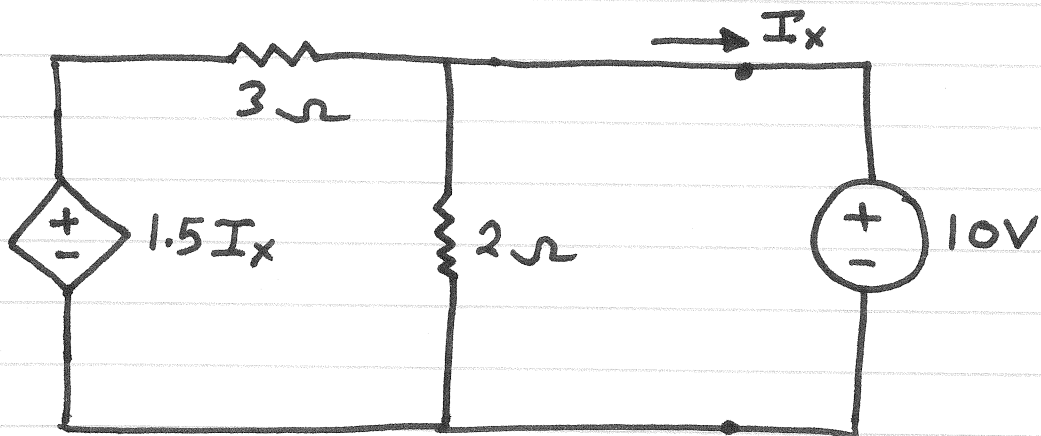


1) To find  $V_{TH}$

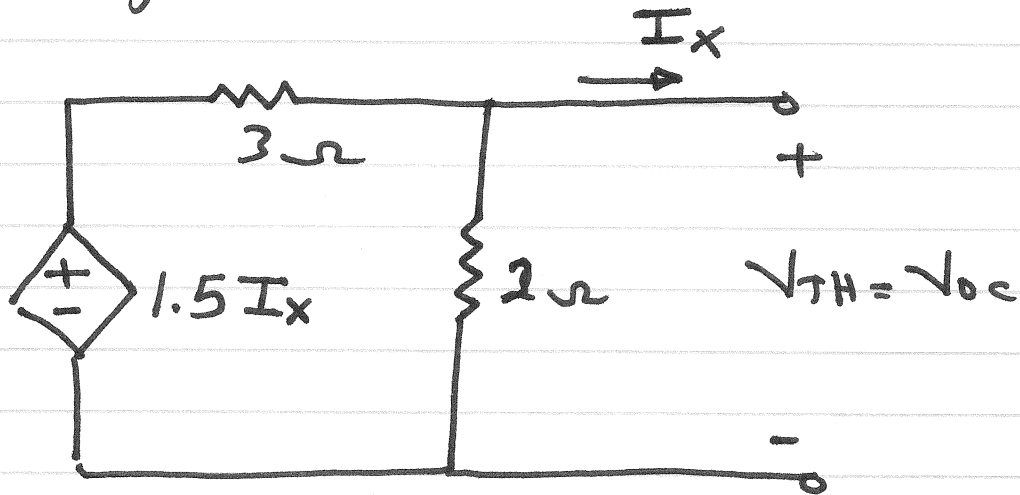


Since there is no independent sources

$$\therefore V_{TH} = 0$$

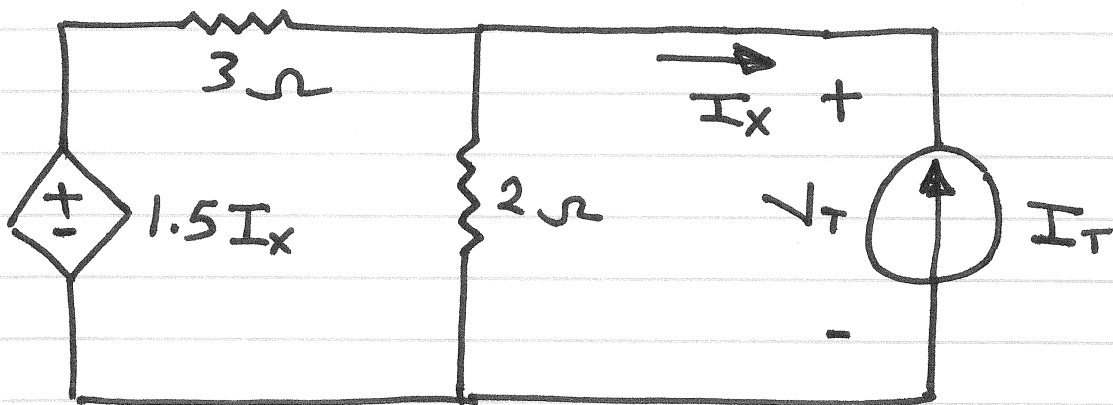2) To find  $R_{TH}$  :  $\frac{V_T}{I_T}$



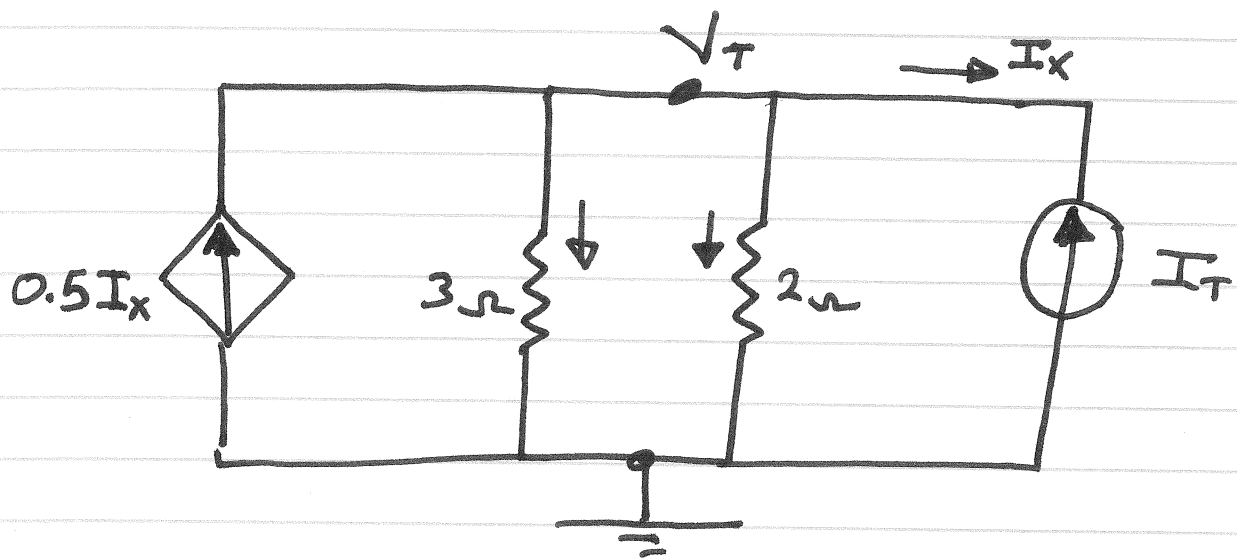


KCL :

$$0.5 I_x + I_T = \frac{V_T}{3} + \frac{V_T}{2}$$

$$I_x = - I_T$$
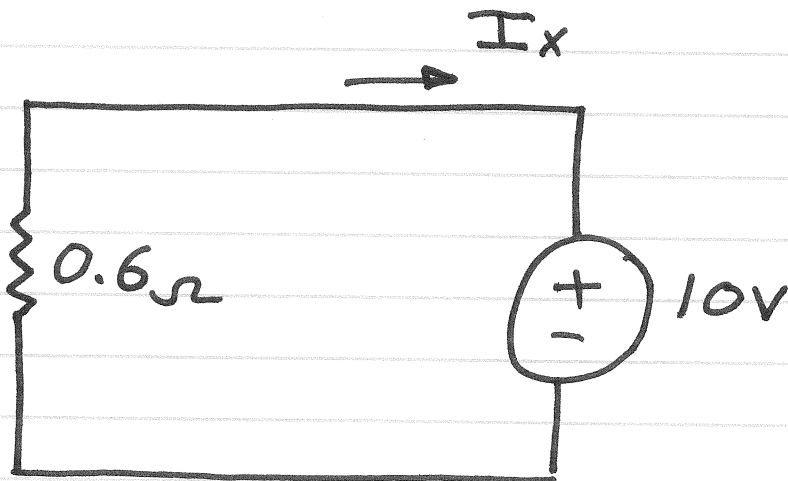
$$\therefore R_{TH} = \frac{V_T}{I_T} = 0.6 \Omega$$



$$I_x = - \frac{10}{0.6} = - 16.67 A$$