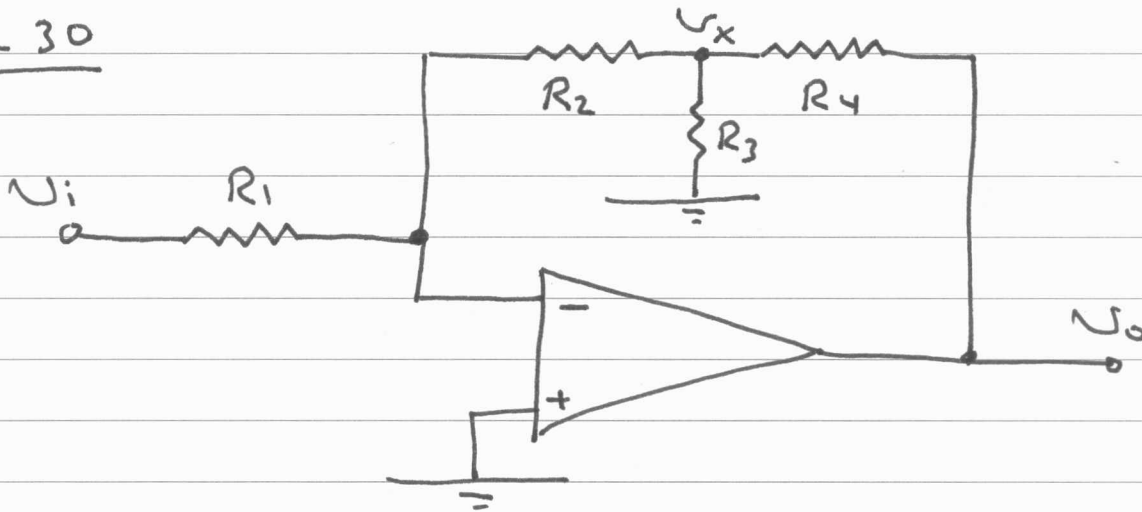


Ch 2 Homework Solutions

2-30



$$\frac{V_i - V(-)}{R_1} + \frac{V_x - V(-)}{R_2} = 0$$

$$V(-) = V(+) = 0$$

$$\therefore \frac{V_x}{V_i} = -\frac{R_2}{R_1}$$

$$V_x = \frac{R_2 \parallel R_3}{R_2 \parallel R_3 + R_4} V_o$$


$$\frac{V_o}{V_x} = 1 + \frac{R_4}{R_3} + \frac{R_4}{R_2}$$

$$\therefore \frac{V_o}{V_i} = \frac{V_o}{V_x} \cdot \frac{V_x}{V_i}$$

$$\frac{V_o}{V_i} = -\frac{R_2}{R_1} \left(1 + \frac{R_4}{R_3} + \frac{R_4}{R_2} \right)$$

-1-

2.33

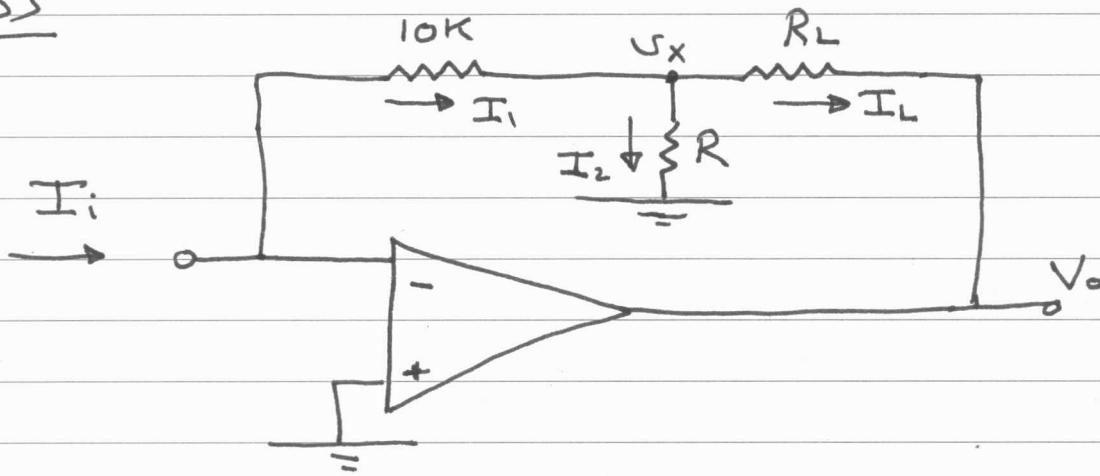

a) $V_x = -10k I_1$

$$V_x = -10k I_i$$

$$I_2 = \frac{V_x}{R} = \frac{-10k I_i}{R}$$

$$I_L = I_1 - I_2$$

$$I_L = I_i - \frac{-10k I_i}{R}$$

$$\therefore I_L = \left(1 + \frac{10k}{R}\right) I_i$$

But $I_L = 20 I_i$

$$\therefore 1 + \frac{10k}{R} = 20$$

$$\therefore R = 0.53k$$

b) $V_o = -R_L I_L - 10k I_i$

$$V_o = -R_L (20 I_i) - 10k I_i$$

$$V_o = -(1k)(20 I_i) - 10k I_i$$

$$V_o = -(30k) I_i$$

$$V_o = -30K I_i$$

$$V_{o,max} = 12V$$


$$V_{o,min} = -12V$$

$$\therefore \text{When } V_o = 12V; I_i = -0.4mA$$

$$\therefore \text{When } V_o = -12V; I_i = +0.4mA$$

$$\therefore 0.4mA \geq I_i \geq -0.4mA$$
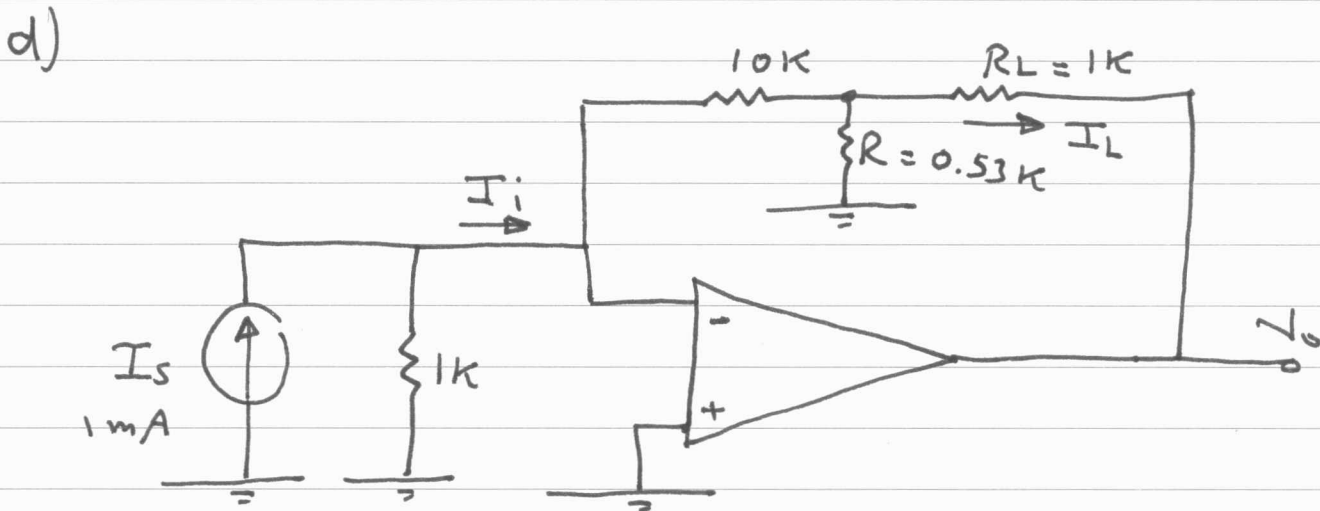
$$c) Z_i = \frac{V_i}{I_i} = \frac{-V_d}{I_i} = \frac{0}{I_i} = 0\Omega$$




$$I_L = 20 I_i$$

$$I_i = I_s$$

$$\therefore I_L = 20 I_s = 20mA$$

2.41

$$V_o = V_1 + 2V_2 - 3V_3 - 4V_4$$

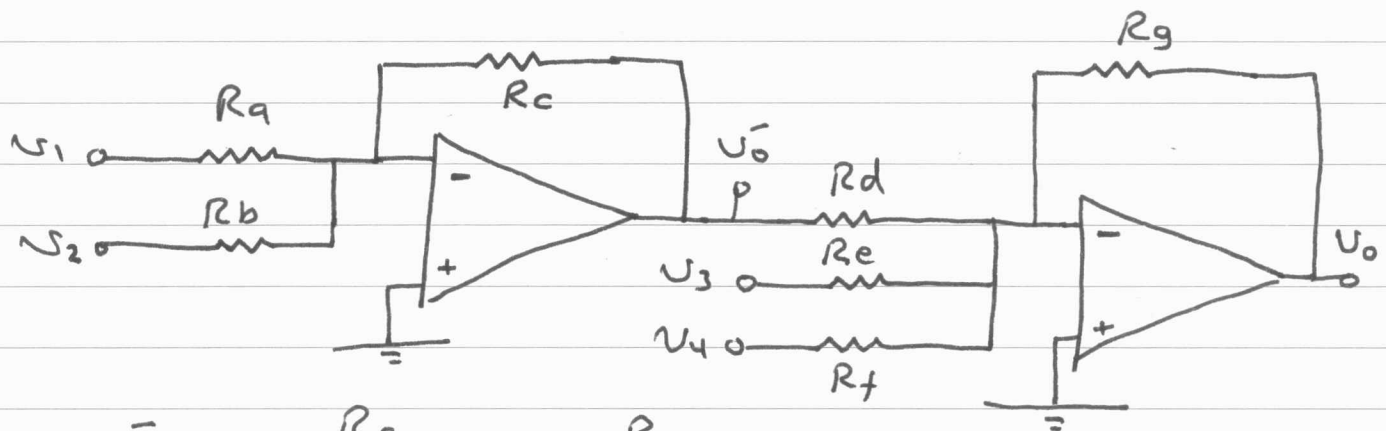

$$V_{0p} = -\frac{R_c}{R_a} V_1 - \frac{R_c}{R_b} V_2$$

$$V_{0p} = -V_1 - 2V_2$$

$$\therefore \frac{R_c}{R_a} = 1 \quad ; \quad \frac{R_c}{R_b} = 2$$

let $R_c = 20k$

$$\therefore R_a = 20k, \text{ and } R_b = 10k$$

$$V_o = -\frac{R_g}{R_d} V_{0p} - \frac{R_g}{R_e} V_3 - \frac{R_g}{R_f} V_4$$


$$V_o = -V_{0p} - 3V_3 - 4V_4$$

$$\therefore \frac{R_g}{R_d} = 1 \quad ; \quad \frac{R_g}{R_e} = 3 \quad ; \quad \frac{R_g}{R_f} = 4$$

let $R_g = 60k$


$$\therefore R_d = 60k \quad ; \quad R_e = 20k, \text{ and } R_f = 15k$$

2.62

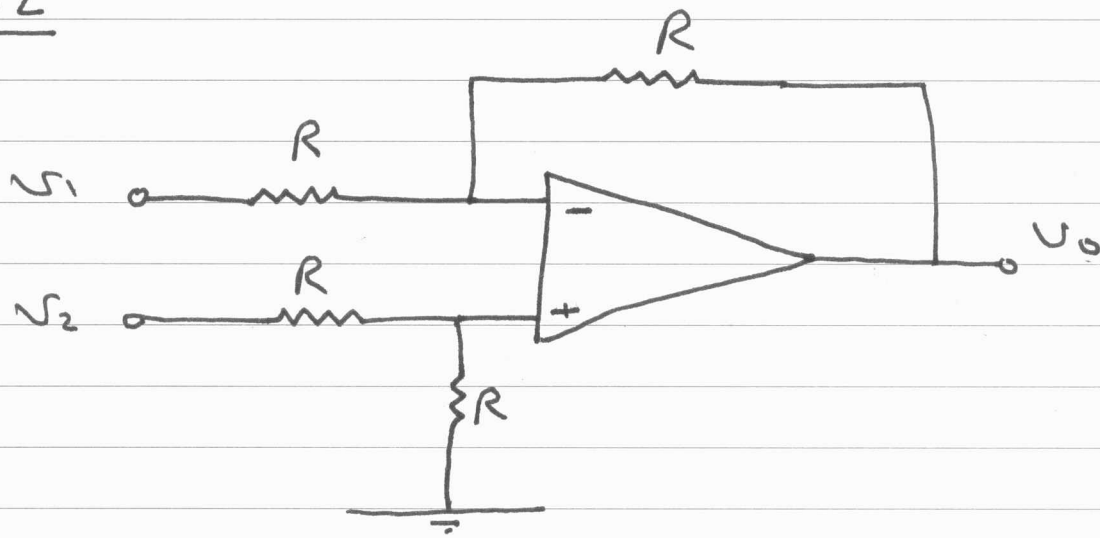


$$Z_1 = R \quad ; \text{ seen by } V_1 \text{ only}$$
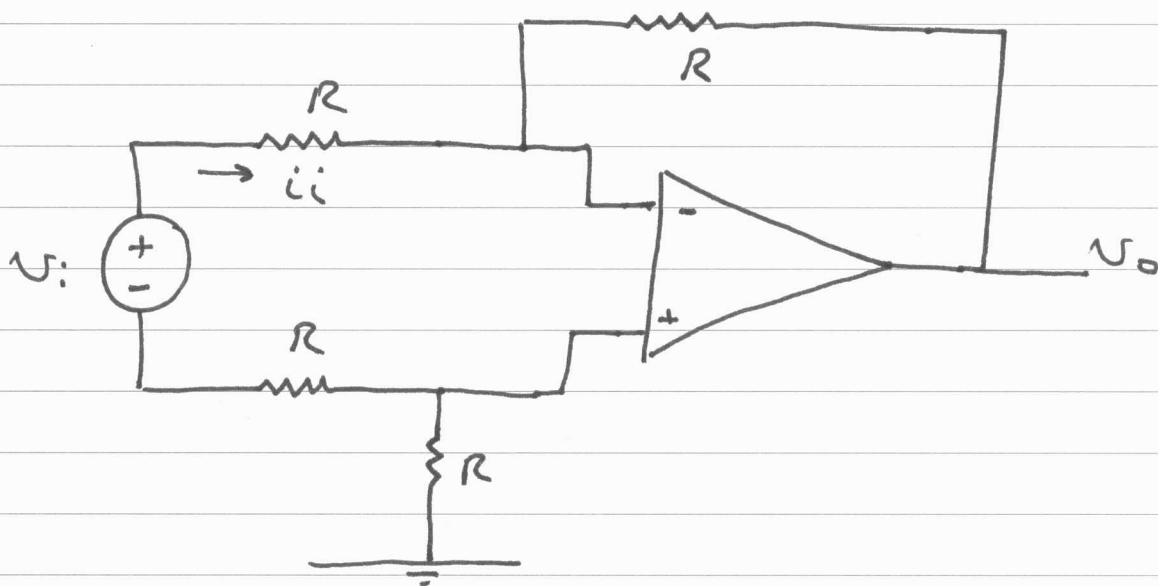
$$Z_2 = 2R \quad ; \text{ seen by } V_2 \text{ only}$$



$$-V_i + R i_i + R i_i = 0$$

$$\therefore \frac{V_i}{i_i} = 2R$$

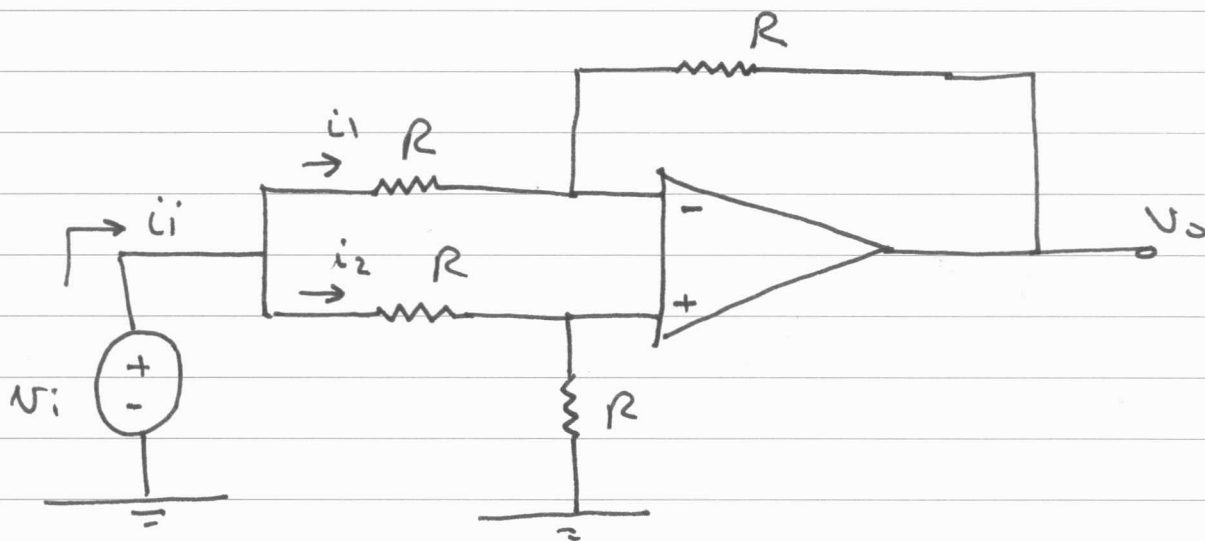

$$i_i = i_1 + i_2$$


$$i_2 = \frac{V(+)}{R} = \frac{V_i}{2R}$$

$$i_1 = \frac{V_i - V(-)}{R} = \frac{V_i - V(+)}{R} = \frac{V_i}{2R}$$

$$\therefore i_i = i_1 + i_2 = \frac{V_i}{R}$$

$$\therefore \frac{V_i}{i_i} = R$$

2.76

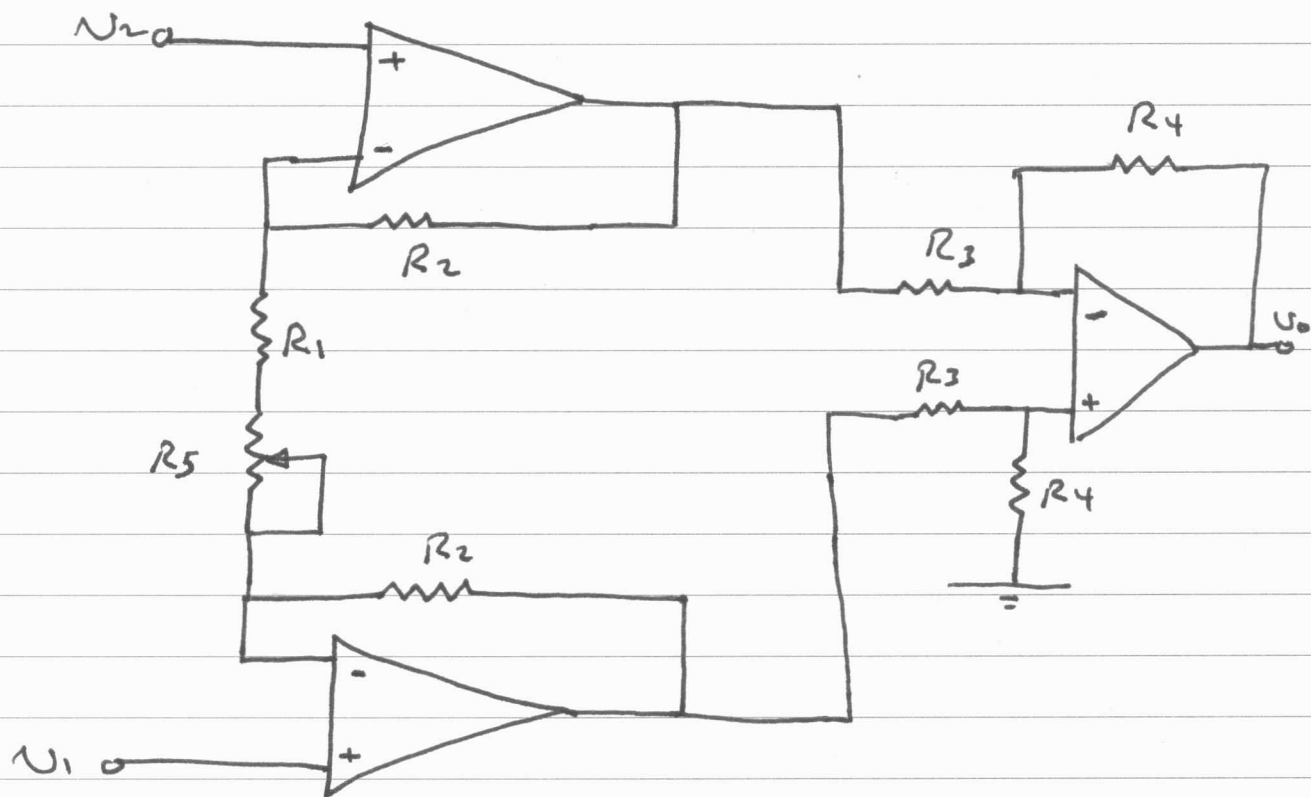

The gain of the second stage = 0.5

$$\therefore \frac{R_4}{R_3} = 0.5$$

$$\text{let } R_4 = 10\text{K} ; \therefore R_3 = 20\text{K}$$

$$R_5(\text{min}) = 0 ; R_5(\text{max}) = 100\text{K}$$

$$A_d = \frac{V_o}{V_d} = \frac{R_4}{R_3} \left(1 + \frac{2R_2}{R_1 + R_5} \right)$$

$$\therefore 1 + \frac{2R_2}{R_1 + R_5} = \begin{cases} 2 & \text{for } R_5 = 100\text{K} \\ 200 & \text{for } R_5 = 0 \end{cases}$$

$$\therefore 1 + \frac{2R_2}{R_1 + R_5} = 2$$

$$1 + \frac{2R_2}{R_1 + 100k} = 2$$

$$\therefore 2R_2 = R_1 + 100k \quad \text{--- (1)}$$

$$\therefore 1 + \frac{2R_2}{R_1} = 200$$

$$\therefore R_2 = 99.5 R_1 \quad \text{--- (2)}$$

Solving (1) and (2)

$$R_1 = 0.505k$$

$$R_2 = 50.25k$$