



BIRZEIT UNIVERSITY

ANSWER BOOKLET

For Instructor's Use

Question	Grade
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	
Total	

Student: <u>Advanced</u>	Number:
Course: Department: <u>asgneh 3^r</u>	Number:
Division:	Instructor:
Date:	
Day	Month Year

Example

Design a negative Edge T-FF.

Solution

① Design specification:

~~State~~ This circuit has 2 inputs (clk and T) and one output Q. The following are all the possible total states

T	clk	Q	stable??
0	0	0	yes
0	0	1	yes
0	1	0	yes
0	1	1	yes
1	0	0	yes
1	0	1	yes
1	1	0	yes
1	1	1	yes

② get the primitive flow table

state	Inputs		Output	Comments
	T	clk	Q	
a	1	1	0	after d or f
b	1	0	1	after a or g
c	1	1	1	after b or h
d	1	0	0	after c or e
e	0	0	0	after d or f
f	0	1	0	after e or a
g	0	0	1	after b or h
h	0	1	1	

→ Primitive flow table

	00	01	11	10
a	-,-	f,-	(a)0	b,-
b	g,-	-,-	c,-	(b)1
c	-,-	h,-	(c)1	d,-
d	e,-	-,-	a,-	(d)0
e	(e)0	f,-	-,-	d,-
f	e,-	(f)0	a,-	-,-
g	(g)1	h,-	-,-	b,-
h	g,-	(h)1	c,-	-,-

③ reducing the number of states by merging the rows


b	a,c X						
c	X	b,d X					
d	b,d X	X	a,c X				
e	b,d X	e,g X b,d	f,h X	✓			
f	✓	e,g X b,d	a,c X f,h	✓	✓		
g	f,h X	✓	b,d X	e,g X b,d	X	e,g X f,h	
h	f,h X a,c	✓	✓	d,a X c,f	e,g X f,h	X	✓
	a	b	c	d	e	f	g

~~pair~~ compatible pairs

(a,b), (b,g), (b,h), (c,h), (d,e), (d,f), (e,g), (g,h)

→ maximal compatibles using merger diagram

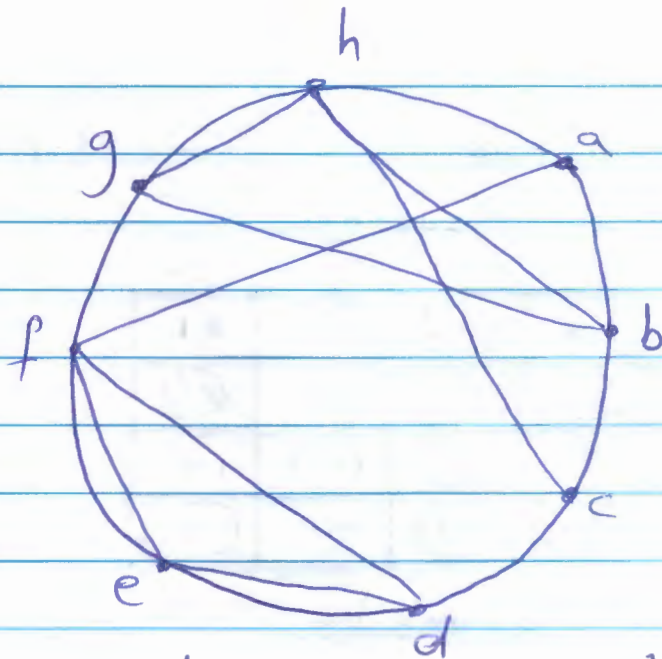$(d, e, f), (b, g, h),$
 $(a, f), (c, h)$



⇒ minimum collection that covers all states and closed "is"

$(a, f), (b, g, h), (c, h), (d, e, f)$
 $\Downarrow \quad \Downarrow \quad \Downarrow \quad \Downarrow$
 $a \quad b \quad c \quad d$


	00	01 TC	11	10
a, f	e, -	(f), 0	(a), 0	b, -
b, g, h	(a), 1	(b), 1	c, -	(b), 1
c, h	g, +	(b), 1	(c), 1	d, -
d, e, f	(e), 0	(f), 0	a, -	(d), 0

=

	00	01 TC	11	10
a	d, -	(a), 0	(a), 0	b, -
b	(b), 1	(b), 1	c, -	(b), 1
c	b, +	(c), 1	(c), 1	d, -
d	(d), 0	(d), 0	a, -	(d), 0

④ state assignment (race-free)

by using transition diagram

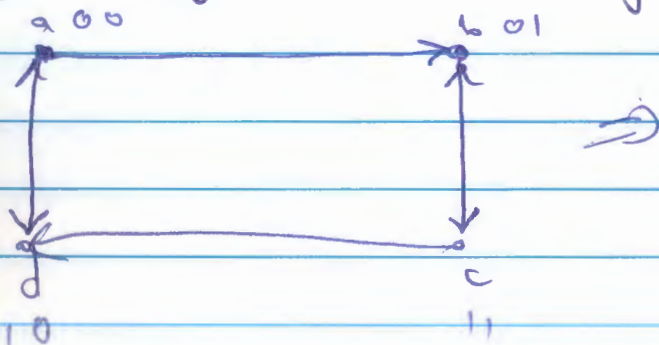

⑤ get the transition table and output map

		TC			
		00	01	11	10
a	$y_1 y_2$	00	00	00	01
	01	01	01	11	01
	11	01	11	11	10
	10	10	10	00	10

Transition Table

		TC			
		00	01	11	10
b	$y_1 y_2$	00	0	0	X
	01	1	1	1	1
	11	1	1	1	X
	10	0	0	0	0

$Q = y_2$ or $Q = y_2$

		TC			
		00	01	11	10
c	$y_1 y_2$	00	0	0	0
	01	0	0	1	0
	11	0	1	1	1
	10	1	1	0	1

$$X_1 = T'C'y_2' + T'cy_1 + TCy_2 + TC'y_1$$

		TC			
		00	01	11	10
d	$y_1 y_2$	00	0	0	1
	01	1	1	1	1
	11	1	1	1	0
	10	0	0	0	0

$$X_2 = y_1'y_2 + T'y_2 + cy_2 + TC'y_1'$$

(Draw the logic Diagram)

or By using SR latch



$y_1 y_2$	TC			
	00	01	11	10
00	1	0	0	0
01	0	0	1	0
11	0	X	X	X
10	X	X	0	X

$y_1 y_2$	TC			
	00	01	11	10
00	0	X	X	X
01	X	X	0	X
11	1	0	0	0
10	0	0	1	0

$$S_1 = y_2 TC + y_2' TC'$$

$$R_1 = y_2 T'C' + y_2' TC$$

in the same way

$$S_2 = y_1' TC'$$

$$R_2 = y_1 TC'$$


Draw the logic diagram

⊗ HAZARDS

Hazards are unwanted switching transients that may appear at the output of a circuit because different paths exhibit different propagation delays.

⊗ Hazards in Combinational circuits

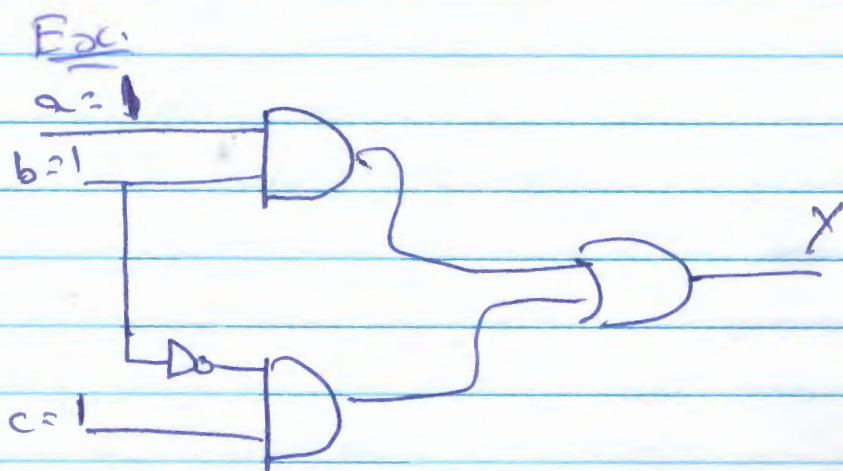This occurs when a single variable change produces a momentary output change when no output should occur.




$$a=1, b=1, c=1 \Rightarrow y=1$$

if b changes to zero

$$\Rightarrow a=1, b=0, c=1 \Rightarrow y=1$$

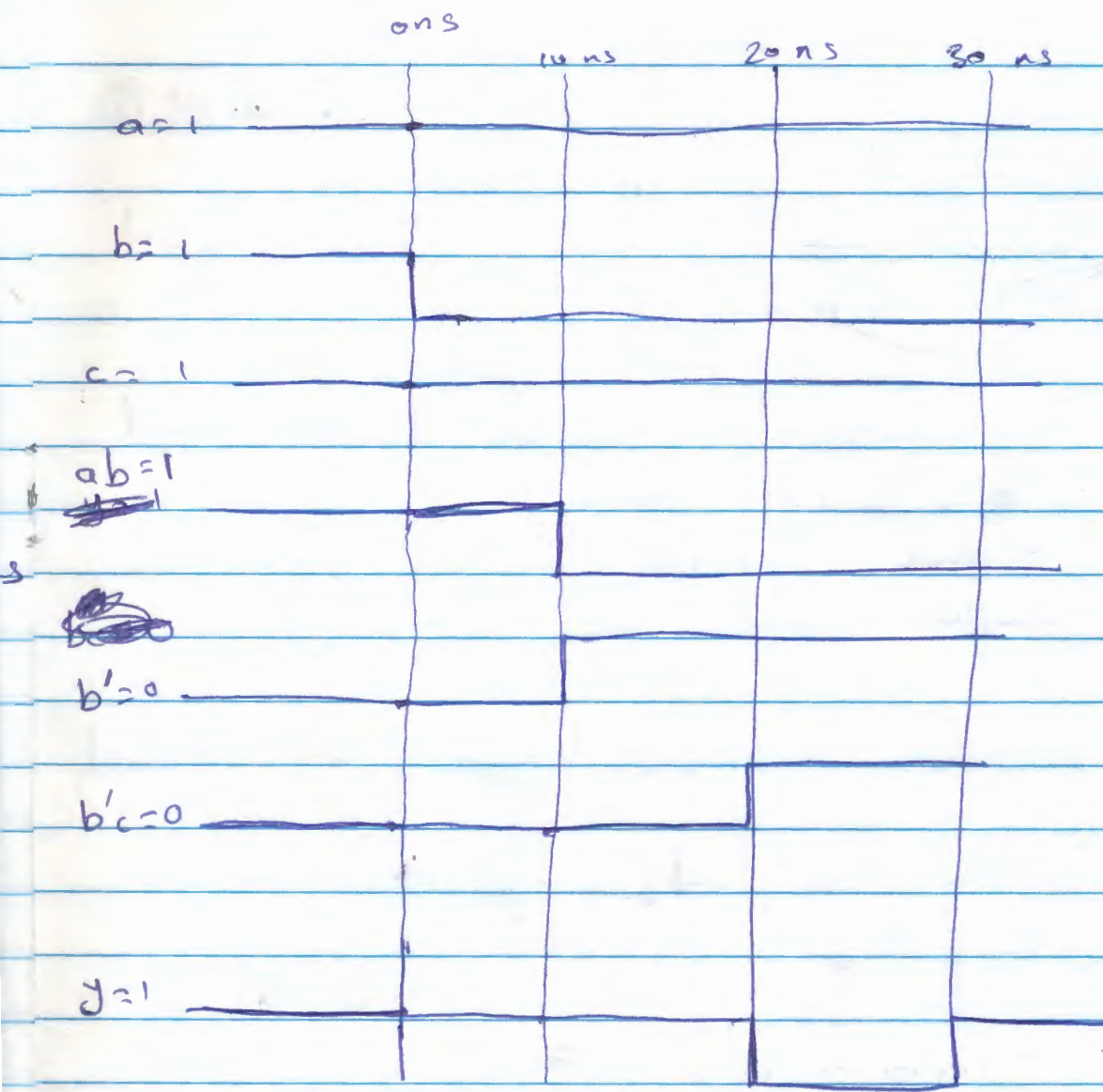but static hazard may occur because of different path delays



error static hazard

in this example we have
 $y = ab + b'c$

\Rightarrow k-map




	bc	00	01	11	10
a \	0		1		
	1	1	1	1	1

$$y = ab + b'c$$

this change will cause static hazard
 (a & c didn't change
 b has changed \Rightarrow the circuit
 move from circle to another


\Rightarrow to remove this type of hazard
 include all the prime
 implicants

$$\Rightarrow y = ab + b'c + ac$$

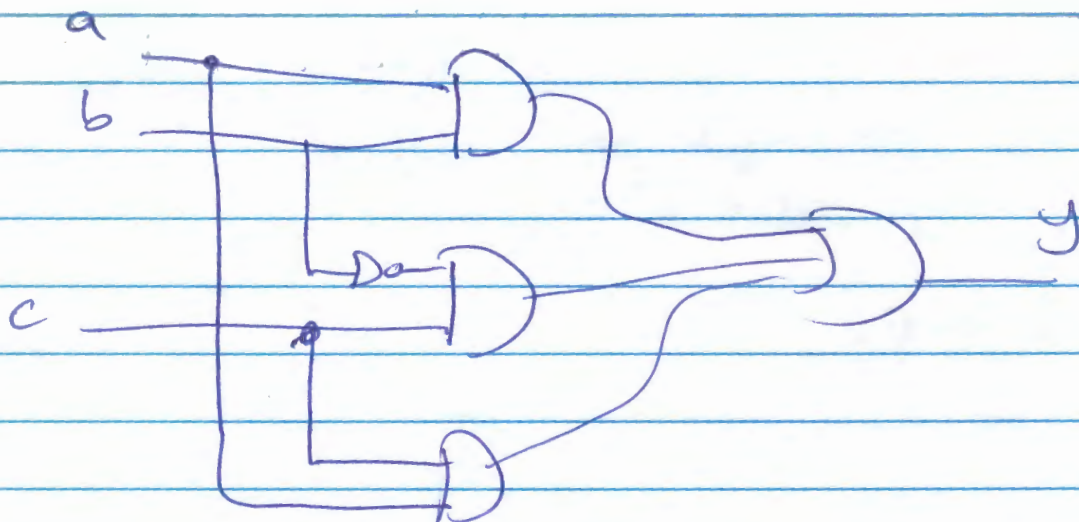

Hazard free circuit


④ types of hazard

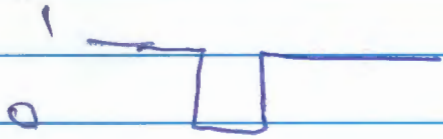

static 1-hazard



static-0-hazard

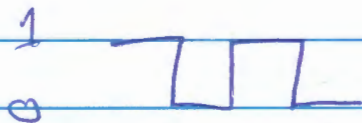

dynamic hazard

removal of static 1-hazard in

(AND-OR
NAND-Circuits) will also remove


0-hazards and dynamic hazards

(Problem in testing??).

⊗ Hazards in sequential circuits

- Hazards in asynchronous circuits may cause the circuit to go to the wrong stable state.

Ex.

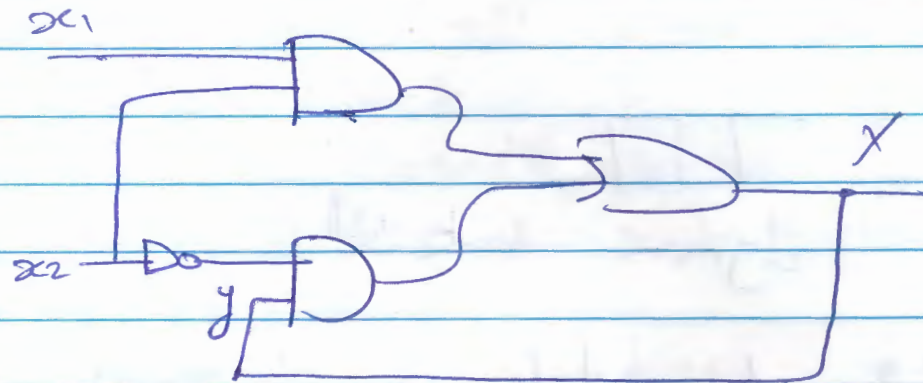

$$Y = x_1 x_2 + x_2 y$$

	$x_1 x_2$			
	00	01	11	10
y				
0	0	0	1	0
1	1	0	1	1

Transition table


if we are in stable total state 111
then x_2 goes to 0 \Rightarrow next stable
total state should be $\begin{matrix} y & x_1 x_2 \\ 1 & 10 \end{matrix}$

but if y changes to 0 (hazard)
then total stable state is 010
error

⊗ Avoidance: the same way like combinational circuits: add a redundant terms for all prime implicants.

④ Implementation with SR latch

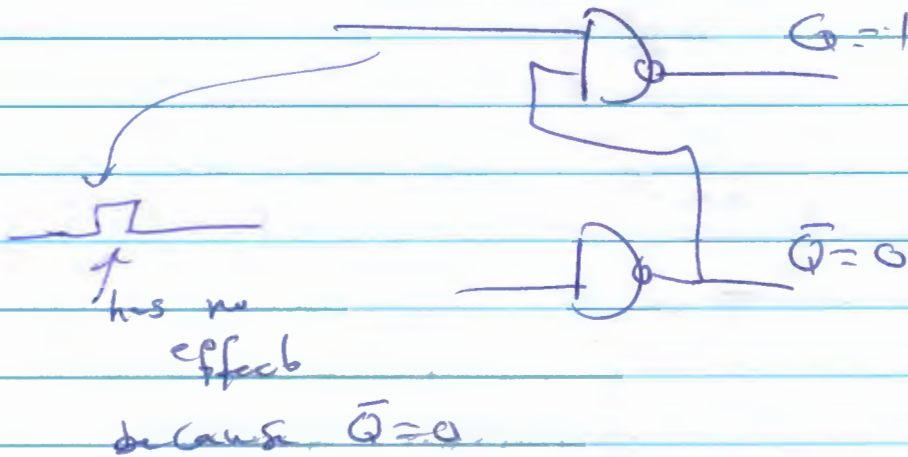we can avoid hazard if we implement the circuits with SR latches



④ note about implementation with SR latch

~~NOR~~

- SR with 2 nor gates

$$y = S + R'y$$

- SR with 2 nand gates

$$y = S' + R y$$

Excitation table

	$Q(t)$	$Q(t+1)$	S	R
this is for SR with nor gates	0	0	0	X
	0	1	1	0
	1	0	0	1
	1	1	X	0

for example if we get

$$S = AB + CD$$

$$R = A'c$$

From this excitation table and we want
to use SR with nand gates

$$\Rightarrow S_{\text{nand}} = S'_{\text{nor}} = (AB + CD)'$$

$$R_{\text{nand}} = R'_{\text{nor}} = (A'c)'$$

