



ANSWER BOOKLET

Student: <u>Digital</u>	Number: <u>10</u>
Course: Department: _____	Number: _____
Division: <u>PLD "2"</u>	Instructor: _____
Date: _____	
Day	Month Year


For Instructor's Use

Question	Grade
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	
Total	

⑧ PAL

- fixed OR array and a Programmable AND array.

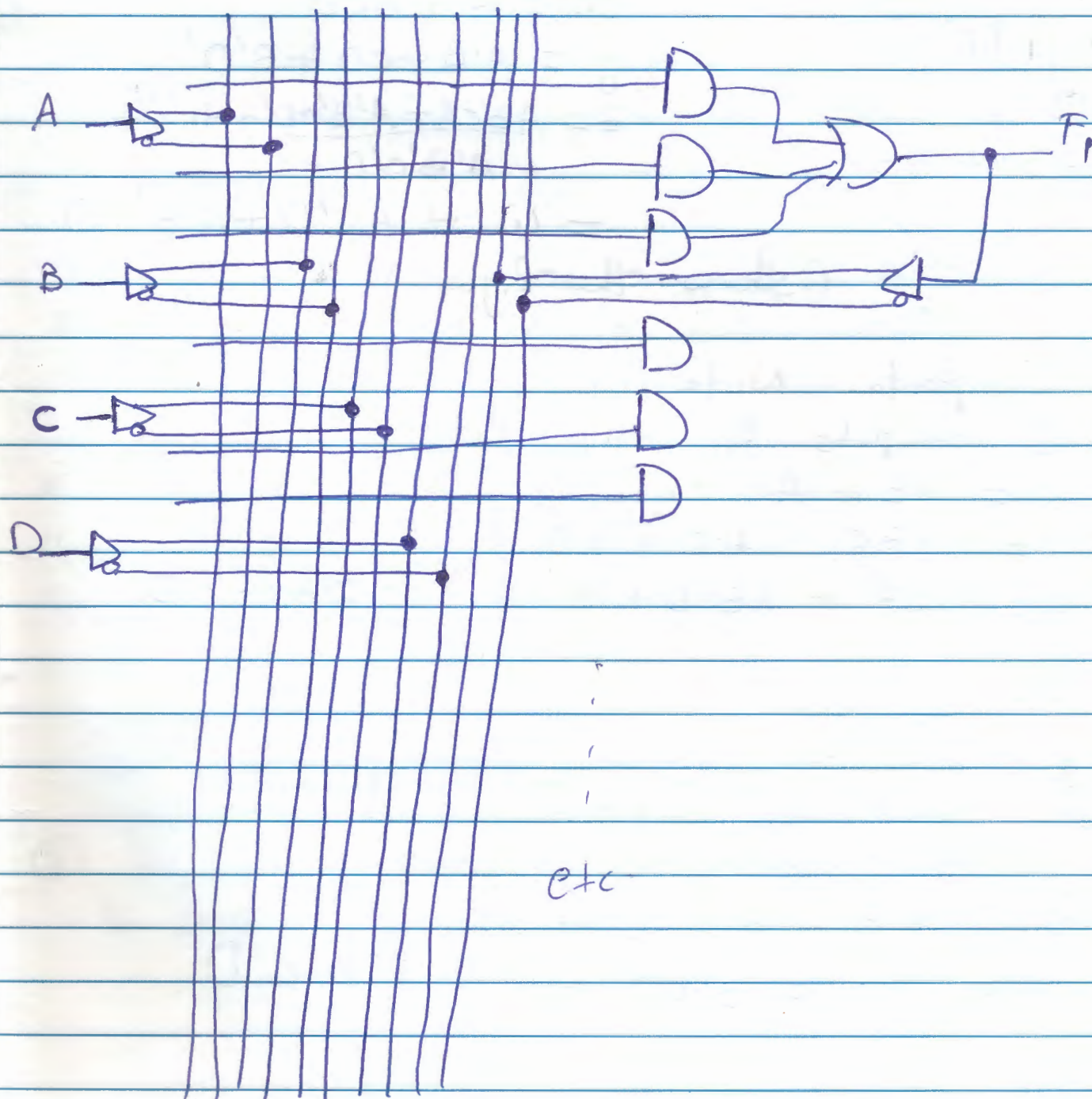- Example of PAL with 4 inputs, 4 outputs, 4 sections of a three-wide AND-OR array (3 programmable AND gates in each section and one fixed OR gate).



$$w(A, B, C, D) = \sum (2, 12, 13)$$

$$x(A, B, C, D) = \sum (7, 8, 9, 10, 11, 12, 13, 14, 15)$$

$$y(A, B, C, D) = \sum (0, 2, 3, 4, 5, 6, 7, 8, 10, 11, 15)$$

$$z(A, B, C, D) = \sum (1, 2, 8, 12, 13)$$

AB \ CD	00	01	11	10
00				①
01				
11	①	①		
10				

⇒ In the same way :-

$$x = A + BCD$$

$$y = A'B + CD + B'D'$$

$$z = ABC' + A'B'cD' + Ac'D' + A'B'c'D$$

$$w = ABC' + A'B'cD'$$

$$= w + Ac'D' + A'B'c'D$$

(show the figure)

⊗ Important Note

3- outputs for this Pal

$$x = AB + AC + CD$$

$$y = A'BC + ACD + BD$$

$$z = A'B + ABCD + B'cD' + c'D + B'c'D$$

x- is ok

y- is ok

z- must be divided such that
(for example)

$$z = A'B + ABCD + m$$

$$\text{where } m = B'cD' + c'D + B'c'D$$

⑧ Programming Table for the previous example:-

product term	AND Inputs				W	outputs
	A	B	C	D		
1	1	1	0	-	-	$W = ABC' + A'B'CD'$
2	0	0	0	0	-	
3	-	-	-	-	-	
4	1	-	-	-	-	$x = A + BCD$
5	-	1	1	1	-	
6	-	-	-	-	-	
7	0	1	-	-	-	$y = A'B + CD + B'D$
8	-	-	1	1	-	
9	-	0	-	0	-	
10	-	-	-	-	1	$z = w + AC'D' + A'B'C'D$
11	1	-	0	0	-	
12	0	0	0	1	-	

Ex. 11

$$z = ABC'D + A'B'CD' + A$$

⑨ for not used AND gate \rightarrow intact
because $A'.A = 0$ (also $B'.B = C'.C \dots$).