



ANSWER BOOKLET

Student: <u>Digital</u>	Number: <u>4</u>
Course: Department:	Number:
Division:	Instructor:
Date: Day Month Year	

Dr. Abdellatif Abu Issa

For Instructor's Use

Question	Grade
1	
2	
3	
4	
5	
6	
7	
8	
9	
10	
11	
12	
Total	

④ The Tabulation Method

④ Determination of Prime Implicants

Ex: $F(x, y, z) = \sum (0, 1, 2, 8, 10, 11, 14, 15)$

Step 1

(a)
w x y z

(b)

(c)

0 0 0 0 ✓

(0,1) 0 0 0 -

(0,2,8,10) - 0 - 0

(0,2) 0 0 - 0 ✓

(0,8,2,10) - 0 - 0

1 0 0 0 1 ✓

(0,8) - 0 0 0 ✓

2 0 0 1 0 ✓

(10,11,14,15) 1 - 1 -

8 1 0 0 0 ✓

(2,10) - 0 1 0 ✓

(10,14,11,15) 1 - 1 -

(8,10) 1 0 - 0 ✓

10 1 0 1 0 ✓

(10,11) 1 0 1 - ✓

11 1 0 1 1 ✓

(10,14) 1 - 1 0 ✓

14 1 1 1 0 ✓

(11,15) 1 - 1 1 ✓

15 1 1 1 1 ✓

(14,15) 1 1 1 - ✓

⇒ Prime implicants are

(0,1) : 0 0 0 - → $w'z'y'$

(0,2,8,10) : - 0 - 0 → $x'z'$

(10,11,14,15) 1 - 1 - → wy

⊗ using decimal notations only for determination of prime implicants

(a)	(b)	(c)
0 ✓	0, 1 (1)	0, 2, 8, 10 (2, 8)
—	(0, 2) (2) ✓	0, 2, 8, 10 (2, 8)
1 ✓	(0, 8) (8) ✓	—
2 ✓	—	10, 11, 14, 15 (1, 4)
8 ✓	2, 10 (8) ✓	10, 11, 14, 15 (1, 4)
—	8, 10 (2) ✓	—
10 ✓	—	—
—	(10, 11) (1) ✓	—
11 ✓	(0, 14) (4) —	—
14 ✓	—	—
—	11, 15 (4) —	—
15 ✓	(14, 15) (1) ✓	—

prime implicants are

Decimal	Binary	Term
0, 1	w x y z	
0, 1 (1)	0 0 0 —	$w'x'z'$
0, 2 (2)	0 0 — 0	
0, 2, 8, 10	— 0 — 0	$x'z'$
10, 11, 14, 15	1 — 1 —	wy

④ Selection of prime implicants that minimize the function

Term	Decimal	0	1	2	8	10	11	14	15
wxyz'									
xz'									
w'x'y'	0, 1 (1)	x	(x)						
xz									
x'z'	0, 2, 8, 10 (2, 8)	x		(x)	x	x			
wy	10, 11, 14, 15 (1, 4)					x	x	x	(x)
		✓	✓	✓	✓	✓	✓	✓	✓

all of them are essential prime implicants \Rightarrow

$$F = w'x'y' + x'z' + wy$$

Ex. $F(w, x, y, z) = \sum (1, 4, 6, 7, 8, 9, 10, 11, 15)$

	(a)	(b)	(c)
0101	1 ✓	1, 9 (8)	8, 9, 10, 11 (1, 2)
0100	4 ✓	4, 6 (2)	8, 9, 10, 11 (1, 2)
1000	8 -	8, 9	
		8, 9 (1) ✓	
0110	6 ✓	8, 10 (2) ✓	
1001	9 ✓		
1010	10 ✓	6, 7 (1)	
		9, 11 (2) ✓	
0111	7 ✓	10, 11 (1) ✓	
1011	11 ✓		
		7, 15 (8)	
1111	15 ✓	11, 15 (4)	

⇒ Prime implicants

Decimal	Binary w x y z	Term
1, 9 (8)		
1, 9 (8)	- 0 0 1	$x'y'z$
4, 6 (2)	0 1 - 0	$w'xz'$
6, 7 (1)	0 1 1 -	$w'xy$
7, 15 (8)	- 1 1 1	$x y z$
11, 15 (4)	1 - 1 1	$w y z$
8, 9, 10, 11 (1, 2)	1 0 - -	$w x'$

Selection of prime implicants

		1	4	6	7	8	9	10	11	15
$\checkmark x'y'z$	1,9	(X)					X			
$\checkmark w'xz'$	4,6		(X)	X						
$w'xy$	6,7			X	X					
xyz	7,15				X					X
wyz	11,15								X	X
$\checkmark wx'$	8,9,10,11					(X)	X	X	X	
		\checkmark	\checkmark	\checkmark		\checkmark	\checkmark	\checkmark	\checkmark	

Essential prime implicants





$x'y'z$, $w'xz'$, wx'

take xyz from the prime implicants for the simplest form

$$\Rightarrow F = x'y'z + w'xz' + wx' + xyz$$


⊕ NAND AND NOR Implementations


⊕ 2. level implementation

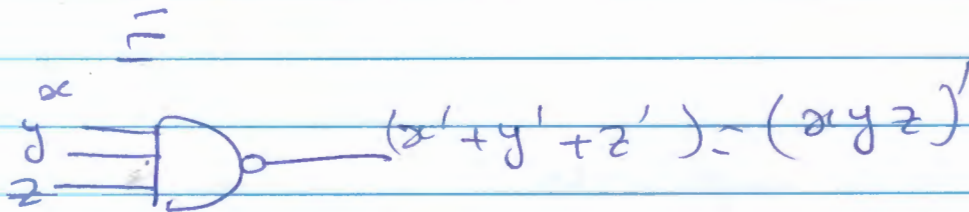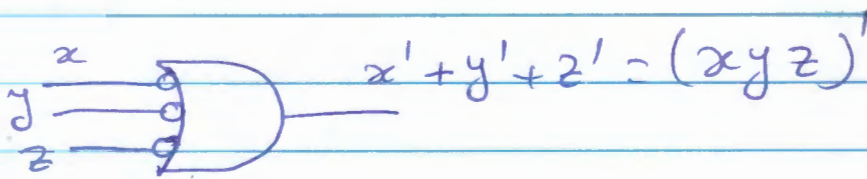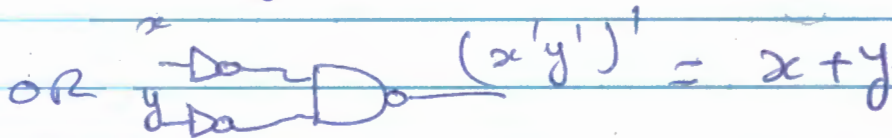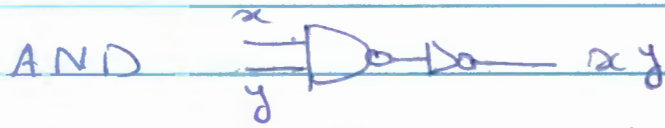

⊕ Two level Implementation

Ex. $F = AB + CD$

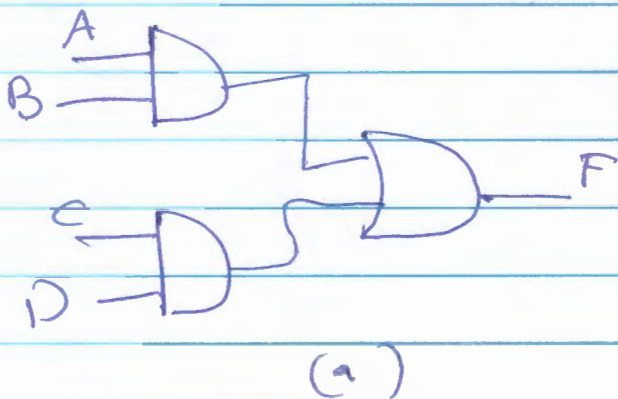


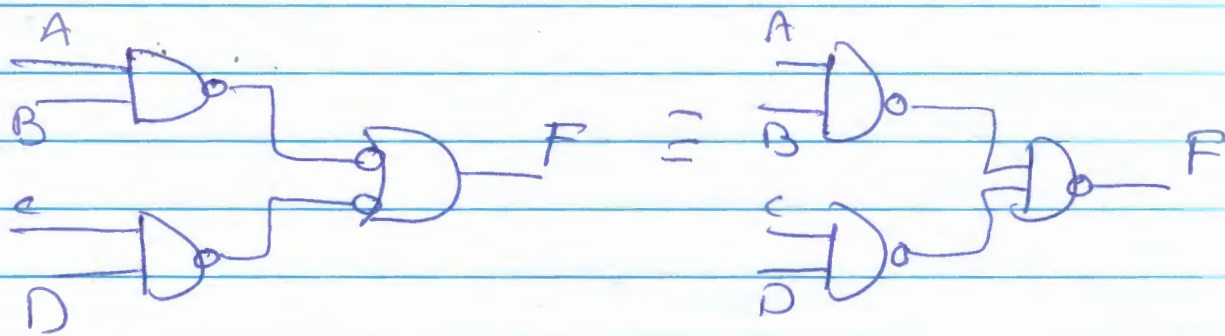



Ex.

$$F(x, y, z) = \sum(1, 2, 3, 4, 5, 7)$$

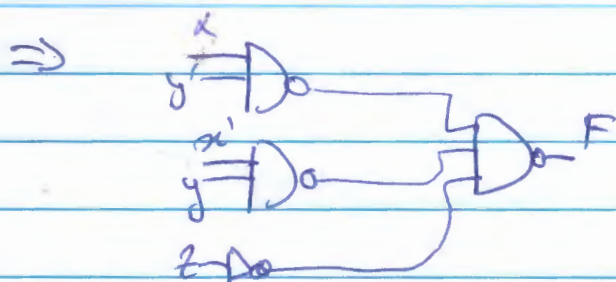
$$\Rightarrow \text{using K-map} \Rightarrow F = xy' + x'y + z$$



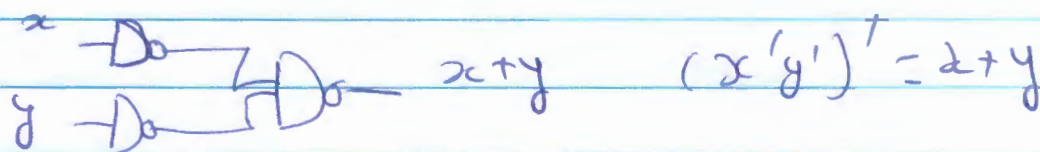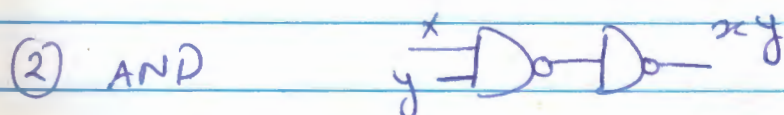④ How NAND and NOR are functional complete




⊗ NOR

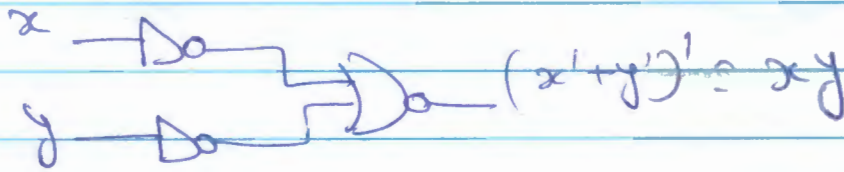

⊗ Multilevel NAND circuit


Ex:

$$F = AC(CD+B) + BC'$$

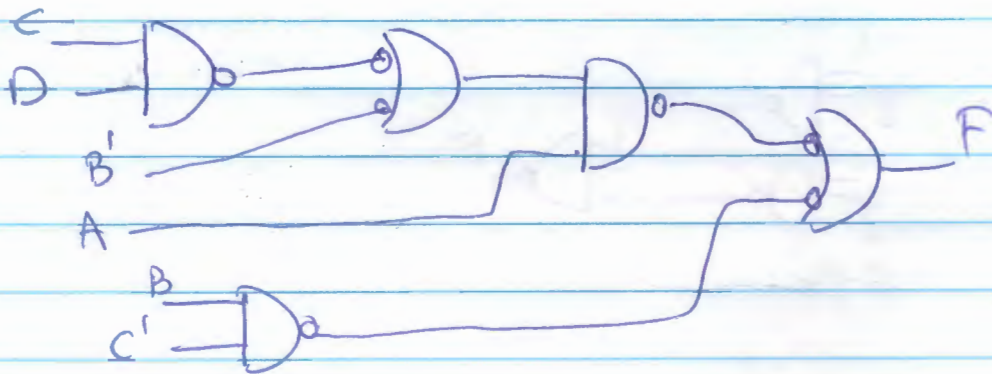


Ex:

$$F = (AB' + A'B)(C+D')$$

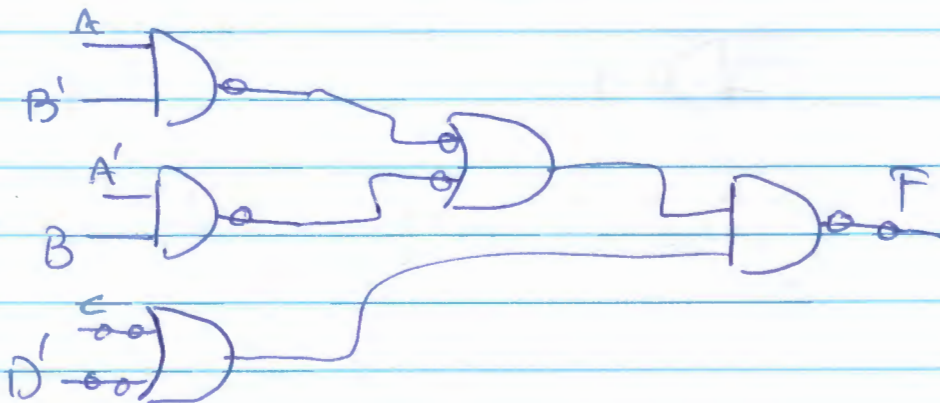


⑥ NOR

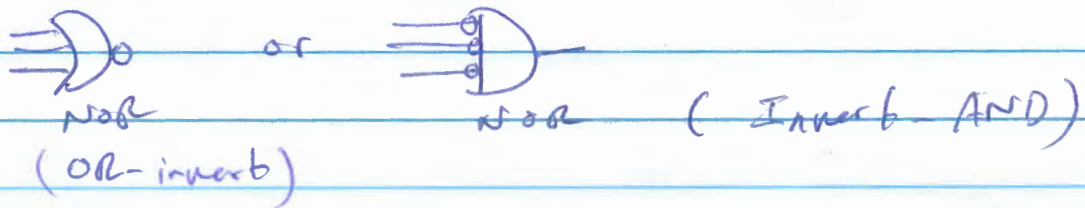


Ex.

$$F = (A + B)(C + D)E$$

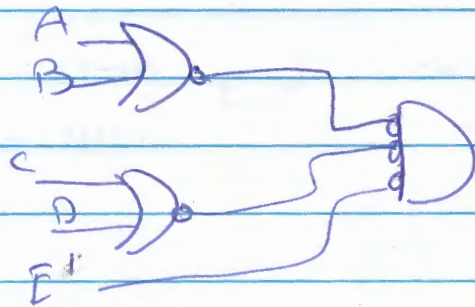

Ex.

$$F = (AB' + A'B)(C + D')$$

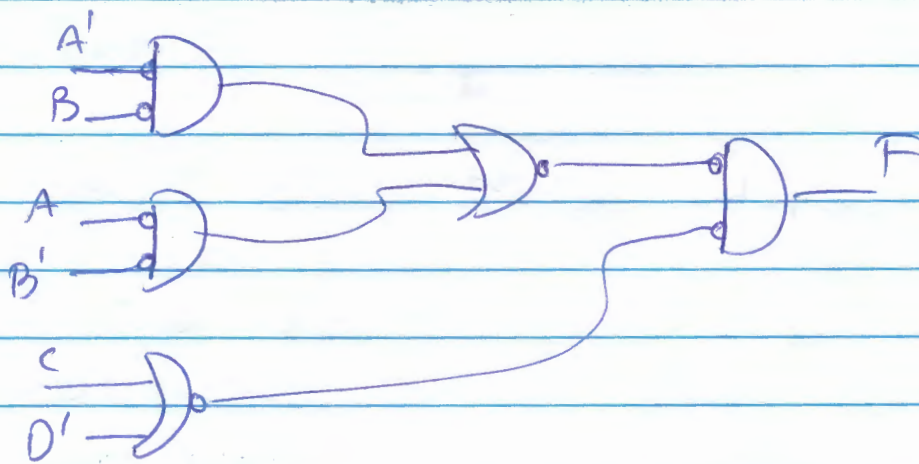

⑩ Wired Logic

⑩ Nondegenerate form

AND

OR

NAND

NOR

} 2 level \rightarrow 16 forms

- 8 degenerate form (eg. AND - AND
NAND - NOR

$$\text{AND-AND} \quad \Rightarrow \quad \text{AND} = \text{AND}$$

NAND-NOR

$$\Rightarrow \text{NAND} = \text{NOR}$$

\equiv

$$\Rightarrow \text{AND-AND}$$

\equiv AND-AND

- non degenerate form (8 forms)

AND-OR

OR-AND

NAND-NAND

NOR-NOR

NOR-OR

NAND-AND


OR-NAND

AND-NOR


$\swarrow \searrow$
dual for each other

Ex: $F = (AB + CD + E)'$


AND-OR-invert

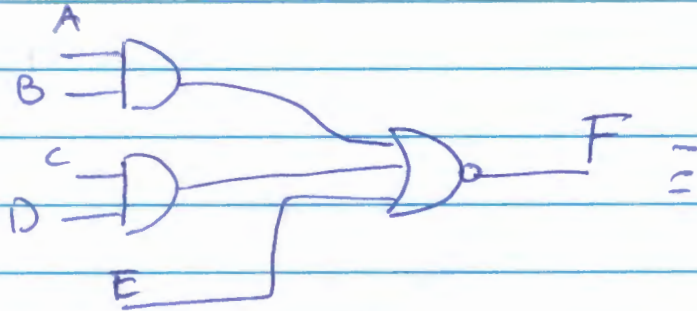

AND-NOR

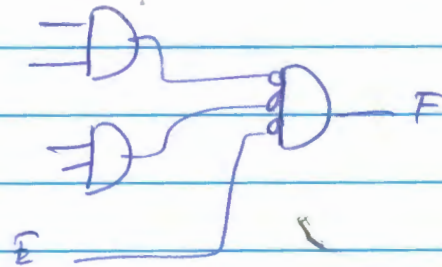


AND-NOR

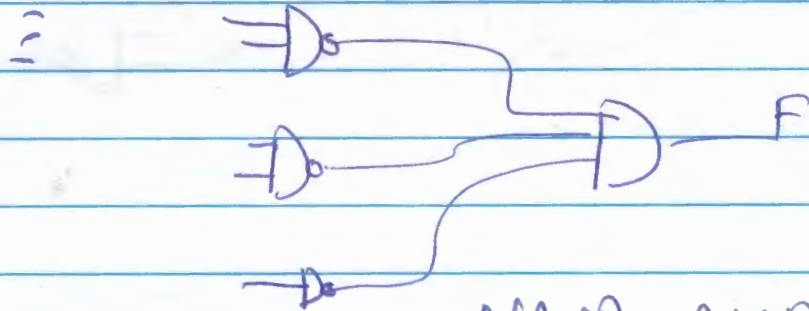


NAND-AND

Ex: $F = [(A+B)(C+D)E]'$


OR-AND-invert

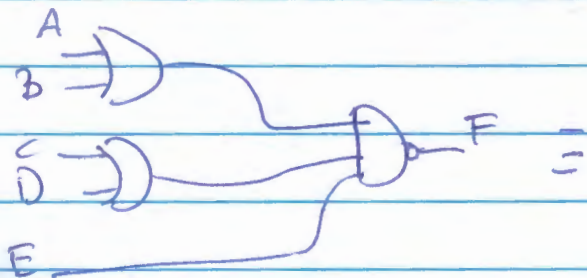

OR-NAND

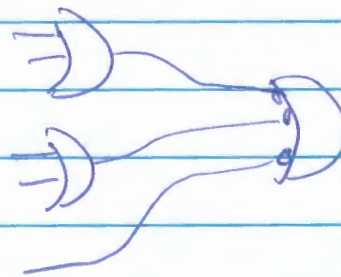

=

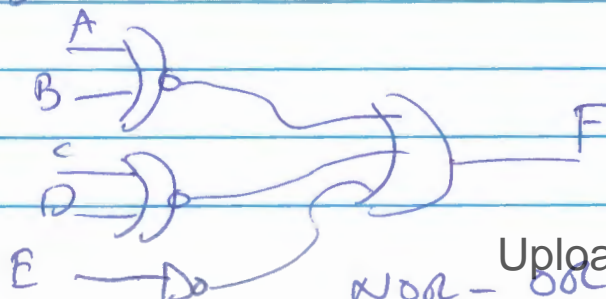

NOR-OR

④ In the last 4 cases, we look to simplify f' , then use inverter to get f .


$F(x,y,z) = (0,6)$

→ Page 93


ex. $f' = x'y + xy' + z$

$$F = (x'y + xy' + z)'$$

① AND - NOR

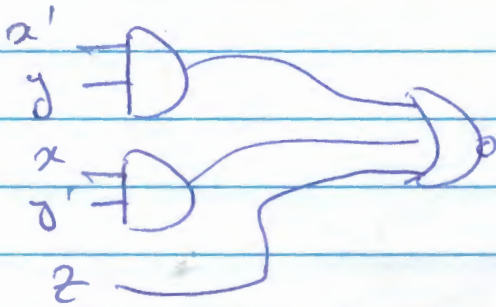

② NAND - AND

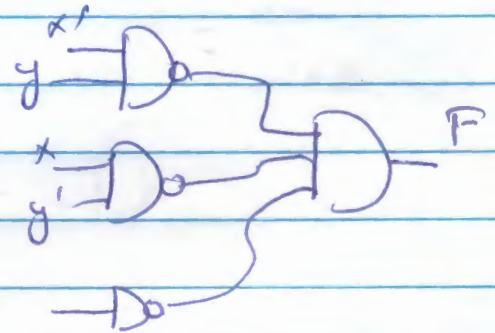


③ OR - NAND

$$(F = x'y'z' + xy'z')$$

$$\rightarrow F' = (x+y+z)(x'+y'+z)$$

$$\rightarrow F = [(x+y+z)(x'+y'+z)]'$$

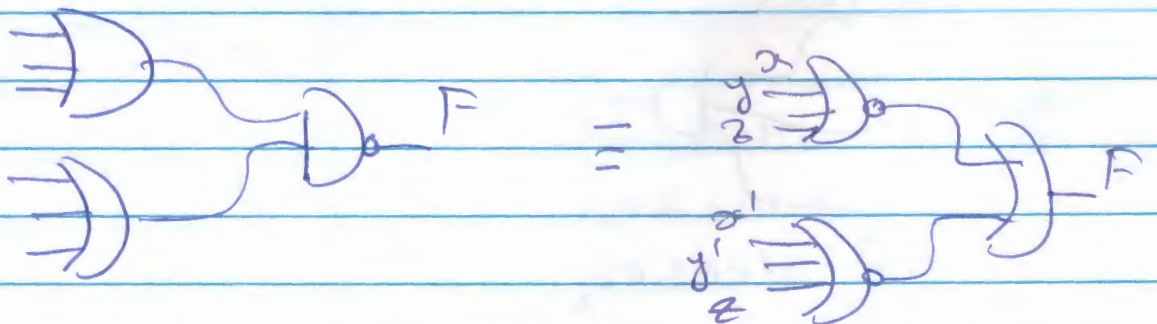

Exclusive-OR function:-

x	y	f
0	0	0
0	1	1
1	0	1
1	1	0

$$F = x \oplus y$$

x \ y	0	1
0	0	1
1	1	0

$$F = xy' + x'y$$

$$(x \oplus y)' = xy + x'y'$$

⊕ The following are some properties of XOR

$$x \oplus 0 = x$$

$$x \oplus 1 = x'$$


$$x \oplus x = 0$$

$$x \oplus x' = 1$$

$$x \oplus y = y \oplus x$$

$$x \oplus y' = x' \oplus y = (x \oplus y)'$$
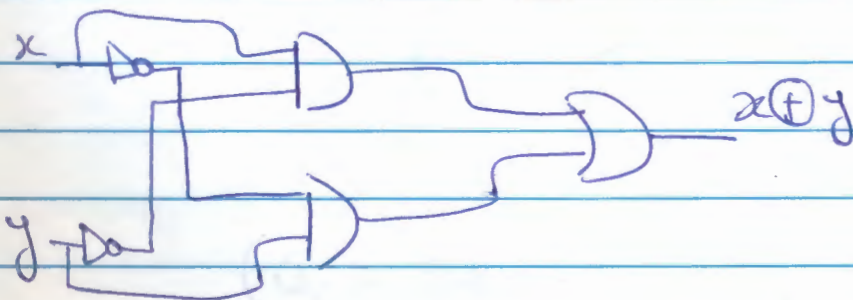
$$(x \oplus y) \oplus z = x \oplus (y \oplus z) = x \oplus y \oplus z$$



⊕ XOR is odd function -

$$A \oplus B \oplus C = (A \oplus B) \oplus C$$

$$= (AB' + A'B)C' + (AB + A'B')C$$

$$= AB'C' + A'BC' + ABC + A'B'C$$

$$= \sum (1, 2, 4, 7)$$

A \ Bc	00	01	11	10
0		1		1
1	1		1	

$\Rightarrow F = (A \oplus B \oplus C)'$ is an even function

<u>True</u>	A	B	C	F
0	0	0	0	0
0	0	0	1	1
0	0	1	0	1
0	0	1	1	0
1	1	0	0	1
1	1	0	1	0
1	1	1	0	0
1	1	1	1	1

⊕ The same thing for $f(A, B, C, D)$

$$f(A, B, C, D) = A \oplus B \oplus C \oplus D$$

$$= (AB' + A'B) \oplus (cD' + c'D)$$

$$= \Sigma (1, 2, 4, 7, 8, 11, 13, 14)$$

* Parity Generation and Checking

- A parity bit is an extra bit included with a binary message to make the number of 1's either odd or even.
- The circuit that generates the binary bit in the transmitter is called a parity generator.
- The circuit that checks the parity in the receiver is called a parity checker.


Ex: 3 bits x, y, z to be transmitted with an even parity \Rightarrow

Three-Bit Message

Parity bit

x	y	z	P
0	0	0	0
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	0
1	1	0	0
1	1	1	1

$$P = x \oplus y \oplus z$$

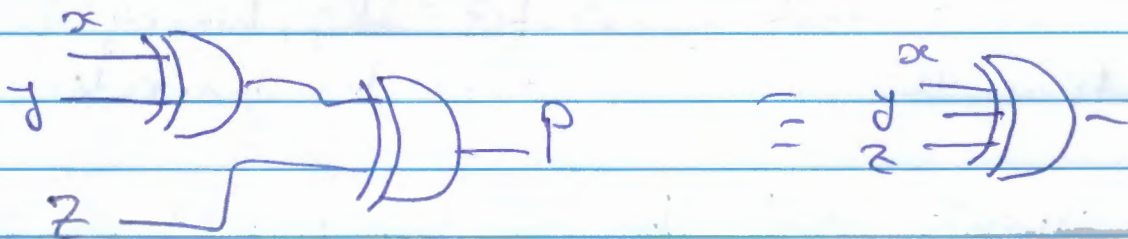

- These 3 bits together with the parity bit are transmitted to their destination

- If the number of 1's in the receiver is odd \rightarrow error occurred during transmission.