
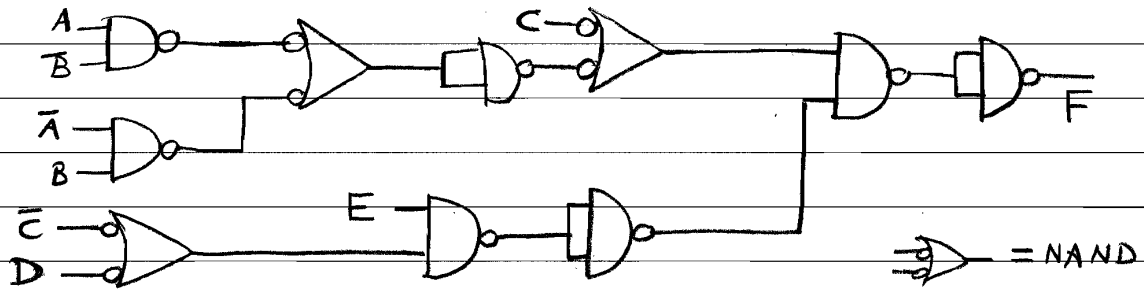



1. a: Using NANDs:

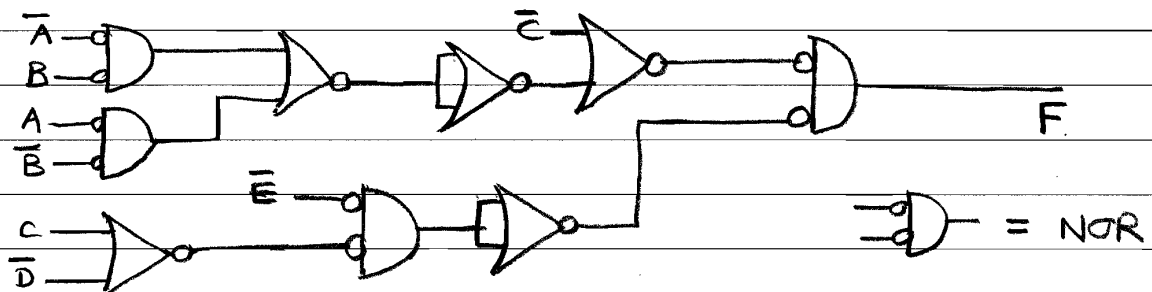

b: Using NORs




2.

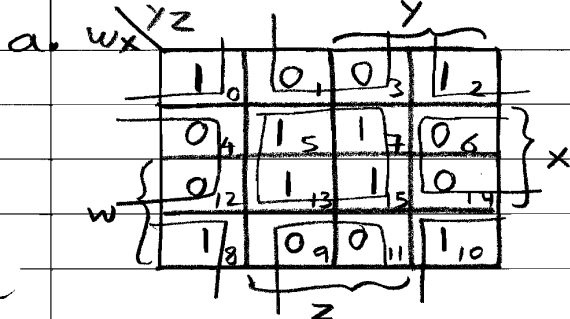


$$F = xz + \bar{x}\bar{z} \quad - (1)$$

$$\bar{F} = x\bar{z} + \bar{x}z \quad - (2)$$

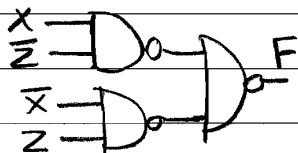b. i. $\text{NAND-AND} = \text{AND-OR} = \text{SOP}$ (Hardware invert)
 $F = \text{SOP} \leftarrow \bar{F} \text{ as SOP from K-map (Eqn 2)}$



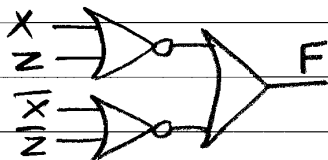ii. $\text{NOR-OR} = \text{OR-AND} = \text{POS}$ (Hardware invert)
 $F = \text{POS} \leftarrow \bar{F} \text{ as POS: } F \text{ as SOP from k-map then invert with DeMorgans to get } \bar{F} \text{ as POS.}$




$$\text{From ① } \bar{F} = xz + \bar{x}\bar{z} = (\bar{x} + \bar{z}) \cdot (x + z)$$

2 b, contd.

iii. $\text{NAND-NAND} = \text{AND-NOT-AND-NOT} = \overbrace{\text{AND-OR}}^{\text{=OR}} = \overbrace{\text{AND-OR}}^{\text{SOP}}$


$F = \text{SOP}$ i.e. get F as a SOP From K-map.

(Eqn 1): $F = XZ + \bar{X}\bar{Z}$

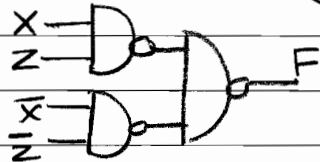

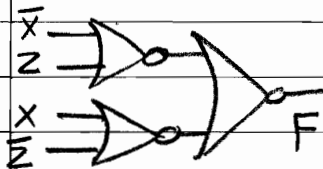iv. $\text{NOR-NOR} = \text{OR-NOT-OR-NOT} = \overbrace{\text{OR-AND}}^{\text{AND}} = \overbrace{\text{OR-AND}}^{\text{POS}}$


$F = \text{POS} = \overline{\overline{\text{SOP}}}$ ← DeMorgan's invert




\bar{F}_{SOP} From eqn (2) = $X\bar{Z} + \bar{X}Z$

$F_{\text{POS}} = \bar{\bar{F}} = \overline{X\bar{Z} + \bar{X}Z} = (\bar{X} + Z)(X + \bar{Z})$

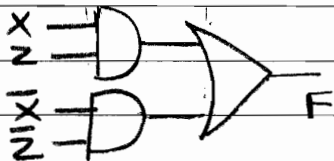
v. $\text{AND-OR} = \text{SOP}$ (Same as iii)



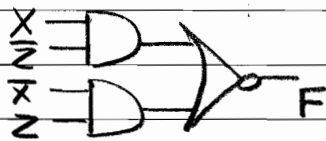
vi. $\text{AND-NOR} = \overbrace{\text{AND-OR}}^{\text{SOP}} - \text{NOT} = \overline{\text{SOP}}$ ← Hardware invert
(Same as i)



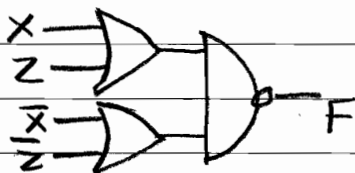vii. $\text{OR-NAND} = \overbrace{\text{OR-AND}}^{\text{POS}} - \text{NOT} = \overline{\text{POS}}$ ← Hardware invert
(Same as ii)



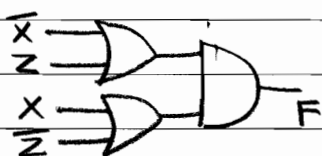viii. $\text{OR-AND} = \text{POS}$ (Same as iv)




of 0's

3.	x_3	x_2	x_1	x_0		y_2	y_1	y_0
0	0	0	0	0	4	1	0	0
1	0	0	0	1	3	0	1	1
2	0	0	1	0	3	0	1	1
3	0	0	1	1	2	0	1	0
4	0	1	0	0	3	0	1	1
5	0	1	0	1	2	0	1	0
6	0	1	1	0	2	0	1	0
7	0	1	1	1	1	0	0	1
8	1	0	0	0	3	0	1	1
9	1	0	0	1	2	0	1	0
10	1	0	1	0	2	0	1	0
11	1	0	1	1	1	0	0	1
12	1	1	0	0	2	0	1	0
13	1	1	0	1	1	0	0	1
14	1	1	1	0	1	0	0	1
15	1	1	1	1	0	0	0	0

Largest # of 0's
= 4 \rightarrow need 3
bits for o/p

By inspection:
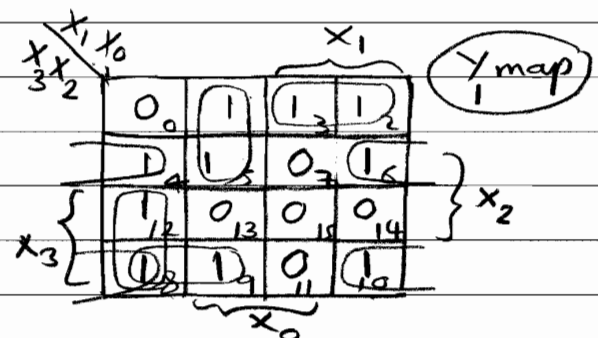
$$y_2 = \bar{x}_3 \bar{x}_2 \bar{x}_1 \bar{x}_0$$




$$y_1 = \bar{x}_3 \bar{x}_2 x_1 + \bar{x}_3 \bar{x}_2 \bar{x}_1 + \bar{x}_3 x_2 \bar{x}_0 + x_3 \bar{x}_2 \bar{x}_0 + x_3 \bar{x}_2 x_1 + x_3 \bar{x}_2 \bar{x}_0$$

Note: other optimal solutions exist.

y_0 can not be simplified

$$y_0 = \sum(1, 2, 4, 7, 8, 11, 13, 14)$$

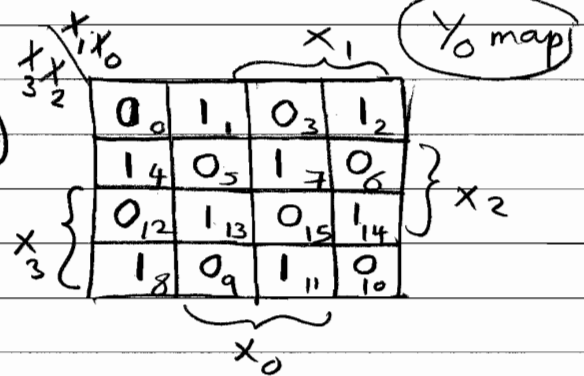
can also represent this canonical form in the corresponding algebraic sum of minterms.



4.

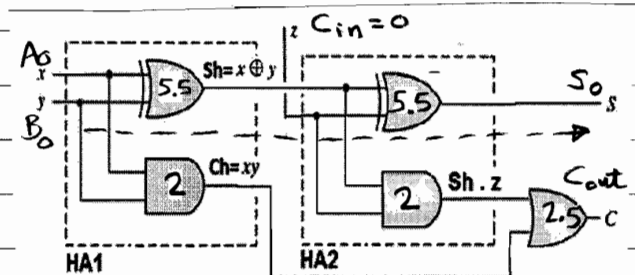a. 1-bit Adder:

- critical path (---)
- Delay = 5.5 + 5.5
= 11 ns.




5-4

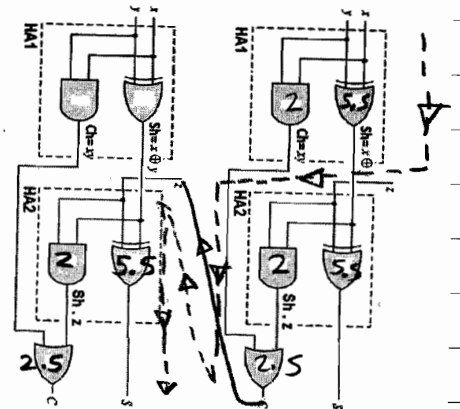b. 2-bit ripple-carry adder:

→ Critical path (---)

$$\rightarrow \text{Delay} = 5.5 + (2 + 2.5) + 5.5 = 15.5 \text{ ns}$$



$$4.2 \text{ \# of additions/sec} = \frac{1 \text{ sec}}{15.5 \text{ ns}} = \frac{10^9}{15.5}$$

$$\approx 64.5 \times 10^6 \text{ additions/sec.}$$

5.

	Inputs			Output		Overflow Occurred? (Yes/No)	Is the result correct? (Yes/No)
	A	B	Subtract/Add [O/P = (A-B) or (A+B)]	C4	S (binary)		
a	0010	0101	0	0	0111	No	Yes
b	1100	1011	1	1	0001	No	Yes
c	0111	1101	0	1	0100	No	Yes
d	1100	0110	1	1	0110	Yes	No

a: addition:
$$\begin{array}{r} 0010 \quad +2 \\ + 0101 \quad +5 \\ \hline 0111 \quad +7 \checkmark \end{array}$$

b: subtraction
$$\begin{array}{r} 1100 = -0100 = (-4) \\ - 1011 = -0101 = (-5) \\ \hline +1 \end{array}$$

c: Addition:
$$\begin{array}{r} 0111 \quad (+7) \\ + 1101 \quad +(-3) \\ \hline 0111 \quad +4 \\ + 1101 \\ \hline 10100 = +4 \checkmark \end{array}$$

$$\begin{array}{r} 1100 \\ + 0101 \\ \hline 10001 = +1 \checkmark \end{array}$$

d: Subtraction:
$$\begin{array}{r} 1100 = -4 \\ - 0110 = +6 \\ \hline -10 \text{ (exceeds } -8) \end{array}$$

→
$$\begin{array}{r} 1100 \\ + 1010 \\ \hline 10110 = +6 \times \\ \text{overflow} \end{array}$$